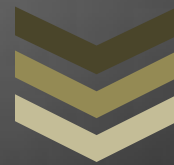


Alternating Current Circuits Solution



Md. Gaffar

Full solution manual of Alternating Current Circuits by
Russel M Kerchnel & George F Corcoran.

E-Book Written By

MAK

E.E.E., CUET'10

CONTENTS

	Page
Network Concepts.....	2
Instantaneous Current.....	14
Effective Current and Voltage Average Power.....	32
Phasor Algebra	53
Sinusoidal signal-phasor circuit analysis.....	63
Non-Sinusoidal Waves.....	119
Coupled Circuits.....	130
Balanced Polyphase Circuite	154
Unbalanced Polyphase Circuits.....	178
Electric Wave Filters.....	204
Transient Analysis.....	222

Chapter-1

Network Concepts

1.1 Given

There branch voltages are, $v_{b1} = (-2 + 3i_{b2})$
 $v_{b2} = (-4 + 2i_{b2})$
 $v_{b3} = 2i_{b3}$

(a) Using mesh analysis (mesh - 1)

$$i_2 (2 + 2) + i_1 (2) = 4$$

or, $i_2 (4) + i_1 (2) = 4 \quad \dots \dots (i)$

Using mesh analysis, (mesh - 2)

$$i_1 (2 + 2 + 1) + i_2 (2) = 2$$

or, $5i_1 + 2i_2 = 2 \quad \dots \dots (ii)$

If i_{b1}, i_{b2}, i_{b3} are the independent variable,

$$i_2 = i_{b2}$$

$$i_{b3} = i_1 + i_2 \quad \text{or, } i_2 = i_{b3} - i_{b1}$$

$$i_{b1} = i_1$$

So equation (i) and (ii) can be written as,

$$2i_2 + i_1 = 2$$

or, $2i_{b2} + i_{b1} = 2$

and $5i_1 + 2i_2 = 2$

or, $5i_{b1} + 2i_{b2} = 2$


Thus,

$$i_{b3} = i_1 + i_2$$

$$2i_{b2} + i_{b1} = 2$$

$$5i_{b1} + 2i_{b2} = 2$$

1.2

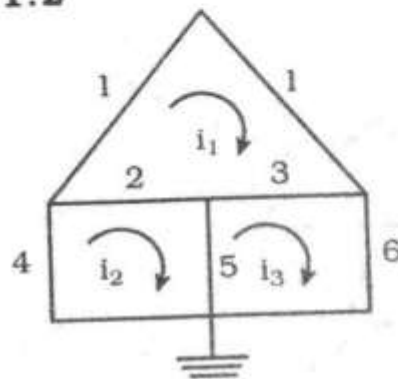

Given, branch resistance,

$$R_{b1} = 2, R_{b2} = 2, R_{b3} = 3, R_{b4} = 4$$

$$R_{b5} = 5, R_{b6} = 6 \text{ ohms}$$

6 The Solution of Alternating Current Circuits

Using mesh analysis.

Mesh-1

$$i_1 (2 + 2 + 2 + 3) + i_2 (-2) + i_3 (-3) = E_1$$

or, $i_1 (9) + i_2 (-2) + i_3 (-3) = e_{s1} + e_{s2} + e_{s3}$

Mesh-2

$$i_1 (-2) + i_2 (4 + 5 + 2) + i_3 (-5) = E_2$$

or, $i_1 (-2) + i_2 (11) + i_3 (-3) = e_{s4} + e_{s5} - e_{s2}$

Mesh-3

$$i_1 (-3) + i_2 (-5) + i_3 (3 + 5 + 6) = E_3$$

or, $i_1 (-3) + i_2 (-5) + i_3 (14) = e_{s6} - e_{s5} - e_{s3}$

Thus,

$$i_1 (9) + i_2 (-2) + i_3 (-3) = e_{s1} + e_{s2} + e_{s3}$$

$$i_1 (-2) + i_2 (11) + i_3 (-5) = e_{s4} + e_{s5} - e_{s2}$$

and, $i_1 (-3) + i_2 (-5) + i_3 (14) = e_{s6} - e_{s5} - e_{s3}$

Number of branch and node (total).

$$b = 37$$

$$\text{and } n_t = 4$$

where,

$$n = (n_t - 1)$$

$$= (4 - 1) = 3$$

and $l = 3$ independently.

(b)

Using mesh analysis,

Mesh-1


$$i_1 (1 + 1 + 1 + 1) + i_2 (-1) + i_3 (-1) = e_s$$

Mesh-2

$$i_1 (-1) + i_2 (1 + 2 + 3) + i_3 (-3) = 0$$

Mesh-3
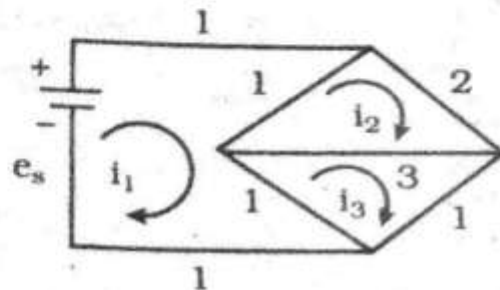
$$i_1 (-1) + i_2 (-3) + i_3 (3 + 1 + 1) = 0$$



Simplifying,

$$i_1 (4) + i_2 (-1) + i_3 (-1) = e_5$$

$$i_1 (-1) + i_2 (6) + i_3 (-3) = 0$$

and, $i_1 (-1) + i_2 (-3) + i_3 (5) = 0$

$$(c) \quad i_1 = \frac{\begin{vmatrix} e_5 & -1 & -1 \\ 0 & 6 & -3 \\ 0 & -3 & 5 \end{vmatrix}}{\begin{vmatrix} 4 & -1 & -1 \\ -1 & 6 & -3 \\ -1 & -3 & 5 \end{vmatrix}} = \frac{e_5 (30 - 9)}{67} = \frac{e_5 21}{67}$$

$$\therefore \frac{i_1}{e_5} \text{ or } i_1 \text{ per } e_5 = \frac{21}{67}$$

$$i_1 = -2.5$$

$$i_2 = -1$$

$$i_3 = -1.07$$

So, $i_{3r} = i_2 - i_3$
 $= 0.07 \text{ amp}$

1.4

(a) Mesh-1

$$i_1 (1 + 2 + 1 + 1) + i_2 (-2) + i_3 (-1) = 8$$

or, $i_1 (5) + i_2 (-2) + i_3 (-1) = 0$

Mesh-2

$$i_1 (-2) + i_2 (1 + 2 + 3) + i_3 (-3) = 0$$

or, $i_1 (-2) + i_2 (6) + i_3 (-3) = 0$

Mesh-3

$$i_1 (-1) + i_2 (-3) + i_3 (3 + 1 + 1) = 0$$

or, $i_1 (-1) + i_2 (-3) + i_3 (5) = 0$

Thus,

$$i_1 (5) + i_2 (-2) + i_3 (-1) = 8$$

$$i_1 (-2) + i_2 (6) + i_3 (-3) = 0$$

$$i_1 (-1) + i_2 (-3) + i_3 (5) = 0$$

So, $i_1 = +2.5 \text{ amp}$

$$i_2 = +1.56 \text{ amp}$$

$$i_3 = +1.43 \text{ amp}$$

$$\therefore \text{total current } i_1 = +2.5 \text{ amp}$$

(b) Power delivered = $8 \times 2.5 = 20 \text{ amp}$

$$\begin{aligned} \text{(c) } i_{3\Omega} &= 1.43 - 1.56 \\ &= +0.13 \text{ amp} \end{aligned}$$

1.5

$$\begin{aligned} \text{Here, } b &= 8 \\ n_t &= 5 \\ n &= n_t - 1 = 4 \end{aligned}$$

$$\text{and } l = 3$$

(b) Number of unknown = number of equation

To make this above equation correct, sufficient data must be given.

$$\begin{aligned} \text{(c) } m_1 &\rightarrow i_1 (1 + 1 + 1) + i_2 (-1) + i_3 (-1) = 0 \quad [\text{m represents mesh}] \\ m_2 &\rightarrow i_1 (-1) + i_2 (2 + 1 + 1 + 1) + i_3 (1) = 0 \\ m_3 &\rightarrow i_1 (-1) + i_2 (1) + i_3 (1 + 1 + 1 + 1) = 0 \end{aligned}$$

Thus,


$$i_1 (3) + i_2 (-1) + i_3 (-1) = 0$$

$$i_1 (-1) + i_2 (5) + i_3 (1) = 0$$

$$\text{and, } i_1 (-1) + i_2 (1) + i_3 (4) = 0$$

$$R_{\text{matrix}} = \begin{vmatrix} 3 & -1 & -1 \\ -1 & 5 & 1 \\ -1 & 1 & 4 \end{vmatrix}$$

determinant of $R_{\text{matrix}} = 50$

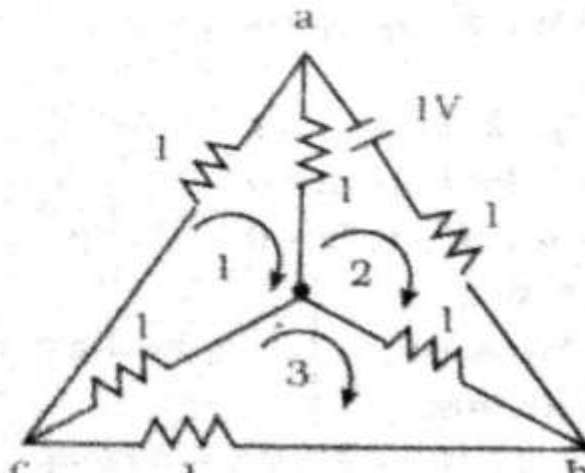1.6 Draw yourself.**1.7 Draw Yourself.****1.8**

Mesh-1

$$(a) i_1 (1 + 1 + 1) + i_2 (-1) + i_3 (-1) = 0$$

Mesh-2

$$i_1 (-1) + i_2 (1 + 1 + 1) + i_3 (-1) = 1$$

Mesh-3

$$i_1 (-1) + i_2 (-1) + i_3 (1 + 1 + 1) = 0$$

Thus, $i_1 (3) + i_2 (-1) + i_3 (-1) = 0$

$$i_1 (-1) + i_2 (3) + i_3 (-1) = 1$$

and, $i_1 (-1) + i_2 (-1) + i_3 (1 + 1 + 1) = 0$

$$i_1 = 0.25$$

$$i_2 = 0.5$$

$$i_3 = 0.25$$

(b) The answer is intuitive.

1.9 Mesh-1


$$(a) i_1 (1 + 2 + 3) + i_2 (-3) + i_3 (-2) = e_{s1}$$

Mesh-2

$$i_1 (-3) + i_2 (1 + 2 + 3) + i_3 (-2) = 0$$

Mesh-3
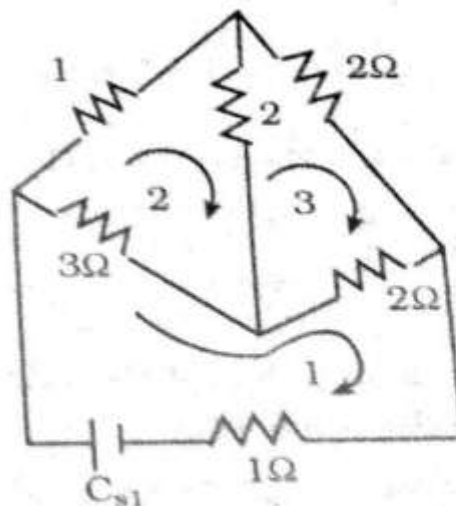
$$i_1 (-2) + i_2 (-2) + i_3 (2 + 2 + 2) = 0$$



Thus,

$$i_1 (6) + i_2 (-3) + i_3 (-2) = e_{s1}$$

$$i_1 (-3) + i_2 (6) + i_3 (-2) = 0$$

and $i_1 (-2) + i_2 (-2) + i_3 (6) = 0$

10 The Solution of Alternating Current Circuits

$$(b) R_{mat} = \begin{vmatrix} 6 & -3 & -2 \\ -3 & 6 & -2 \\ -2 & -2 & 6 \end{vmatrix} = 90$$

1.10 Mesh-1

$$i_1 (1 + 2 + 2 + 1) + i_2 (-1) + i_3 (-2) = e_{s1}$$

Mesh-2

$$i_1 (-1) + i_2 (3 + 2 + 2 + 1) + i_3 (2) = e_{s1}$$

Mesh-3

$$i_1 (-3) + i_2 (2) + i_3 (1 + 2 + 3 + 2) = 0$$

Thus,

$$i_1 (6) + i_2 (-1) + i_3 (-2) = e_{s1}$$

$$i_1 (-1) + i_2 (8) + i_3 (2) = e_{s1}$$

$$\text{and } i_1 (-3) + i_2 (2) + i_3 (8) = 0$$

11. (a)

Mesh-1

$$i_1 (1 + 1 + 1 + 1) + i_2 (1 + 1 + 1) + i_3 (1 + 1) + i_4 (1 + 1) = -e_{s1} + e_{s2} = e_{s2} - e_{s1}$$

$$\text{or, } i_1 (4) + i_2 (2) + i_3 (2) + i_4 (2) = e_{s2} - e_{s1}$$

Mesh-2

$$i_1 (1 + 1) + i_2 (1 + 1 + 1) + i_3 (-1) + i_4 (-1) = e_{s2}$$

Mesh-3

$$i_1 (1 + 1) + i_2 (-1) + i_3 (1 + 1 + 1 + 1) + i_4 (1) = 0$$


Mesh-4

$$i_1 (1 + 1) + i_2 (-1) + i_3 (1) + i_4 (1 + 1 + 1) = -e_{s1}$$

$$(b) R_{matrix} = \begin{vmatrix} 4 & 2 & 2 & 2 \\ 2 & 3 & -1 & -1 \\ 2 & -1 & 4 & 1 \\ 2 & -1 & 1 & 3 \end{vmatrix}$$

$R_{determinat}$ = do yourself (use + three independent equation)

1.12 Using Nodal analysis.

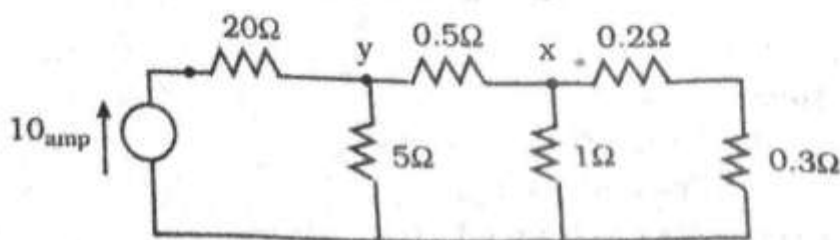

Node X,

$$v_x \left(\frac{1}{0.5} + \frac{1}{1} + \frac{1}{0.5} \right) + v_y \left(-\frac{1}{0.5} \right) = 0$$

Node Y,

$$v_x \left(-\frac{1}{0.5} \right) + v_y \left(\frac{1}{5} \right) = +10$$

So, (a) $v_x = -6.67$ volt

(b) $v_y = -16.67$ volt

1.13


$$b = 6$$

$$n_t = 3$$

$$n = n_t - 1 = 2$$

$$\therefore l = b - n = 4$$

(b)

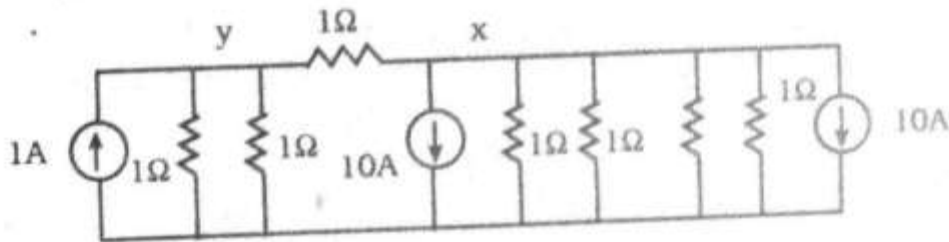

1.14

Node X

$$v_x (1 + 1 + 1) + v_y (-1) + = -1 - 10 = -11$$

$$\text{or, } v_x (3) + v_y (-1)$$

Node Y


$$v_x (-1) + v_y (1 + 1 + 1) = +1$$

$$\text{or, } v_x (-1) + v_y (3) = 1$$

$$\text{Thus, } v_x = -4$$

$$v_y = -1$$

1.15

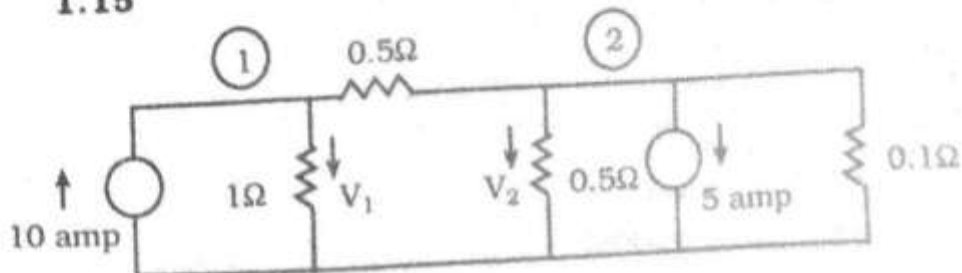

Nodal analysis :**Node-1**

$$v_1 (1 + 0.5) + v_2 (-0.5) = 10$$

Node-2

$$v_1 (0.5) + v_2 (0.5 + 0.5 + 0.1) = -5$$

$$\text{Thus, } v_1 (1.5) + v_2 (-0.5) = 10$$

$$\text{and } v_1 (-0.5) + v_2 (1.1) = -5$$

$$\text{so, } v_1 = 6.07 \text{ volt}$$

$$\text{and } v_2 = -1.785 \text{ volt}$$

1.16 The answer is intuitive and similar to number 15.**1.17**

from fig 30 (a)

$$v_1' = v_2'$$

$$I = i_{11} = 1.6 \text{ amp}$$

$$v_1' = v_2'$$

$$= 1.6 \times (1 + 0.6)$$

$$= (1.6)^2 = 2.56 \text{ volt}$$

from fig 30 (c)

$$v_1''' = 1 \text{ v}$$

$$v_1''' (-0.5) + v_2''' (0.5 + 0.6)$$

$$= -1.21$$

$$= 0.6$$

$$v_1''' (-0.5) + v_2''' (1.1)$$

$$v_2''' (1.1) = 1.1$$

$$v_2''' = 1 \text{ v}$$

from fig 30 (e)

$$v_1^v = v_2^v = 0$$

$$\text{So, } v_1 = v_1' + v_1'' + v_1''' + v_1^{iv} + v_1^v$$

$$= 2.56 - 1.1 + 0 + 0$$

$$= 1.46 \text{ volt}$$

$$v_2 = v_2' + v_2'' + v_2''' + v_2^{iv} + v_2^v$$

$$= 2.56 - 2.1 + 1 + 0 + 0$$

$$= 1.46 \text{ volt}$$

1.18 Draw yourself

from fig 30 (b)

$$v_1'' - v_2'' = 1 \text{ - (i)}$$

$$v_1'' (1 + 0.5) + v_2'' (-0.5)$$

$$= -0.6$$

so, $v_1'' = -1.1 \text{ volt}$

$$v_2'' = -2.1 \text{ volt}$$

from fig 30 (d)

$$v_1^{iv} = 0 \quad -1_{22}$$


$$v_1^{iv} (-0.5) + v_2^{iv} (0.5 + 0.6)$$

$$= -1.1$$

$$v_2^{iv} = \frac{-1.1}{1.1} = -1 \text{ vo}$$

from fig 30 (f)

$$v_1^{vi} = v_2^{vi} = 0$$

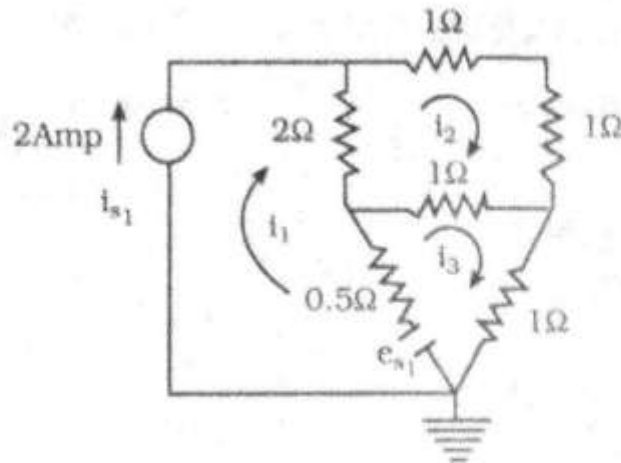1.20 Draw yourself**1.21****Mesh-1**

$$i_1 = 2 \text{ amp}$$

Mesh-2

$$i_1 (-2) + i_2 (2 + 1 + 1) + i_3 (-1\Omega) = +e_{s2}$$

$$\text{or, } i_1 (-2) + i_2 (4) + i_3 (-1) = 2$$

Mesh-3

$$i_1 (-0.5) + i_2 (-1) + i_3 (1 + 0.5) = -e_{s2}$$

Thus,

$$i_1 (-2) + i_2 (4) + i_3 (-1) = 2$$

$$\text{or, } i_2 (4) + i_3 (-1) = 6$$

$$\text{and } i_1 (-0.5) + i_2 (-1) + i_3 (1.5) = -2$$

$$i_2 (-1) + i_3 (1.5) = -1$$

$$\text{so, } i_2 = 1.6 \text{ A and } i_3 = 0.4 \text{ A}$$

$$V_a = (1 + 1) i_2$$

$$= 2 \times 1.6$$

$$= 3.2 \text{ Volts.}$$


(b)

$$\begin{aligned}
 &= \sum_{n=-\infty}^{\infty} c_n e^{jn\omega_0 t} \\
 &= \sum_{n=-\infty}^{\infty} \left[\frac{5}{-j3\pi} (e^{-j3\pi} - 1) + \left(\frac{-5}{2\pi} \right) \times \frac{1}{-3j} (e^{-6\pi j} - e^{j3\pi}) \right] \times e^{jnt}
 \end{aligned}$$

(c) Do yourself

6.10 (a) Same to number 9.

6.11.

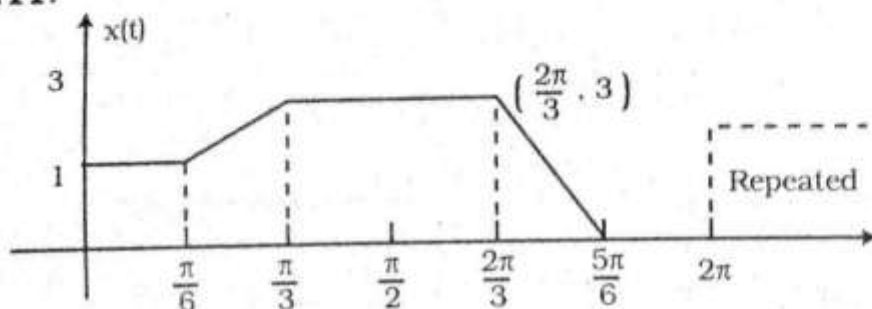

$$\begin{aligned}
 c_n &= \frac{1}{2\pi} \int_0^{2\pi} x(t) e^{-jnt} dt \\
 &= \frac{1}{2\pi} \left[\int_0^{\pi/6} e^{-jnt} dt + \int_{\pi/6}^{2\pi/3} \left(\frac{2}{\pi/3} t \right) e^{-jnt} dt + \int_{2\pi/3}^{5\pi/6} 3e^{-jnt} dt \right. \\
 &\quad \left. + \int_{5\pi/6}^{2\pi} \left[\frac{18}{\pi} (t - 2\pi/3) + 3 \right] dt \right]
 \end{aligned}$$

As these integrations are easier to do and can be evaluated by by parts formula, try yourself.

6.12 Not important

6.13 Not important

6.14

$$\begin{aligned}
 V &= 4 \sin \omega t - 3 \cos \omega t - 7.66 \sin 2 \omega t + 6.43 \cos 2 \omega t \\
 &\quad - 2 \sin 3 \omega t - 1.5 \cos 3 \omega t \\
 &= \sqrt{4^2 + 3^2} \sin (\omega t - \tan^{-1} 4/3) - \sqrt{(7.66)^2 + (6.43)^2} \\
 &\quad \sin (2 \omega t - \tan^{-1} \frac{7.66}{6.43}) - \sqrt{2^2 + 1.5^2} \sin (3 \omega t + \tan^{-1} 2/1.5) \\
 &= 5 \sin (\omega t - 53.13) - 10 \sin (2 \omega t - 49.98) \\
 &\quad - 2.5 \sin (3 \omega t + 53.13)
 \end{aligned}$$

Chapter-2 Instantaneous Current, Voltage, and Power

2.1

(a) Frequency,

$$f = \frac{PN}{120} = \frac{10 \times 360}{120} = 30 \text{ Hz}$$

Here given,

$$\begin{aligned} \text{Pole } P &= 10 \\ N &= 360 \text{ rpm} \end{aligned}$$

(b) Here,

$$f = \frac{PN}{120}$$

$$N = \frac{120f}{P}$$

For $f = 25 \text{ Hz}$
 $N = 500 \text{ rpm}$
 $f = 60 \text{ Hz}$
 $N = 1200 \text{ rpm}$

$f = 30 \text{ Hz}$
 $N = 60 \text{ rpm}$

$f = 50 \text{ Hz}$
 $N = 1000 \text{ rpm}$

2.2 Here,

$$f = \frac{PN}{120}$$

$$\begin{aligned} P &= \frac{120f}{N} \\ &= \frac{120 \times 50}{300} \\ &= 20 \text{ poles} \end{aligned}$$

2.3 Here,

$$\begin{aligned} \omega_e &= 2\pi f \\ &= 314.159 \text{ rad/sec} \end{aligned}$$

This is the electrical angular velocity.

$$\begin{aligned} \omega_m &= 2\pi \times \frac{N}{60} \\ &= 31.41 \text{ rad/sec} \end{aligned}$$

2.4 Here,

$$i = i_m \sin(\omega t + \theta)$$

where, at $t = 0$, $i = 1.5 \text{ A}$, $i_{\max} = 1.732$ and $f = 1591 \text{ KHz}$

$$\begin{aligned} \text{so, } 1.5 &= 1.732 \sin(2\pi \times 1591 \times 10^3 \times 0 + \theta) \\ &= 1.732 \sin\theta \end{aligned}$$

$$\therefore \sin\theta = \frac{1.5}{1.732} = 0.866$$

$$\theta = 60.0029 \approx 60^\circ$$

2.5 If we express the sine wave described in the question,

$$i = i_{\max} \sin(2\pi \times 50 \times t + \theta)$$

where, $i_{\max} = 10 \text{ amp}$

$$\text{so, } i = 10 \sin(100\pi t + \theta)$$

(i) Angular velocity $\omega = 2\pi f = 2\pi \times 50 = 100\pi \text{ rad/sec}$

2.6 If we express the sine wave described in the question.

$$i = i_{\max} \sin (2\pi ft + \theta)$$


$$= 10 \sin (2\pi \times ft + \theta) = 10 \sin (377t + \theta)$$

where, $\omega = 377 \text{ rad/s}$ and $i_{\max} = 10 \text{ amp}$

$$\text{frequency } f = \frac{\omega}{2\pi} = \frac{377}{2\pi} = 60.0014 = 60 \text{ Hz}$$

2.7

(a)

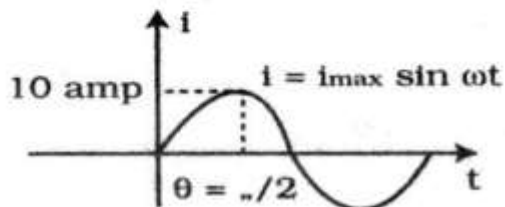

letting, $\theta = 0^\circ$

$$\text{so, } i = i_{\max} \sin \left(\omega t - \frac{\pi}{2} \right)$$

$$= 10 \sin \left(\omega t - \frac{\pi}{2} \right)$$

(b) Here,

$$i = 10 \sin (\omega t + \theta)$$

$$-5 = 10 \sin (314.15t + \theta)$$

$$\text{so, } \sin \theta = -0.5$$

$$\theta = -30 = -\frac{\pi}{6}$$

$$\therefore i = 10 \sin (314.15t - \pi/6)$$

2.8 Given,

$$e = 100 \sin 157t \text{ volt}$$

(a) maximum value = 10

$$(b) \text{ frequency} = \frac{157}{2\pi} = 25 \text{ Hz}$$

(c) for $e = 100 \sin (157t + 130)$

maximum value = 100

$$\text{frequency} = \frac{157}{2\pi} = 25 \text{ Hz}$$

2.9 Page 51, oscillogram 1

$$T = \frac{1}{60} \text{ and rate of change of voltage} = \frac{dv}{dt}$$

Here,

$$v = -140 \sin(377t)$$

$$\text{so, } \frac{dv}{dt} = -140 \times 377 \cos 377t$$

$$= -52780 \cos 377t$$

So the maximum ROC of voltage = 52780

Thus the minimum ROC of voltage = -52780

2.10 Given,

$$i = 10 \sin(\omega t - 30^\circ) \quad \dots \quad (i)$$

$$\text{so, } \frac{di}{dt} = 10 \times \omega \cos(\omega t - 30^\circ)$$

$$\text{at } t = t, 3265 = 10 \times 377 \cos(377t - 30^\circ)$$

$$\text{or, } 30^\circ = (377t)^\circ - 30^\circ \text{ and } \omega t = 60^\circ$$

$$\text{or, } \frac{\pi}{6} = 377t - \frac{\pi}{6}$$

$$\text{or, } t = 2.77 \times 10^{-3}$$

From equation (i)

$$i = 10 \sin(60^\circ - 30^\circ)$$

$$= 5 \text{ amp}$$

(b) for $i = 2000$ amp

$$i = i_{\max} \sin(\omega t - 30^\circ)$$

$$\text{or, } \frac{di}{dt} = i_{\max} \times \omega \cos(\omega t - 30^\circ)$$

$$\text{or, } 2000 = 10 \times 377 \cos(377t - 30^\circ)$$

$$\text{or, } \cos(377t - 30^\circ) = 0.599$$

$$\text{or, } 377t - 30^\circ = 53.167^\circ$$


$$\text{so, } i = 10 \sin 53.167 = 8 \text{ amp}$$

2.11

$$i = I_m \sin(\omega t + \theta)$$

$$\frac{di}{dt} = I_m \frac{d}{dt} \sin(\omega t + \theta)$$
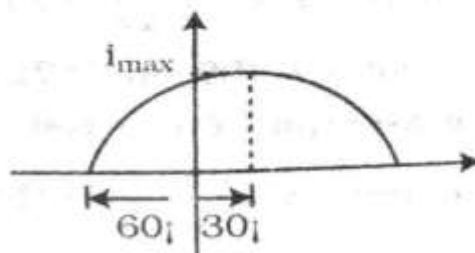
$$= I_m \times \omega \cos(\omega t + \theta)$$



$$\frac{di}{dt} = I_m \times 2\pi \times 50 \cos(2\pi \times 50 \times t + \theta)$$

Where at $t = 30^\circ$ phase shift of value zero.

$$\frac{di}{dt} = 2000$$

$$\theta = 30^\circ$$

$$\text{so, } 2000 = I_m \times 2\pi \times 50 \cos (2\pi \times 50 \times 0 + 30^\circ)$$

$$\text{or, } 2000 = I_m \times 315 \cos 30^\circ$$

$$\text{or, } I_m = 7.33 \text{ amp}$$

2.12

$$v = 100 \sin (\omega t - 30^\circ) \text{ phase} = \omega t - 30^\circ$$

$$\text{and } i = 10 \sin (\omega t - 60^\circ) \text{ phase} = \omega t - 60^\circ$$

$$\therefore \text{ phase difference} = \omega t - 30^\circ - \omega t + 60^\circ$$

$$= 30^\circ$$

[Tips, take voltage as reference or vice versa.]

So the voltage leads the current by 30° .

2.13

$$v = 100 \cos (\omega t - 30^\circ)$$

$$i = 10 \sin (\omega t - 60^\circ)$$

Here,

$$\phi_v - \phi_i = \omega t - 30^\circ + \omega t + 60^\circ$$

$$= 30^\circ$$

so v leads i or i lags v .

2.14 Given,

$$\text{voltage } v = 100 \cos \omega t$$

$$i_{\max} = 10 \text{ amp}$$

$$\text{A cycle} = 2\pi \text{ radian} \quad [\text{Tips : cos should be reference}]$$

$$\frac{1}{6} \text{ cycle} = \frac{\pi}{3} \text{ radian}$$


$$\text{so, } i = i_{\max} \cos (\omega t + 60^\circ)$$

$$= 10 \cos (\omega t + 60^\circ)$$

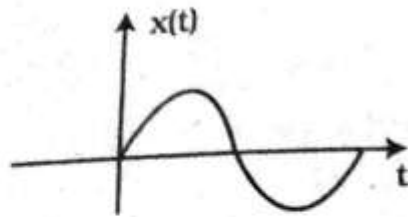
2.15 (a) $x(t) = K \sin (2\pi ft)$

$$f_s = 2\frac{f}{3}$$

Then the sampled signal has period
discrete signal.




After sampling (approximately)

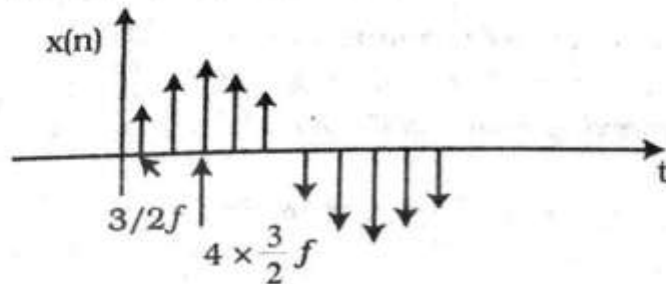

(b) Do yourself.

Tips : For one cycle

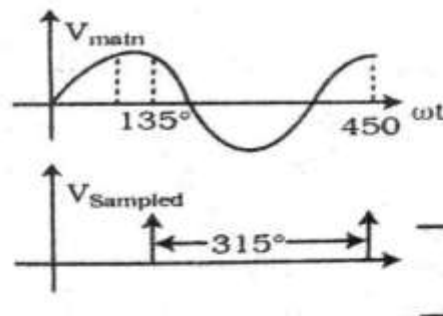

2.16

Given,

$$I_{max} = 90 \text{ amp}$$

$$\omega t_1 = 60^\circ$$

$$= \frac{\pi}{3}$$

$$\text{or, } t_1 = \frac{\pi}{3 \times 2\pi \times 50}$$

$$= 0.0033 \text{ sec}$$

$$\text{for } \omega t_2 = 225^\circ$$

$$\text{or, } t_2 = \frac{225 \times \pi}{180 \times 2\pi \times 50} = 0.0125$$

$$\therefore t_2 - t_1 = 0.0125 - 0.0033 = 0.0092 \text{ sec}$$

Ans : The difference between 60° and 225° is -0.0092 sec .

Finding instantaneous value of this sinusoidal a.c.,

$$i = 90 \sin 60^\circ$$

$$= 90 \times \frac{\sqrt{3}}{2} = 77.94 \text{ amp}$$

2.17

Given,

$$i = 1 + 0.50 \sin 1885t - 0.1 \cos 3770t \text{ amp}$$

$$\text{or } i = 1.0 + 0.5 \sin \alpha - 0.1 \cos 2\alpha \text{ amp}$$

where $\alpha = 1885t$ radians if t is expressed in seconds.

(a) Sine wave :

$$\omega = 2\pi f$$

$$1885 = 2\pi f$$

$$f = 300 \text{ Hz}$$

Cosine wave :

$$\omega = 2\pi f$$

$$3770 = 2\pi f$$

$$f = 600 \text{ Hz}$$

(b) When,

$$\sin \alpha = 1$$

$$\therefore \alpha = \frac{\pi}{2}$$

we have,

$$i = 1.0 + 0.5 \sin \frac{\pi}{2} - 0.1 \cos \pi = 1.6 \text{ amp}$$

when,


$$\sin \alpha = -1$$

$$\therefore \alpha = -\frac{\pi}{2}$$


we have,

$$i = 1 + 0.50 \sin \left(-\frac{\pi}{2}\right) - 0.1 \cos (-\pi) = 0.6 \text{ amp}$$

(c)

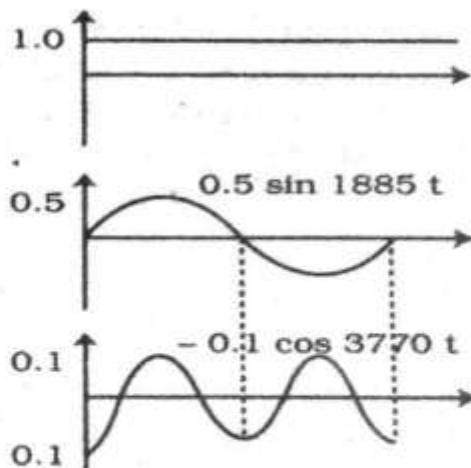

Combining graph, (approximately)

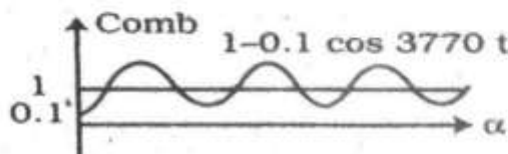

2.18 Given,

$$v = 150 \cos 314t \text{ and } R = 30 \text{ ohms}$$

$$(a) \quad i = \frac{150}{30} \cos 314t = 5 \cos 314t$$

$$(b) \quad f = \frac{\omega}{2\pi} = \frac{314}{2\pi} = 50 \text{ Hz}$$

$$(c) \quad P = vi = 150 \cos 314t \times 5 \cos 314t \\ = 750 \cos^2 314t$$

$$= \frac{1}{2} (1 + \cos 2 \times 314t) \times 750 \quad [\text{Tips : Simplification is important in EEE}]$$

$$= 375 + 375 \cos 628t \text{ watts}$$

(d) Frequency of power variation,

$$f = \frac{\omega}{2\pi} = \frac{628}{2\pi} = 100 \text{ Hz}$$

2.19 Given,

$$i = 5 \sin (110t + 30^\circ) \quad \text{and } R = 20 \Omega$$

$$(a) \quad v = 5 \sin (110t + 30^\circ) \times 20 = 100 \sin (110t + 30^\circ) \text{ v}$$

$$(b) \quad f_v = \frac{110}{2\pi} = 17.5 \text{ Hz}$$

$$(c) \quad P = vi = 100 \sin (110t + 30^\circ) \times 5 \sin (110t + 30^\circ) \\ = 500 \sin_2 (110t + 30^\circ)$$

$$= 250 \times 2 \sin^2 (110t + 30^\circ)$$

$$= 250 \times [1 - \cos 2 (110t + 30^\circ)]$$

$$= 250 \times [1 - \cos (220t + 60^\circ)]$$

$$= 250 - 250 \cos (220t + 60^\circ)$$

$$(d) \quad f_p = \frac{220}{2\pi} = \frac{220}{2\pi} = 35 \text{ Hz}$$

2.20 Given,

$$v = 100 \cos (\omega t + 60^\circ), \quad R = 10 \Omega$$

$$(a) \quad i = \frac{100}{10} \cos (\omega t + 60^\circ) = 10 \cos (\omega t + 60^\circ)$$

$$(b) \quad p = vi = 100 \cos (\omega t + 60^\circ) \times 10 \cos (\omega t + 60^\circ) \\ = 1000 \cos^2 (\omega t + 60^\circ)$$

$$= 500 \times 2 \cos^2 (\omega t + 60^\circ)$$

$$= 500 \times [1 + \cos 2 (\omega t + 60^\circ)]$$

$$= 500 + 500 \cos (2\omega t + 120^\circ) \text{ watts}$$

(c) Maximum power, when $\cos(2\omega t + 120^\circ) = 1$


$$\therefore P_{\max} = 500 + 500 = 1000 \text{ watts}$$

(d) Minimum power, when $\cos(2\omega t + 120^\circ) = -1$

$$P_{\min} = 500 - 500 = 0 \text{ watts.}$$

$$(e) P_{\text{av}} = \frac{V_m I_m}{2} \cos \theta = \frac{100 \times 10}{2} \cos \theta \quad \begin{array}{l} \text{[where } \theta = 0^\circ \\ \text{means phase shift} \\ \text{= 0]} \end{array}$$

$$= 500 \text{ watts}$$

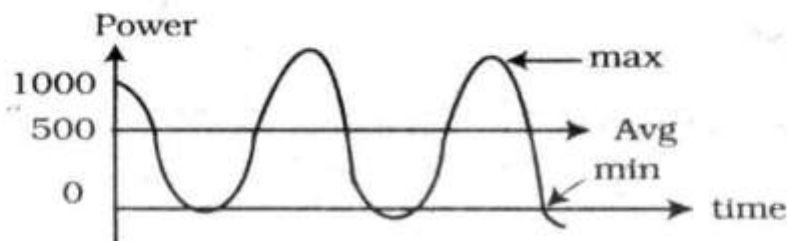

2.21 Given, $i = 10 \sin 377t$

$$(a) \frac{di}{dt} = 10 \times 377 \cos 377t$$

\therefore maximum value = $10 \times 377 = 3770$ amp
when, $\cos 377t = 1$

$$(b) X_L = \omega L \text{ where inductance } L = 100 \text{ mH}$$

$$= 377 \times 100 \times 10^{-3} = 37.7 \Omega$$

$$\therefore V_{\max} = I_{\max} X_L = 10 \times 37.7 = 377$$

So voltage equation,

$$v = 10 \times 37.7 \sin(377t + 90^\circ) = 377 \sin(377t + 90^\circ)$$

where, $V_{\max} = 377$ volt

2.22 Given, $v = -150 \sin 377t = 150 \sin(377t + 180^\circ)$

$$\text{and } i = 10 \cos 377t = 10 \sin(377t + 90^\circ)$$


As voltage angle differs from the current angle ($180^\circ - 90^\circ$) or 90°

So voltage leads current by 90° .

From the definition of inductive circuit, the impedance is inductive.

$$\therefore \text{impedance function, } \frac{150}{10} \angle 90 = 15 \angle 90$$
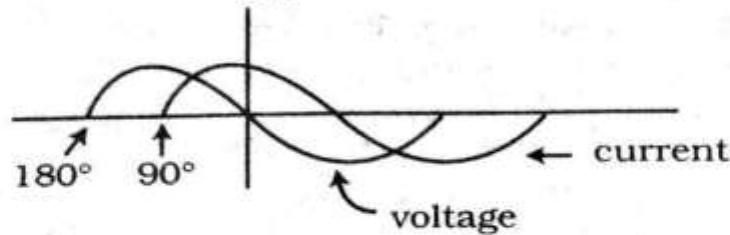
$$\text{Now, } 377L = 15, L = \frac{15}{377} = 0.0398 \text{ henry}$$



2.23 Given,

$$v = 100 \sin (377t + 30^\circ)$$

$$L = 0.025654 \text{ H}$$

$$\text{so, } x_L = \omega L = 377 \times 0.02654 = 10 \Omega$$

$$\text{(a) Current, } v = ix_L$$

$$i = \frac{v}{x_L} = \frac{100}{10} \sin (377t + 30^\circ - 90^\circ)$$

[From the definition, currents lag from voltage.]

$$= 10 \sin (377t - 60^\circ)$$

$$\text{(b) } P = v_i = (377t + 30^\circ) \times 10 \sin (377t - 60^\circ)$$

$$= -1000 \sin (377t + 30^\circ) \cos (377t - 60^\circ + 90^\circ)$$

$$= -1000 \sin (377t + 30^\circ) \cos (377t + 30^\circ)$$

$$= -500 \sin 2(377t + 30^\circ)$$

$$= -500 \sin (754t + 60^\circ)$$

$$\text{(c) } P_{av} = -\frac{v_m I_m}{2} \cos \theta = \frac{100 \times 10}{2} \cos 90^\circ = 0 \text{ watts}$$

$$\text{(d) } P = -500 \times 754 \cos (754t + 60^\circ)$$

finding differentiation,

$$\frac{dp}{dt} = -500 \times 754 \cos (754t + 60^\circ)$$

finding maximum value,

$$\left(\frac{dp}{dt} \right) = 0 \text{ so, } \cos (754t + 60^\circ) = 0$$

$$\text{(e) Energy stored} = \frac{v_m I_m}{2\omega} = \frac{100 \times 10}{2 \times 377} = 1.326 \text{ joule}$$

2.24 Given, $i = 5 \sin 300t$

$$\text{(a) Impedance function is } 300 \times 0.2 \angle 90^\circ = 60 \angle 90^\circ$$

$$(b) P = v_i$$

where,

$$\begin{aligned} v &= 300 \sin (300t + 90^\circ) \\ &= 300 \cos 300t \quad [c] \\ &= 300 \cos 500t \times 5 \sin 300t \\ &= 1500 \sin 300t \cos 300t \\ &= 750 \sin 600t \end{aligned}$$

$$\begin{aligned} \text{Stored energy } (\omega_2) &= \int_0^{0.05} 750 \sin 600t \\ &= \frac{-750}{600} [\cos 600t]_0^{0.05} \\ &= \frac{-750}{600} \left(\frac{\sqrt{3}}{2} - 1 \right) \\ &= 0.1675 \text{ Joules} \end{aligned}$$

2.25 Given,

$$v = 200 \cos (157t + 30^\circ)$$


$$\text{and } i = 5 \sin (157t - 150^\circ)$$

$$\text{so, voltage } v = 200 \sin (157t + 30^\circ + 90^\circ)$$


$$\text{or, } v = 200 \sin (157t + 120^\circ)$$

$$i = 5 \sin (157t - 150^\circ)$$

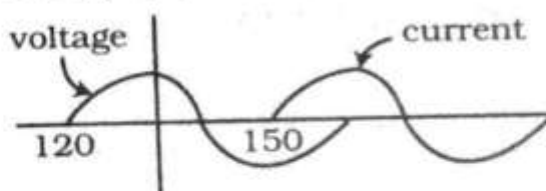Voltage is leading by $(120^\circ - (-150^\circ))$ or 270°



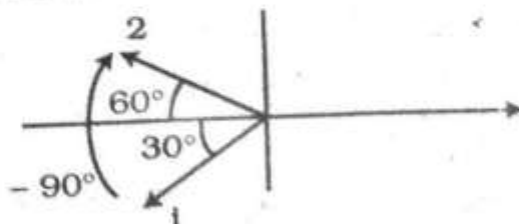Similarly it could be said as leading by -90°
Similarly it could be said as leading by 90°



$$z = \frac{200}{5} \angle -90^\circ = 40 \angle -90^\circ \text{ ohms}$$

The circuit parameter is capacitor $x_c = \frac{1}{\omega c}$

$$\text{or, } 40 = \frac{1}{157c}$$

$$\therefore c = 159.23 \times 10^{-6} \text{ F} \\ = 159.23 \mu\text{F}$$

2.26

$$v = 100 \sin 377t$$

$$c = 530.5 \mu\text{F} \text{ and } \omega = 377$$

$$x_c = \frac{106}{377 \times 530.5 \mu} = 50 \Omega$$

$$(a) \ i = \frac{100}{5} \sin(377t + 90^\circ) = 20 \sin(377t + 90^\circ)$$

$$(b) \ P = vi = 100 \sin(377t) \times 20 \sin(377t + 90^\circ) \\ = 1000 \sin 754t \text{ [using } \sin 2\theta = 2\sin\theta \cos\theta]$$

(c) ω_c (energy max in capacitor)

$$= \frac{v_m i_m}{2} = \frac{100 \times 20}{2 \times 377} = 2.65 \text{ Joules}$$


When the current is in maximum $I_m = 20$ amp
and $\omega_c = 0$ when the current $i_{\min} = 0$

2.27

$$v = 200 \sin 377t, \ x_L = \frac{200}{10} = 20 \text{ ohm}$$

$$(a) \ L = \frac{x_L}{\omega} = \frac{20}{377} = 53.05 \text{ mH}$$

$$(b) \ R_L = 20 \Omega$$

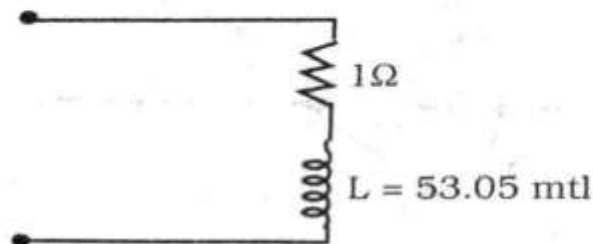


$$L = 53.05 \text{ mH}$$

$$X_{RL} = 20 \Omega$$

$$X_L = \sqrt{20^2 - 1^2} = 19.975 \Omega$$
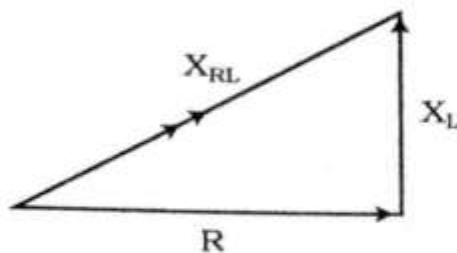
$$L = \frac{X_L}{\omega} = 52.98 \text{ mH}$$



$$\begin{cases} X_{RL} = \sqrt{R^2 + X_L^2} \\ \theta_L = \tan^{-1} \frac{X_L}{R} \end{cases}$$

In phasor form,

$$X_{RL} = R + X_L$$

[Tips : You can do the sum, multi, div and solution by using calculator.]

2.28 Given,

$$R = 10 \Omega \quad X_L = 2\pi fL = 7.854 \Omega \quad v_m = 150 \text{ v}$$

$$(a) \quad X_{RL} = \sqrt{R^2 + X_L^2} \angle \tan^{-1} \frac{X_L}{R}$$

$$= \sqrt{10^2 + 7.854^2} \angle \tan^{-1} \frac{7.854}{10}$$

$$= 12.71 \angle 38.15^\circ$$

$$(b) \quad v = 150 \sin 157t \quad [\text{An expression}]$$

$$(c) \quad i = \frac{150}{12.71} \sin (157t - 38.15^\circ) = 11.8 \sin (157t - 38.15^\circ)$$

$$(d) \quad P = \frac{11.8 \times 150}{2} \cos 38.15^\circ - 885 \cos 38.15 \cos 314t$$

$$+ 885 \sin 38.15^\circ \sin 314t$$

$$= 695.96 - 695.96 \cos 314t + 545.68 \sin 314t \text{ watts}$$

$$P_{av} = \frac{V_m I_m}{2} \cos \theta = \frac{11.8 \times 150}{2} \cos 38.15^\circ = 695.96 \text{ watts}$$


[Remember the average is always equal to dc value = a]

$$(e) \quad \text{Reactive voltampere} = \frac{V_m I_m}{2} \sin \theta = \frac{150 \times 11.8}{2} \times \sin 38.15$$

$$= 546.68 \text{ vA}$$

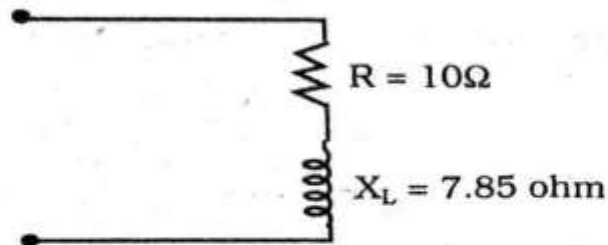2.29

$$x_{RL} = 10 + 7.85 = 12.71 \angle 38.13$$



$$(a) z_{RL} = \sqrt{R^2 + x_L^2} \angle \tan^{-1} \frac{x_L}{R} = 12.7 \angle 38.2^\circ$$

$$(b) v = 150 \sin(157t + \theta) \text{ where } \theta = \text{phasor shift}$$

$$75 = 150 \sin(157t + \theta) \text{ at } t = 0$$

$$\text{or, } \sin\theta = \frac{1}{2}$$

$$\text{or, } \theta = 30^\circ$$

$$\therefore \text{ expression } v = 150 \sin(157t + 30^\circ)$$

$$(c) \text{ As current lags the voltage by } 38.2^\circ$$

$$\therefore i = \frac{150}{12.7} \sin(157t + 30^\circ - 38.2^\circ) = 11.8 \sin(157t - 8.2^\circ)$$

$$(d) P = \frac{v_m i_m}{2} \cos\theta - \frac{v_m i_m}{2} \cos 2\omega t \cdot \cos\theta = \frac{v_m i_m}{2} \sin 2\omega t \sin\theta$$

$$= \frac{150 \times 11.8}{2} \cos 38.2 - \frac{150 \times 11.8}{2} \cos(314t - 16.2)$$

$$\cos 38.2 + \frac{150 \times 11.8}{2} \sin(314t - 16.2) \sin 38.2$$


$$= 695.48 - 695.48 \cos(314t - 16.2) + 547.29 \sin(314t - 16.2)$$

$$= 695.48 - 665.8 \cos 314t - 194.03 \sin(314t)$$

$$+ 525.56 \sin 314t - 152.69 \cos 314t$$

$$P_{av} = \frac{v_m i_m}{2} \cos\theta = \frac{150 \times 11.8}{2} \times \cos 38 =$$

695.48 watts

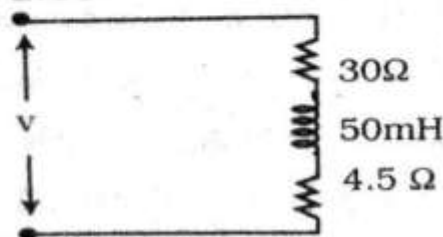2.30

$$\text{Total, } R = 34.5 \Omega$$

$$x_L = 18.85 \text{ ohm}$$

$$x_{RL} = \sqrt{34.5^2 + 18.85^2}$$

$$\angle \tan^{-1} \frac{18.85}{34.5}$$

$$= 39.31 \angle 28.65$$

(a) $i = \frac{100}{39.31} \cos(377t - 28.65)$
 $= 2.54 \cos(377t - 28.65)$

(b) $P = v_i = 100 \cos 377t \times 2.54 \cos(377t - 28.65)$
 $= 254 \cos 377t (0.87756 \cos 377t + 0.4794v \sin 377t)$

Real power = 114.9 + 114.9 cos 754t watt

Avg. power = 114.9 watts

(d) Reactive voltampere = 60.88 sin 754t

Average volue = 0 [∴ sin wave has no area under one cycle]

(e) $x_L = \omega L = 18.89 \text{ ohm}$

2.31 Given, $i = 10 \cos 157t$ $R = 15 \text{ ohms}$ and $L = 0.0637$

(a) $x_L = 0.0637 \times 157 = 10 \text{ ohm}$

$x_{RL} = \sqrt{15^2 + 10^2} \angle \tan^{-1} \frac{10}{15} = 18.03 \angle 33.69^\circ$

so, $v = 18.03 \times 10 \cos(157t + 33.69)$
 $= 180.3 \cos(157t + 33.69)$

(b) $P = v_i = \frac{180.3 \times 10}{2} \cos 33.69 - 901.5 \cos 314t \cdot \cos 33.69$
 $+ 90.15 \sin 314t \sin 33.69$
 $= 750 - 750 \cos 314t + 500 \sin 314t \text{ watts}$



2.32

(a) $x_c = \frac{106}{\omega c} = \frac{106}{2\pi \times 60 \times 8} = 331.572 \text{ ohm}$

(b) $v_c = \frac{106}{2\pi \times 6 \times 106 \times 800} = 33.157 \text{ ohm}$

2.33

$R = 151 \text{ ohm}$

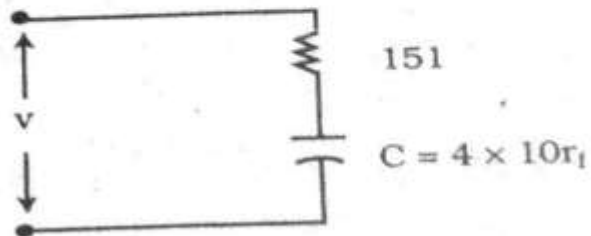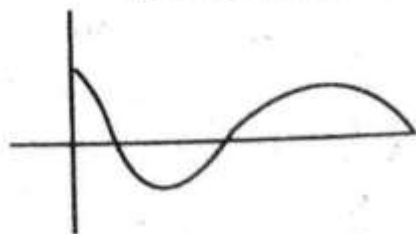

Reactance, $x_c = \frac{1}{\omega c} = (2\pi \times f \times c) = 75.58 \text{ ohm}$

28 The Solution of Alternating Current Circuits

(a) $v = 15 \cos (2\pi \times 500t) = 15 \cos 3141.6 t$

(b) $z_{RC} = \sqrt{151^2 + (-x_c)^2} \angle \tan^{-1} \frac{-x_c}{R} = 170.69 \angle -27.79^\circ$


(c) $i = \frac{15}{170.69} \cos (319.6t + 27.79)$
 $= 0.0879 \cos (314.6t + 27.79)$

(d) $P = vi = 15 \cos 3141.6t \times 0.0879 \cos (3141.6t + 27.79)$
 $= 1.3185 \cos 3141.6t (0.8847 \cos 3141.6t - 0.466 \sin$
 $\qquad\qquad\qquad v 3141.6t)$
 $= 0.583 + 0.583 \cos 6282 t - 0.307 \sin 6282t$

2.34 This theory is proved at page 68-69.

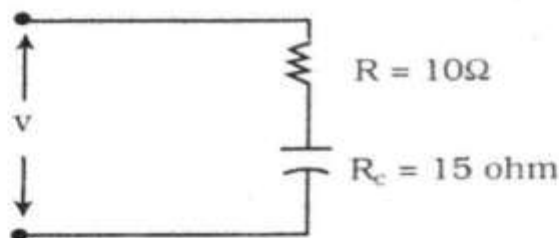2.35

$$x_c = \frac{106}{220 \times 303} = 15 \text{ ohm}$$



$$v_c = 150 \sin (220t - 60^\circ)$$

$$i = \frac{150}{15} \sin (220t - 60^\circ + 90^\circ)$$

$$= 10 \sin (220t + 30^\circ) \text{ Amp.}$$

How. $z_{RC} = \sqrt{10^2 + (-15)^2} \angle \tan^{-1} \frac{-15}{10} = 18.03 \angle -56.3$

∴ Voltage drop across the entire circuit is

$$v = 18.03 \times 10 \sin (220t + 30 - 56.3^\circ)$$

$$= 180.3 \sin (220t - 26.3^\circ) \text{ volt}$$

2.36 $x_c = \frac{v_m}{I_m} = \frac{20}{0.01} = 2000 \text{ ohm}$ $x_c = \frac{106}{\omega c}$

$$c = \frac{106}{\omega x_c} = \frac{106}{2\pi \times 2000 \times 2000} = 0.03978 \mu\text{F}$$


$$x_L = \omega L = 157 \times 0.1$$

$$= 15.7 \text{ ohm}$$

$$x_C = \frac{106}{\omega C} = \frac{106}{157 \times 200}$$

$$= 31.85 \text{ ohm}$$

2.37

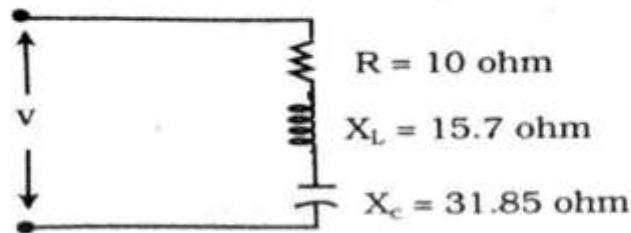

a) $i = 10 \sin 157t$,

and voltage $v = iR$
 $= 10 \times 10 \sin 157 t$
 $= 100 \sin 157 t \text{ volts}$

(b) $v_L = L \frac{di}{dt} = 0.1 \times \frac{d}{dt} (10 \sin 157 t)$
 $= 0.1 \times 10 \times 157 \cos 157t$
 $= 157 \cos 157t$

(c) $v_C = \frac{q}{C} = \int \frac{i dt}{C}$
 $= \frac{106}{C} \int 10 \sin 157t dt$
 $= \frac{106}{200} \times \frac{1}{157} \times 10 - \cos 157t$
 $= -318.5 \cos 157t$

From charging law

$$q = vC$$

$$\text{and } i = \frac{dv}{dt}$$

$$q = \int i dt$$

(d) Total voltage drop,


$$V_{\text{drop}} = v_R + v_L + v_C$$

$$= 100 \sin 157t + 157 \cos 157t + 318.5 \cos 157t$$

(e) $x_{RLC} = \sqrt{10^2 + (15.7 - 31.85)^2}$
 $= 18.99 = 19 \text{ ohm}$

2.38 This theory is proved at page 74.75.

$$2.39 \quad i = I_m \sin (t\sqrt{LC})$$

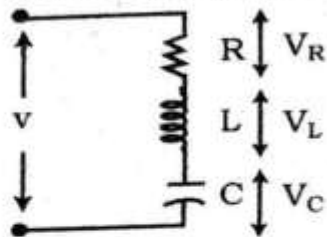

$$v_R = I_m R \sin (t\sqrt{LC})$$

$$v_L = L \frac{di_L}{dt}$$

$$= L \int I_m \sin (t\sqrt{LC}) dt$$

$$= L \sqrt{LC} I_m \cos (t\sqrt{LC})$$

$$= I_m L \sqrt{LC} \cos (t\sqrt{LC})$$

$$v_C = \frac{1}{C} \int I_m \sin (t\sqrt{LC}) dt$$

$$= -\frac{1}{C} \times I_m \times \frac{1}{\sqrt{LC}} \cos (t\sqrt{LC})$$

$$\begin{aligned} \therefore W_L &= i_L v_L \\ &= I_m \sin (t\sqrt{LC}) \times I_m \sqrt{LC} \cos (t\sqrt{LC}) \\ &= \frac{I_m^2 \sqrt{LC}}{2} \times L \sin (2t \sqrt{LC}) \end{aligned}$$


$$\begin{aligned} \text{and } W_C &= I_m \sin (t\sqrt{LC}) \times -\frac{1}{C} \times I_m \times \frac{1}{\sqrt{LC}} \cos (t\sqrt{LC}) \\ &= \frac{-I_m^2 \sin (2\sqrt{LC}t)}{2C\sqrt{LC}} \end{aligned}$$

$$\text{so, } W_L + W_C = I_m^2 \left(\frac{L\sqrt{LC}}{2} - \frac{1}{2C\sqrt{LC}} \right) \sin (2\sqrt{LC} t)$$

$$\text{When the circuit resonant at } T = \frac{1}{2\pi \sqrt{LC}} \quad \text{or } \omega = \frac{1}{\sqrt{LC}}$$

The energy stored by the capacitor will be equal to the energy supplied by the inductor and vice - versa. Thus oscillation is produced in LC circuit Versa.

2.40

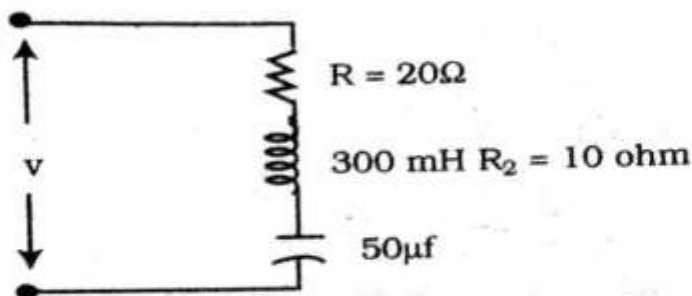

$$\begin{aligned} \text{(a) } Z_{RLC} &= \sqrt{(20 + 10)^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} \\ &= \sqrt{(30)^2 + \left(157 \times 300 \times 10^{-3} - \frac{1}{30 \times 10^{-6} \times 157}\right)^2} \\ &= 85.71 \Omega \end{aligned}$$

$$\begin{aligned} \text{(b) } i &= \frac{100 \angle -90^\circ}{20 + 10 + 47 - 1j - 127.388 j} \\ &= 1.167 \angle -20.488 \\ &= 1.167 \cos(157t - 20.488) \end{aligned}$$

$$\begin{aligned} \text{(c) } P &= vi \\ &= 100 \angle -90^\circ \times 1.167 \angle -20.488 \\ &= 116.67 \angle -110.488 \end{aligned}$$

(d) Avg power = -40.83

(e) Do yourself having experienced with previous similar mathematics.

(f) $v_R = 23.34$

2.41 $v = 282.8 \sin 500t$
and $i = 5.656 \sin(500t - 36.870)$

In phasor algebra,

$$v = 282.8 \angle 0^\circ$$

$$\text{and } i = 5.656 \angle -36.87^\circ$$

$$\begin{aligned} Z &= \frac{282.8}{5.656 \angle -36.87^\circ} \\ &= 50 \angle 36.87 \end{aligned}$$

Let it is a RLC circuit,

$$\sqrt{(x_L - x_C)^2 + R^2} \angle \tan^{-1} \frac{(-x_C + x_L)}{R}$$

$$= 50 \angle 36.8$$


$$(x_L - x_C)^2 + R^2 = 50 - 11)$$

$$\text{and } \frac{x_L - x_C}{R} = \tan 36.87$$

$$\begin{aligned} \text{where, } x_C &= \frac{1}{\omega C} = \frac{1}{500 \times 100 \mu} \\ &= 20 \Omega \end{aligned}$$

Chapter-3
Effective Current and Voltage Average Power


- 3.1** $i(10) = 20$
 $i(20) = 10$ amp

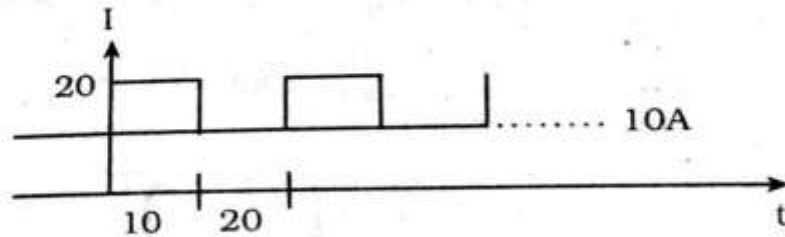

$$i_{\text{eff}} = \sqrt{\frac{20^2 \times 10 + 10^2 \times 20}{30}}$$

$$= 14.14 \text{ amp}$$

- 3.2 (a)**

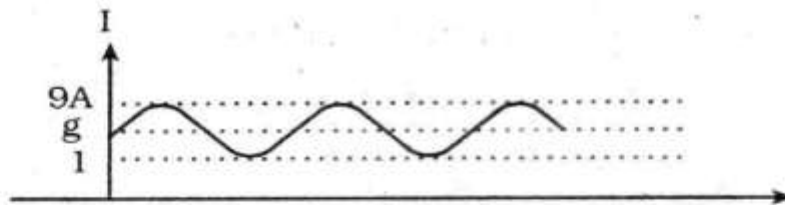

(b) $i(t) = 5 + 4 \sin \omega t$

(c) $i_{\text{avg}} = 5$ amp

(d) $i_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T (5 + 4 \sin \omega t)^2 dt}$

$$i_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T (5 + 4 \sin \omega t)^2 dt}$$

$$= \sqrt{\frac{2}{T} \int_0^T (25 + 40 \sin \omega t + 16 \sin^2 \omega t) dt}$$

$$\begin{aligned}
 &= \sqrt{\frac{2}{T} \left[25 \times \frac{T}{2} + \frac{40}{\omega} \cos \frac{\omega T}{2} - \frac{40}{\omega} + \frac{1}{2} \times 16 - \frac{16}{2 \times 2\omega} \sin 2\omega \frac{T}{2} \right]} \\
 &= \sqrt{\frac{2}{T} \left[\frac{25T}{2} + \frac{40}{\omega} (-1) - \frac{40}{\omega} + 8 - 0 \right]} \\
 &= 5.75 \text{ amp}
 \end{aligned}$$

$$\therefore i = 50t$$

$$\text{form factor} = \frac{I_{\text{rms}}}{I_{\text{avg}}}$$

$$\begin{aligned}
 I_{\text{rms}}^2 &= \frac{1}{T} \int_0^T (50t)^2 dt \\
 &= \frac{1}{3} \int_0^3 50^2 \times t^2 dt \\
 &= \frac{1}{3} \times 50^2 \times \frac{t^3}{3} \Big|_0^3 \\
 &= \frac{1}{3} \times 50^2 \times \left[\frac{3^3}{3} - 0 \right] \\
 &= \frac{1}{3} \times 50^2 \times 3^2 \\
 &= 7500
 \end{aligned}$$

$$I_{\text{rms}} = 86.60$$

$$\therefore \text{form factor} = \frac{86.60}{75} = 1.155$$

$$\begin{aligned}
 I_{\text{avg}} &= \frac{1}{T} \int_0^T 50t dt \\
 &= \frac{50}{3} \frac{t^2}{2} \Big|_0^3 \\
 &= \frac{50}{3} \times \frac{3^2}{2} \\
 &= \frac{50}{2} \times 3 \\
 &= 25 \times 3 = 75
 \end{aligned}$$

3.4 From the previous math $i_{\text{eff}} = 86.6$ amp

$$\therefore \text{crest factor} = \frac{50}{86.6} = 0.577$$

3.5 $i_1 = 5 \sin \omega t$

$$i_2 = 10 \sin(\omega t + 60^\circ)$$

$$i_2 - i_1 = 10 \sin(\omega t + 60^\circ) - 5 \sin \omega t$$

$$= 8.66 \angle 90^\circ$$

$$= 8.66 \sin(\omega t - 90^\circ)$$

3.6 $R = 5 \text{ ohm}$

$$L = \frac{10}{377}$$


$$V = V \angle 0^\circ$$

$$X_L = \omega L = 10 \Omega$$


$$I = \frac{V \angle 0^\circ}{50 + (10 - 16)j}$$

34 The Solution of Alternating Current Circuits

$$X_C = 15\Omega = \frac{V \angle 0^\circ}{50 - 5j}$$
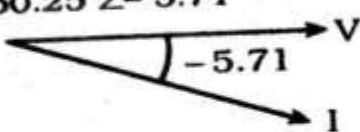
$$= \frac{V \angle 0^\circ}{50.25 \angle -5.71}$$

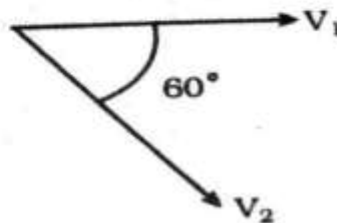
3.7 $V_1 = 100 \angle 0^\circ$
 $V_2 = 100 \angle -60^\circ$



(a) So $V = V_1 + V_2$
 $= 100 \angle 0^\circ + 100 \angle -60^\circ$
 $= 173.2 \angle 30^\circ$


(b) $V = V_1 - V_2$
 $= 100 - 100 \angle -60^\circ$
 $= 100 \angle 60^\circ$

3.8 Average current.

$$I = \sqrt{\frac{1}{60} (20 \times 15)}$$

$$= 10 \text{ amp}$$

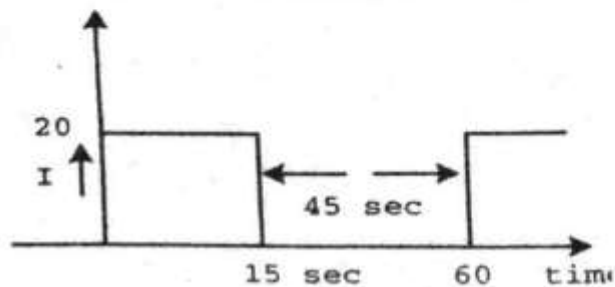[Tips : Average $x_{\text{signal}} = \frac{\text{Area (integration)}}{\text{total time}}$]



Total time period

$$T = 15 + 45 = 60 \text{ sec}$$

Let, the resistance of the elevator be R.

$$\text{so, } P = I^2 R = \frac{W}{T} = \frac{I^2 R t}{T}$$

$$\therefore I^2 = \frac{I^2 t}{T} = \frac{20^2 \times 15}{60} = 100 \text{ amp or } I = 10 \text{ amp}$$

\therefore Total work done in one cycle

$$W = I^2 R t = 20^2 \cdot R \cdot 15 \\ = 6000 R$$


$$\text{Now, } P = \frac{W}{t} = \frac{6000 R}{60} = 100R$$

Let, the equivalent continuous current be I_1

$$P = I_1^2 R = 100R$$

$$\text{or, } I_1 = 10 \text{ amp}$$

3.9

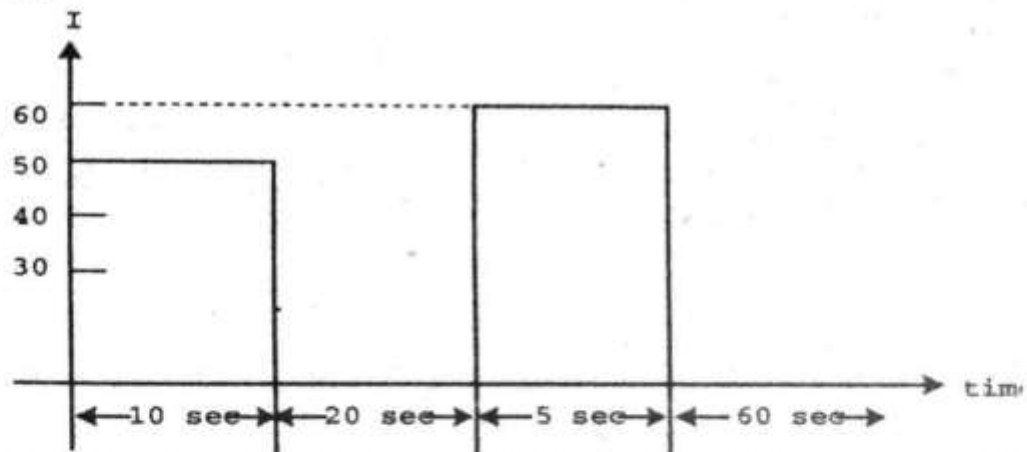

Substituting the value $x_L = (20R \tan 36.87) / 50$ equation (i)

$$(20 + R \tan 36.87 - 20)^2 + R^2 = 50$$

$$\text{or, } (0.75)^2 R^2 + R^2 = 50$$

$$\text{or, } (0.5625 + 1) R^2 = 50$$

$$\text{or, } R^2 = \frac{50}{1.5625}$$

$$\text{or, } R^2 = 32$$

$$\text{or, } R = 5.65 \Omega$$

$$\therefore \text{ Resistance } R = 5.65 \Omega$$

Now, substituting the value at

$$\begin{aligned} X_L &= 20 + R \tan 36.87 \\ &= 20 + 4.243 \\ &= 24.243 \Omega \end{aligned}$$

$$\begin{aligned} \text{so, } L &= 0.0485 \text{ H} \\ &= 48.5 \text{ mH} \end{aligned}$$

So, $R = 5.65 \Omega$, $L = 48.5 \text{ mH}$ are the rest of the circuit parameter.

Power needed until the motor gets overheated,

$$\begin{aligned} P &= \sqrt{50^2 \times 10 + 60^2 \times 5} \\ &= 207.36 \text{ watt} \end{aligned}$$

3.10 The period,

$$T = 0.3 + 0.5 + 0.4 + 0.5 + 0.3 = 2 \text{ sec}$$

(a) Average current,

$$\begin{aligned} I_{av} &= \frac{10 \times 0.3 + 0.5 \times 15 + 50 \times 0.4 + 15 \times 0.54 + 10 \times 0.3}{2} \\ &= 20.5 \text{ amp} \end{aligned}$$

$$\begin{aligned} \text{(b) } I &= \sqrt{\frac{10^2 \times 0.3 + 15^2 \times 0.5 + 50^2 \times 0.4 + 10^2 \times 0.3 + 15^2 \times 0.5}{2}} \\ &= 25.35 \text{ amp} \end{aligned}$$

3.11

(a) d.c ammeter shows the average current. So, the reading will be 20.5 A

a - c ammeter shown the effective current. So, the reading will be 25.35A

(b) a - c reading should be employed.


3.12 Energy produced in one cycle is

$$\begin{aligned} \text{(a) } I^2 R t &= 25.35^2 \times 5 \times 2 = 6426.23 \text{ Joules} \\ &= \frac{6426.23}{4.184} = 1535.9 \text{ cal} \end{aligned}$$

{ 1 cal = 4.2 Joules}

$$\text{(b) } P = I^2 R = 25.39^2 \times 5 = 3213.1 \text{ watt}$$

3.13

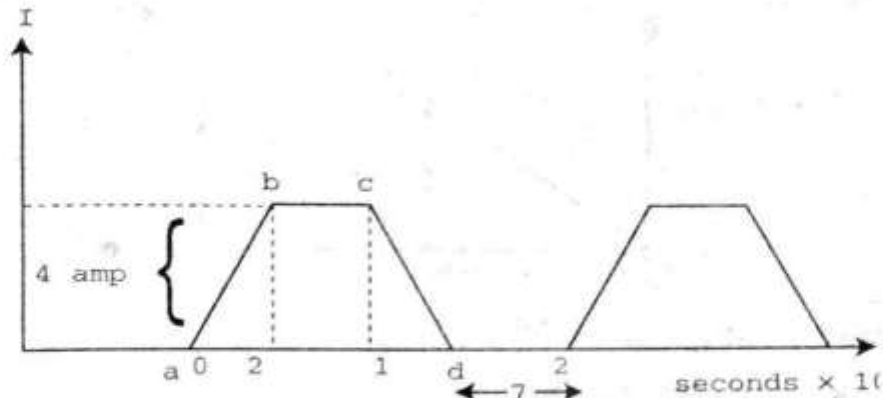

Time period $T = (2 + 1 + 217) \times 10^{-4} \text{ sec} = 12 \times 10^{-4} \text{ sec}$

(a) Frequency $n = \frac{1}{T} = \frac{1}{12 \times 10^{-4}} = 833.33 \text{ Hz}$

Eq. of the curve as is,

$$i = \frac{4}{2 \times 10^{-4}} t$$

or, $i = 2 \times 10^4 t$

From figure we see that curve cd is similar to ab.

(b)
$$I_{av} = \frac{\int_0^{2 \times 10^{-4}} 2 \times 10^4 t dt + 4 \times 1 \times 10^{-4} + \int_0^{2 \times 10^{-4}} 2 \times 10^4 t dt}{12 \times 10^{-4}}$$

$$= \frac{2 \times 2 \times 10^4 \int_0^{2 \times 10^{-4}} t dt + 4 \times 10^{-4}}{12 \times 10^{-4}}$$

$$= \frac{4 \times 10^4 \times \frac{1}{2} (2 \times 10^{-4})^2 + 4 \times 10^{-4}}{12 \times 10^{-4}}$$


$$= \frac{12 \times 10^{-4}}{12 \times 10^{-4}} = 1 \text{ amp}$$

(c)
$$I = \sqrt{\frac{2 \times \int_0^{2 \times 10^{-4}} (2 \times 10^4 t)^2 dt + 4^2 \times 10^{-4}}{12 \times 10^{-4}}}$$

$$= \sqrt{\frac{2 \times 4 \times 10^8 \times \frac{t^3}{3} \Big|_0^{2 \times 10^{-4}} + 4^2 \times 10^{-4}}{12 \times 10^{-4}}}$$

$$= \frac{\sqrt{\left(\frac{64}{3} + 16\right) \times 10^{-4}}}{12 \times 10^{-4}} = 1.76 \text{ amp}$$

3.14

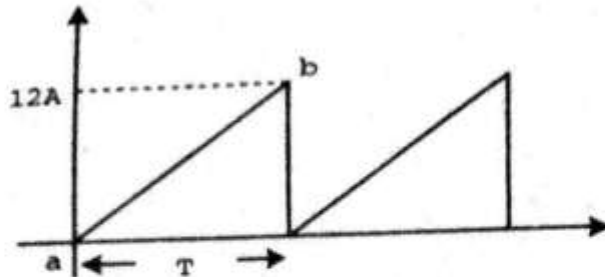

Equation of ab in $i = \frac{12}{T} t$

\therefore a - c meter reading.


$$\begin{aligned} I &= \sqrt{\frac{1}{T} \int_0^T \left(\frac{12}{T} t\right)^2 dt} \\ &= \sqrt{\frac{1}{T} \times \frac{144}{T^2} \times \frac{t^3}{3} \Big|_0^T} \\ &= \sqrt{\frac{1}{T} \times \frac{144}{T^2} \times \frac{T^3}{3}} \\ &= \frac{12}{\sqrt{3}} = 6.93 \text{ A} \end{aligned}$$

3.15 Slop = $\tan(\pi - \theta) = -\tan\theta$ equation of line ab

$$\frac{i-0}{0-10} = \frac{t-T}{T-0}$$

or, $\frac{i}{-10} = \frac{t-T}{T}$


or, $i = \frac{-10t}{T} + 10$

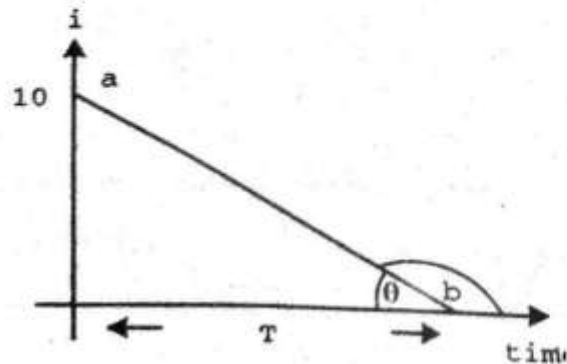

$\therefore i = \frac{-10}{T} t + 10$

$$\begin{aligned}
 I_{\text{rms}} &= \sqrt{\frac{1}{T} \int_0^T \left(\frac{100t^2}{T^2} + 2 \left(\frac{-10t}{T} \right) 10 + 100 \right) dt} \\
 &= \sqrt{\frac{1}{T} \left(\frac{100T^3}{T^2 \times 3} + 2 \left(\frac{-10}{2T} \right) 10 + 100T \right) dt} \\
 &= \sqrt{\frac{1}{T} \left(\frac{100T}{3} - 100T + 100T \right)} \\
 &= \sqrt{\frac{100}{3}} = 5.77 \text{ A}
 \end{aligned}$$

3.16

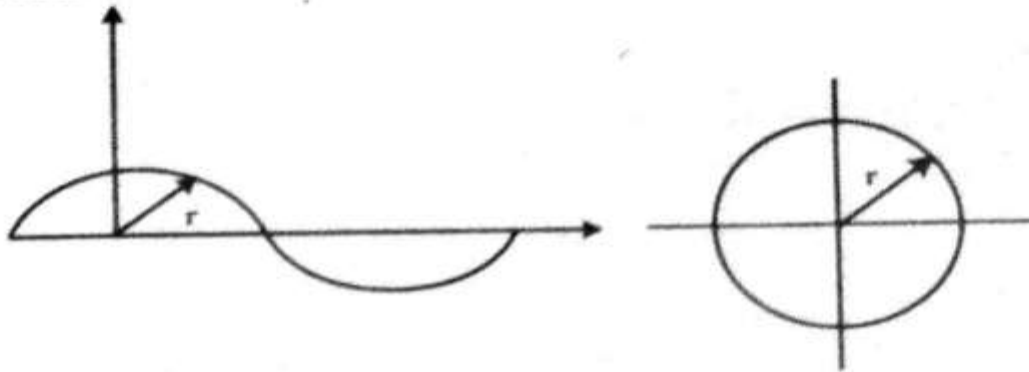

As sine function is a circular function.

The equation of the circle is

$$t^2 + i^2 = p^2$$

$$i = \sqrt{p^2 - t^2}$$

$$= \sqrt{\frac{p^2 - t^2}{2p}} dt$$

$$\therefore I_{\text{rms}} = \sqrt{\frac{\int_{-p}^p i^2 dt}{\int_{-p}^p dt}}$$

$$= \sqrt{\frac{1}{2p} \left[p^2 t - \frac{t^3}{3} \right]_{-p}^p}$$


$$= \sqrt{\frac{1}{2p} p^2 (p + p) - \frac{p^3 + p^3}{3}}$$

$$= \sqrt{\frac{4}{6} p^2}$$

$$= 0.816 P \cdot \text{amp}$$

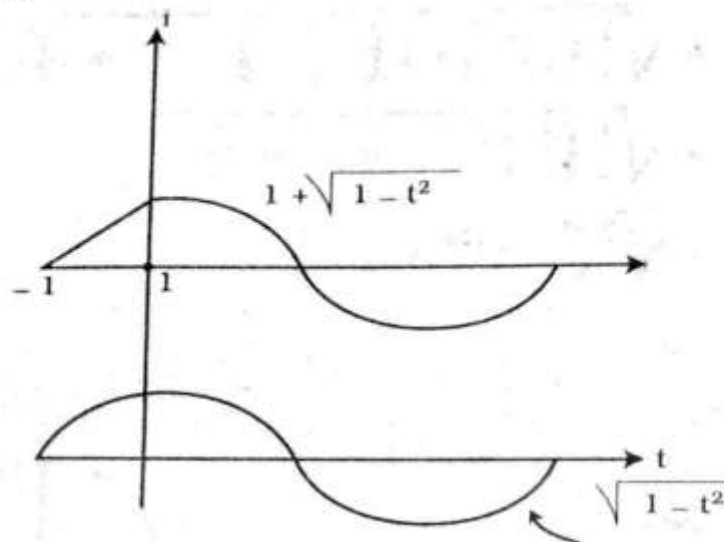3.17

$$\therefore E_{q^n} \text{ of the resultant current} = 1 + \sqrt{1-t^2}$$



$$\begin{aligned} \therefore I_{\text{rms}} &= \sqrt{\int_{-1}^1 \frac{1 + \sqrt{1-t^2}}{1+1} dt} \\ &= \sqrt{\int_{-1}^1 \frac{1 + 2\sqrt{1-t^2} + 1 - t^2}{2} dt} \\ &= \sqrt{\int_{-1}^1 \frac{(2 + 2\sqrt{1-t^2} - t^2)}{2} dt} \end{aligned}$$

$$\text{As we know, } \int \sqrt{1-t^2} dt = \frac{t\sqrt{1-t^2}}{2} + \frac{1}{2} \sin^{-1} t$$

$$\begin{aligned} \text{so, } \int_{-1}^1 \sqrt{1-t^2} dt &= \left[\frac{t\sqrt{1-t^2}}{2} + \frac{1}{2} \sin^{-1} t \right]_{-1}^1 \\ &= \frac{1}{2} \sin^{-1} 1 - \frac{1}{2} \sin^{-1} (-1) = \frac{1}{2} \times 180^\circ = 90^\circ \end{aligned}$$

$$\text{or, } \int_{-1}^1 \sqrt{1-t^2} dt = \frac{\pi}{2}$$

$$\int_{-1}^1 2 dt = 2t \Big|_{-1}^1 = 4$$

$$\text{and } \int_{-1}^1 t^2 dt = \frac{t^3}{3} \Big|_{-1}^1 = 0$$

[odd function]

$$\begin{aligned} \text{so, } I_{\text{rms}} &= \sqrt{\int_{-1}^1 \frac{(2 + 2\sqrt{1-t^2-t^2})}{2} dt} \\ &= \sqrt{\frac{4 + \frac{2\pi}{2}}{2}} \\ &= \sqrt{2 + \frac{\pi}{2}} \\ &= 1.89 \text{ amp} \end{aligned}$$

$$\begin{aligned} \text{3.18 Form factor} &= \frac{I_{\text{rms}}}{I_{\text{avg}}} \\ &= \frac{6.93 \text{ A}}{I_{\text{avg}}} \quad [\text{From ans of 14}] \end{aligned}$$

Here,

$$\begin{aligned} I_{\text{avg}} &= \frac{1}{T} \int_0^T \frac{12}{T} t dt \\ &= \frac{1}{T} \times \frac{12}{T} [t^2]_0^T \\ &= \frac{12}{T^2} \times T^2 \\ &= 12 \end{aligned}$$

$$\text{So, form factor} = \frac{6.93}{12} = 0.5775$$

Here, 19, 20, 21, 22 are same in mathematical procedure. I am giving an example of 21 for help to find the procedure.

3.19

$$\begin{aligned} e_{\text{rms}} &= \sqrt{\frac{1}{T} \int_0^T (100 \sin \omega t + 60 \sin(5\omega t + 30^\circ))^2 dt} \\ &= \sqrt{\frac{1}{T} \int_0^T [100^2 \sin^2 \omega t + 2 \times 100 \times 60 \sin \omega t \sin(5\omega t + 30^\circ) \\ &\quad + 60^2 \sin^2(5\omega t + 30^\circ)] dt} \\ &= \sqrt{\frac{1}{T} \int_0^T 100^2 \sin^2 \omega t dt + \int_0^T 2 \times 100 \times 60 \sin \omega t \sin(5\omega t + 30^\circ) \\ &\quad + \int_0^T 60^2 \sin^2(5\omega t + 30^\circ) dt} \end{aligned}$$

it is intotive that the integration can be done easily from your previous

Mathematical experience

42 The Solution of Alternating Current Circuits

3.20

$$e_{rms} = \sqrt{\frac{1}{T} \int_0^T [100^2 \sin^2 \omega t + 2 \times 100 \times 60 \sin \omega t \cos 3 \omega t + 60^2 \cos^2 3 \omega t] dt}$$

$$= \sqrt{\frac{1}{T} \left[\int_0^T 100^2 \sin^2 \omega t dt + \int_0^T 2 \times 100 \times 60 \sin \omega t \cos 3 \omega t dt + \int_0^T 60^2 \cos^2 3 \omega t dt \right]}$$

It is intuitive that the integration can be done easily from your past mathematical experience.

$$e_{avg} = \sqrt{\frac{2}{T} \left[\int_0^{\frac{T}{2}} 100 \sin \omega t + \int_0^{\frac{T}{2}} 60 \cos 3 \omega t \right]}$$

$$= \sqrt{\frac{2}{T} \left[\frac{100}{\omega} \cos \frac{\omega T}{2} - \frac{100}{\omega} + \frac{60}{\omega} \sin \frac{3 \omega T}{2} - 0 \right]}$$

$$= \sqrt{\frac{2}{T} \left[+ \frac{100}{\omega} + \frac{100}{\omega} \right]}$$

$$= \sqrt{\frac{2}{2\pi} [+ 200]}$$

$$= \sqrt{\frac{200}{\pi}} = 7.978 \text{ amp}$$

3.21

$$e_{rms} = \sqrt{\frac{1}{T} \left[\int_0^T 100^2 \sin^2 \omega t dt - \int_0^T 40 \times 100 \times 2 \sin \omega t \sin 3 \omega t dt + \int_0^T 40^2 \sin^2 3 \omega t dt \right]}$$

It is intuitive that the integration can be done easily from your previous experience.

3.22

$$e_{avg} = \sqrt{\frac{1}{T} \left[\int_0^{\frac{T}{2}} 100 \sin \omega t - \int_0^{\frac{T}{2}} 40 \sin 3 \omega t dt \right]}$$

It is intuitive that the integration can be done easily from your past experience.

Hence form factor = $\frac{e_{rms}}{e_{avg}}$

3.23

$$\begin{aligned}
 e_{\text{rms}} &= \sqrt{\frac{1}{T} \int_0^T e^2} \\
 &= \sqrt{\frac{2}{T} \int_0^{T/2} (100 \sin \omega t - 40 \sin 3\omega t)^2 dt} \\
 &= \sqrt{\frac{2}{T} \left[\int_0^{T/2} (100)^2 \sin^2 \omega t - 2 \times 100 \times 40 \sin \omega t \sin 3\omega t \right. \\
 &\quad \left. + (40)^2 (1 - \cos 6\omega t) dt \right]} \\
 &= \sqrt{\frac{2}{T} \int_0^{T/2} [10^4 (1 - \cos 2\omega t) - 2 \times 100 \times 40 (\cos 4\omega t - \cos 2\omega t) \\
 &\quad + (40)^2 (1 - \cos 6\omega t)] dt} \\
 &= \sqrt{\frac{2}{T} \left[10^4 \int_0^{T/2} (1 - \cos 2\omega t) dt - \int_0^{T/2} 2 \times 100 \times 40 (\cos 4\omega t - \cos 2\omega t) dt \right. \\
 &\quad \left. + \int_0^{T/2} (40)^2 (1 - \cos 6\omega t) dt \right]}
 \end{aligned}$$

. The answer is intuitive.

3.24 Rectangular wave**3.25** Square wave's form factor.**3.26** Peak factor = $\frac{\text{max}^m \text{ value}}{\text{rms value}}$

(a) sine wave,

$$\begin{aligned}
 I_{\text{rms}} &= \sqrt{\frac{2}{T} \int_0^{T/2} \sin^2 \omega t dt} \\
 &= \sqrt{\frac{2}{T} \int_0^{T/2} \frac{1}{2} (1 - \cos 2\omega t) dt} \\
 &= \sqrt{\frac{2}{2T} \left(\frac{T}{2} - \frac{\sin 2\omega t}{2\omega} \Big|_0^{T/2} \right)} \\
 &= \sqrt{\frac{2}{2T} \left(\frac{T}{2} - \frac{\sin 2\omega \frac{T}{2}}{2\omega} \right)} \\
 &= \sqrt{\frac{2}{2T} \left(\frac{T}{2} \right)} \\
 &= \sqrt{\frac{1}{2}} = 0.707
 \end{aligned}$$

\therefore Peak factor = $\sqrt{2}$

44 The Solution of Alternating Current Circuits


(b) rectangular wave.

$$\begin{aligned}
 I_{\text{rms}} &= \sqrt{\frac{1}{T} \int_0^T a^2 dt} \\
 &= \sqrt{\frac{1}{T} \times a^2 T} \\
 &= a
 \end{aligned}$$

$$\therefore \text{Peak factor} = \frac{a}{a} = 1$$

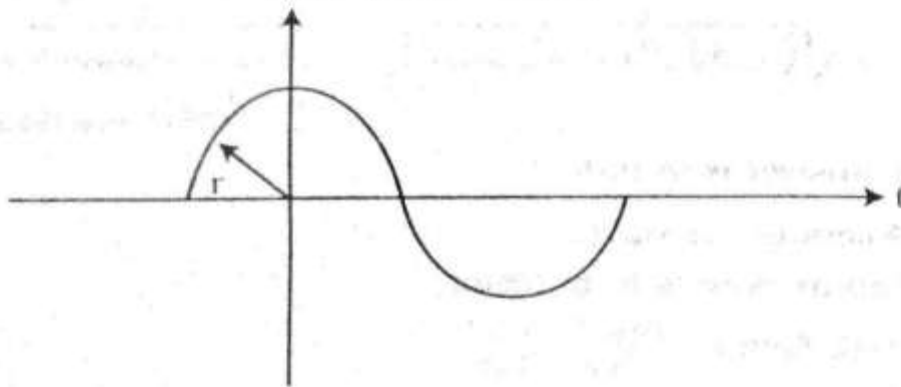3.27

$$\text{Creast factor} = \frac{\text{max}^m \text{ value}}{\text{rms value}} = \frac{50}{25.35} = 1.972 \text{ amp}$$



let, the radius be r

From problem (16) we have $I_{\text{rms}} = 0.816 r$

$$\begin{aligned}
 I_{\text{avg.}} &= \frac{1}{2r} \int_r^r \sqrt{r^2 - t^2} dt \\
 &= \frac{1}{2r} \left[\frac{t \sqrt{r^2 - t^2}}{2} + \frac{r^2}{2} \sin^{-1} \frac{t}{r} \right]_r^r \\
 &= \frac{1}{2r} \left[0 + \frac{r^2}{2} \sin^{-1} 1 - 0 - \frac{r^2}{2} \sin^{-1} (-1) \right] \\
 &= \frac{1}{2r} \cdot r^2 \cdot \frac{\pi}{2} = \frac{\pi r}{4} = 0.785 r
 \end{aligned}$$

$$\therefore \text{Creast factor} = \frac{I_{\text{max}}}{I_{\text{rms}}} = \frac{r}{0.816r} = 1.225$$


$$\text{and from factor} = \frac{I_{\text{rms}}}{I_{\text{av}}} = \frac{0.816 r}{0.786 r} = 1.04$$

3.28

$$i_1 = 30 \sin (\omega t + 60^\circ) = 30 \angle 60^\circ$$

$$i_2 = 20 \sin (\omega t - 20^\circ) = 20 \angle -20^\circ$$
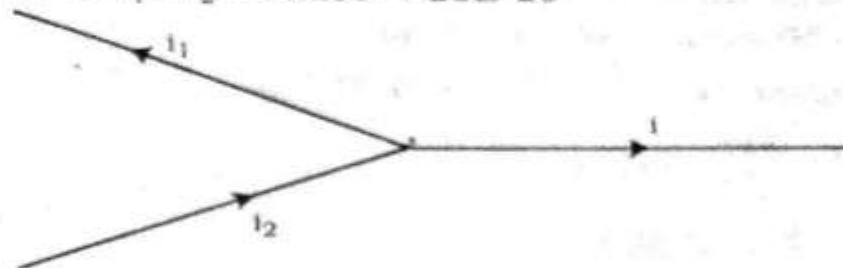
$$\therefore i = i_1 + i_2 = 30 \angle 60^\circ + 20 \angle -20^\circ$$



$$\therefore i = 15 + j 25.98 + 18.79 - j 6.84 = 38.83 \angle 29.53$$


$$\therefore i = 38.83 \sin (\omega t + 25.53)$$

$$\therefore \text{Effective current} = \frac{38.83}{\sqrt{2}} = 27.65 \text{ A}$$

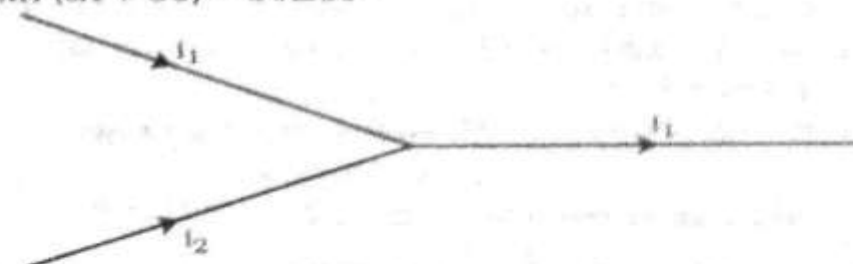3.29

$$i = 40 \sin (\omega t - 40^\circ) = 40 \angle -40^\circ$$

$$i = 50 \sin (\omega t + 80^\circ) = 50 \angle 80^\circ$$



$$i = i_1 + i_2 \quad \text{or} \quad i_2 = i - i_1 = 50 \angle 80^\circ - 40 \angle -40^\circ$$

$$\text{or, } i_2 = 8.68 + j 49.24 - 30.64 + j 25.71$$

$$= 70 \angle 106.05^\circ$$

$$\therefore i_2 = 70 \sin (\omega t + 106.05) \text{ A}$$

3.30 $I = 25 \text{ A}$, $V = 220 \text{ v}$, $\cos \theta = 0.88$

$$\therefore \text{Power} = VI \cos \theta = 25 \times 220 \times 0.88 = 4040 \text{ watt}$$

$$\text{VARs } VI \sin \theta = 25 \times 220 \times \sqrt{1 - (0.88)^2} = 2612.36 \times V_{\text{arb}}$$

$$\text{Reactive factor, } \sin \theta = \sqrt{1 - \cos^2 \theta} = \sqrt{1 - (0.88)^2} = 0.475$$

3.31 $I = 10 \text{ A}$, $V = 200 \text{ v}$, $\cos \theta = 0.8$

$$\therefore \text{Power} = VI \cos \theta = 10 \times 220 \times 0.8 = 1760 \text{ watts}$$

$$\therefore \text{Reactive volt - ampere} = VI \sin \theta = 10 \times 220 \times \sqrt{1 - (0.8)^2}$$

$$= 1320 \text{ VARs}$$

46 The Solution of Alternating Current Circuits

Reactive factor, $\sin\theta = \sqrt{1 - \cos^2\theta} = \sqrt{1 - (0.8)^2} = 0.6$
 volt - ampere = $VI = 10 \times 220 = 2200 \text{ VA}$

3.32

$$V = 20 \sin(\omega t + 30) = 200 \angle 30$$

$$i = 50 \sin(\omega t + 60) = 50 \angle 60$$

$$\therefore \text{Impedence} = \frac{200 \angle 30}{50 \angle 60} = 4 \angle 0.30$$

$$\text{Now, } V = \frac{200}{\sqrt{2}} = 141.42 \text{ v}$$

$$I = \frac{50}{\sqrt{2}} = 35.36 \text{ A}$$

$$\text{Average power, } P = VI \cos\theta = 141.42 \times 35.36 \times \cos(-30^\circ)$$

$$= 4330.6 \text{ w}$$

$$\text{volt - ampere} = VI = 141.42 \times 35.36 = 5000 \text{ var}$$

$$\text{Power factor} = \cos(-30^\circ) = 0.866$$

3.33


$$I = 15 \text{ A, } V = 220 \text{ v, } \theta = 72^\circ$$

(when current is lagging, the $\cos\theta$ is lagging power $P = VI \cos\theta$
 $\cos\theta = 15 \times 220 \cos 72^\circ$ factor and vice - versa)
 $= 1019.75 \text{ r}$

$$\text{Reactive power} = VI \sin\theta = 15 \times 220 \times \sin 72$$

$$= 3138.49 \text{ vars}$$
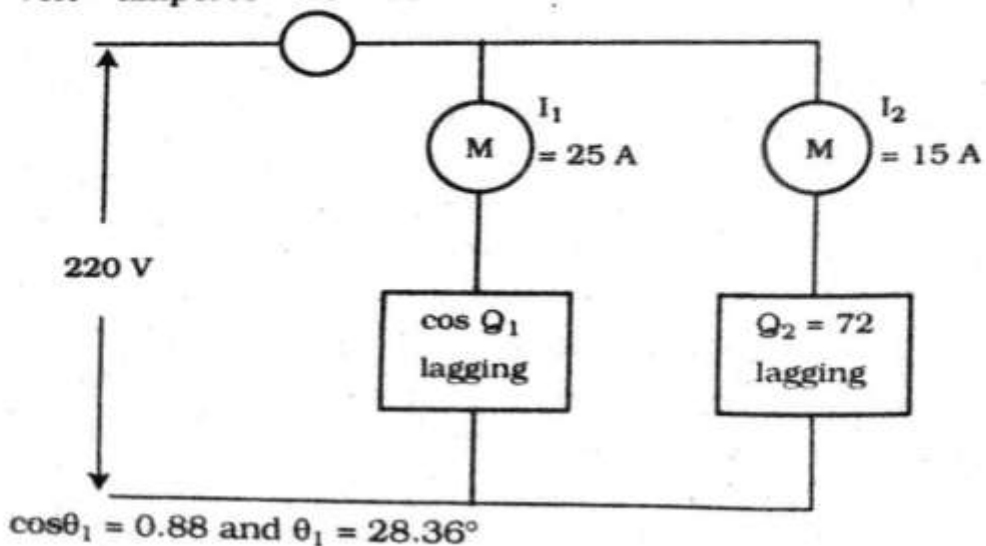
$$\text{volt - amperes} = VI = 15 \times 220 = 3300 \text{ VA}$$



Since the p.f is lagging power factor,

$$\therefore I_1 = 25 \angle -28.36$$

$$I_2 = 15 \angle -72^\circ$$

$$\therefore I = I_1 + I_2 = 25 \angle -28.36 + 15 \angle -72^\circ$$


$$= 37.32 \angle -44.46^\circ$$

$$\therefore \text{volt - ampere} = VI = 220 \times 37.32 = 8210.4 \text{ VA}$$

$$\therefore \text{total current } I = 37.32 \text{ A}$$

$$\text{Power, } P = VI \cos\theta = 8210.4 \cos 44.46^\circ = 5860.09 \text{ watt}$$

3.34

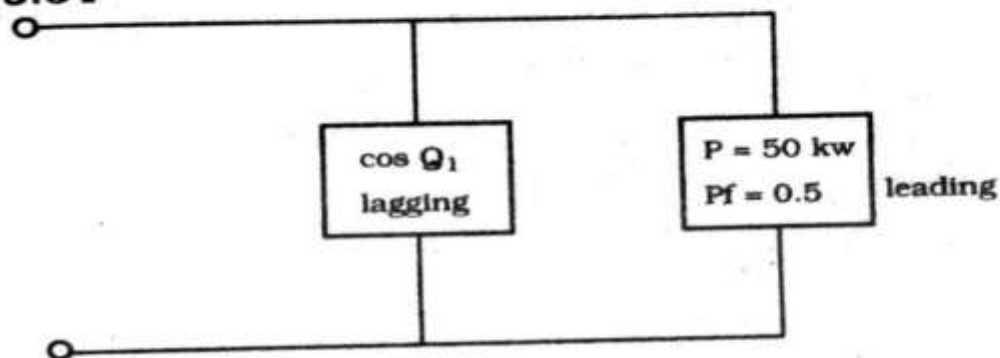

$$\cos\theta_1 = 0.8 \quad \therefore \theta_1 = 36.37$$

$$\cos\theta_2 = 0.9 \quad \therefore \theta_2 = 80^\circ$$

Since power factor is lagging, $I_1 = 250 \angle -36.87^\circ$

$$\text{Now, } VI_2 \cos\theta_2 = 50 \times 10^3 \text{ or, } 220 \times I_2 \times 0.05 = 50 \times 10^3$$

$$\therefore I_2 = 454.55 \text{ A}$$

Since leading power factor,

$$\therefore I_2 = 454.55 \angle 60^\circ$$

$$I = I_1 + I_2 = 250 \angle -35.87^\circ + 454.55 \angle 60^\circ$$

$$= 491.86 \angle 29.6937$$

$$\therefore \text{line current} = 491.86 \text{ amp}$$

Power current is leading, p.f is leading.

3.35

$$v = 200 \sin \omega t$$

$$\therefore v = \frac{200}{\sqrt{2}} \angle 0$$

$$[\text{RMS} = \text{Peak}/\sqrt{2}]$$

$$\therefore Z = \frac{141.421 \angle 0^\circ}{35.355 \angle 60^\circ} = 42 \angle 60^\circ$$

$$i_1 = 50 \cos (\omega t - 30^\circ)$$

$$= 50 \sin (\omega t - 30^\circ + 90^\circ)$$

$$= 50 \sin (\omega t + 60^\circ)$$

$$I = \frac{50}{\sqrt{2}} \angle 60^\circ = 35.35 \angle 60^\circ$$

48 The Solution of Alternating Current Circuits

$$\therefore \text{Average power} = VI \cos\theta = 141.421 \times 35.355 \cos 60^\circ = 2500 \text{ WAh}$$

$$\text{Vars} = VI \sin\theta = 4330 \text{ vars}$$

$$\text{Power factor} = \cos 60^\circ = 0.5$$

3.36

$$VI \sin\theta = 600 \dots \dots (i)$$

$$VI \cos\theta = 800 \dots \dots (i)$$

Now,

$$VA = \sqrt{(\text{real})^2 + (\text{imaginary})^2} = \sqrt{(VI \cos\theta)^2 + (VI \sin\theta)^2} \\ = \sqrt{600^2 + 800^2} = 1000 \text{ VA}$$

$$\text{Power factor } \cos\theta = \cos 36.87^\circ = 0.8$$


$$\text{Reactive factor } \sin\theta = \sin 36.87^\circ = 0.6$$

3.37

$$X_L = \omega L$$

$$= 2\pi \times 60 \times 20 \text{ mH}$$

$$= 7.54 \text{ ohm}$$

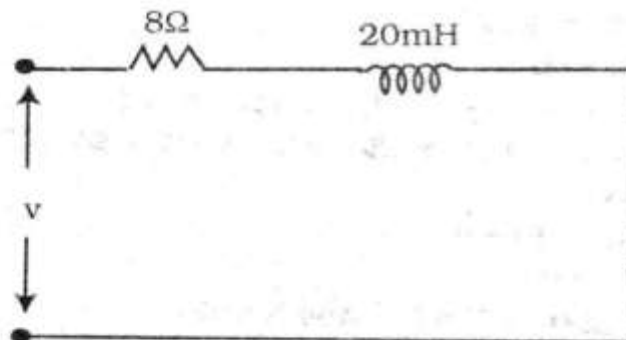

$$Z = 8 + 7.54 = 11 \angle 33.3^\circ \text{ current} = \frac{110}{11} = 10 \text{ amp}$$

$$\text{Power, } P = VI \cos\theta = 110 \times 10 \times \cos 43.3 = 800.5 \text{ A}$$

3.38


$$Z_1 = 6 + j(48 - 40) = 10 \angle 53.13$$

$$Z_2 = 7 - j2 = 7.28 \angle -15.95$$

$$\therefore Z_{\text{circuit}} = \frac{Z_1 \times Z_2}{Z_1 + Z_2} \\ = \frac{10 \angle 53.13 \times 7.28 \angle -15.95}{6 + j8 + 7 - 2j}$$

$$= \frac{72.8 \angle 37.18}{14.32 \angle 24.78}$$

$$= 5.08 \angle 12.4$$

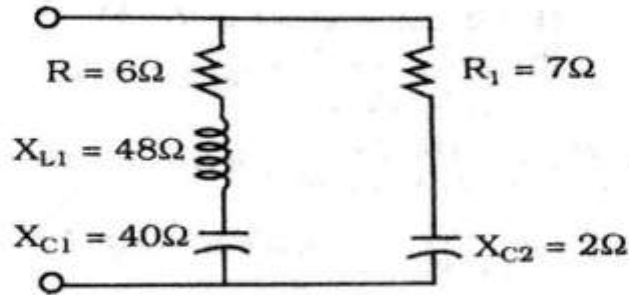

$$\text{Current} = \frac{100}{5.08} = 19.88 \text{ amp}$$

$$\text{Total power} = VI \cos\theta = 100 \times 19.68 \cos 12.4 = 1922 \text{ W}$$

$$I_1 = \frac{V}{Z_1} = \frac{100}{10} = 10 \text{ A}$$

$$\therefore P_1 = VI_1 \cos\theta_1 = 100 \times 10 \cos 53.13 = 600 \text{ W}$$

$$I_2 = \frac{V}{Z_2} = \frac{100}{7.28} = 13.74$$

$$\therefore P_2 = 100 \times 13.74 \cos(-15.95) = 1321.1 \text{ W}$$

3.39


$$X_{L1} = \omega L = 2 \times 60 \times 0.05$$

$$= 18.85 \text{ ohm}$$

$$X_{C2} = \frac{106}{377 \times 100} = 26.530 \text{ hm}$$

$$Z_1 = 10 + j 18.85 = 21.338 \angle 62$$
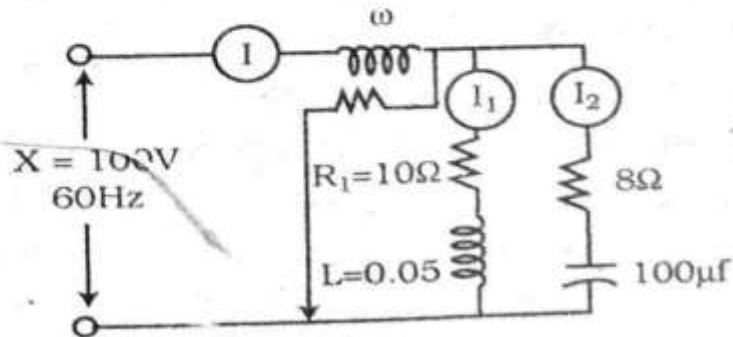
$$Z_2 = 8 - j26.53 = 27.71 \angle -73.22$$



∴ Impedence of the circuit is-

$$\begin{aligned} Z_0 &= \frac{Z_1 \times Z_2}{Z_1 + Z_2} \\ &= \frac{21.388 \angle 62 \times 27.71 \angle -73.22}{21.338 \angle 62 + 27.71 \angle -73.22} \\ &= \frac{591.276 \angle -11.22}{19.57 \angle -23.1} = 30.213 \angle 11.88 \end{aligned}$$

$$\therefore I = \frac{V}{Z_0} = \frac{100 \angle 0}{30.213 \angle 11.86} = 3.31 \angle -11.88^\circ$$

$$I_1 = \frac{V}{Z_1} = \frac{100 \angle 0}{21.338 \angle 62} = 4.606 \angle -62$$

$$I_2 = \frac{V}{Z_2} = \frac{100 \angle 0}{27.71 \angle -73.22} = 3.61 \angle 13.22$$

$$P = V \cos \theta = 100 \times 3.31 \times \cos 11.88 = 323.91 \text{ W}$$

∴ The ammeter readings will be $I_1 = 4.686 \text{ A}$

$$I_2 = 3.61 \text{ A}$$

$$I = 3.31 \text{ A}$$

∴ The watt meter readings will be $P = 323.91 \text{ W}$

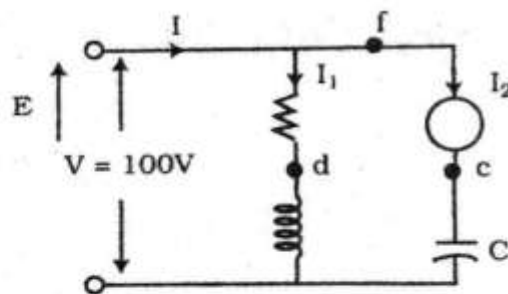


Fig. (a)

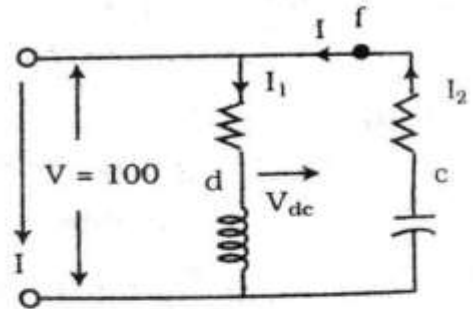


Fig. (b)

(c) According to kirchoffs voltage law

$$-V_{dc} + V_{cf} + V_{fd} = 0$$

$$V_d = v_{cf} - V_{fd} = V_{fc} - V_{fd} = I_1 R_1 - I_2 R_2$$

$$= 4.686 \angle -62 \times 10 - 3.61 \angle 73.22 \times 8$$

$$= 22 - 41.375 - 8.338 - 27.65$$

$$= 70.364 \angle -78.8 \text{ V}$$

(d) for fig (b)

According to kirchoff's voltage law-

$$V_{dc} + V_{cf} + V_{fd} = 0$$

$$\text{or, } V_{dc} = V_{cf} - V_{fd} = V_{df} - V_{cf}$$

$$= 3.61 \angle 73.32 \times 8 - 4.686 \angle -62 \times 10$$

$$= 8.338 + 27.65 - 22 + 41.375$$

$$= 70.364 \angle 101.2^\circ \text{ volt}$$

3.40 $R_1 = 8 \text{ omh}$

$$L_1 = 0.025$$

$$X_{L1} = \omega l = 2\pi \times 0.025 \times 60 = 0.157 \times 60 = 9.42$$

$$X_{C1} = \frac{1}{\omega C} = \frac{1}{2\pi \times 120\pi f \times 60}$$

$$= \frac{1}{2\pi \times 120 \mu f \times 60}$$

$$= 22.10 \Omega$$

$$I_1 = \frac{100}{8 + 9.42j}$$

$$= 8.09 \angle -49.66 \text{ A}$$

$$I_2 = \frac{100}{8 - 22.10j}$$

$$= 4.254 \angle 70.100 \text{ A}$$

(b) Do yourself

$$(c) V_{dc} = 10 \times 8.09 \angle -49.66 - 8 \times 4.254 \angle 70.1$$

$$= 102.157 \angle -66.469$$

3.41 (a) $I = I_1 + I_2 = 7.027$

(b) $\omega = VI \cos \theta$


$$= 100 \times 7.027 \times \cos (17.955)$$

$$= 668.477 \text{ watts.}$$

3.42 Do yourself with help of previous math

3.43 Do yourself with help of 39.

3.44

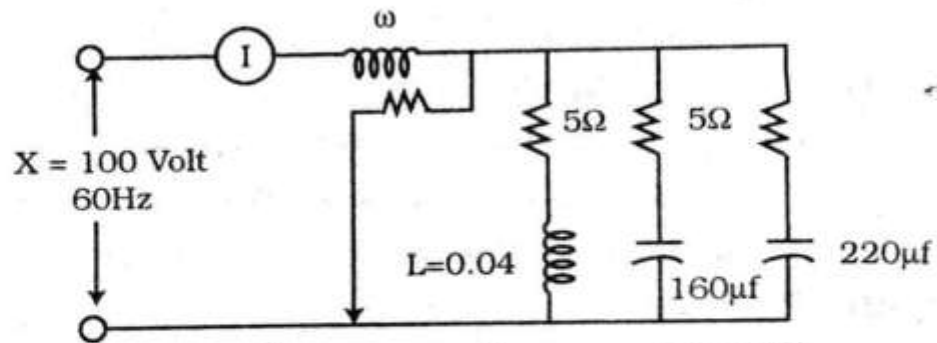

$$Z_1 = 8 + \frac{-j}{2\pi \times 60 \times 220\mu}$$

$$= 8 - 12.057j$$

$$Z_2 = 5 + \frac{-j}{2\pi \times 60 \times 160\mu}$$

$$= 5 + \frac{-j}{0.0603}$$

$$= 5 - 16.58j$$

$$Z_3 = 5 + 15.079j$$

$$P = VI \cos\theta$$

$$= 100 \times 9.165 \times \cos 35.42$$

$$= 746.879 \text{ watt}$$

$$Z_{total} = z_1 || z_2 || z_3$$

$$= (8 - 12.057j) || (5 - 16.58j) || (5 + 15.079j)$$


$$= 10.91 \angle -35.42$$

$$I = \frac{V}{Z_{total}}$$

$$= \frac{100}{10.91} = 9.165 \angle 35.42$$

3.45

(a)

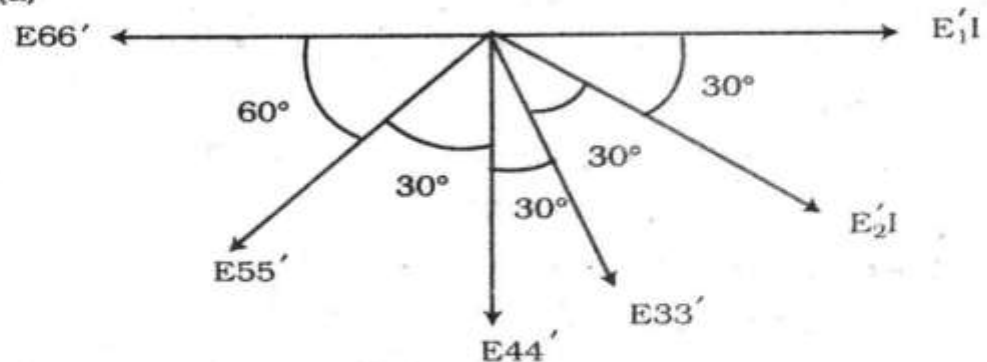

$$(b) E_{13}' = E_{35}' = E \angle -60^\circ$$

$$(c) E_{13} = E \angle 0 - E \angle -60^\circ$$

$$= E \angle 60^\circ$$

$$(d) E_{greatest} = E + E \angle -30 + E \angle -60 + E \angle -90 + E \angle -120 + E \angle -150$$

$$= (3.86 \angle -75) E$$

(e) Do yourself

Chapter-4
Phasor Algebra
(As applied to A—C circuit Analysis)

4.1 $3 + 4j = 5\angle 53.1$

4.2 $10e^{-j120} = 10\angle -120 = -5 - j8.66$

4.3 $14\angle 60^\circ + 20\angle 15^\circ = 263 + j17.3$

[Tips : you can do it easily by scientific calculator]

4.4

$$A = 40\angle 120^\circ$$


$$B = 20\angle -40^\circ$$

$$C = 26.46\angle 0^\circ$$

Hence,

$$\begin{aligned} A + B + C &= 40\angle 120^\circ + 20\angle -40^\circ + 26.46\angle 0^\circ \\ &= 21.78 + j21.78 = 30.8\angle 45^\circ \end{aligned}$$

4.5

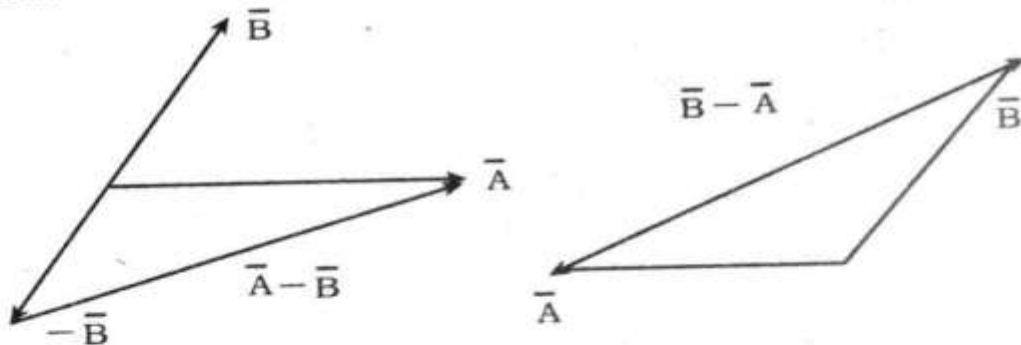

4.6

$$A = 42\angle 200^\circ$$

$$B = 20\angle -40^\circ$$

$$C = 24.25 + j14$$

$$\therefore (A + C) - B = 32.95\angle 157.7^\circ$$

4.7

$$A = 5 - 4j$$

$$B = 2 + 3j$$

$$\therefore AB = (5 - 4j)(2 + 3j)$$

$$= 22 + j7$$

$$= 23.09\angle 17.65$$

4.8

$$A = 20 + j20$$

$$B = 30\angle -120^\circ$$

$$C = 5 + j0$$

$$(a) A + B + C$$

$$= 20 + j20 + 30\angle -120^\circ + 5$$

$$= 11.67\angle -31^\circ$$

$$(b) (A + B) C$$

$$= 39.05\angle -50.2^\circ$$

$$(c) ABC = (20 + j20) (30\angle -120^\circ) (5) = 4242\angle -75^\circ$$

$$4.9 A = 40\angle 105^\circ \text{ and } B = 5 + j8.66$$

$$\frac{A}{B} = 4\angle 45^\circ$$

4.10

$$A = 20 + j20$$

$$B = 30\angle -120^\circ$$

$$C = 5\angle 0^\circ$$

$$(a) \frac{A + B}{C}$$

$$= \frac{5 - 5.98}{5}$$

$$= 1.56\angle -50.103^\circ$$

$$(b) \frac{BC}{A}$$

$$= \frac{30\angle -120^\circ}{5}$$

$$= 6\angle -120^\circ$$

$$4.13 A = 52\angle 70^\circ$$

Here,

$$\frac{15\angle 70^\circ}{(3 - j4)} + \log_e (8 + j5)$$

$$= \frac{15\angle 70^\circ}{3 - j4} + (\log_e 9.433 \times e^{j32^\circ})$$

$$= 0.6 + j3.07$$

4.14

$$K = 12.9$$

$$L = 0.056 \text{ H}$$

$$C = 78 \mu\text{f}$$

$$\begin{aligned} \text{(a) } Z_{\text{RLC}} &= 12.9 + j\left(\omega L - \frac{1}{\omega C}\right) \\ &= 12.9 + j\left(2\pi \cdot 60 \times 0.056 - \frac{1}{2\pi \times 60 \times 78 \times 10^{-6}}\right) \\ &= 12.9 + j(21.11 - 34) \\ &= 12.9 - 12.897j \end{aligned}$$

$$\text{(b) } I = 10\angle 30^\circ$$

$$\begin{aligned} V &= I Z_{\text{RLC}} \\ &= (10\angle 30^\circ)(12.9 - 12.897j) \\ &= 182.4\angle -15^\circ \end{aligned}$$

4.15

$$\begin{aligned} V_g &= E_g - I Z_g \\ &= (500\angle 0^\circ) - (27.1\angle 49.4^\circ)(6.32\angle 71.6^\circ) \\ &= 500\angle 0^\circ - 171.3\angle 121^\circ \\ &= 606\angle -14^\circ \end{aligned}$$

$$V_g = 606\angle -14^\circ$$

$$\therefore \text{ total power} = V_g I \cos\theta + I_2 R + E_g I \cos\theta = 8810 \text{ watts}$$

4.16

$$\begin{aligned} \text{(a) } (5 + j8) + (-2 - j4) \\ &= 3 + 4j \end{aligned}$$

$$\begin{aligned} \text{(b) } (-12 + 6j) - (30 - 20j) \\ &= -42 + 26j \end{aligned}$$

$$\begin{aligned} \text{(c) } (16 - 12j)(-5 + 8j) \\ &= 16 + 188j \end{aligned}$$

4.17

$$Z_1 = 2 + 3j$$

$$Z_2 = 3 - 7j$$

$$Z_{\text{eq}} = Z_1 + Z_2$$

$$= 5 - 4j$$

$$= 6.4\angle -38.66^\circ$$

4.18

- (a) $100\angle-30$
 (b) $100\angle-45$
 (c) $100\angle-120$

4.19

- (a) $8 + 6j$
 $= 10\angle 36.889$
 (b) $-57.36 + j81.92$
 $= 100\angle 124.99$

4.20

$$Z = 10\angle 30$$

According to question,

$$10\angle-10^\circ$$

4.21

- (a) $(8 + 6j) (10\angle-120) (\cos 36.87^\circ - j\sin 36.87^\circ) (0.1 e^{j60})$
 $= 10\angle-60$
 (b) $\frac{(34.2 + j94) (10\angle-30) (30\angle 60)}{(20\angle 40^\circ) (50\angle 30^\circ)}$
 $= 330\angle 30^\circ$

4.22


- (a) $\sqrt{4.5 - 7.79j} + \log_e 10\angle 172$
 $= \sqrt{8.99} \angle \frac{60}{2} + \log_e 10 + \log_e 10 + \log_e e^{j172}$
 $= 3\angle-30^\circ + \log_e 10 + j172$
 (b) $\sqrt{\frac{(940 + j342)}{10j10}}$
 $= \sqrt{\frac{1000.28\angle 20}{10j10}}$
 $= \frac{\sqrt{1000.28} \angle 10}{\sqrt{10} \angle 5}$
 $= \frac{31.63\angle 10}{3.162\angle 5}$
 $= 10\angle 5$

4.23

$$\begin{aligned} & \sqrt[3]{\frac{10\angle 45^\circ \times 5_{e^{j60}} \times (-4047 - j2.94)}{1 - j1.732}} \\ &= \frac{\sqrt[3]{10\angle 15} \times \sqrt[3]{5\angle 30} \times \sqrt[3]{5\angle -48}}{\sqrt[3]{2\angle -10^\circ}} \end{aligned}$$

In this chapter, problem no 16 + 0 23. Can be solved with calculator directly so try it yourself.

4.24

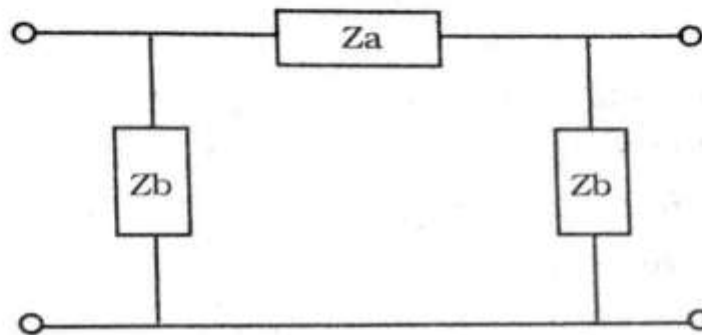

$$\begin{aligned} \text{(a) } Z_0 &= \sqrt{Z_a Z_b} = \sqrt{10\angle 68 \times 25000\angle -90} \\ &= \sqrt{250000\angle (-90 + 68)} \\ &= \sqrt{250000\angle -22} \\ &= 500\angle -\frac{22}{2} \\ &= 500\angle -11 \end{aligned}$$

$$\begin{aligned} \text{(b) } r &= \sqrt{\frac{Z_a}{Z_b}} \\ &= \sqrt{\frac{25000\angle -90}{10\angle 68}} \\ &= \sqrt{2500\angle -158} \\ &= 50\angle -79 \end{aligned}$$

[Tricks : find in polar form then,

$$\sqrt{Z} = \sqrt{\text{magnitude}} \angle \frac{\text{Angle}}{2}$$

4.25 A voltage of $125\angle 40$ volts

$$V = 125\angle 40$$

$$Z = 2 + j8$$

$$I = \frac{125\angle 40}{2 + j8} = 15.158\angle -35.96$$

4.26

$$Z_1 = (1 - j3)$$

$$Z_2 = (3 + 6j)$$

$$I = 10 \text{ amp}$$

$$(a) \quad 10 \angle 0 = \frac{Z_2}{Z_1 + Z_2} \times I$$

$$\begin{aligned} I &= \frac{(Z_1 + Z_2)}{Z_1} \times 10 \\ &= \frac{6.708 \angle 63.434}{1} \times 10 \\ &= 67.08 \angle 63.43 \end{aligned}$$

$$(b) \quad I_0 = I_1 + I_2$$

$$\text{or, } I_2 = I_0 - I_1$$

$$\begin{aligned} &= 67.08 \angle 63.43 - \frac{10}{0} \\ &= 20 + 60j \end{aligned}$$

4.27

$$\begin{aligned} Z_{OT} &= \sqrt{Z_1 Z_2 + \frac{Z_1^2}{4}} \\ &= \sqrt{(30 \angle 86.0) (10 \angle -90^\circ) + \frac{(30 \angle 86)^2}{4}} \\ &= \sqrt{77.16 \angle 7.736} \\ &= 8.78 \angle 3.868 \end{aligned}$$

4.28

$$\begin{aligned} &\sqrt{\frac{125 \angle -90^\circ}{5 \angle 90^\circ}} \\ &= 1.61 \pm j \frac{\pi}{2} \end{aligned}$$

4.29

$$\alpha + j\beta$$

$$\begin{aligned} &= 2 \log_e \left(\sqrt{1 + \frac{Z_1}{Z_1 Z_2}} + \sqrt{\frac{Z_1}{4 Z_2}} \right) \\ &= 2 \log_e \left(\sqrt{1 + \frac{25.14 \angle -90^\circ}{795 \angle 90}} + \sqrt{\frac{25.14 \angle -90}{795 \angle 90}} \right) \end{aligned}$$

$$= 2 \log_e (\sqrt{0.968} + \sqrt{0.03} \angle 90^\circ)$$

$$= 2 \log_e 0.99 e^{j \frac{9.98}{180^\circ}}$$

$$\alpha + j\beta = 2 \times \log_e 0.99 + 2 \times \frac{j 9.98}{180}$$

$$\alpha = 2 \times \log_e 0.99 = 0.02$$

$$\beta = 2 \times \frac{9.98}{180} = 0.11$$

4.30 Similar to 29

4.31

$$V_m = V - ZI$$

$$V = 100 \angle 0^\circ$$

$$Z = 15 \angle 80^\circ$$

$$I = 10 \angle -30^\circ$$

$$V_m = 100 - 15 \angle 80^\circ \times 10 \angle -30^\circ = 160.47 \angle -65.61$$

4.32

$$(a) \quad (12 + a) + jb = 20 + j10$$

$$12 + a = 20$$

$$a = 8$$

$$b = 10$$

4.33

$$a + 10 = 100 \cos \beta$$

$$50 = 100 \sin \beta$$

$$\beta = \sin^{-1} \frac{50}{100} = 30^\circ$$

$$a + 10 = 100 \times 50 \sqrt{3}$$

$$a = -10 + 50 \sqrt{3}$$

4.34

$$V = 100 - j50 = 111.8 \angle -26.56$$

$$I = -2 - j8 = 8.246 \angle -104.03$$

$$P_{\text{absorb}} = 111.8 \times 8.246 \cos (-26.56 + 104.03)$$

$$= 200 \text{ watts}$$

4.35

$$\text{Vart} = 111.8 \times 8.246 \times \sin (-26.56 + 104.03)$$


$$= 900 \text{ vars}$$

4.36 As total power

$$VI$$

$$= 111.8 \angle -26.56 \times 8.246 \angle +104.03$$

$$= 200 + 900j$$

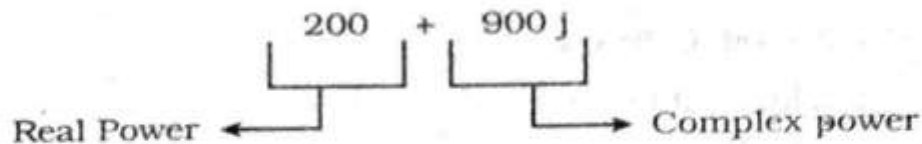**4.37**

$$V = 40 \angle 80$$


$$I_1 = 5 \angle 30^\circ$$

$$I_2 = (-6 + j8)$$

$$\therefore I_0 = I_1 + I_2 = 5 \angle 30 + (-6 + j8) = 10.63 \angle 100$$

$$\therefore \text{Complex power} = 40 \angle 80 \times 10.63 \angle -100$$

$$= 425.2 \angle -20 = 400 - 145j$$

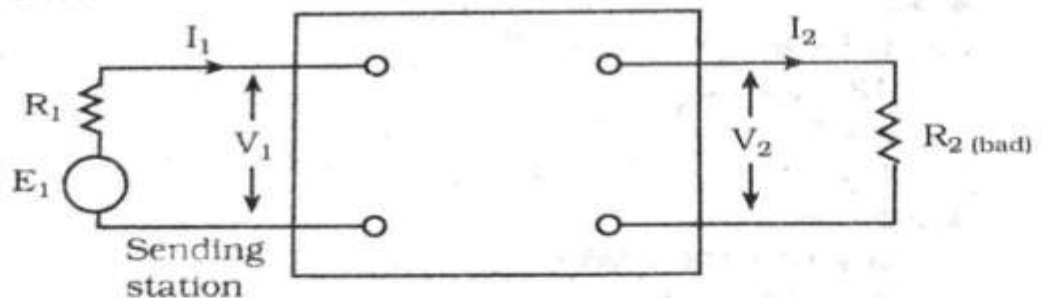4.38

Here,

$$R_1 = 200 \Omega$$

$$R_2 = 20 \times 10^3 \Omega$$

$$V_2 = (0.1 \angle 114.6) E_1$$

$$Y = \alpha + j\beta = \log_e \frac{Z_T}{2\sqrt{R_1 R_2}}$$

$$I_{2(\text{OPT})} = \frac{E_1}{2\sqrt{200 \times 20 \times 10}} = \frac{E_1}{4000}$$

$$I_{2(\text{actual})} = \frac{E_1}{200 + 20 \times 10^3} = \frac{0.1 \angle 14 E_1}{20200}$$

$$\begin{aligned} \therefore Y = \alpha + j\beta &= \log_e \frac{Z_T}{2\sqrt{R_1 R_2}} \\ &= \log_e \frac{I_{2(OPU)}}{I_{2(\text{general})}} \\ &= \log_e \frac{20200}{4000 \times 0.1 \angle 114} \\ \alpha + j\beta &= \log_e (50.5 \angle -114) \\ &= \log_e 50.5 - j \frac{114}{180} \\ \therefore \alpha + j\beta &= 3.92 - j0.633 \end{aligned}$$


4.39

$$R_1 = 200$$

$$R_2 = 20,000$$

$$I_2 = \frac{E_1}{4000} \text{ amp}$$


$$\begin{aligned} \alpha + j\beta &= \log_e \frac{Z_T}{2\sqrt{R_1 R_2}} \\ &= \log_e \frac{I_{2(OPU)}}{I_{2(\text{actual})}} \\ &= \log_e \frac{E_1}{4000} \\ &= \log_e \frac{E_1}{4000} \\ &= \log_e I = 0 \end{aligned}$$

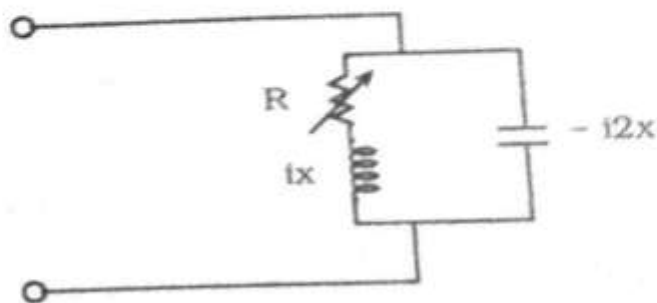4.40

$$Z = \frac{(R + jX)(-2jX)}{R + jX - 2jX}$$

for $R = 0$
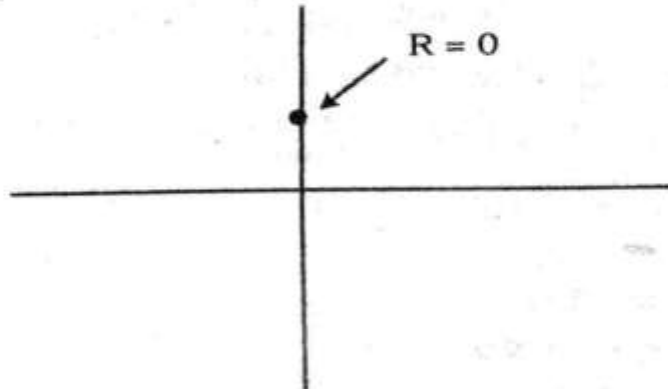
$$\begin{aligned} Z &= \frac{(jX)(-2jX)}{jX - 2jX} \\ &= \frac{(-2) X^2 (-1)}{j(-2) X^2} \\ &= j \end{aligned}$$



Similarly find other values yourself.


$$\begin{aligned} \text{(c) } A \cos \omega t &= A \frac{e^{j\omega t} + e^{-j\omega t}}{2} \\ &= \frac{A}{2} e^{j\omega t} + \frac{A}{2} e^{-j\omega t} \end{aligned}$$

(1) is a sinusoidal circular function with a anticlockwise rotation.

(2) is a sinusoidal circular function with a clockwise rotation.

Chapter-5
Sinusoidal signal - phasor circuit analysis

5.1

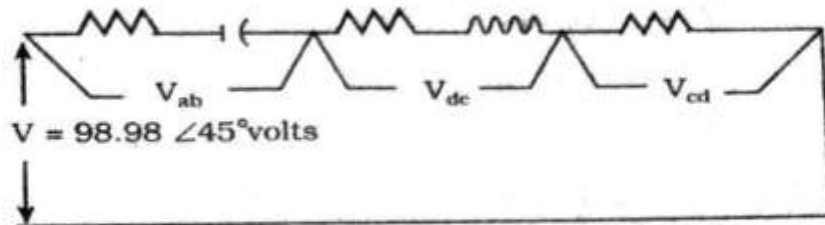


(a)
$$I = \frac{V}{Z} = \frac{98.98 \angle 45}{2 - j4 + 3 + j11 + 2 + j0} = \frac{98.98 \angle 45}{7 - j7} = 10 \angle 0$$

$$V_{ab} = I Z_{ab} = (10 + j0) \cdot (2 - j4) = 44.7 \angle -63.45 \text{ volts}$$

$$V_{bc} = I Z_{bc} = (10 + j0) (3 + j11) = 30 + j110 = 114 \angle 74.75 \text{ volts}$$


$$V_{cd} = I Z_{cd} = (10 + j0) (2 + j0) = 20 + j0 = 20 \angle 0^\circ \text{ volts}$$

(b)

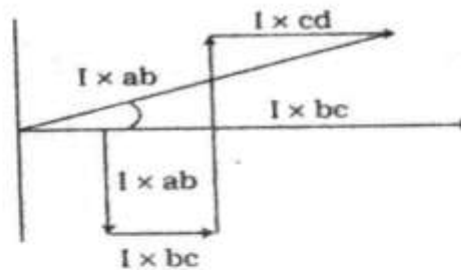


Funicular or string vector diagram of ckt.

(c)

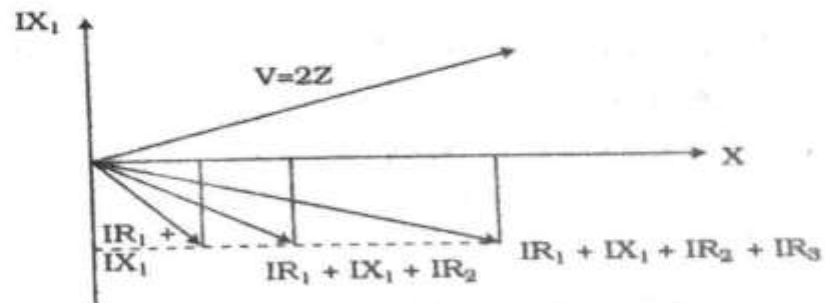

Polar vector diagram of ckt.


5.2

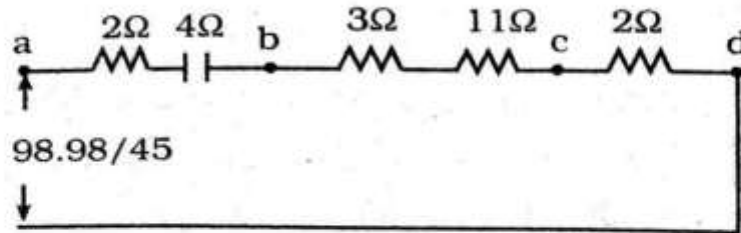

$$I = \frac{98.98 \angle 45}{(2 - i4 + 3 + 11i + 2)}$$

$$= 9.9 \angle 0$$

(b)

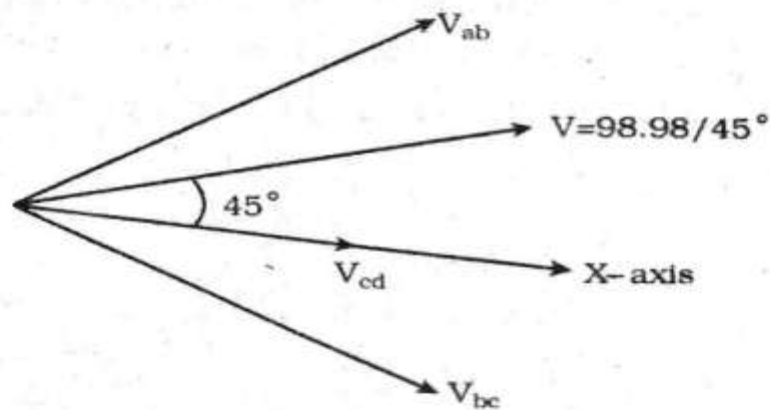

(c) Do yourself

$$(i) P_R = 10^2 \times 2 + 10^2 \times 2 + 10^2 \times 3$$

$$= 700 \text{ Watt}$$

$$(ii) P_R = VI \cos \theta$$

$$= 98.98 \times 10 \times \cos 45^\circ$$

$$= 699.89 = 700 \text{ Watt}$$

(iii) Do yourself

5.3


$$P = I^2 R = 10^2 \times (2 + 3 + 2) = 700 \text{ watts}$$

$$P = VI \cos \theta = 98.98 \angle 45^\circ \times 10 \angle 0$$

$$= 989.8 \cos 45 = 99.89429 = 700 \text{ watt}$$

$$\begin{aligned}
 P &= vi + v'i' \\
 &= 69.989 \times 10 + 69.989 \times 0 \\
 &= 699.89 \approx 700 \text{ watts}
 \end{aligned}$$

Y = Admittance

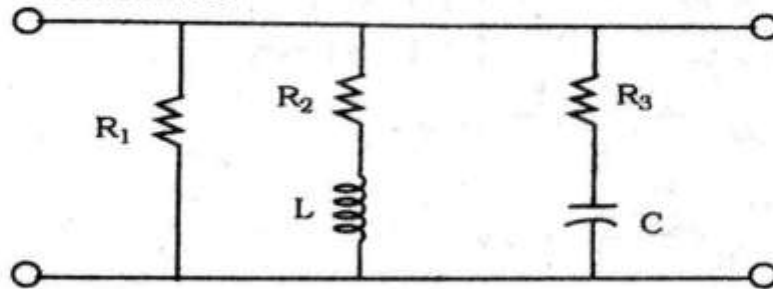

$$Y_1 = \frac{1}{Z} = \frac{1}{10 + j0} \times 0.1 + j0 \text{ ohm}$$

$$Y_2 = \frac{1}{20 + j10} = 0.025 - j0.025$$

$$\therefore g_2 = 0.025 \quad b_2 = 0.025$$

$$Y_3 = \frac{1}{30 - j40} = 0.012 + j0.016$$

$$\therefore g_3 = 0.012, \quad b_3 = 0.016$$

$$\therefore \text{Resulting } g = g_1 + g_2 + g_3$$

$$= 0.1 + 0.025 + 0.012 = 0.137 \text{ ohm}$$

$$b = b_1 + b_2 + b_3 = 0 + 0.025 - 0.016 = 0.009 \text{ ohm}$$

$$g_1 = \frac{R_1}{Z_1^2} = \frac{10}{10 + j0} = 0.1 \text{ ohm}$$

$$b_1 = \frac{X_1}{Z_1^2} = \frac{0}{100} = 0$$

$$g_2 = \frac{R_2}{Z_2^2} = \frac{20}{800} = 0.025$$

$$b_2 = \frac{20}{800} = 0.025$$

$$g_3 = \frac{R_3}{Z_3^2} = 0.012$$

$$b_3 = \frac{-40}{2500} = -0.016$$

(c) In phase component of resulting current = $V_g = 40 \times 0.137 = 5.48 \text{ amp}$

Quadrature component of the resulting current

$$V_b = 40 \times 0.009 = 0.36 \text{ amp}$$

5.4 Problems

(a) $\theta = \cos^{-1} 0.866$ $= 30^\circ$ lagging	for resonance $X_L = X_C$ But for p.f = 0.866 it is different
---	---

$$\angle \tan^{-1} \frac{(2\lambda f l - \frac{1}{2\pi f l})}{R} = \angle 30$$

$$\frac{2\pi f l - \frac{1}{2\pi f l}}{R} = 0.5773$$

$$\frac{X_L - X_C}{R} = 0.5773$$

$$X_L = 100 \times 0.5773 + 200$$

$$= 57.73 + 200 = 257.73$$

$$L = \frac{X_L}{2\pi f} = \frac{257.73}{377} = 0.683$$

for leading similarly,

$$X_L = 142.3 \text{ ohms and } L = 0.377$$

5.5 For resonance,

$$X_C = X_L$$

$$= \frac{R^2 + X_L^2}{X_L}$$

$$= \frac{100^2 + 200^2}{200}$$

$$= 250 \Omega$$

$$I_{\max} = \frac{100}{\sqrt{100^2 + (250 - 200)^2}}$$

$$= 0.894 \text{ ampere}$$

$$\therefore V_{\max} = 8.94 \times 250 \times 10^{-1} = 223.5 \text{ Volts}$$

5.6

$$f = \frac{1}{2\pi} \sqrt{\frac{1}{L_C}}$$

$$= 920 \text{ KHz}$$

(b) f = Same as it depends upon L_C

$$(c) f = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$

and $Z = R + j(X_L - X_C)$

$$X_L = \omega L = 2\pi \times 10^6 \times 150 \times 10^{-6} = 942.47$$

$$X_C = \frac{1}{\omega C} = 795.77$$

$$(i) Z_1 = 1 + (942.47 - 795.77)j = 1 + 146.69j$$

$$(ii) Z_2 = 3 + (942.47 - 795.77)j = 3 + 146.69j$$

5.7

Problem-6.

(a) Draw a graph of OV where per inch voltage = 100 V

(b) Draw a graph of OC where per inch current = 20 A

(c) Draw ob, where $R_2 = 0$

$$I = \frac{V}{R + R_2 + jX}$$

$$= \frac{346.4}{2 + 0 + j(3.464)}$$


$$= 86.6 \angle -59.99$$

(d) Do yourself in graph page.


$$(e) P_{\max} = V \times I_{1d_{\max}}$$

find $I_{1d_{\max}}$ from the graph
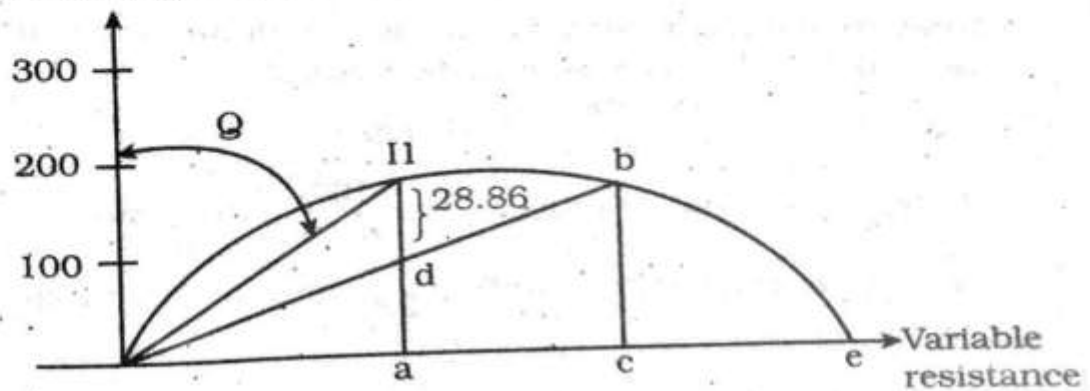
$$\text{Then, } P_{\max} = 346.4 \times 28.86$$



5.8

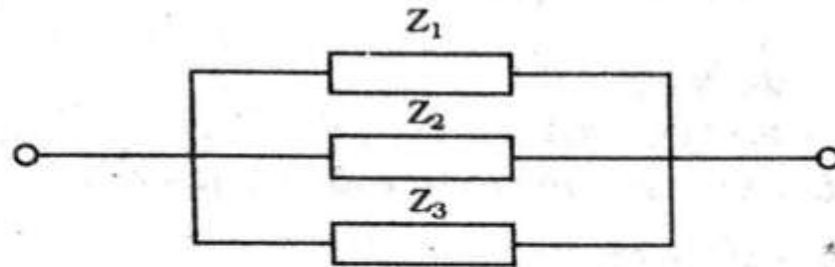

$$z_1 = 10 + j0$$

$$z_2 = 20 + 20j$$

$$z_3 = 30 - 40j$$

(a)	$Y_1 = \frac{1}{z_1} = 0.1$	$g_1 = 0.1$	$b_1 = 0$
	$Y_2 = 0.025 - 0.025j$	$g_2 = 0.025$	$b_2 = 0.025$
	$Y_3 = 0.012 + 0.016j$	$g_3 = 0.012$	$b_3 = 0.016$

(b) $g = g_1 + g_2 + g_3$
 $= 0.137 \Omega^{-1}$
 $b = 0.009 \Omega^{-1}$

(c) $I = VY = V(g - jb) = Vg - jVb$

So $I_{\text{in phase}} = Vg = 5.48 \text{ amp}$

$I_{\text{quadrature}} = Vb = 0.36 \text{ amp}$

5.9 Given here, $R_c = 1 \text{ ohm}$, $X_c = 10 \text{ ohm}$ $R_L = 60 \text{ ohm}$

$V = 100 \text{ v}$ When X_L is varied, quadrature component of current in inductive branch will be maximum when it is equal to the radius of circle made by locus of it.

$$\text{i.e. } I_L \sin\theta_L = \frac{V}{2R_L} = \frac{100}{2 \times 6} = 8.33 \text{ amp}$$

$$\text{When } R_L = 4 \text{ ohm, } I_L \sin\theta_L = \frac{V}{2R_L} = \frac{100}{2 \times 4} = 12.5 \text{ amp}$$

We know that, when $I_c \sin\theta_c > \frac{X}{2R_L}$ resonance cannot be obtained.

When, $I_c \sin\theta_c = \frac{V}{2R_L}$ resonance will occur. When $I_c \sin\theta_c < \frac{V}{2R_L}$ will occur twice

$$\begin{aligned} 11R_L = 6, I_0 \sin\theta_0 &= \frac{V}{\sqrt{R_0^2 + X_0^2}} \sin \tan^{-1} \frac{X_c}{R_0} \\ &= \frac{100}{\sqrt{1 + 100}} \times \sin \tan^{-1} \frac{X_c}{R_c} \\ &= 9.95 \times 0.99 \\ &= 9.9 \text{ amps} \end{aligned}$$

Again, $\frac{V}{2R_L} = 8.33$ amps which is less than $I_c \sin\theta_c$


\therefore resonance can be obtained when $R = 4$ ohm, $\frac{V}{2R_L} = 12.5$ amps

\therefore Resonance will occur at two points.

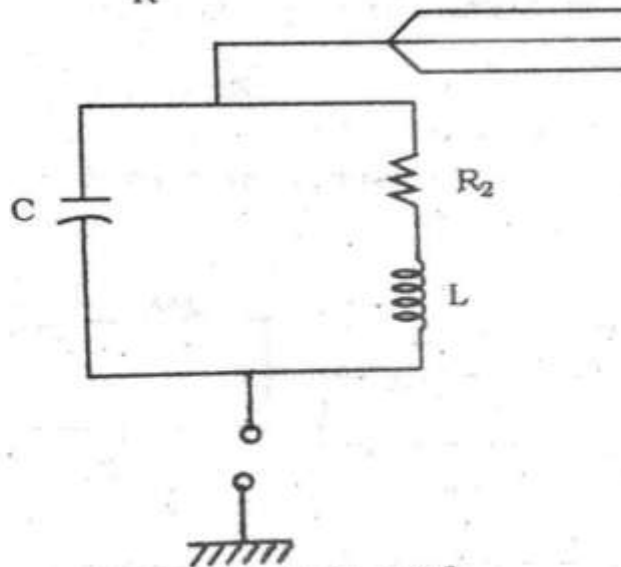5.9

$$L = 250 \times 10^{-6} \text{ henry}$$

$$F = 10^6 \text{ Hz, } \frac{X_L}{R} = 170$$



$$\begin{aligned} \text{Now, } X_L = \omega L &= 2\pi \times 10^6 \times 250 \times 10^{-6} \\ &= 1570.8 \end{aligned}$$

$$\therefore R = \frac{X_L}{170} = \frac{1570.8}{170} = 9.24 \text{ ohm}$$

(a) For resonance,

$$\frac{X_L}{R_L^2 + X_L^2} = \frac{X_C}{R_C^2 + X_C^2} \quad \left[\because R_C = 0 \quad X_C = \frac{1}{\omega C} \right]$$

$$\text{or, } \frac{X_L}{R_L^2 + X_L^2} = \omega C$$

$$\text{or, } C = \frac{1570.8}{2\pi \cdot 10^6 \{ (9.24)^2 + (1570.8)^2 \}} = 101.3 \times 10^{-12} \text{ f}$$

$$(b) \quad \omega_m = \frac{1}{\sqrt{LC}} = \frac{1}{L\omega_m^2} = \frac{1}{X_L\omega_m} = \frac{1}{1570.8 \times \omega_m}$$

$$(c) \quad \frac{1}{CR_L} = \frac{250 \times 10^{-6}}{101.3 \times 10^{-12} \times 9.24} = 267090.6 \text{ ohm}$$

$$(d) \quad Y = 9 - j b_2 + j b_c = \frac{R_1}{R_L^2 + X_L^2} - j \frac{X_2}{R_2^2 + X_L^2} + j \omega C$$

$$= \frac{9.24}{(9.24)^2 + (1555)^2} - j \frac{1555}{(9.24)^2 + (1555)^2} + j 2\pi \times 990$$

$$\times 10^3 \times 101.3 \times 10^{-11}$$

$$= 3.82 \times 10^{-6} - j 6.43 \times 10^{-4} + j 6.3 \times 10^{-4}$$

$$= 3.82 \times 10^{-6} - j 1.294 \times 10^{-5}$$


$$Z = \frac{1}{Y} = \frac{1}{3.82 \times 10^{-6} - j 1.29 \times 10^{-5}}$$

$$= \frac{1}{1.349 \times 10^{-5} \angle -73.5}$$

$$= 74105 \angle 73.5$$

5.10 Graphical measurement needed so you should try yourself.

5.11

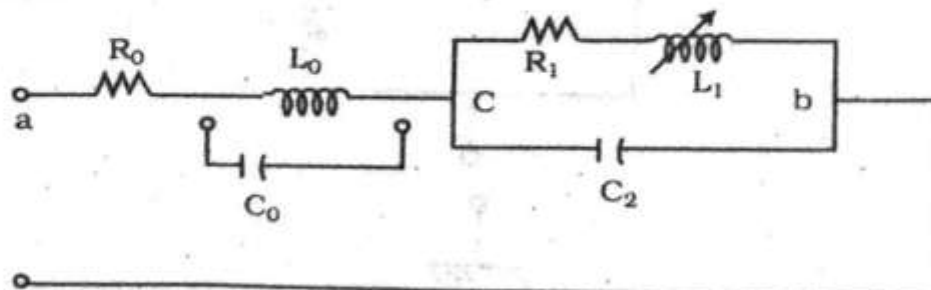

$$R_0 = 20 \Omega$$

$$R_1 = 40 \Omega$$

$$C_2 = 0.05 \mu$$

(a) For parallel resonance at 15000 Hz $b_s = bc$

$$\text{or, } \frac{\omega L}{R_1^2 + \omega^2 L^2} = \omega C$$

$$\text{or, } \omega^2 L^2 C = R_1^2 C - L = 0$$

$$\text{or, } \omega^2 L^2 C - L + R_1^2 C = 0$$

$$L = \frac{+1 \pm \sqrt{1 - 4 \cdot \omega^2 \cdot C \cdot R_1^2 C}}{2\omega^2 C}$$

$$L = \frac{+1 \pm \sqrt{1 - 4(2\pi \times 15000 \times 0.05 \times 10^{-6} \times 40)^2}}{2 \times (2\pi \times 15000)^2 \times 0.05 \times 10^{-6}}$$

$$= \frac{1 + 0.92622}{888.264}$$

$$= 2.17 \times 10^{-3} \text{ H (taking + ve)}$$

$$\text{or, } 0.083 \times 10^{-3} \text{ (taking - ve)}$$

$$X_{bc} = S_{L1} = \frac{R_1}{Z^2} = \frac{40}{40^2 + (\omega L)^2}$$

$$= \frac{40}{40^2 + (2\pi \times 15000 \times 2.17 \times 10^{-3})^2}$$

\therefore for lower conductance (i.e higher impedance)

we shall take 2.17×10^{-3}

(b) For 45000 Hz, $X_{L1} = 2\pi \times 45000 \times 2.17 \times 10^{-3} = 613.55$

ohm

$$X_{C2} = \frac{1}{2\pi \times 45000 \times 0.05 \times 10^{-6}} = 70.74 \text{ ohm}$$

$$\therefore Z_{bc} = \frac{(40 + j613.55) \times (-j70.74)}{(40 + j613.55) + (-j70.74)} = \frac{43493.682 \angle 3.73}{544.28 \angle 85.78}$$

$$= 79.91 \angle -89.51$$

$$= 0.68 - j79.9 \text{ be in predominantly capacitive}$$

(c) An inductive reactance of 79.9 ohm should be placed in series with R_0 to produce series resonance

$$\therefore L_0 = \frac{79.9}{2\pi \times 45000} = 0.283 \times 10^{-3} \text{ H}$$


(d) Z_{ab} at 45000 Hz = $0.68 - j79.9 + j79.9 + 26 = 20.68 \text{ ohm}$

$$Z_{ab} \text{ at } 15000 \text{ Hz} = Z_{bc} + Z_{ac} = \frac{1}{Y_{bc}} = Z_{ac}$$

72 The Solution of Alternating Current Circuits

$$\begin{aligned}
 \text{(e)} \quad & 1085.687 + 20 + j2\pi \times 15000 \times 0.283 \times 10^{-3} \\
 & = 2205.687 + j26.67 \\
 & = 1106 \angle 1.38 \\
 \therefore Z_{ab} & = 1106 \text{ ohm}
 \end{aligned}$$

5.12

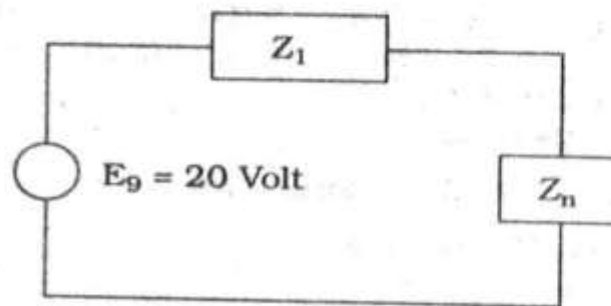

$$Z_1 = 0.5 + j1.5 + 4j = 2 + j5$$

$$\therefore Z_{\text{load}} = 2 - j0.5 \text{ ohm}$$

$$P_{\text{max}} = \frac{E_g^2}{4R_1} = \frac{20^2}{4 \times 2} = 50 \text{ watts}$$

$$\text{Current (I)} = \frac{20}{2 + j5 + 2 - j0.5} = 5 \text{ amps}$$


$$\begin{aligned}
 \text{5.13 } K & = \pm \frac{X_r}{R_r} \pm 5, R_r = \frac{Z_1}{\sqrt{1 + K^2}} = \frac{\{(1.5 + 0.5)^2 + (1 + 4)^2\}^{1/2}}{\sqrt{1 + 5^2}} \\
 & = 1.056 \text{ ohm}
 \end{aligned}$$

$$X_r = KR_r = \pm 5 \times 1.056 = \pm 5.28$$

$$\begin{aligned}
 \text{for positive } K, P_r & = I^2 R_r = \frac{E_g^2 R_r}{(R_1 + R_r)^2 + (X_1 + X_r)^2} \\
 & = \frac{20^2 \times 1.056}{(2 + 1.056)^2 + (5 + 5.28)^2}
 \end{aligned}$$

$$\begin{aligned}
 \text{for negative } K, P_r & = \frac{20^2 \times 1.056}{(3.056)^2 + (5 - 5.28)^2} \\
 & = 44.85
 \end{aligned}$$

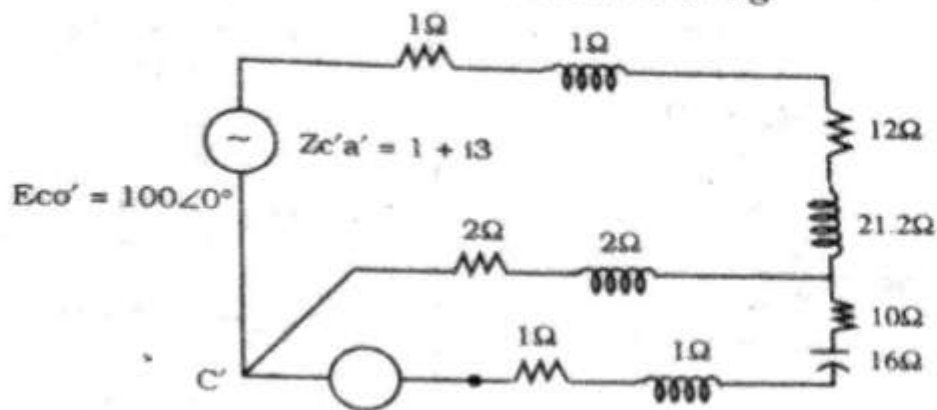5.14 Calculate the current in branch ac of fig.



$$E_{c'b'} = 100\angle 30$$

$$Z_{c'b'} = 1 + j3$$

$$\text{Assuming } E_{c'b'} = 0, \quad Z_{c'a'ac} = 1 + j3 + 1 + j1 + 12 + j21.2 \\ = 14 + j25.2$$


$$Z_{c'b'bc} = 1 + j3 + 1 + j1 + 15 - j16.6 = 17 - j12.6$$

$$Z_{c'b'bed} = \frac{(17 - j12.6)(2 + j2)}{17 - j12.6 + 2 + j2} = \frac{(17 - j12.6)(2 + j2)}{19 - j10.6} \\ = \frac{21.16\angle -36.54 \times 2.82\angle 45}{21.75\angle -29.15} = \frac{59.67\angle 8.46}{21.75\angle -29.15} \\ = 2.74\angle 37.64 = 2.17 + j1.67$$

$$\therefore Z_{a'acbc'} = 14 + j25.2 + 2.17 + j1.67 = 16.17 + j26.87 \\ = 31.36\angle 58.96$$

$$\therefore I_{a'ac} = \frac{100\angle 0}{31.36\angle 58.96} = 3.18\angle -58.93 = 1.64 - 2.72j$$

5.15

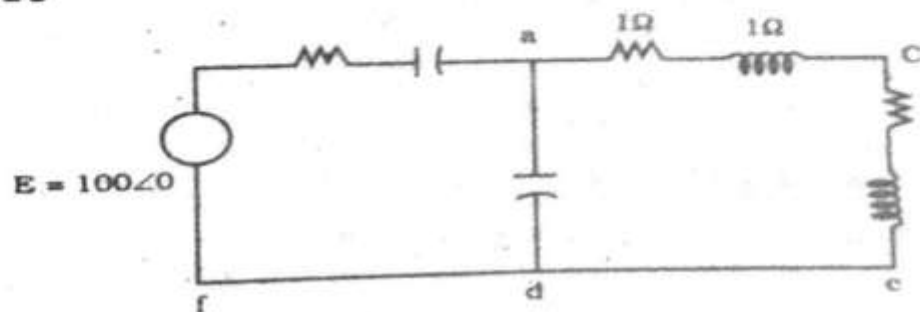

74 The Solution of Alternating Current Circuits

$$V_{ac} = 81 + j26 \text{ volts}$$

$$I_{ad} = \frac{81 + j26}{-j10}$$

$$= \frac{-26 + j81}{10}$$

$$= -2.6 + j8.1$$

$$I_{ef} = \frac{V_{ce}}{Z_{af}}$$

$$= \frac{(9.16 \angle 76.5) (2.55 - j0.621)}{2 - j2}$$

$$= 8.5 \angle 187.81^\circ$$

$$= -2.6 + 8.1j \text{ amp}$$

$$Z_{ec} = \frac{(2 - 2j)(3 + 4j)}{2 - 2j + 3 + 4j}$$

$$= \frac{6 + 8 - 6j + 8j}{5 + 2j}$$

$$= \frac{14 + 2j}{5 + 2j}$$


$$= \frac{(14 + 2j)(5 - 2j)}{25 + 4}$$

$$= \frac{1}{29} (70 + 4 + j10 - j28)$$

$$= \frac{1}{29} (7.4 - j18)$$

$$= 2.55 - j0.621 \text{ ohm}$$

5.16

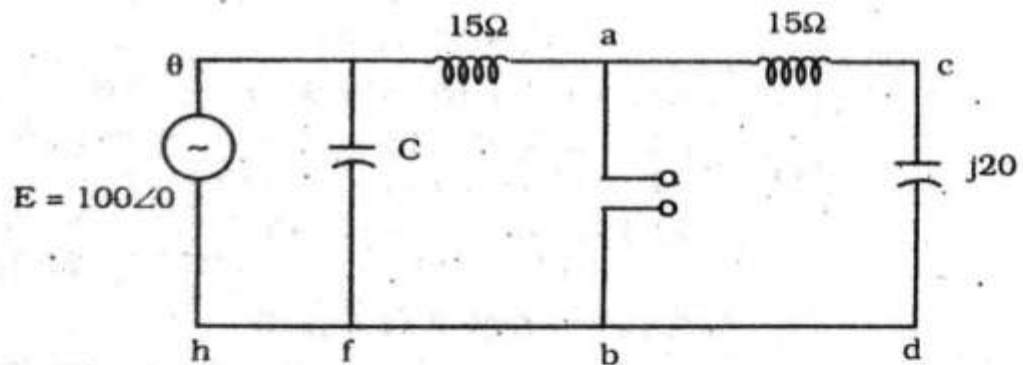

$$Z_{eacd} = 5j + 5j - 20j = -10j = 10 \angle -90^\circ$$

$$Z_{feacd} = \frac{10 \angle -90 \times 20 \angle -90}{-j10 - j20}$$

$$[\because Z_{ef} = -20j = 20 \angle -90^\circ]$$

$$= \frac{200 \angle -180}{20 \angle -90} = 6.66 \angle -90$$

$$\therefore \text{total } I = \frac{100 \angle 0}{6.66 \angle -90} = 15 \angle 90 = 15j$$

Assuming $E_{O'a'} = 0$

Then, $Z_{O'a'ac} = 14 + j25.2$, $Z_{cc'} = Z = 2j$

$$\begin{aligned} \therefore Z_{a'acdc'} &= \frac{(14 + 25.2j)(2 + 2j)}{(14 + j25.2) + (2 + 2j)} \\ &= \frac{(14 + j25.2)(2 + 2j)}{16 + j25.2} \\ &= \frac{81.27 \angle 105.94}{31.55 \angle 59.53} \\ &= 2.57 \angle 46.41 = 1.77 + 1.86j \end{aligned}$$

$$\begin{aligned} \therefore Z_{a'acbc'a'} &= 17 - 12.6j + 1.77 + 1.86j \\ &= 18.77 - 10.74j \\ &= 21.67 \angle -27.77 \end{aligned}$$

$$\begin{aligned} \therefore I_{c'bc} &= \frac{100 \angle 90}{21.62 \angle -29.97} \\ &= 4.62 \angle 119.77 = 2.29 + j4.01 \end{aligned}$$

$$\begin{aligned} \therefore I_{ca2} &= \frac{(2 + 2j)}{(2 + 2j) + 14 + 25.2j} \times 4.62 \angle 119.77 \\ &= 0.41 \angle 105.24 \end{aligned}$$

$$\begin{aligned} \therefore I_{ac} &= I_{a'ac1} - I_{ca2} \\ &= 1.64 - j2.72 - (-j0.1 + j0.39) \\ &= 1.64 - j2.72 + j0.1 - j0.39 \\ &= (1.74 - j3.11) \text{ amp} \end{aligned}$$

$$I_{of} = \frac{100 \angle 0}{-j20} = \frac{100}{20 \angle -90^\circ} = 5 \angle 90 = 5j$$

$$\therefore I_{ea} = 15j - 5j = 10j$$

$$V_{ea} = j10 \times 5j = j^2 50 = -50 \text{ volts}$$

$$\therefore \text{voltage of ab} = 100 - (-50) = 150 \angle 0^\circ \text{ volts}$$


$Z_{eaf} = 5j$ [\therefore when 9h point is shorted the current will not flow through ef]

$$Z_{eca} = 5j - 20j = 15 \angle 90$$

$$Z_0 = (5j) \parallel (15j) = 7.5j$$

$$I_b = \frac{V_{ab}}{Z_0 + Z_L} = \frac{15}{7.5j + 10 - 7.5j} = 15 \angle 0$$

5.17

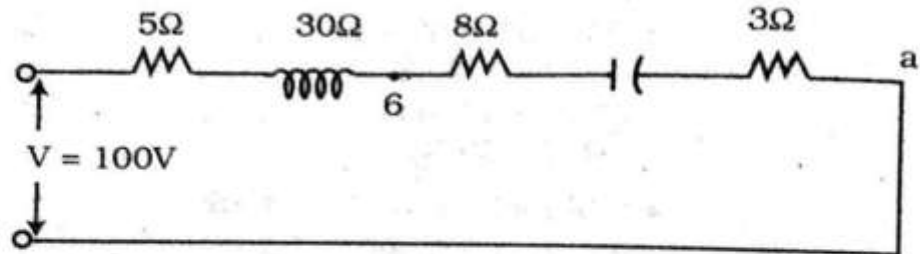

$$Z = Z_{ab} + Z_{bc} + Z_{cd} = 5 + j30 + 8 - j18 + 3 + 16 + j12$$


$$\therefore I = \frac{100\angle 0}{16 + j12} = \frac{100\angle 0}{20\angle 36.869} = 5\angle -36.86 = 16 - 12j \text{ amp}$$

$$\begin{aligned} V_{ab} &= I Z_{ab} = 5\angle -36.869 \times (5 + 30j) \\ &= 152 \angle 43.6686 = 109.94 + 104.95j \end{aligned}$$


$$\begin{aligned} V_{bc} &= I Z_{bc} = 5\angle -36.869 \times (8 - j18) \\ &= 98.48 \angle -102.9065 \\ &= -21.996 - j95.99 \text{ volt} \end{aligned}$$

$$V_{cd} = I Z_{cd} = 3(16 - j12) = 48 - j36 \text{ volt}$$

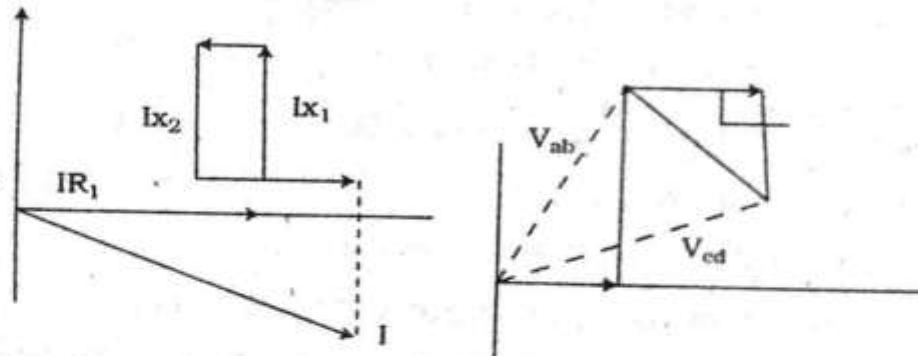
$$\text{Power factor} = \frac{R}{Z} = \frac{16}{20} = 0.8 \text{ lagging}$$



5.18

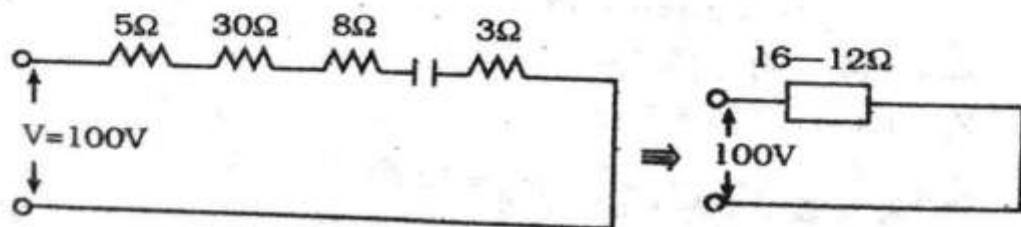

Adding a Resistance.

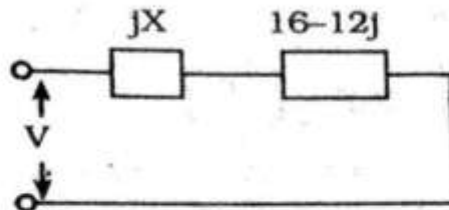


$$\text{So } \tan^{-1} \frac{X-12}{16} = 0.6$$

$$\text{So } \frac{X-12}{16} = 0.01047$$

$$\text{or, } X-12 = 0.16755$$

$$\text{or, } X = 12.167$$

5.19

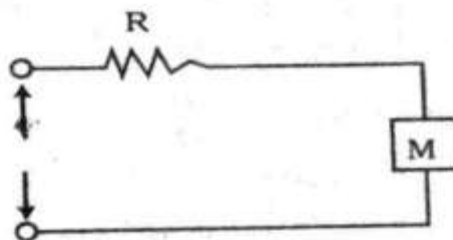

It is clear from the problem that $V_R = 110 \text{ V}$

Now I_R should be deducted.

$$\text{So } P = \frac{1}{4} \times 0.6 \times 746 = 111.9 \text{ Watt}$$

$$\text{VA} = 186.5 \text{ VA}$$

$$\text{So } I_R = I_M = \frac{186.5}{2110} = 1.695 \angle -53.13 \text{ A}$$

$$\text{So, } R = \frac{110}{1.695} = 64.896 \Omega$$

5.20

$$P = VI \cos \theta \text{ or } 300 = 120 \times 5 \times \cos \theta \therefore \theta = 60^\circ$$

Since lagging p.f. \therefore voltage is leading

$$\text{Now, } I^2 R_L = 300 \text{ or } R_L = \frac{300}{5^2} = 12 \text{ ohm}$$

$$\text{Now, } \tan 60^\circ = \frac{X_{\text{load}}}{R_{\text{load}}} \therefore X_{\text{load}} = 20.78 \text{ ohm}$$

$$Z = \sqrt{12^2 + (X_L - X_C)^2}$$

78 The Solution of Alternating Current Circuits


Now, $I = \frac{V}{Z}$ or, $Z = \frac{240}{\sqrt{12^2 + (X_L - X_C)^2}}$

or, $12^2 + (X_L - X_C)^2 = \left(\frac{240}{5}\right)^2$

or, $X_L - X_C = \pm \sqrt{48^2 - 12^2} = \pm 46.476$

or, $X_C = 20.78 \pm 46.476 = 67.256$

or, -25.696 (it is inductive) hence

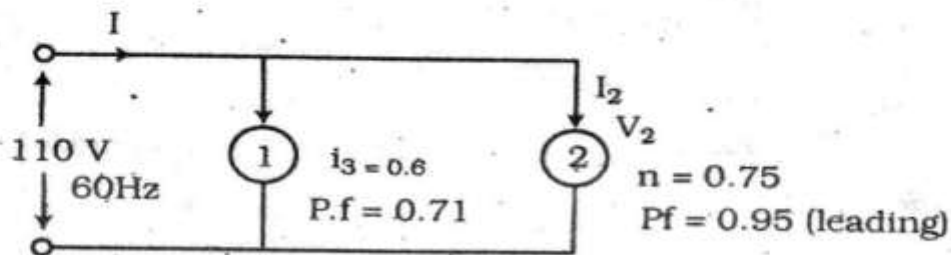

$P = VI_1 \cos\theta = 746 \times \frac{1}{3} \times \frac{100}{60}$

$\therefore I_1 = \frac{\left[746 \times \frac{1}{3} \times \frac{100}{60}\right]}{(110 \times 0.7)} = 5.382 \text{ amp}$

$\cos\theta = 0.7 \therefore \theta_1 = 45.57^\circ$

Since current is lagging

$\therefore I_1 = 5.382 \angle -45.57^\circ \quad [\cos\theta_2 = 0.95 \therefore \theta_2 = 18.19^\circ]$

$I_2 = \frac{746 \times \frac{100}{75}}{110 \times 0.95} = 4.76$

Since power factor is leading

$\therefore I_2 = 4.76 \angle 18.19^\circ$


Now,

$$\begin{aligned} I &= I_1 + I_2 \\ &= 5.382 \angle -45.57^\circ + 4.76 \angle 18.19^\circ \\ &= 3.768 - j3.843 + 4.52 + j1.49 \\ &= 8.617 \angle -15.83^\circ \end{aligned}$$

$P = VI \cos\theta = 110 \times 3.617 \cos(-15.83) = 911.8 \text{ watts}$

Resultant power factor = $\cos(-15.83^\circ) = 0.962$ lagging

5.21

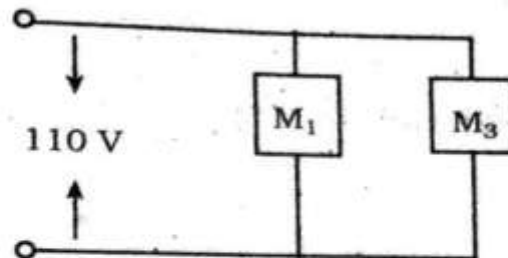

$$P_1 = \frac{1}{3} \times 746 \times 0.6 = 149.2 \text{ W}$$

$$P_2 = \frac{1}{2} \times 746 \times 0.75 = 279.75 \text{ W}$$


$$VA_1 = \frac{149.2}{0.70} = 213.142 \text{ VA}$$

$$VA_2 = \frac{289.75}{0.95} = 294.473 \text{ VA}$$

So, $I_1 = \frac{213.142}{110} = 1.937 \text{ A}$

$$I_2 = \frac{294.473}{110} = 2.677 \text{ A}$$

5.22

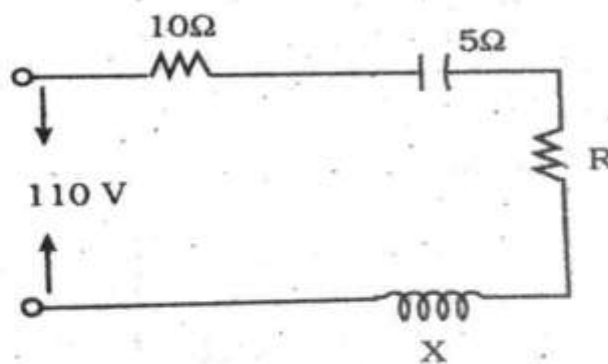

Now,

$$I^2 R = 50$$

or, $I^2 = \frac{50}{R}$ (i)

$$V_X = XI$$

Now, $V_X I = 100 \text{ vars}$

or, $X I^2 = 100$

$$I^2 = \frac{100}{X} \text{ (ii)}$$

From equation (i) and (2)

$$\frac{50}{R} = \frac{100}{X}$$

$$\therefore X = 2R$$

$$\text{Now, } Z = \sqrt{(100 + R)^2 + (X - 5)^2}$$

Now,

$$V = ZI$$

$$\text{or, } V^2 = Z^2 I^2$$

$$\text{or, } 100^2 = \{(10 + R)^2 + (2R - 5)^2\}$$

$$\text{or, } 100^2 = (100 + 20R + 4R^2 - 20R + 25) \times \frac{50}{R}$$

$$\text{or, } 250R^2 - 10000R + 6250 = 0$$

$$\text{or, } R^2 - 40R + 25 = 0$$

$$\therefore R = \frac{40 \pm \sqrt{1600 - 100}}{2}$$

$$= 39.36 \text{ ohm}$$

$$\therefore X' = 78.72 \text{ ohm or, } 1.72 \text{ ohm}$$


5.23

$$P = VI \cos\theta$$

$$\therefore \cos\theta = \frac{1150}{115 \times 10} = 1$$

$$R = \frac{V}{I} = \frac{115}{10} = 11.5 \text{ volts}$$
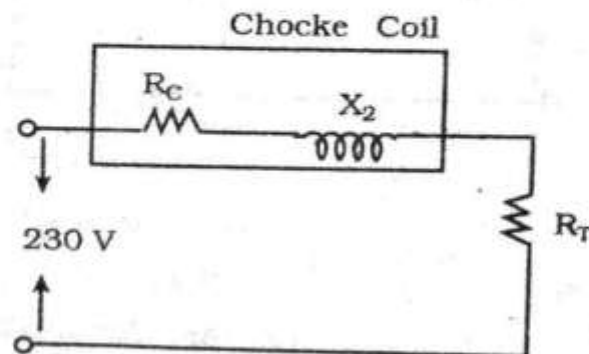
$$\frac{X_L}{R_0} = 5 \text{ i.e. } X_L = 5R_C$$



$$Z_{CKI} = R + R_0 + j \times L = 11.5 + j0.5 R_C$$

Now,

$$I = \frac{V}{Z} \quad \text{i.e. } 10 = \frac{230}{\sqrt{(11.5 + R_C)^2 + (5R_C)^2}}$$

$$\text{or. } (11.5 + R_C)^2 + 25R_C^2 = 23^2$$

$$\text{or. } 26R_C^2 + 23R_C - 396.75 = 0$$

$$\text{or. } R_C = \frac{-23 \pm \sqrt{529 + 41262}}{52}$$

$$= 3.49 \text{ ohm}$$

$$\therefore X_L = 17.45$$

$$\text{(a) } Z_{\text{coil}} = 3.49 + j17.45 = 17.8 \angle 78.69^\circ \text{ ohms}$$

$$\text{(b) } Z_{\text{ckt}} = (11.5 + 3.45) + j 17.45 = 23 \angle 49.34^\circ \text{ ohms}$$

$$\text{P.f.} = \cos (49.34) = 0.652$$

5.24 For series resonance,

$$X_L = X_C$$

Reactance present in the ckt = $30 - 18 = 12$ ohm

Hence, we need 12 ohm capacitive reactance.


Now,

$$\frac{1}{2\pi \times 60 \times C} = 12$$

$$\text{or. } C = \frac{106}{2\pi \times 60 \times 12}$$

$$= 221 \mu\text{f}$$

5.25

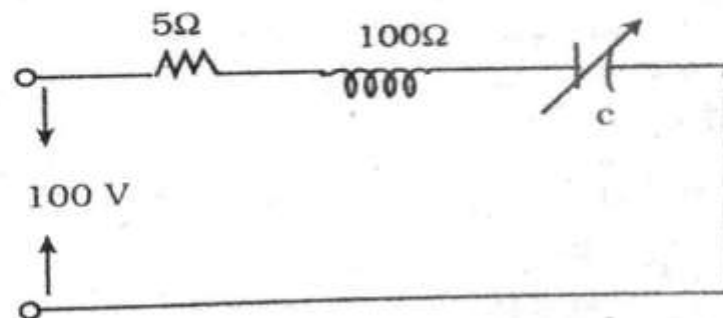

For max voltage across C

$$\text{(a) } X_C = \frac{R^2 + X_L^2}{X_L} = \frac{5^2 + 100^2}{100} = 100.29 \text{ ohm}$$

82 The Solution of Alternating Current Circuits

Now,

$$I = \frac{100}{\sqrt{5^2 + (100 - 100.25)^2}} = 19.975 \text{ A}$$

Now,


$$V_C = IX_C = 19.975 \times 100.25 = 2002.5 \text{ V}$$

$$(b) X_C = \frac{100^2 + 100^2}{100} = 200$$

$$\therefore I = \frac{100}{100^2 + 100^2} = 0.005 \text{ A}$$

$$\therefore V_C = IX_C = 200 \times 0.005 = 1 \text{ V}$$

5.26

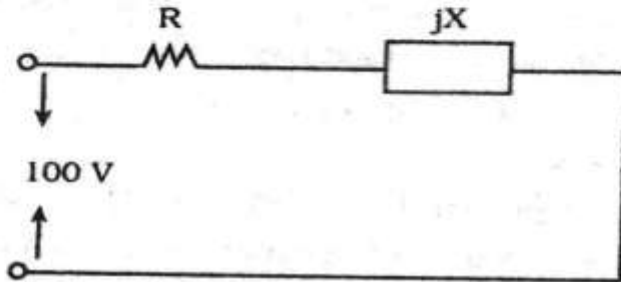

$$VI = 1000$$

$$\text{or, } 100 I = 1000$$

$$\text{or, } I = 10 \text{ A}$$

$$I = \frac{100}{\sqrt{8^2 + X^2}}$$

$$\text{or, } 100 = \frac{100^2}{8^2 + X^2}$$

$$\text{or, } 8^2 + X^2 = 100$$

$$\therefore X = \pm 6 \text{ ohm}$$

5.27

$$Q = \frac{f_m}{\Delta f}$$

$$\text{or, } \frac{f_m}{100} = 50$$

$$\therefore f_m = 5000 \text{ Hz}$$

So the frequency limits on $(5000 - \frac{100}{2})$ and $(5000 + \frac{100}{2})$

i.e. 4950 and 5050

5.28

$$\begin{aligned}
 \text{(a) } f_m &= \frac{1}{2\pi} \\
 &= \frac{1}{\sqrt{LC}} \\
 &= \frac{1}{2\pi \sqrt{1000 \times 10^{-3} \times 10 \times 10^{-2}}} \\
 &= 159154.94 \text{ Hz}
 \end{aligned}$$

$$\begin{aligned}
 \text{(b) } Q &= \frac{1}{R_s} \sqrt{\frac{L}{C}} \\
 &= \frac{1}{1000} \sqrt{100 \times 10^{-3} \times 10 \times 10^{-12}} = 100
 \end{aligned}$$

$$\begin{aligned}
 \text{(c) } Q &= \frac{f_m}{\Delta f} = \frac{\omega_m}{\delta \omega} \\
 \therefore \Delta \omega &= \frac{1 \times 10^6}{100} = 10^4
 \end{aligned}$$

$$\begin{aligned}
 \therefore \omega_m &= 1 \times 10^6 \text{ rad/sec} \\
 \text{So, } \omega_2 &= (1 \times 10^6 + \frac{10^4}{2}) = 1005000 \text{ rad/sec} \\
 \omega_1 &= (1 \times 10^6 - \frac{10^4}{2}) = 995000 \text{ rad/sec}
 \end{aligned}$$

$$\begin{aligned}
 \text{(d) } X_C &= \frac{1}{2\pi f_C} = \frac{1}{2\pi \times 159 \times 10^3 \times 10 \times 10^{-12}} \\
 &= 100097.45 \text{ Ohm}
 \end{aligned}$$

Now,

$$2\pi fL = \frac{X_C^2 + R^2}{X_C}$$

$$\therefore L = \frac{X_C^2 + R^2}{X_C \times 2\pi f} = 100.2 \times 10^{-3} \text{ H} = 100.2 \text{ mH}$$

5.29

$$\text{(a) } b_L = bc$$

$$\text{or, } \frac{X_L}{R_L^2 + X_L^2} = \frac{X_C}{R_C^2 + X_C^2}$$

$$\text{or, } \frac{X_L}{X_L^2 + 31.25^2} = \frac{40}{900 + 1600}$$

$$\text{or, } 40 X_L^2 + 2500 X_L - 39002.5 = 0$$

$$\text{or, } X_L = \frac{-2500 \pm \sqrt{2500^2 + 4 \times 40 \times 39062.5}}{2 \times 40} = 31.29 \text{ ohm}$$

$$(b) I_C = \frac{100 \angle 0}{30 - j40} = 2 \angle 53.13^\circ$$

$$OM = L_C = 2$$

$$MP = \frac{V}{2R_L} = \frac{100}{2 \times 31.5} = 1.6$$

$$\angle OMP = 180 - 53.13^\circ = 126.87^\circ$$

$$\begin{aligned} OP &= \sqrt{OM^2 + MP^2 - 2OM \cdot MP \cos \angle OMP} \\ &= \sqrt{2 + 1.6^2 - 2 \times 2 \times 1.6 \cos 126.87} \\ &= 3.225 \end{aligned}$$

Now,


$$I_m = OP - PQ = 3.225 - 1.6 = 1.625$$

$$\therefore Z_{\max} = \frac{100}{1.625} = 61.54$$

Now,

$$\angle MOP = \cos^{-1} \frac{OM^2 + OP^2 - MP^2}{2OM \cdot OP} = 23.38^\circ$$
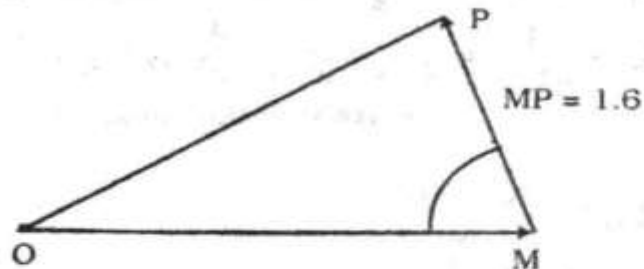
$$\text{Now, } \theta = \theta_C - \angle MOP = 29.75^\circ$$



Where,



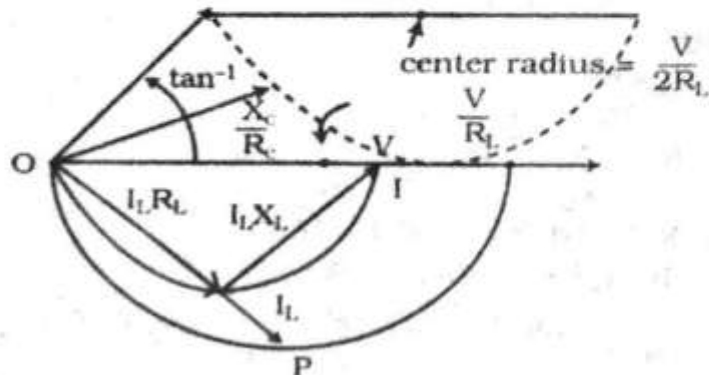


Fig : Locus of I as L is varied

Final picture when L is varied,

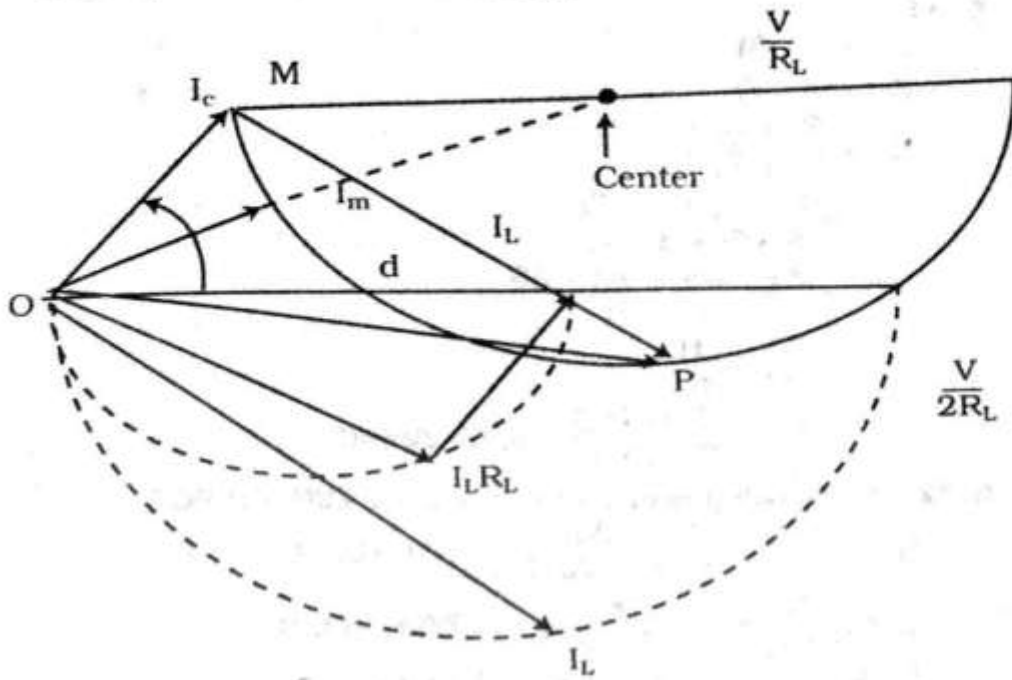

5.30

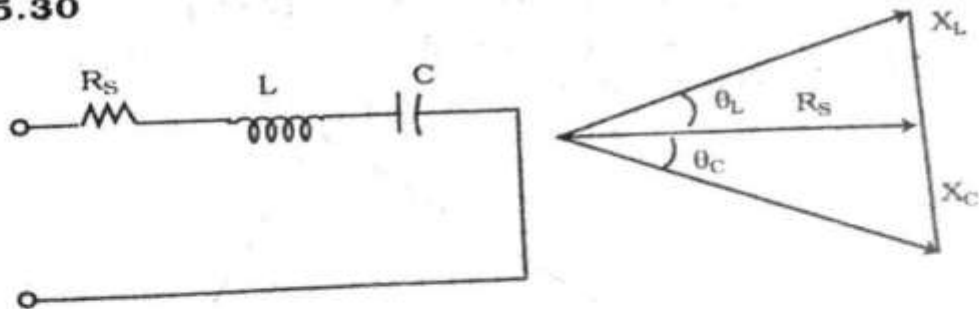

(a) Now,

$$\begin{aligned} \theta_s &= \frac{\text{Reactive factor of the coil}}{\text{power factor of the coil}} \\ &= \frac{\sin \theta_L}{\cos \theta_L} = \tan \theta_L \end{aligned}$$

(b) Power factor of the coil.

$$\cos \theta_L = \frac{1}{\sec \theta_L} = \frac{1}{\sqrt{1 + \tan^2 \theta_L}} = \frac{1}{\sqrt{1 + Q_s^2}}$$

$$\text{where. } Q_s = \frac{X_L}{R_s} = \frac{\omega_m L}{R_s}$$

5.31

$$Z_1 = 8 - 5j$$

$$Z_2 = 3 + 7j$$

$$Z = \frac{Z_1 \times Z_2}{Z_1 + Z_2}$$

$$= \frac{(8 - 5j)(3 + 7j)}{8 - 5j + 3 + 7j}$$

$$= \frac{24 - 15j + 56j + 35}{11 + 2j}$$

$$= \frac{59 + 41j}{11 + 2j}$$

$$= \frac{71.84 \angle 34.796}{11.18 \angle 10.3}$$

$$= 6.43 \angle 24.45$$

5.32 \therefore overall power factor = $\cos 24.796 = 0.907$

$$I_1 = \frac{100}{8 - 5j} = \frac{100}{9.433 \angle -32.605} = 10.6 \angle 32$$


$$I_2 = \frac{100}{3 + 7j} = \frac{100}{7.615 \angle 66.8} = 13.13 \angle -66.8$$

$$I = I_1 + I_2 = 10.6 \angle 32 + 13.13 \angle -66.8$$

$$= 8.99 + 5.61j + 5.17 - 12.06j$$

$$= 15.55 \angle -24.48$$

25 volt = 1", 5A = 1"

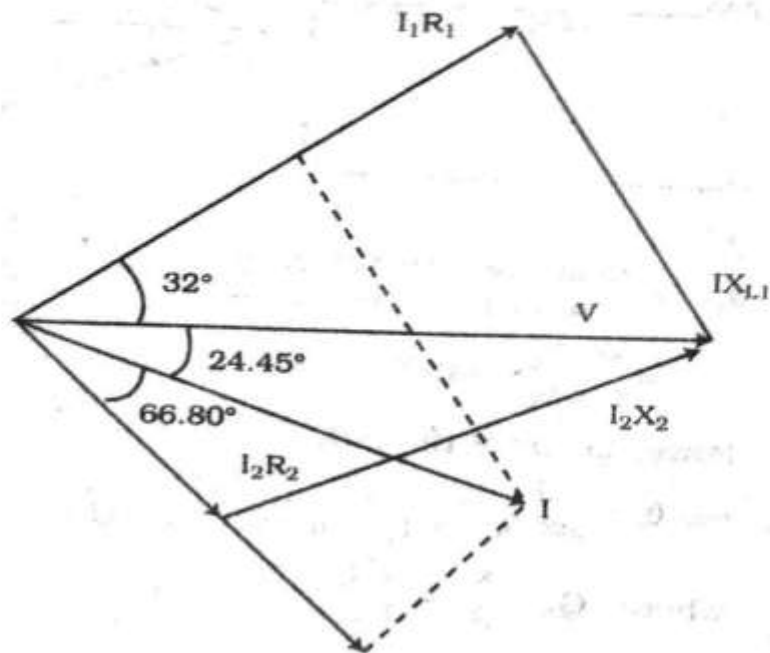


5.33 Here given,

$$R_L = 12 \Omega$$

$$X_L = 16 \Omega$$

$$X_C = ?$$

$$R_C = 0$$

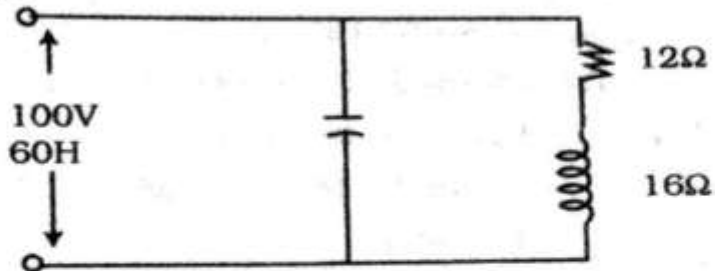

At resonance,

$$\frac{X_L}{R_L^2 + X_L^2} = \frac{X_C}{R_C^2 + X_C^2}$$

$$\frac{16}{12^2 + 16^2} = \frac{X_C}{0^2 + X_C^2} = \frac{1}{X_C}$$

$$\therefore X_C = \frac{12^2 + 16^2}{16} = 25 \text{ ohm}$$

$$\text{or, } \frac{1}{2\pi f_C} = C$$

$$\therefore C = \frac{1}{50\pi} \times 10^6 = 106.1 \mu\text{f}$$

5.34


(1) When P.f = 0.8 lagging

$$\theta = \cos^{-1} 0.8 = 36.86 \text{ lagging}$$

$$Z_L = 12 + j16 = 20 \angle 53.13^\circ$$

$$X_C = 0 - jX_C = X_C \angle -90^\circ$$
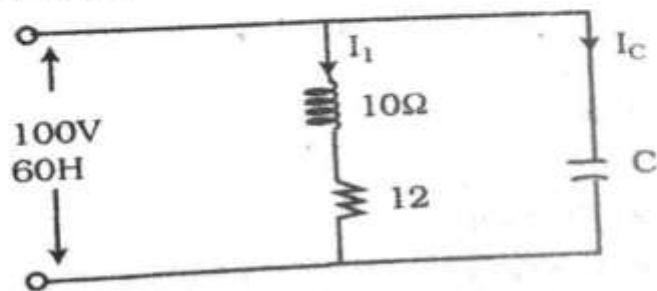
$$\therefore I_L = \frac{10 \angle 0}{20 \angle 53.13} = 5 \angle -53.13^\circ$$



$$I_C = \frac{100 \angle 0}{X_C \angle -90^\circ} = \frac{100 \angle 90^\circ}{X_C}$$

88 The Solution of Alternating Current Circuits

From the vector we get,

$$I_{XL} = I_L \cos 53.15^\circ = 3$$

$$I_{YL} = I_L \sin 53.15^\circ = 40 \text{ omp}$$

$$I' = I_{XL} \tan 36.88^\circ$$

$$= 3 \times \tan 36.88^\circ = 2.2508$$


$$= 1.75 \text{ amp}$$

$$\therefore |X_C| = \frac{100}{1.75} = 57.143$$

$$\therefore C = \frac{1}{2\pi f X_C} \times 10^6 = 46.42 \mu f$$

When, P.f = 0.8 leading
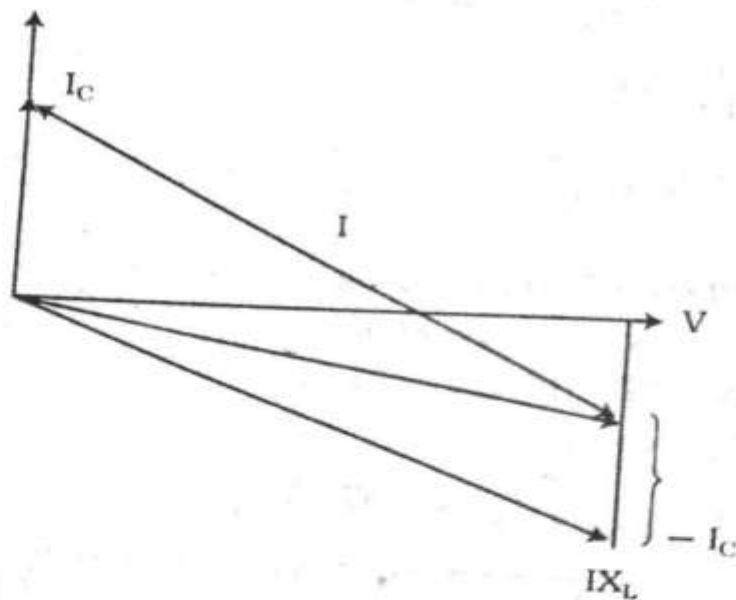
$$\theta = \cos^{-1} 0.8 = 36.87^\circ \text{ leading}$$



In this case

$$I_C = I_{YL} = I'$$


$$= 4 + 2.2508$$

$$= 6.2508 \text{ amp}$$

$$\therefore X_C = \frac{100}{6.2508} = 15.991$$

$$\therefore C = \frac{1 \times 10^6}{2 \times 3.14 \times 60 \times 15.991}$$

$$= 156.8 \mu f$$

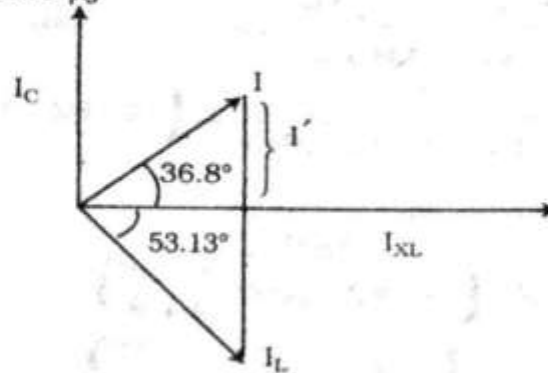

5.35

$$Y_1 = 0.03 - j0.04$$

$$Y_2 = \frac{1}{R}$$

$$Y = 0.03 + \frac{1}{R} = j0.04$$

Impedance angle,

$$\theta = -\tan^{-1} \frac{-0.04}{0.03 + \frac{1}{R}} \quad [P.f \cos\theta = 0.8 \quad \theta = 36.86^\circ]$$


$$= 36.86 = \tan^{-1} \frac{-0.04}{0.03 + \frac{1}{R}}$$

$$\text{or, } \frac{-0.04}{0.03 + \frac{1}{R}} = -0.75$$

$$\text{or, } 0.0225 + 0.75 \frac{1}{R} = 0.04$$

$$\text{or, } \frac{1}{R} = \frac{0.04 - 0.0225}{0.75} \quad [\therefore R = 42.86 \Omega]$$

5.36

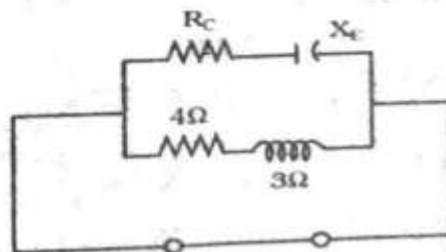

$$X_C = 5$$

$$\therefore X_C = 5R_C$$

$$\begin{aligned}
 Z &= \frac{(4 + 3j)(R - 5Rj)}{4 + j3 + R - 5Rj} \\
 &= \frac{(5 \angle 36.87^\circ)(5.1R \angle -78.69^\circ)}{\sqrt{(4 + R)^2 + (3 - 5R)^2}} \angle \tan^{-1} \frac{3 - 5R}{4 + R} \\
 &= \frac{25.5R}{\sqrt{(4 + R)^2 + (3 - 5R)^2}} \angle \left(-41.82 - \tan^{-1} \frac{3 - 5R}{4 + R} \right)
 \end{aligned}$$

Now,

$$\begin{aligned}
 I \angle \theta &= \frac{V \angle 0^\circ}{Z \angle \left(-41.82 - \tan^{-1} \frac{3 - 5R}{4 + R} \right)} \\
 &= \frac{V}{Z} \angle \left(41.82 + \tan^{-1} \frac{3 - 5R}{4 + R} \right)
 \end{aligned}$$

$$\therefore \theta = 41.82 + \tan^{-1} \frac{3 - 5R}{4 + R}$$

Now, $\theta = \cos^{-1} 0.8 = 36.87$ (since leading)

$$\therefore 36.87 = 41.82 + \tan^{-1} \frac{3 - 5R}{4 + R}$$

$$\text{or, } \frac{3 - 5R}{4 + R} = \tan^{-1} (-4.85)$$


$$\text{or, } 3 - 5R = 0.0866(4 + R)$$

$$\therefore R = 0.681 \text{ ohm}$$

Now,

$$X_C = 5 \times 0.681 = 3.405 \text{ ohm}$$
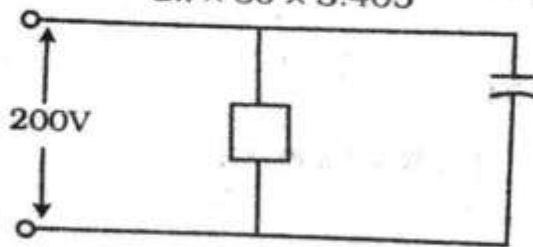
$$\therefore C = \frac{1}{2\pi \times 60 \times 3.405} = 779 \mu\text{f}$$



Now,

$$I^2 R = P$$

$$\text{or, } R = \frac{5 \times 10^3}{41.67^2}$$

$$= 2.80 \text{ ohm}$$

Now,

$$41.67 = \frac{200}{\sqrt{2.88^2 + X_L^2}}$$

$$\text{or, } X_L^2 = \frac{200^2}{41.67^2} - 2.88^2$$

$$\therefore X_L = 3.81 \text{ ohm}$$

$$P = VI \cos \theta$$

$$\text{or, } 5 \times 10^3 = 200 \times I \times 0.6$$

$$\therefore I = 41.67 \text{ A}$$

$$\theta = \cos^{-1} 0.6 = 53.13$$

Now,

$$I = 41.67 \angle -53.13$$

Now, for $P.f = 1$ we have

$$b_L = b_C$$

$$\text{or, } \frac{3.84}{2.88^2 + 3.84^2} = \frac{1}{X_C}$$

$$\therefore X_C = 6 \text{ ohm}$$

Now, volt - amp

$$= V_C I_C = \frac{V_C^2}{X_C} = \frac{200^2}{6}$$

$$= 6.67 \times 10^3 \text{ volt amp}$$

$$= 6.67 \text{ KVA}$$

5.37

5.38

5.39


$$\text{5.40 KVA} = \frac{KW}{P.f} = \frac{2000}{0.8} = 2500$$

$$\text{Required cost} = \$ 2500 \times (200 \times 0.08) = \$40,000$$

$$\text{KVA} = \frac{2000}{1} = 2000$$

$$\therefore \text{Required cost} = 200 \times 200 \times 0.08 = \$32000$$

5.41

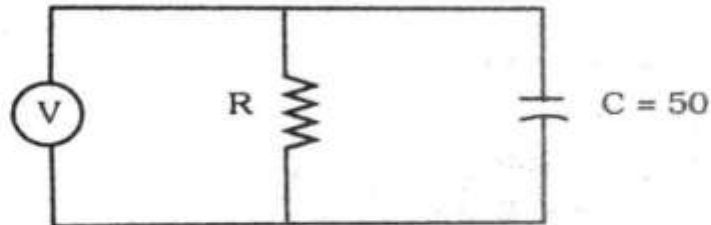

Here given, $C = 50 \mu f$, $P.f = 0.6$, $R = ?$, $f = 60 \text{ Hz}$

We know that,

$$X_C = \frac{10^6}{2\pi f C \mu f} = \frac{10^6}{2\pi \times 60 \times 50}$$

$$= 53.05 \text{ ohm}$$

Here, $\cos\theta = 0.6$ $\theta = \cos^{-1} 0.6 = 53.13^\circ$

$$\tan\theta = \frac{X_C}{R}$$

$$\therefore \tan(53.13) = \frac{53.05}{R}$$

$$\therefore R = 39.78 \text{ ohm}$$

5.42


$$f_m = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{100 \times 10^6 \times 400 \times 10^{-12}}}$$

$$= 795.775 \times 10^3 \text{ Hz}$$

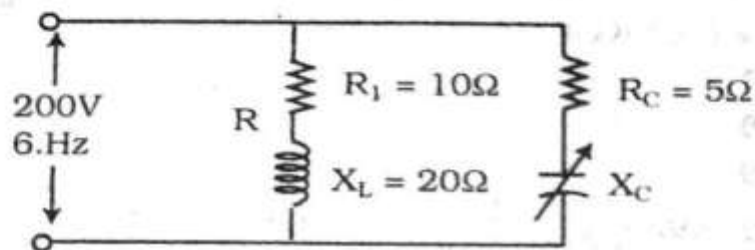5.43. For resonance

$$b_L = b_C$$

$$\frac{20}{10^2 + 20^2} = \frac{X_C}{X_C^2 + 5^2}$$



$$\text{or, } X_C^2 - 2500 X_C = 25 \times 20 = 0$$

$$\text{or, } X_C^2 - 25 X_C = 25 = 0$$

$$\therefore X_C = \frac{25 \pm \sqrt{25^2 - 4 \cdot 25}}{2}$$

$$= 23.96 \text{ ohm}$$

$$\text{or, } 1.044 \text{ ohm}$$

$$|I_C| = \frac{200}{\sqrt{5^2 + 23.96^2}} = 8.172 \text{ A}$$

$$\therefore P_C = 8.172^2 \times 5 = 333.9 \text{ W}$$

$$|I_C| = \frac{200}{\sqrt{5^2 + 1.044^2}} = 39.156 \text{ A}$$

$$\therefore P_C = 7665.96 \text{ W}$$

5.44 For max^m impedance current will be min.

$$I_L = \frac{200 \angle 0}{10 + j20}$$


$$= 8.944 \angle -63.43^\circ$$

For triangle ABP

$$AB = |I_L| = 8.94$$

$$BP = \frac{V}{2R_C} = \frac{200}{2 \times 5} = 20$$
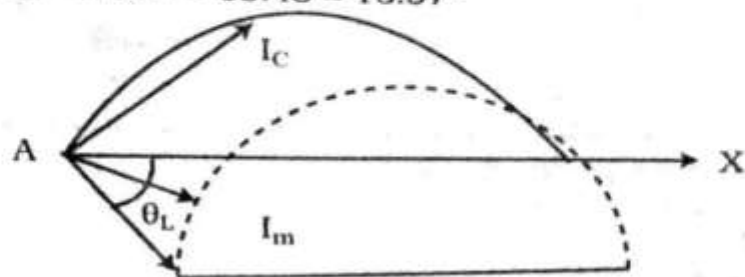
$$\angle ABP = 180^\circ - 63.43 = 16.57^\circ$$



Now,

$$AP = (AB^2 + BP^2 - 2AB \cdot BP \cos \theta \angle ABP)^{1/2} = 25.3$$

$$|I_m| = 25.3 - 20 = 5.3A$$

$$\angle PAB = \cos^{-1} \frac{AB^2 + AP^2 - BP^2}{2AB \cdot AP} = 44.97^\circ$$

$$\therefore \angle PAX = 63.43 - 44.97 = 18.46^\circ$$

$$\therefore I_m = 5.3 \angle -18.46^\circ$$

Now,

$$\begin{aligned} I_C &= I_m - I_L \\ &= 5.3 \angle -18.46 - 8.94 \angle -63.43^\circ \\ &= 1.03 + j6.32 \\ &= 6.4 \angle 80.74 \end{aligned}$$

Now,

$$6.4 = \frac{200}{\sqrt{5^2 + X_C^2}}$$

$$\text{or, } |X_C| = 30.85 \text{ ohm}$$

$$\therefore C = \frac{1}{2\pi \times 60 \times 30.85} = 85.98 \mu f$$

5.45 From the circle diagram, there will be only one resonance.


when.

$$I_L \sin \theta_L = \frac{V}{2R_C}$$

$$\text{or, } R_C = \frac{200}{18.94 \sin 63.43} = 12.506 \text{ ohm}$$

Hence any value of R_C over 12.506 ohm will prevent the possibility of attaining resonance.

5.46.

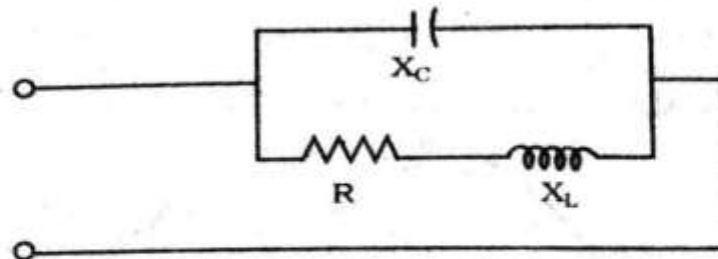

For unity power factor

$$b_L = b_C$$

$$\frac{X_L}{R^2 + X^2} = \frac{1}{X_C}$$

$$X_L^2 - X_L X_C + R^2 = 0$$

$$X_L = \frac{X_C \pm \sqrt{X_C^2 - 4R^2}}{2}$$

$$= \frac{X_C}{2} \pm \sqrt{\frac{X_C}{4} - R^2}$$

5.47


$$Y = j\omega C + \frac{1}{R}$$

$$Y = \sqrt{\frac{1}{R^2} + (\omega C)^2} \angle \tan^{-1} \frac{\omega C}{\frac{1}{R}}$$


$$Y = f = \frac{\omega}{2\pi}$$

Plot the graph (semi-log graph of which X is used as log scale) of given values.

5.48 (a) Vector diagram.

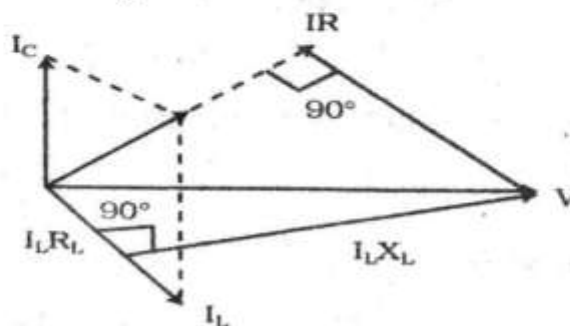

(b)

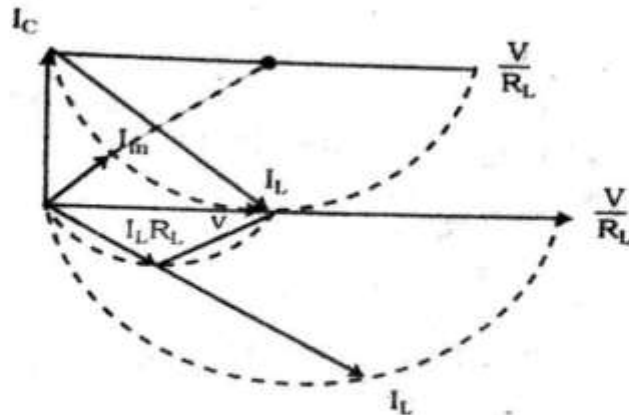

when X_L is swept from 0 to ∞

(c) Analytically,

$$b_L = bc$$

$$\frac{X_L}{R^2 + X_L^2} = \frac{1}{X_C}$$

or, $\frac{X_L}{64 + X_L^2} = \frac{1}{20}$

or, $X_L^2 - 20X_L + 64 = 0$

or, $X_L = \frac{20 \pm \sqrt{20^2 - 4 \times 64}}{2}$

$$= \frac{20 \pm 12}{2}$$

$$= 10 \pm 6$$

$$= 16\Omega \text{ or } 4\Omega$$

(d) $I_C = \frac{120}{20} = 60 \angle -90^\circ$

$$I_L = \frac{120}{2 \times 16} = 3.75 \angle 90^\circ \text{ [neglecting } R = 8 \text{ ohm]}$$

$$OP = \sqrt{6^2 + 3.75^2 - 2 \cdot 6 \cdot 3.75 \cos(90 + 90^\circ)}$$

$$= 4.684$$

\therefore Minimum current,

$$i_m = 6 - 4.684$$

$$= 1.316 \text{ amp}$$

we have assumed that $X_L = 16$ for $i_m = 1.316$ amp

5.49When, $R_L = R_C$

$$(a) \quad f = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.05 \times 200 \times 10^{-6}}} = 50.33 \text{ Hz}$$

$$(b) \quad \frac{X_C}{R_C^2 + X_C^2} = \frac{X_L}{R_L^2 + X_L^2}$$

$$\begin{aligned} \text{or, } R_C^2 &= \frac{X_C (R_L^2 + X_L^2)}{X_L} - X_C^2 \\ &= \frac{35.37 (20^2 + 14.14^2)}{14.14} - 35.37^2 \end{aligned}$$

$$\therefore R_C = 15.8 \text{ ohm}$$

(c) For parallel resonance, irrespective of frequency

$$R_L = R_C = \sqrt{\frac{L}{C}}$$


$$\text{or, } 30^2 = \frac{L}{100 \times 10^{-6}}$$

$$L = 0.04 \text{ Henry}$$

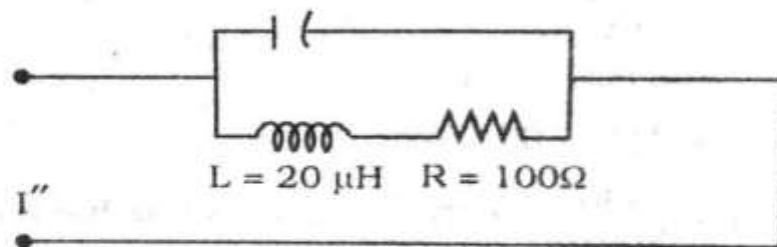5.50

$$X_L = 5 \times 10^7 \times 20 \times 10^{-6} = 1000 \Omega$$

$$X_C = \frac{1}{5 \times 10^7 \times 20 \times 10^{-12}} = 1000 \Omega$$



$$g_L = \frac{100}{100^2 + 1000^2} = 9.9 \times 10^{-5} = 0.0001$$

$$b_L = \frac{1000}{100^2 + 1000^2} = 9.9 \times 10^{-4} = 0.001$$

$$b_C = \frac{1}{X_C} = \frac{1}{1000} = 0.001$$

$$(b) V = IZ = 2 \times 10^{-3} \times 10049.9 \angle -5.7 = 20.09 \angle -5.7$$

$$Z = \frac{Z_1 Z_2}{Z_1 + Z_2} = 10019.9 \angle -5.7^\circ$$

$$(c) OP = \frac{1}{g} \sqrt{\frac{C}{L}} = \frac{1}{0.0001} \sqrt{\frac{20 \times 10^{-12}}{20 \times 10^{-6}}} = 10$$

$$(d) Z = \frac{Z_L Z_C}{Z_L + Z_C}$$

$$= \frac{(R + j\omega L) \left(-j \frac{1}{\omega C}\right)}{R + j\omega L - \frac{j}{\omega C}}$$

$$= \frac{\frac{L}{C} - j \frac{R}{\omega C}}{R + j \left(\omega L - \frac{1}{\omega C}\right)}$$

$$= \frac{\left(\frac{L}{C}\right) - \frac{jR}{\omega C} \left\{R - j \left(\omega L - \frac{j1}{\omega C}\right)\right\}}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\therefore R_z = \frac{\frac{RL}{C} - \frac{R}{\omega C} \left(\omega L - \frac{1}{\omega C}\right)}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$= \frac{\left(\frac{RL}{C} - \frac{RL}{C} + \frac{R}{\omega^2 C^2}\right) \omega^2 C^2 R}{R^2 \omega^2 C^2 + (\omega^2 LC - 1) R^2 \omega^2 C^2 + (\omega^2 LC - 1)}$$

5.52

$$R_z = \frac{R}{R^2 \omega^2 C^2 + (\omega^2 LC - 1)^2}$$

R_z will be max when the denominator of the above expression will be max^m

Now,

$$\frac{d}{d\omega} [R^2 \omega^2 C^2 + (\omega^2 LC - 1)^2] = 0$$

$$\text{or, } 2\omega R^2 C^2 + 2(\omega^2 LC - 1) \omega LC = 0$$

$$\therefore \omega = 0, \text{ But then line voltage will be dc}$$

Again,

$$R^2C^2 + 2LC(\omega^2LC - 1) = 0$$

$$\text{or, } R^2C + 2L(\omega^2LC - 1) = 0$$

$$\text{or, } \omega^2 = \frac{2L - R^2C}{2L^2C}$$

$$\text{or, } \omega = \frac{2L}{2L^2C} - \frac{R^2C}{2L^2C}$$

$$\text{or, } \omega = \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}} \text{ rad/sec}$$

$$\begin{aligned} \text{(b) } \omega &= \sqrt{\frac{1}{20 \times 10^{-6} \times 20 \times 10^{-12}} \times \frac{100^2}{2(20 \times 10^{-6})^2}} \\ &= 4.9875 \times 10^7 \text{ rad/sec} \end{aligned}$$

$$\text{(c) } \omega = \frac{1}{\sqrt{LC}} = 5 \times 10^7 \text{ rad/sec}$$

$$\begin{aligned} \text{5.53 } R_{z\max} &= \frac{R}{\{LC\omega^2 - 1\} + R^2\omega^2C^2} \\ &= \frac{100}{(20 \times 10^{-6} \times 20 \times 10^{-12} \times 4.9875^2 \times 10^{14} - 1)^2 + (100 \times 4.9875 \times 10^7 \times 20 \times 10^{-12})} \\ &= 10025.06 \end{aligned}$$


$$\text{5.54 } \omega = \frac{0.1}{\sqrt{LC}} = \frac{0.1}{\sqrt{20 \times 10^{-6} \times 20 \times 10^{-12}}} = 5 \times 10^7$$

$$Q_p = \frac{1}{9\omega L} = \frac{1}{0.0001 \times 5 \times 10 \times 20 \times 10^{-6}} = 10$$

$$\text{5.55 } i_L = \frac{V}{R_S^2 + (\omega_m L)^2}$$

Since, $R_S^2 \ll \omega_m^2 L^2$
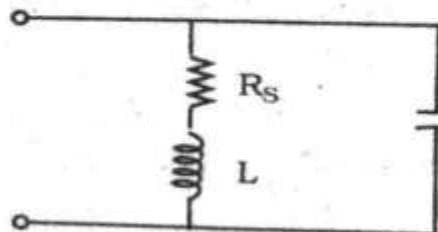
$$\therefore i_L = \frac{V}{\omega_m L}$$



$$\text{given that, } \omega = \frac{Li_L^2}{2} + \frac{CV^2}{2} = \frac{L}{2} \cdot \frac{V^2}{\omega_m^2 L^2} + \frac{CV^2}{2}$$

Again,

$$\omega_m = \frac{1}{\sqrt{LC}} \text{ (given)}$$

$$\text{or, } \frac{V^2}{2\omega_m^2 L} + \frac{CV^2}{2}$$

$$\text{or, } \frac{CV^2}{2} + \frac{CV^2}{2} = \omega$$

$$\therefore C = \frac{\omega}{V^2}$$

Now, given that

$$\begin{aligned} Q_p &= \frac{\omega_m C}{g} \\ &= \frac{\omega_m}{g} \times \frac{\omega}{V^2} \\ &= \frac{\omega_m \omega}{V^2 g} \end{aligned}$$

5.56

(a) $R_C = 10 \text{ ohm}$

$$\begin{aligned} \therefore g_C &= \frac{R_C}{R^2 + X_C^2} \\ &= \frac{R_C}{R_C^2 + \frac{1}{\omega^2 C^2}} \\ &= \frac{R_C}{R_C^2 + \frac{LC}{C^2}} \\ &= \frac{R_C}{R_C^2 + \frac{L}{C}} \\ &= \frac{10}{100 + \frac{20 \times 10^{-6}}{20 \times 10^{-12}}} \\ &= 9.999 \times 10^{-6} \text{ mho} \end{aligned}$$

\therefore So equivalent parallel resistance of two capacitor is

$$\frac{1}{g_C} = \frac{1000}{0} \text{ ohm}$$

100 The Solution of Alternating Current Circuits

(b) Now,



$$\begin{aligned}
 g_L &= \frac{100}{10000 + \omega^2 L^2} \\
 &= \frac{100}{10000 + \frac{1}{LC} \times L^2} \\
 &= \frac{100}{10000 + \frac{L}{C}} \\
 &= \frac{100}{10000 + \frac{20 \times 10^{-6}}{20 \times 10^{-12}}} \\
 &= 9.9 \times 10^{-5} \text{ mho}
 \end{aligned}$$

$\therefore E_q$ parallel resistance of the inductor $\frac{1}{g_L} = 10100 \text{ ohm}$

Hence, eq. resistance of the parallel ckt is

$$\begin{aligned}
 &\frac{100010 \times 10100}{100010 + 10100} \\
 &= 9173.56 \text{ ohm}
 \end{aligned}$$

5.57

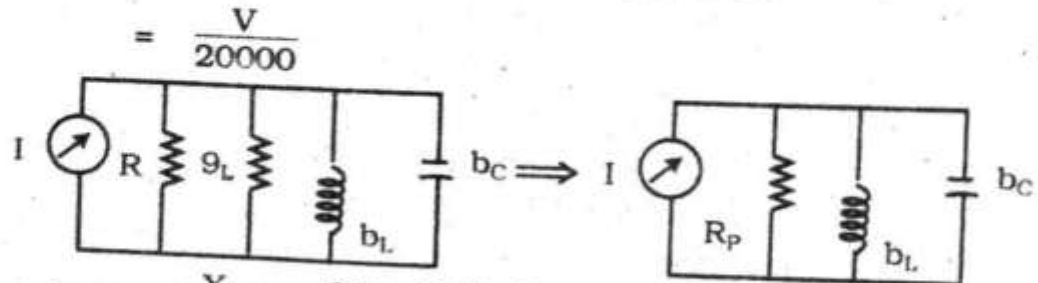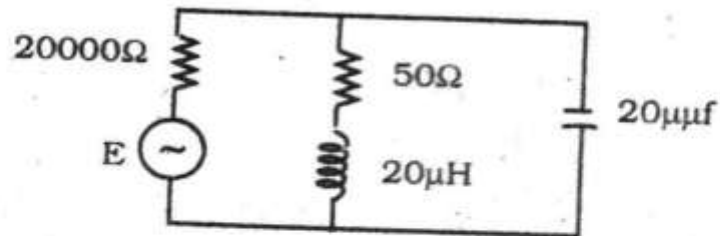

$$\begin{aligned}
 b_L &= \frac{X_L}{R^2 + X_L^2} = \frac{20 \times 10^{-6} \times 5 \times 10^7}{50^2 + (1000)^2} = \frac{1000}{1002500} \\
 &= 9.975 \times 10^{-4} \text{ mho}
 \end{aligned}$$

$$b_C = \frac{1}{X_C} = \frac{1}{5 \times 10^7 \times 20 \times 10^{-12}} = 0.001 \text{ mho}$$

$$R = 20,000$$

$$g_L = \frac{50}{50^2 + (1000)^2} \cdot R_L = \frac{1}{g_L} = \frac{50^2 + 1000^2}{50} = 20050 \text{ ohm}$$

$$\text{Now, } R_p = \frac{20000 \times 20050}{20000 + 20050} = 10012.5 \text{ ohm}$$

$$(b) \quad g_p = \frac{1}{g} \sqrt{\frac{L}{C}} = 10012.5 \sqrt{\frac{20 \times 10^{-12}}{20 \times 10^{-6}}} = 10.01$$


$$(c) \quad Q_s = \frac{\omega_m L}{R_s} = \frac{5 \times 10^7 \times 20 \times 10^{-6}}{50} = 20$$

5.58

$$(a) \quad I = \frac{E}{R_p} = \frac{200}{20000} = 0.01 \text{ A}$$

$$(b) \quad V = IR_p = 0.01 \times 10012.5 = 100.125 \text{ V}$$

5.59

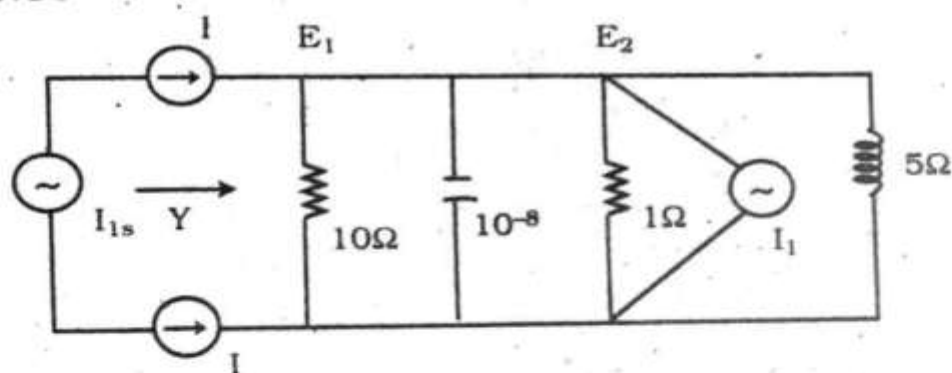

$$\begin{aligned} Y &= \frac{1}{10} + \omega \times 10^{-6} + \omega \times 10^{-7} + \frac{1}{1} + \frac{1}{5} \\ &= 0.1 + \omega \times 10^{-6} + \omega \times 10^{-7} + 1 + 0.2 \\ &= 1.3 + \omega \times 10^{-6} + \omega \times 10^{-7} \end{aligned}$$

where,

$$I_1 = 0.1 E_1$$

$$\text{so, } Y_1 = \frac{I_1}{E_1} = 0.1$$

$$\begin{aligned} Y_{\text{total}} &= Y + Y_1 \\ &= 1.3 + \omega \times 10^{-6} + \omega \times 10^{-7} + 0.1 \\ &= 1.4 + \omega \times 10^{-6} + \omega \times 10^{-7} \end{aligned}$$

where, $\omega = 10^6 \text{ rad/sec}$

102 The Solution of Alternating Current Circuits


$$\begin{aligned} \text{so, } Y_{\text{total}} &= 1.4 + 10^6 \times 10^{-6} + 10^6 \times 10^{-7} \\ &= 1.4 + 1 + 0.1 \\ &= 2.5 \end{aligned}$$

5.60

$$Z_1 = 10 + 30j$$

$$Z_2 = 5 + 10j$$

$$Z_3 = 4 - 16j$$

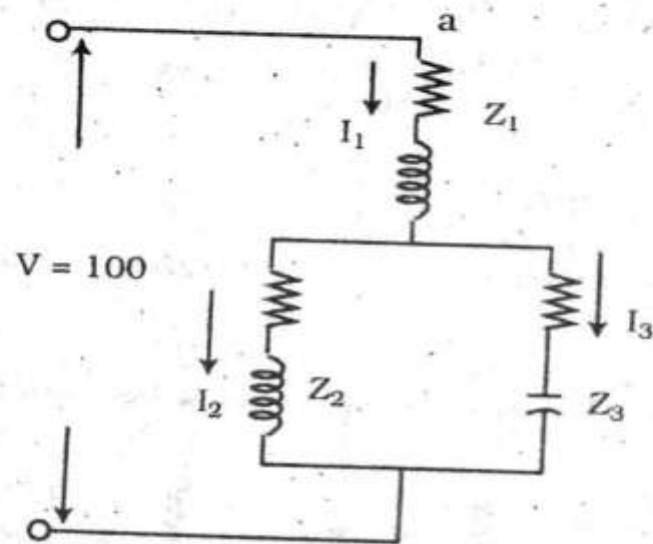

$$\begin{aligned} Z_{bc} &= \frac{Z_2 Z_3}{Z_2 + Z_3} \\ &= \frac{(5 + j10)(4 - j6)}{5 + j10 + 4 - j6} \\ &= \frac{20 + 160 + j(40 - 80)}{9 - j16} \\ &= 15.89 + j6.15 \\ &= 17.04 \angle 21.16^\circ \end{aligned}$$

5.61

$$\begin{aligned} Z_{ac} &= Z_{bc} + Z_{ab} \\ &= 15.89 + j6.15 + 10 + j30 \\ &= 25.89 + j36.15 \\ &= 44.46 \angle 54.39^\circ \text{ ohm} \end{aligned}$$

$$(a) \quad I_1 = \frac{V}{Z_{ac}} = \frac{100}{44.46 \angle 54.39} = 2.25 \angle -54.4^\circ \text{ amp}$$

$$V_{ab} = I_1 Z_1 = (2.25 \angle -54.4) (10 + j30) \\ = (2.25 \angle -54.4) (31.62 \angle 71.6)$$

$$V_1 = 71.15 \angle 17.2 = 67.98 + j20.99$$

$$\therefore V_{bc} = 100 - 67.98 - j20.99 \\ = 32.02 - j20.99 = 39.29 \angle -33.25$$

$$I_2 = \frac{38.29 \angle -33.25}{5 + j10} \\ = \frac{38.29 \angle -33.25}{11.18 \angle 63.43} = 3.45 \angle -96.7^\circ \text{ amp}$$

$$\text{similarly, } I_3 = 2.33 \angle 42.7^\circ$$

$$(c) \quad \text{Watts} = VI \cos \theta = 100 \times 2.25 \sin 54.39 = 131$$


$$\text{Vars} = VI \sin \theta = 100 \times 2.25 \sin 54.39 = 183$$

5.62

$$P_1 = I_1^2 R_1 = (2.25)^2 (10) = 50.625 \text{ watts}$$

$$P_2 = I_2^2 R_2 = (3.43)^2 (5) = 58.8 \text{ watts}$$
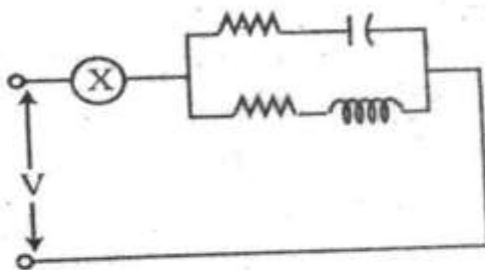
$$P_3 = I_3^2 R_3 = (2.33)^2 (4) = 21.7 \text{ watts}$$



$$Z_{ab} = \frac{(3 - 4j)(1 - j10)}{3 - 4j + 1 + j10} = 9.969 \angle -25.12 = 6.31 - j2.96$$


$$\text{Now, } \tan \cos^{-1} 0.707 = \frac{X - 2.96}{6.31}$$

$$\text{or, } \pm 1 = \frac{X - 2.96}{6.31}$$

$$\text{taking } \pm \text{ ve } \quad X = 9.27 \text{ ohm (inductive)}$$

$$\text{taking } -\text{ve } \quad X = 3.35 \text{ ohm (capacitive)}$$

5.63

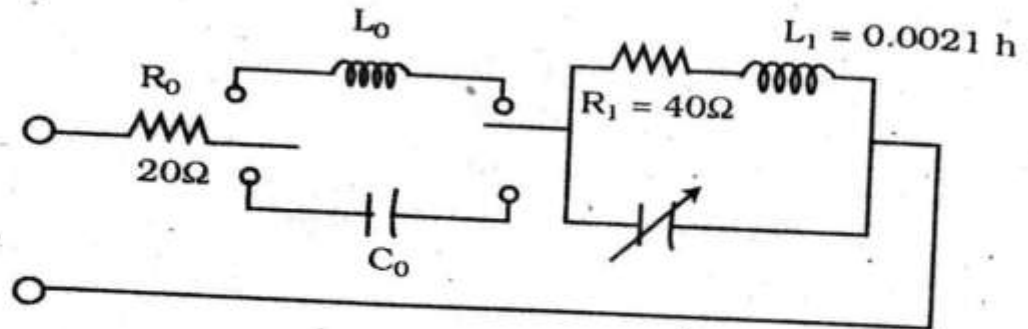

From 15000 Hz - $X_{L1} = 2\pi \times 15000 \times 0.002 = 188.496$ ohm

(a) For parallel resonance $b_L = b_C$ or $\frac{188.496}{40^2 + 188.496} = \omega C_L$
 $C_2 = 5.39 \times 10^{-8} = 0.0539 \mu\text{F}$

(b) Now,

$$Z_{bc} = \frac{(40 + j2\pi \times 45000 \times 0.002) (-j \times \frac{1}{2\pi \times 45000 \times 5.39 \times 10^{-8}})}{40 + j(2\pi \times 45000 \times 0.002 - 5.39 \times 10)} = 74.23 \angle -89.49^\circ \text{ (capacitive)}$$


$f = 1592$ Hz

$\therefore \omega = 2\pi f = 10003$ rad/sec

$X_{L1} = \omega L_1 = 1000.3$ ohm

$X_{L2} = \omega L_2 = 500.1$ ohms

$X_C = \frac{1}{\omega C} = 1000$ ohms

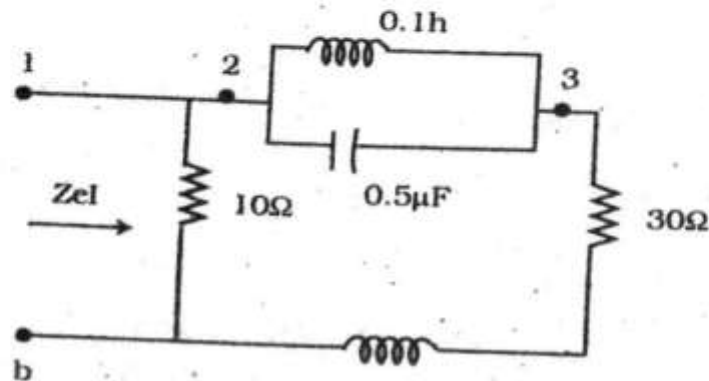


$$\begin{aligned} Z_{12} &= \frac{(j1000.3)(-j1000)}{j1000.3 - j1000} \\ &= \frac{1000300}{j0.583} \\ &= -j171578 \end{aligned}$$

$$Z_{13} = 30 + j500.1 - j1715780 = 30 - j1715280$$

$$\begin{aligned} Z_{ab} &= \frac{(30 - j1715780)(10)}{40 - j1715280} \\ &= (1715280 \angle 90^\circ)(10) = 10 \angle 0 \end{aligned}$$

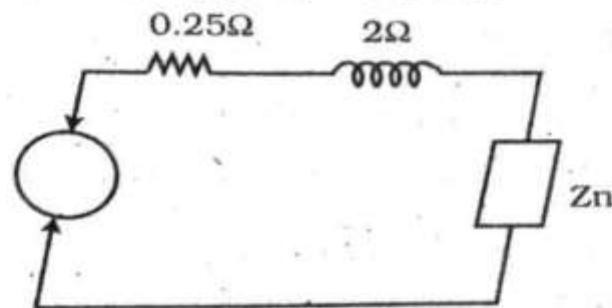5.65

$$Z_1 = (0.25 + 0.5) + j(1 + 2) = 0.75 + j3$$



∴ For max. power $Z_r = 0.75 - j3$

$$\begin{aligned} I &= \frac{20}{0.75 + j3 + 0.75 - j3} \\ &= \frac{20}{1.5} = 13.33 \text{ A} \end{aligned}$$

∴ $P_{\text{load}} = I^2 R = 13.33^2 \times 0.75 = 133.33 \text{ W}$

$P_{\text{ine loss}} = I^2 \times 0.25 = 44.44 \text{ W}$

$P_{\text{loss}} = I^2 \times 0.5 = 88.89 \text{ W}$

5.66

$$(a) P_r = I^2 R_r = \frac{E_s^2 R_r}{(R_1 + R_r)^2 + (X_1 + X_r)^2}$$

load power would be max^m

∴ if X_r is zero, since all the terms in the eqⁿ is constant.

∴ The condition is $X_r = 0$

$$(b) P_r = \frac{20^2 \times 0.75}{(0.75 + 0.75)^2 + 3^2} = 26.67 \text{ W}$$

5.67 $P_r = \frac{E_g^2 R_r}{(R_1 + R_r)^2 + X_1^2}$ - Now, $\frac{dP_r}{dR_r} = 0$

or $R_r^2 = X_1^2 = X_1^2 + R_1^2$

Again, for max^m power $R_r = \frac{Z_1}{\sqrt{1 + K^2}}$

here,

$$K = \frac{X_r}{R_r} = 0$$

or, $Z_1 = \sqrt{X_1^2 + R_1^2} = \sqrt{0.75^2 + 3^2} = 3.092 \text{ ohm}$

Now,

$$I = \frac{20}{0.75 + j3 + 3.092} = \frac{20}{4.87 \angle 37.98^\circ} = 4.1 \angle -37.98^\circ$$

$$P_{\text{load}} = |I|^2 \times R_r = 51.98 \text{ W}$$

$$P_{\text{line}} = |I|^2 \times 0.25 = 4.2 \text{ W}$$

$$P_{\text{gen}} = |I|^2 \times 0.5 = 8.4 \text{ W}$$

5.68 $K = \frac{X_r}{R_r} = 5$ for max^m P_r , we have $R_r = \frac{Z_1}{\sqrt{1 + K^2}}$

$$= \frac{0.75^2 + 3^2}{\sqrt{1 + 5^2}} = 0.606 \text{ ohm}$$


$$= 5R_5 = 3.03 \text{ ohm}$$

$$Z_{\text{load}} = 0.606 - j3.03$$

$$I = \frac{20}{(0.75 + 0.606)^2 + (3 - 3.03)^2} = 14.74 \text{ A}$$

$$\therefore P_{\text{max}} = (14.74)^2 \times 0.606 = 131.76$$

5.69

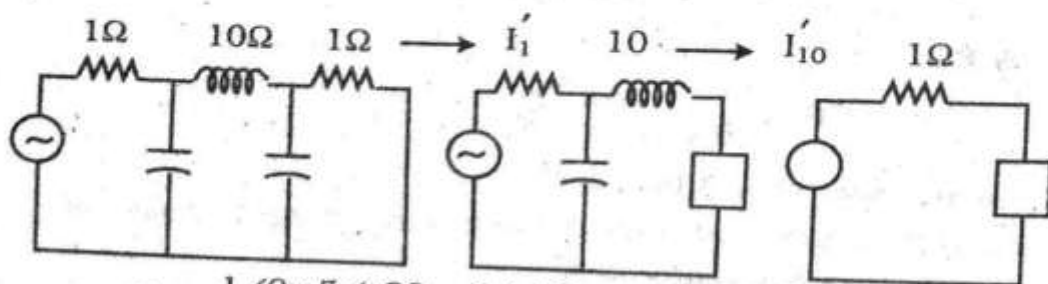

$$Z_p = \frac{1 \angle 0^\circ \times 5 \angle -90^\circ}{1 + j0 + 0 - j5} = \frac{5 \angle -90^\circ}{1 - j5} = \frac{5 \angle -90^\circ}{5.9 \angle -78.69^\circ} = 0.98 \angle -11.31^\circ$$

$$Z_1 = 0 + j10 + 0.96 - j0.192 = 0.96 + j9.8 = 9.85 \angle 84.1$$

$$\begin{aligned} Z_p &= \frac{5 \times 1 \angle -90 \times 9.85 \angle 84.4}{0.96 + j9.8 - j5} \\ &= \frac{49.25 \angle -5.6}{0.96 + j4.8} = \frac{49.25 \angle -5.6}{4.9 \angle 76.69} \\ &= 10 \angle -82.29 = 1.34 - j9.91 \end{aligned}$$


$$Z_{eq} = 1 + 1.34 - j9.91 = 2.34 - j9.91 = 10.18 \angle -76.71$$

$$I_1' = \frac{100 \angle 0}{10.18 \angle -76.71} = 9.82 \angle 76.71$$

$$I_{10}' = I_1' \times \frac{5 \angle -90^\circ}{0 - j5 + 0.96 + j9.8} = \frac{9.82 \angle 76.71 \times 5 \angle -90}{4.90 \angle 78.69}$$

$$I_1' = I_1 \times \frac{5 \angle -90}{0.96 + j4.8} = 10.02 \angle -91.98 = 0.35 - j10$$
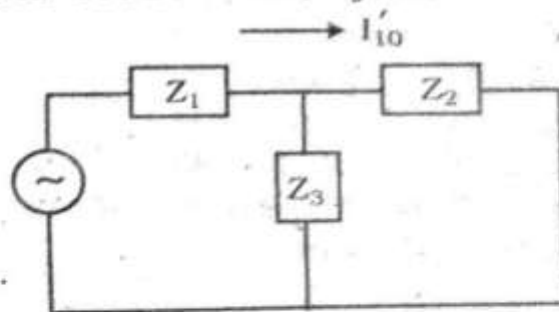
$$\begin{aligned} Z_2' &= I_{10}' \times \frac{Z_3}{Z_2 + Z_3} = I_{10}' \times \frac{5 \angle -90}{1 + j0 + 0 - j5} \\ &= \frac{10.02 \angle -91.98 \times 5 \angle -90^\circ}{5.09 \angle -78.69} \\ &= 9.84 \angle -103.29 = -2.26 - j9.58 \end{aligned}$$



when,

$$F_1 = 0, I_2 = \frac{50 \angle 60}{10.18 \angle -76.71} = 4.91 \angle 138.71 = 3.57 + j3.37$$

$$\begin{aligned} I_2 &= I_2 + I_2' = -2.26 - j9.58 - 3.57 + j3.37 \\ &= 8.52 \angle -133.19^\circ \end{aligned}$$

5.70

$$Z_1 = 10 + j30 \text{ ohms}$$

$$Z_2 = 5 + j10 \text{ ohms}$$

$$Z_3 = 4 - j16 \text{ ohms}$$

108 The Solution of Alternating Current Circuits

If $100\angle 0$ volts remains at the branch 1. calculation of the currents are as follows :

$$\begin{aligned} Z_{\text{ckt}} &= Z_1 + \frac{Z_2 Z_3}{Z_2 + Z_3} = (10 + j30) + \frac{(5 + j10)(4 - j16)}{5 + j10 + 4 - j16} \\ &= 10 + j10 + \frac{20 + 160 + j(48 - 8)}{9 - j16} \\ &= 10 + j30 + \frac{1620 + 240 + j(1080 - 360)}{81 + 36} \\ &= 44.47 \angle 54.38^\circ \text{ ohms} \end{aligned}$$

$$\begin{aligned} \therefore I &= \frac{100}{44.47 \angle 54.38} \\ &= 2.25 \angle 54.38^\circ \text{ amps} \end{aligned}$$

$$\begin{aligned} I_1 Z_1 &= (2.25 \angle 54.38^\circ)(31.62 \angle 71.54^\circ) \\ &= 71.145 \angle 17.185 \\ &= 67.969 + j21 \end{aligned}$$


$$\begin{aligned} V_2 &= 100 + j0 - 67.969 - j21 \\ &= 32 - j21 \\ &= 38.3 \angle -33.25^\circ \end{aligned}$$

$$\begin{aligned} I_3 &= \frac{38.3 \angle -33.25^\circ}{4 - j16} \\ &= 2.32 \angle 42.7^\circ \text{ amp} \end{aligned}$$

Now, if the $100\angle 0$ volts is inserted in branch 3, the resulting current in branch 1 would be equal to I_3 , according to the reciprocity theorem. Therefore, in this case

$$I_1 = 2.32 \angle 42.7^\circ \text{ amp}$$

5.71

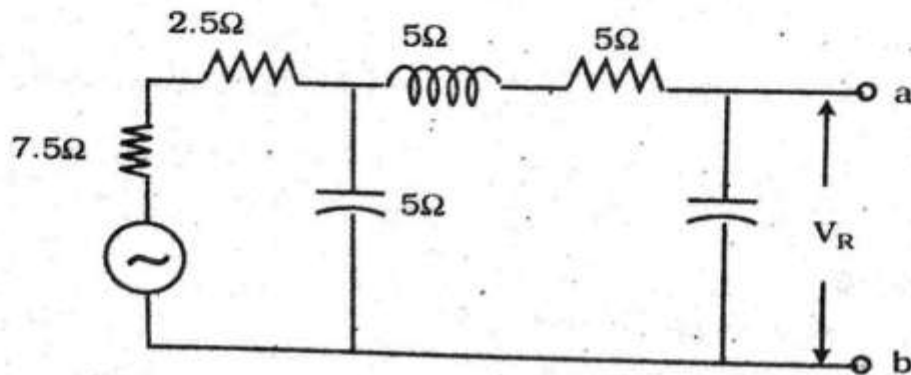

$$200 = (7.5 + j(2.5 - 5)) I_1 + j5I_2$$

$$0 = j5I_1 + (5 + j(5 - 5 - 5))I_2$$

$$\text{or. } I_1 = \frac{5 - 5j}{-j5} I_2$$


$$= \left(-\frac{1}{j} + 1 \right) I_2 = (1 + j) I_2$$

$$\text{Now, } 200 = (7.5 - 2.5j)(1 + j) I_2 + j5I_2 = (10 + 5j + 5j) I_2$$

$$\text{or. } I_2 = \frac{200}{10 + j10} = 14.14 \angle -45^\circ$$

$$V_R = (-5j) \times I_2 = (5 \angle -90^\circ)(14.14 \angle -45^\circ) = 70.7 \angle 135 = 50 - j50$$

Now,

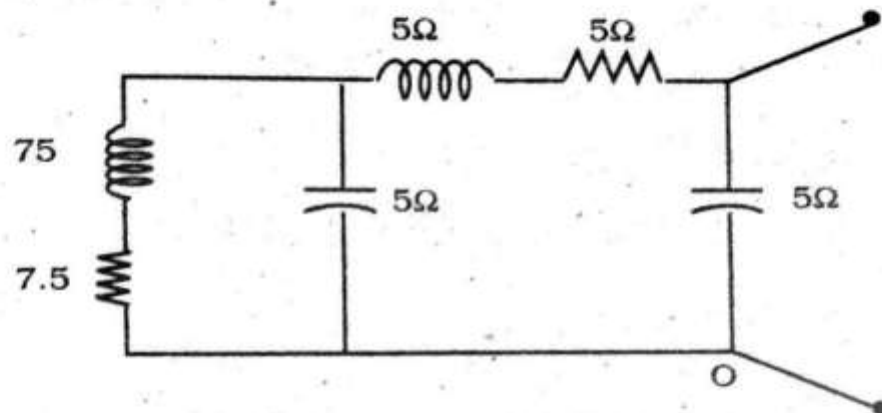


$$Z = \frac{(8.06 \angle 7.13)(5 \angle -90)}{8 + j1 - j5} = \frac{40.30 \angle 82.87}{8.94 \angle -26.57} = 4.5 \angle -56.3^\circ$$

$$\therefore I_{ab} = \frac{70.7 \angle -135^\circ}{2.5 + 1.46 + j(6.78 - 3.74)}$$

$$= \frac{70.7 \angle -135}{5 \angle 37.5} = 14.14 \angle -172$$

5.72

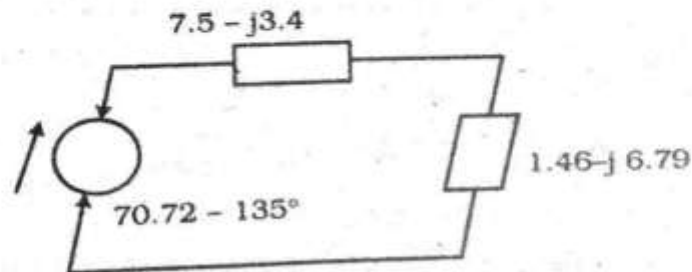

$$Z_1 = 1 + j1 + 2 + j3 = 5 \angle 53.13$$

$$Z_2 = 1 + j3 + 2 + j1 = 3 + j4 = 5 \angle 53.13$$

$$Z_3 = -j5 = 5\angle -90^\circ$$


$$\begin{aligned} Z &= \frac{Z_1 Z_3}{Z_1 + Z_3} \\ &= \frac{5\angle 53.13 \times 5\angle -90}{3 + j4 - j5} \\ &= \frac{25\angle -36.87}{3 - j1} \\ &= \frac{25\angle -36.87}{3.16\angle -18.43} \\ &= 7.91\angle -18.44 \end{aligned}$$

$$Z = 7.5 - j2.5 + 3 + j4 = 10.5 + j1.5 = 10.61\angle 8.13$$

$$I_1' = \frac{100\angle 0}{10.61\angle 8.13} = 9.43\angle -8.13$$

$$\begin{aligned} Z &= \frac{Z_2 \times Z_3}{Z_2 + Z_3} \\ &= \frac{5\angle 53.13 \times 5\angle -90}{3 + j4 - j5} = 7.5 - j2.5 \end{aligned}$$

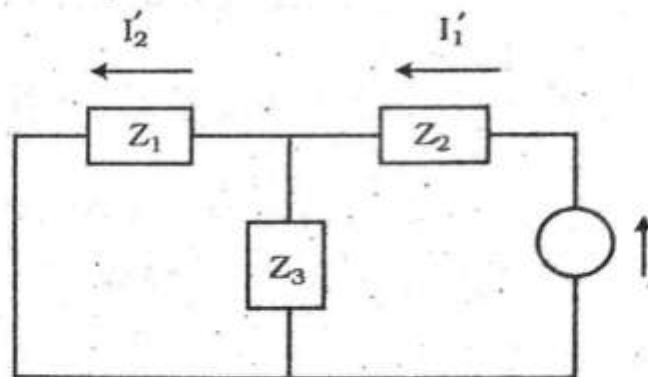
$$I_2'' = \frac{50\angle 26.59}{10.61\angle 8.13} = 4.71\angle 18.46$$



$$\begin{aligned} I_1'' &= I_2'' \times \frac{Z_3}{Z_2 + Z_3} \\ &= 4.71\angle 18.46 \times \frac{5\angle -90}{3.16\angle 18.43} \\ &= 7.45\angle -53.11 \end{aligned}$$

$$\begin{aligned} \therefore I_1 &= I_1'' - I_1' = 4.47 - 5.96j - 9.33 + j1.33 \\ &= 6.71\angle -136.39 \end{aligned}$$

5.73

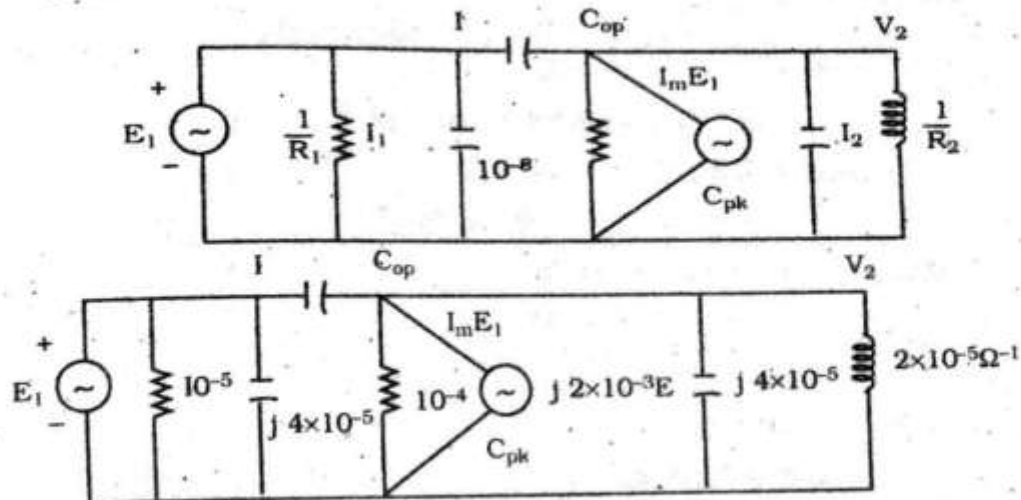

at Node g_1 .

$$V_{g1} = E_1$$

at Node g_2 .


$$V_{g2} \times (10^{-4} + j4 \times 10^{-5} + 2 \times 10^{-5}) - v_{g1} (j0.5 \times 10^{-5}) = 2 \times 10^{-3} E_1$$

$$V_{g2} (10^{-4} + j4 \times 10^{-5} + 2 \times 10^{-5} + 0.5 \times 10^{-5}) - E_1 (j0.5 \times 10^{-5}) = 2 \times 10^{-3} E_1 \quad [\text{Replacing } V_{g1} = E_1]$$

$$V_{g2} (10^{-4} + j4 \times 10^{-5} + 2 \times 10^{-5} + 0.5 \times 10^{-5}) = E_1 (j0.5 \times 10^{-5} + 2 \times 10^{-3})$$

$$V_{g2} = \frac{1 \angle 0^\circ (j0.5 \times 10^{-5} + 2 \times 10^{-3})}{(10^{-4} + j4 \times 10^{-5} + 2 \times 10^{-5} + 0.5 \times 10^{-5})} = 15.25 \angle -17.60$$

5.74

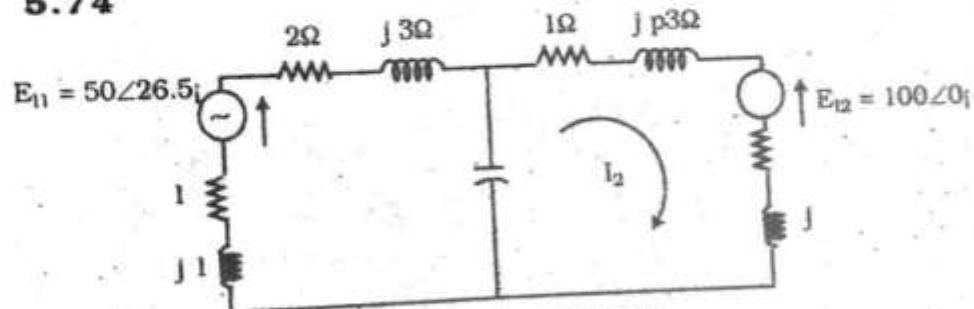

Using loop current method, we have

$$I_A = 6.72 \angle -136.39^\circ$$

$$\therefore V_{ab} = (6.72 \angle -136.39^\circ) (1 \angle 0) = 6.72 \angle -136.39^\circ$$

Now,

$$Z_{PQ} = \frac{(3 + j4)(5 \angle -90^\circ)}{3 + 4j - 5j} = \frac{25 \angle -36.87^\circ}{3.16 \angle -18.43^\circ}$$

$$= 7.91 \angle -18.44 = 7.5 - j2.5$$

$$Z_{PQR} = 7.5 - j2.5 + j(1 + 3)$$

$$= 9.5 + j1.5 = 9.62 \angle 8.97^\circ$$

Which is parallel to 10 hm


$$\therefore Z = \frac{(9.62 \angle 8.97)(1 \angle 0)}{9.6 + j1.571}$$

$$= \frac{9.62 \angle 8.97}{10.6 \angle 8.11}$$

$$= 0.907 \angle 0.81$$


$$= 0.907 + j0.013$$

So the thevenin's equivalent ckt is

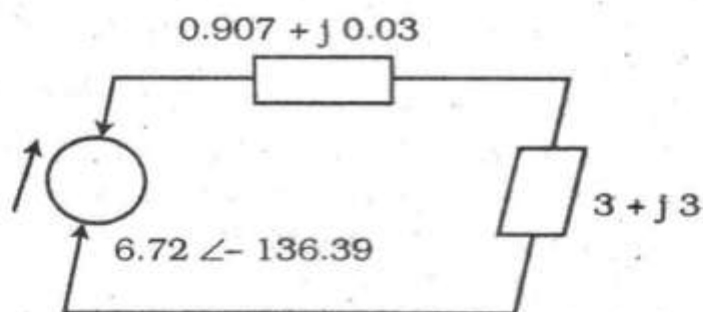

$$\therefore I = \frac{6.72 \angle 136.39}{3.907 + j3.013} = 1.36 \angle -174$$

5.75

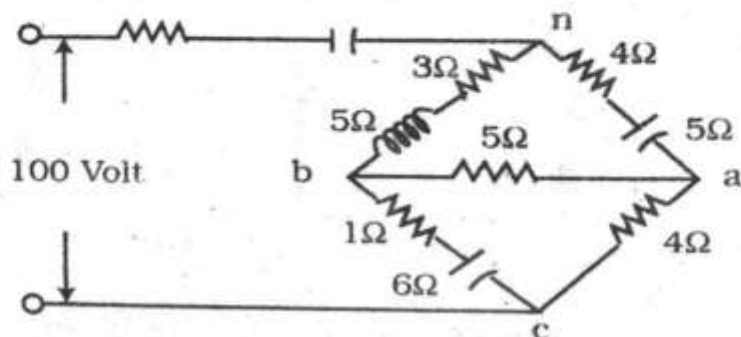

$$Z_{ca} = \frac{(5 - j30)(10 + j6)}{136} = \frac{50 + 180 - j300 + j30}{136}$$

$$= 1.69 - j1.99$$


$$Z_{ba} = \frac{(1 - j6)(4)}{10 - j6} = \frac{(4 - j24)(10 + j6)}{136}$$

$$= 2.09 - j1.59$$

$$Z_{bc} = \frac{20}{10 - j6} = 1.47 + j0.88$$

$$Z_{nbd} = 3 + j5 + 1.69 - j1.96 = 4.69 + j3.01$$
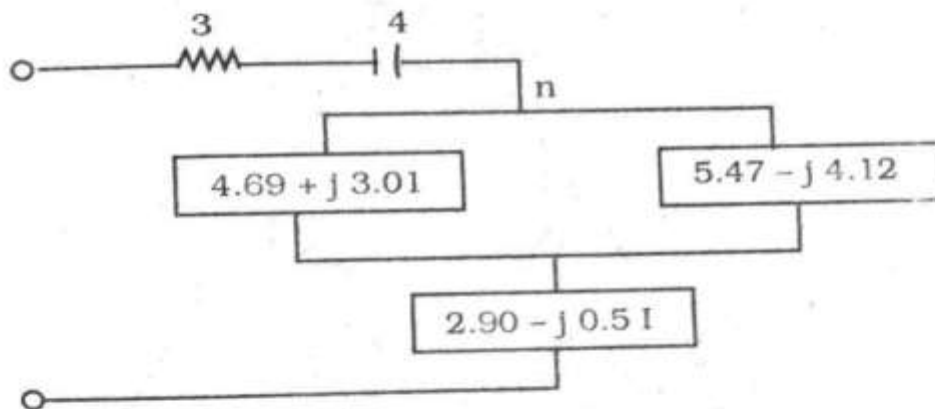
$$Z_{nad} = 5j + 1.47 + j0.88 = 5.47 - j4.12$$



$$Z_{nac} = \frac{(4.69 + j3.02)(5.47 - j4.12)}{4.69 + j3.01 + 5.47 - j4.12}$$

$$= \frac{(5.573 \angle 32.69)(6.85 \angle -36.90)}{10.22 \angle -6.23}$$

$$= 3.735 \angle 1.93 = 3.73 + j0.126$$

$$Z_{nc} = 3.73 + j0.126 + 2.09 - j1.59$$




$$= 5.82 - j1.454$$

$$\therefore Z_{ckt} = 3 - j4 + 5.82 - j1.464$$


$$= 8.82 - j5.464$$

$$= 10.375 \angle 31.78^\circ$$


5.78

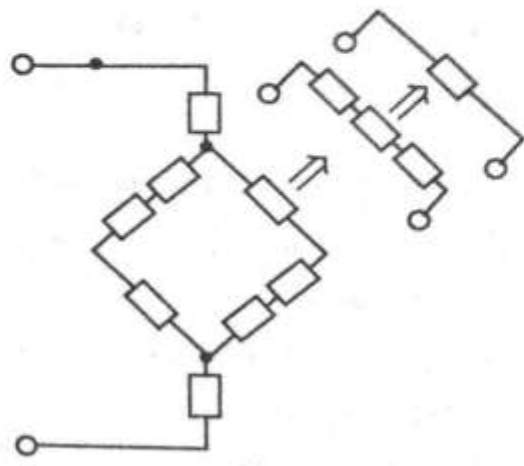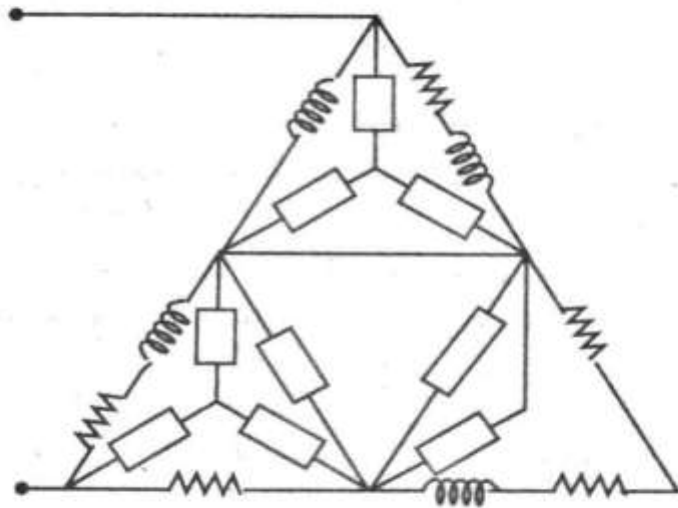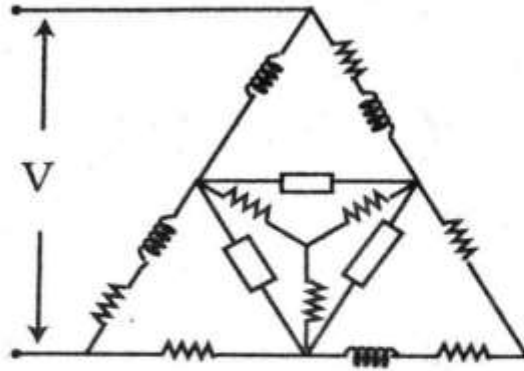

5.79

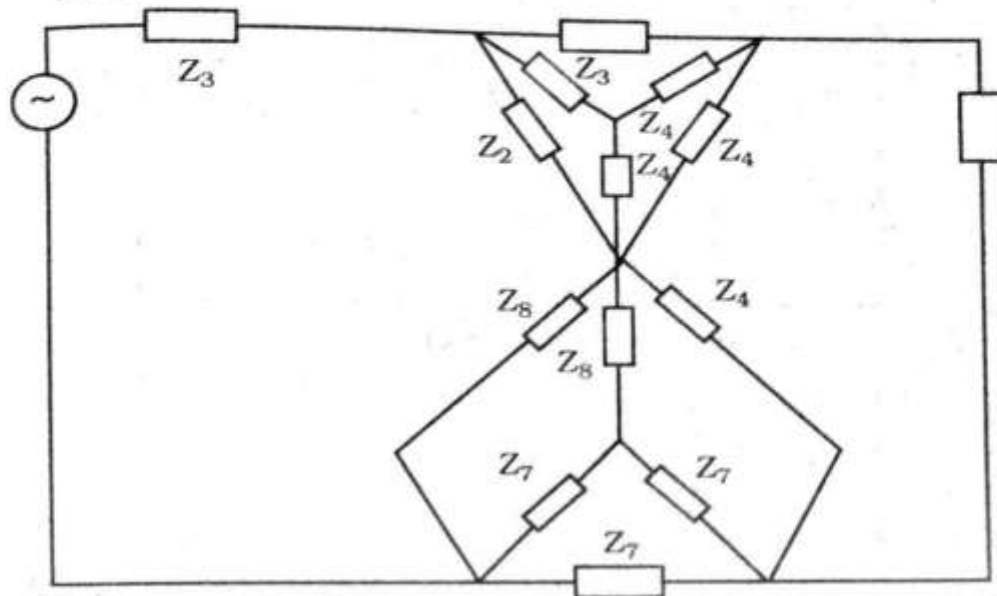

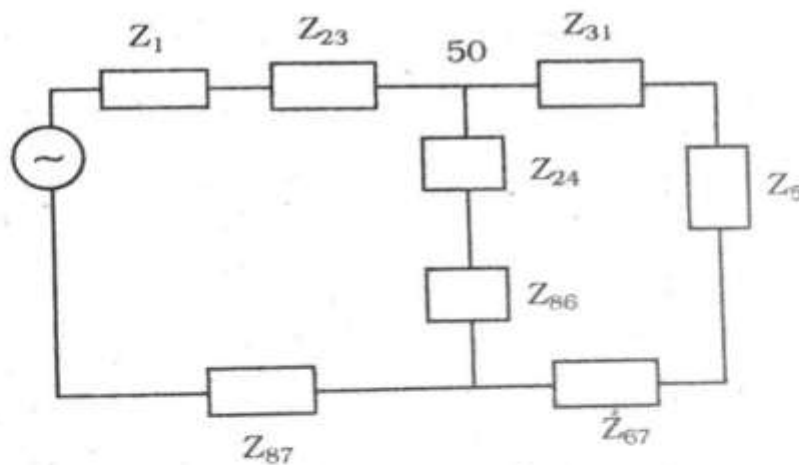The current $I_3 = 0$ i.e. the current through Z_5 is zero, if $Z_{15} = 0$ i.e. if the points P and Q are short circuited.




Hence,

$$Z_{PQ} = 0$$

$$\text{or, } Z_{24} + Z_{66} = 0$$

$$\text{or, } \frac{Z_2 Z_4}{Z_2 + Z_3 + Z_4} + \frac{Z_6 Z_8}{Z_6 + Z_7 + Z_8} = 0$$
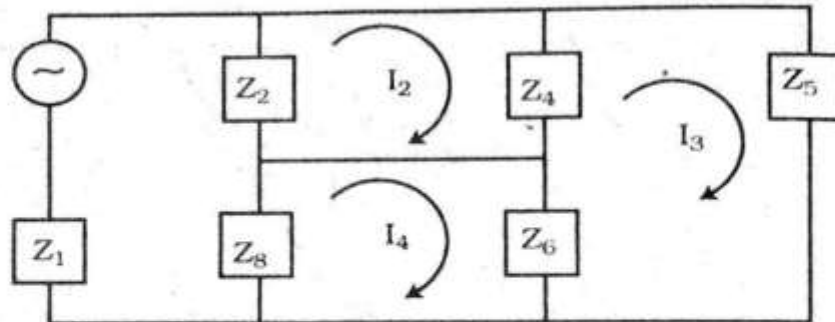
$$\text{or, } Z_2 Z_4 (Z_6 + Z_7 + Z_8) + Z_6 Z_8 (Z_2 + Z_3 + Z_4) = 0$$




Z_1, Z_3, Z_4 are in delta connection

When transformed to star,

$$Z_{23} = \frac{Z_2 Z_3}{Z_2 + Z_3 + Z_4}$$

$$Z_{34} = \frac{Z_3 Z_4}{Z_2 + Z_3 + Z_4}$$
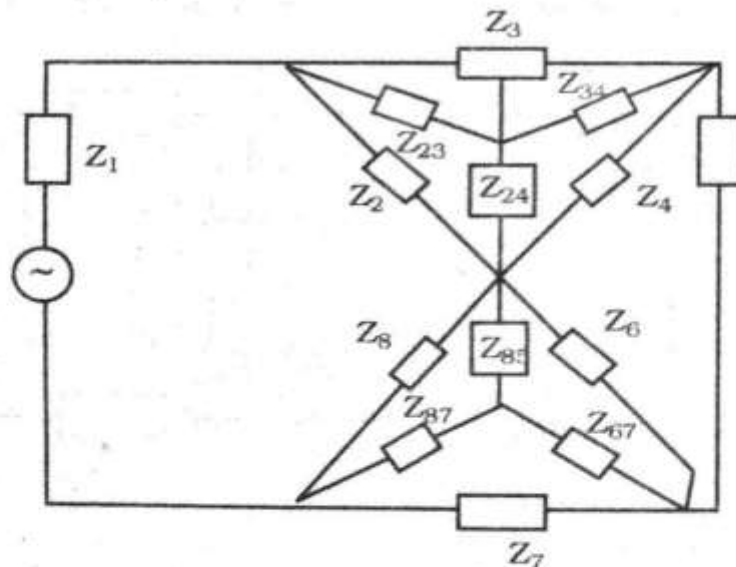
$$Z_{24} = \frac{Z_2 Z_4}{Z_2 + Z_3 + Z_4}$$




$$Z_{67} = \frac{Z_6 Z_7}{Z_6 + Z_7 + Z_8}$$

$$Z_{78} = \frac{Z_7 Z_8}{Z_7 + Z_8 + Z_5}$$

$$Z_{86} = \frac{Z_8 Z_6}{Z_8 + Z_6 + Z_7}$$

What relationship between the Z's of fig. will make $I_3 = 0$ regardless of the magnitude of E_{in} .

Z_2, Z_3, Z_4 are in delta connection

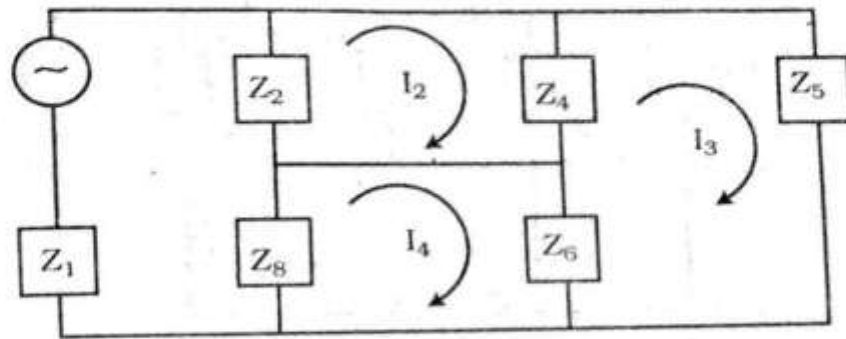

$$Z_{23} = \frac{Z_2 Z_3}{Z_2 + Z_3 + Z_4}, \quad Z_{34} = \frac{Z_3 Z_4}{Z_2 + Z_3 + Z_4}, \quad Z_{24} = \frac{Z_2 Z_4}{Z_2 + Z_3 + Z_4}$$

Z_6, Z_7, Z_8 are transformed to star connection.


$$Z_{68} = \frac{Z_6 Z_8}{Z_6 + Z_7 + Z_8}, \quad Z_{78} = \frac{Z_7 Z_8}{Z_6 + Z_7 + Z_8}, \quad Z_{67} = \frac{Z_6 Z_7}{Z_6 + Z_7 + Z_8}$$

Now, when $Z_{24} + Z_{68} = 0$ then $I_3 = 0$ of any magnitude of E_{in} .

The relationship is $Z_{24} + Z_{68}$


$$= \frac{Z_2 Z_4}{Z_2 + Z_3 + Z_4} + \frac{Z_6 Z_8}{Z_6 + Z_7 + Z_8} = 0$$

5.80

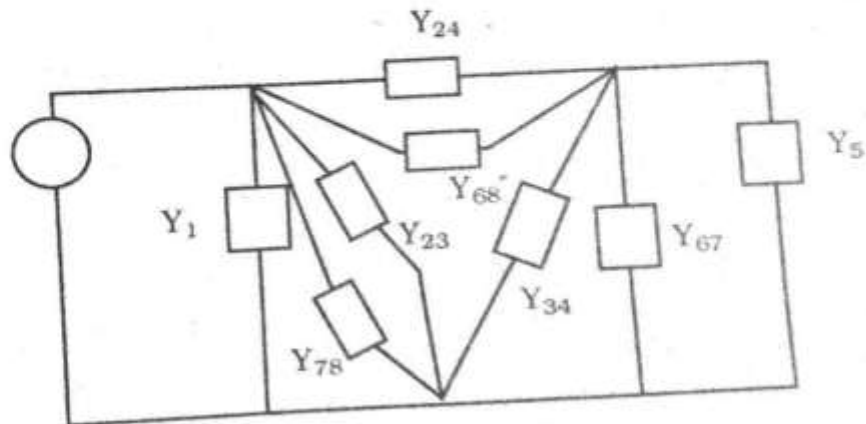

Chapter-6 Non-Sinusoidal Waves

6.1

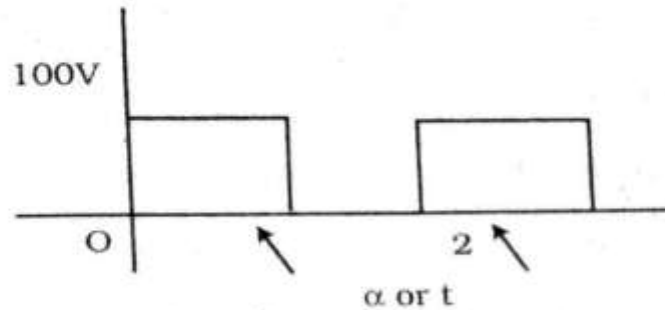

$$C_n = \frac{1}{\pi} \int_0^{\pi} 100 e^{-jnt} dt \quad \left| \quad \omega_n = \frac{2\pi}{2\pi} = 1 \right.$$

$$= \frac{1}{\pi} \int_0^{\pi} 100 e^{-jnt} dt$$

$$= \frac{1}{-jn\pi} 100 \times e^{-jnt} \Big|_0^{\pi}$$

$$= \frac{1}{-jn\pi} \times 100 \times [e^{-jn\pi} - 1]$$

$$= \frac{j100}{n\pi} [e^{-jn\pi} - 1]$$

$$e = \sum_{n=-\infty}^{\infty} n e^{jn\omega t}$$

$$= \sum_{n=-\infty}^{\infty} \frac{j100}{n\pi} [e^{-jn\pi} - 1]$$

Problem 2. Do yourself.

6.2 Problem-3 Do yourself

6.3 Problem-4

$$i = 85.50 \sin(\omega t - 15^\circ) + 26.2 \sin(3\omega t + 92) + 6.5 \sin(5\omega t + 214.2) + 2.39 \sin(7\omega t - 32.7)$$

$$= -85.50 \cos(\omega t + 75) - 26.2 \cos(3\omega t + 92 + 90) - 6.5 \cos(5\omega t + 214.2 + 90^\circ) - 2.39 \sin(7\omega t - 32.7 + 90^\circ)$$

$$= -85.50 \cos(\omega t + 75) - 26.2 \cos(3\omega t + 182)$$

$$- 6.5 \cos(5\omega t + 304.2) - 2.39 \sin(7\omega t + 57.3)$$

$$6.5 \quad i' = 10 \sin(\omega t + 30^\circ) + 2 \sin 7\omega t$$

$$\text{and, } i'' = 35 \sin(\omega t - 10) + 7 \sin(7\omega t + 80^\circ)$$

$$\frac{di'}{dt} = 10 \cos(\omega t + 30) + 2 \times 7 \cos 7\omega t$$

$$\frac{di''}{dt} = 35 \cos(\omega t - 10) + 7 \times 7 \cos(7\omega t + 80^\circ)$$

$$\text{So } \frac{di'}{dt} = \text{variation of } i'$$

$$\frac{di''}{dt} = \text{variation of } i''$$

$$\text{and } \frac{di''}{dt} = 35 \cos(\omega t - 10) + 49 \cos(7\omega t + 80^\circ)$$

$$= 35 \cos(\omega t - 30^\circ + 360) + 49 \cos(7\omega t + 80^\circ + 360^\circ)$$

$$\text{Here, } \frac{10}{35} = \frac{14}{47} = \frac{2}{7}$$

phase shift should be = 20°

and at 7th harmonics = 80°

Phase differ is not acceptable.

\therefore they are not alike.

6.6

$$V = V_{m1} \sin(\omega t + \alpha_1) + V_{m3} \sin(3\omega t + 30^\circ)$$

$$V_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T (V_{m1}^2 + V_{m3}^2) dt}$$

$$V_{\text{eff}} = \sqrt{\frac{1}{T} \int V^2 dt}$$

$$= \sqrt{\frac{1}{T} \int [V_{m1} \sin(\omega t + \alpha_1) + V_{m3} \sin(3\omega t + 30^\circ)]^2 dt}$$

$$= \sqrt{\frac{1}{T} \int [V_{m1}^2 \sin^2(\omega t + \alpha_1) + 2V_{m1}V_{m3} \sin(\omega t + \alpha_1) \sin(3\omega t + 30^\circ) + V_{m3}^2 \sin^2(3\omega t + 30^\circ)] dt}$$

$$= \sqrt{\frac{1}{T} [V_{m1}^2 \int \sin^2(\omega t + \alpha_1) + 2V_{m1}V_{m3} \int \sin(\omega t + \alpha_1) \sin(3\omega t + 30^\circ) + V_{m3}^2 \int \sin^2(3\omega t + 30^\circ)] dt}$$

expand $\sin(\omega t + \alpha_1) \sin(3\omega t + 30^\circ)$ as $\cos(A - B) - \cos(A + B)$

Then use the T(period) for one defined frequency as ω , 2ω , 4ω and solve the integration as simple.

6.7 Problem

$$e = 100 \sin \omega t + 50 \sin (5\omega t - 80^\circ) - 40 \cos (7\omega t + 30^\circ) \text{ Volt J}$$

$$i = 30 \sin(\omega t + 60^\circ) + 20 \sin(5\omega t - 50^\circ) + 10 \sin(7\omega t + 60^\circ)$$

So.

$$\begin{aligned} P &= vi \cos \theta \\ &= \frac{100 \times 30}{2} \cos (0 - 60) + \frac{50 \times 20}{2} \cos (-80 + 50) \\ &\quad + \frac{(-40)(10)}{2} \cos (30 - 60^\circ) \\ &= 750 + 433.0127 - 173.205 \\ &= 1009.8077 \text{ watt J} \end{aligned}$$

6.8 Problem

$$\text{Effective voltage} = \sqrt{\frac{100^2 + 50^2 + 40^2}{2}} = 83.964 \text{ Volt}$$

$$\text{Effective current} = \sqrt{\frac{30^2 + 20^2 + 10^2}{2}} = 26.4575 \text{ Volt}$$

Power from the previous problem $P = 1009.8077$

VA from the previous problem

$$= 100 \times 20 + 50 \times 26 + (-40) \times 10 = 3600 \text{ Watt J}$$

$$\text{Power factor} = \frac{1009.8077}{3600} = 0.28$$

$$\theta = 73.709$$

$$\text{So } v_{eq} = \sqrt{2} \times 83.964 \sin \omega t \text{ Volts}$$

$$i_{eq} = \sqrt{2} \times 26.4575 \sin(\omega t + 73.709)$$

6.9 (a) Here

$$\begin{aligned} c_3 &= \frac{1}{2\pi} \left[\int_0^\pi 10e^{-j3t} dt + \int_\pi^{2\pi} (-5)e^{-j3t} dt \right] \\ &= \frac{1}{2\pi} \times \frac{10}{-j3} [e^{-j3\pi} - 1] + \frac{(-5)}{-3j \times 2\pi} \times [e^{-6\pi j} - e^{j3\pi}] \\ &= \frac{1}{2\pi} \times \frac{10}{-j3} [e^{-j3\pi} - 1] + \frac{(-5)}{-3j \times 2\pi} \times [e^{-6\pi j} - e^{j3\pi}] \\ &= \frac{5}{-j3\pi} [e^{-j3\pi} - 1] + \frac{(-5)}{2\pi \times -3j} \times [e^{-6\pi j} - e^{j3\pi}] \end{aligned}$$

So, $a_3 = \frac{c_3}{2}$ where $e^{-j3\pi} = \cos(-3\pi) + j \sin(-3\pi)$ and so on.


(b)

$$\begin{aligned}
 &= \sum_{n=-\infty}^{\infty} c_n e^{jn\omega_0 t} \\
 &= \sum_{n=-\infty}^{\infty} \left[\frac{5}{-j3\pi} (e^{-j3\pi} - 1) + \left(\frac{-5}{2\pi} \right) \times \frac{1}{-3j} (e^{-6\pi j} - e^{j3\pi}) \right] \times e^{jnt}
 \end{aligned}$$

(c) Do yourself

6.10 (a) Same to number 9.

6.11.

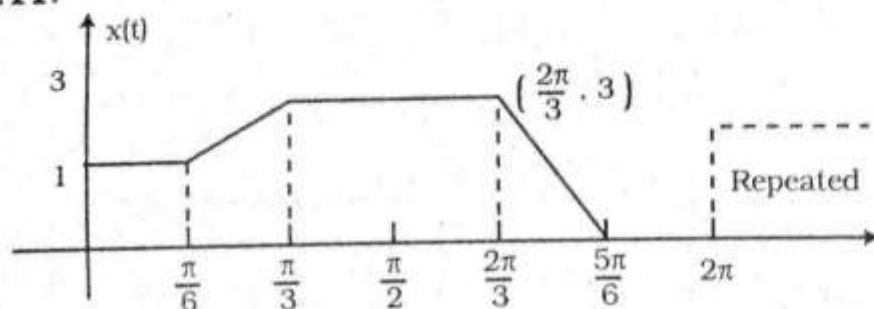

$$\begin{aligned}
 c_n &= \frac{1}{2\pi} \int_0^{2\pi} x(t) e^{-jnt} dt \\
 &= \frac{1}{2\pi} \left[\int_0^{\pi/6} e^{-jnt} dt + \int_{\pi/6}^{2\pi/3} \left(\frac{2}{\pi/3} t \right) e^{-jnt} dt + \int_{2\pi/3}^{5\pi/6} 3e^{-jnt} dt \right. \\
 &\quad \left. + \int_{5\pi/6}^{2\pi} \left[\frac{18}{\pi} (t - 2\pi/3) + 3 \right] dt \right]
 \end{aligned}$$

As these integrations are easier to do and can be evaluated by by parts formula, try yourself.

6.12 Not important

6.13 Not important

6.14

$$\begin{aligned}
 V &= 4 \sin \omega t - 3 \cos \omega t - 7.66 \sin 2 \omega t + 6.43 \cos 2 \omega t \\
 &\quad - 2 \sin 3 \omega t - 1.5 \cos 3 \omega t \\
 &= \sqrt{4^2 + 3^2} \sin (\omega t - \tan^{-1} 4/3) - \sqrt{(7.66)^2 + (6.43)^2} \\
 &\quad \sin (2 \omega t - \tan^{-1} \frac{7.66}{6.43}) - \sqrt{2^2 + 1.5^2} \sin (3 \omega t + \tan^{-1} 2/1.5) \\
 &= 5 \sin (\omega t - 53.13) - 10 \sin (2 \omega t - 49.98) \\
 &\quad - 2.5 \sin (3 \omega t + 53.13)
 \end{aligned}$$


6.15 Not important

6.16 Not important

6.17 Not important

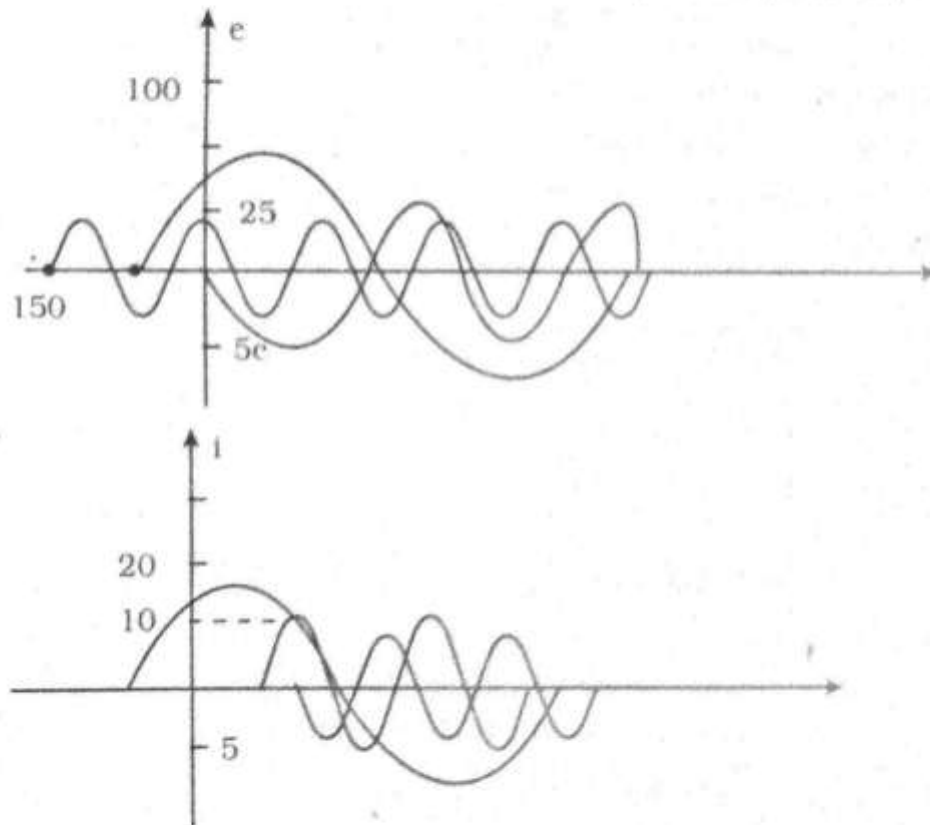6.18 $e = 100 \sin(\omega t + 30^\circ) - 50 \cos 2\omega t + 25 \sin(5\omega t + 150^\circ)$

and, $i = 20 \sin(\omega t + 40^\circ) + 10 \sin(2\omega t + 30^\circ) - 5 \sin(5\omega t - 50^\circ)$



$$\text{ratio} = \frac{100}{20} = \frac{50}{10} = \frac{25}{5}, \text{ phase difference} = 10^\circ$$

So it is symmetric.

6.19 Similar to 18

6.20

$$v = 100 \sin(\omega t + 70^\circ) - 60 \sin(2\omega t - 30^\circ) + 30 \sin(3\omega t - 60^\circ)$$

$$i = 50 \cos(\omega t - 60^\circ) + 30 \sin(2\omega t + 70^\circ) - 15 \cos(3\omega t - 90^\circ)$$

$$\begin{aligned} \text{From } v &= 100 \sin(\omega t - 60 + 90) + 60 \sin(2\omega t + 70 + 180^\circ) \\ &\quad + 30 \sin(3\omega t - 90 + 3 \times 90^\circ) \\ &= 100 \sin(\omega t + 30) + 60 \sin(2\omega t + 250) + 30(3\omega t + 180^\circ) \\ \text{ratio} &= \frac{100}{100} = \frac{60}{60} = \frac{30}{60} = 1 \text{ and phase shift } 30^\circ \end{aligned}$$

$$\mathbf{6.21} \quad e = 100 \sin(\omega t - 20) + 50 \sin(3\omega t + 60) - 25 \cos(5\omega t - 30^\circ)$$

$$\text{and, } i = 20 \cos(\omega t - 60^\circ) - 10 \sin(3\omega t + 15^\circ) + 5 \sin(5\omega t - 70^\circ)$$

$$\text{ratio } r = \frac{100}{20} = \frac{50}{10} = \frac{25}{5} = 5$$

$$\text{Phase shift} = 10^\circ$$

$$\text{at 3rd harmonics} = 30^\circ$$

$$\text{and at 5th harmonics} = 50^\circ$$

So they are not alike.

6.22

$$\begin{aligned} V_{\text{eff}} &= \sqrt{\frac{100^2 + 50^2 + 25^2}{2}} \\ &= 81.0093 \text{ volt} \end{aligned}$$

$$\begin{aligned} i_{\text{eff}} &= \sqrt{\frac{20^2 + 10^2 + 5^2}{2}} \\ &= 22.9128 \text{ amp} \end{aligned}$$

6.23

$$\begin{aligned} V &= 100 \sin(\omega t + 30^\circ) - 40 \sin(2\omega t - 30^\circ) \\ &\quad + 40 \sin(2\omega t + 30^\circ) + 20 \cos(5\omega t - 30^\circ) \end{aligned}$$

$$\begin{aligned} \therefore V_{\text{eff}} &= \sqrt{\frac{100^2 + 40^2 + 40^2 + 20^2}{2}} \\ &= \sqrt{\frac{13600}{2}} \\ &= 82.462 \end{aligned}$$

6.24 The voltmeter value of the complex wave,

$$\begin{aligned} V &= \sqrt{\frac{100^2 + 70^2 + 50^2}{2}} \\ &= \sqrt{8700} \\ &= 93.2737 \text{ volt} \end{aligned}$$

6.25

$$i = 2.5 + \frac{30}{\pi} \sin x + \frac{30}{3\pi} \sin 3x + \frac{30}{5\pi} \sin 5x + \frac{30}{7\pi} \sin 7x + \frac{30}{9\pi} \sin 9x + \dots$$

or, $I_{m(ac)}^2 = 100 - 16$

or, $I_{m(ac)} = \sqrt{84} = 9.165$

6.26 in sketch yourself

(a) $i = 5 + 2 \sin(754 t)$

$$\frac{di}{dt} = 2 \times 754 \cos(754 t)$$

$$= 1508 \cos(754 t)$$

$\therefore \cos(754 t) = 0$

$$754 t = 1$$

$$t = \frac{1}{754}$$

(b) $I_{m(ac)} = 0.5(7 - 1)$

$$= 3 \text{ volt}$$

(c) $V_{eff} = \sqrt{\frac{5^2 + 2^2}{2}}$

$$= 3.81 \text{ volt}$$

6.27 (a) $i = I_{dc} + I_{m(ac)} \sin x$

yes, $I_{m(ac)}$ is the maximum value.

(b) $i = I_{dc} + I_{m(ac)} \sin x$

$$I_{eff} = \sqrt{\frac{I_{dc}^2 + I_{m(ac)}^2}{2}}$$

So $I_c = 4$ and

$$4 \times 25 = 16 + I_{m(ac)}^2$$

$$\frac{I_{m2}}{I_{m1}} \times 100 = \frac{(I_{max} + I_{min}) - 2I_0}{(I_{max} - I_{min})/2}$$

$$= \frac{0.5(I_{max} - I_{min}) - I_0}{(I_{max} - I_{min})}$$

$$(c) \text{ Percent distortion} = (I_{m2}/I_{m1}) \times 100$$

$$I_{m1} = 0.5(I_{\max} - I_{\min})$$

$$\text{or, } 2I_{m1} = (I_{\max} - I_{\min})$$

$$\text{and } 4I_{m2} = (I_{\max} + I_{\min}) - 2I_b$$

$$I_{\max} + I_{\min} = 4I_{m2} + I_b$$

$$\text{and } I_{\max} - I_{\min} = 2I_{m1}$$

$$2I_{\max} = (4I_{m2} + 2I_b + 2I_{m1})$$

$$I_{\max} = (2I_2 + I_b + I_{m1})$$


$$\text{and } 2I_{\min} = 4I_{m2} + 4I_b - 2I_{m1}$$

$$I_{\min} = (2I_{m2} + I_b - I_{m1})$$

So find the ratio and I_{\max} , I_{\min} from the above equations.

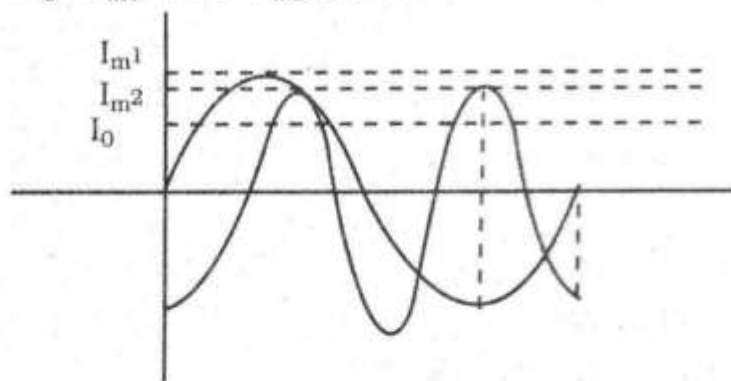6.28 Do yourself

$$\mathbf{6.29} \quad i = I_0 + I_{m1} \sin x - I_{m2} \cos 2x$$



$$I_{\max} = I_0 + I_{m1} + I_{m2}$$

$$= (I_0 - I_{m2}) + I_{m1} + 2I_{m2}$$

$$I_b = I_0 - I_{m2}$$

$$\text{So, } I_{\max} \text{ (with a - c grid excitation)} = I_b + I_{m1} + 2I_{m2}$$

$$I_{\min} \text{ (with a - c grid excitation)} = I_b - I_{m1} + 2I_{m2}$$

$$I_{m1} = 0.5(I_{\max} - I_{\min})$$

$$I_{m2} = \frac{(I_{\max} + I_{\min}) - 2I_b}{4}$$

$$\begin{aligned} \therefore i_{\text{eff}} &= \sqrt{(2.5)^2 + \left(\frac{30}{\pi}\right)^2 + \left(\frac{30}{3\pi}\right)^2 + \left(\frac{30}{5\pi}\right)^2 + \left(\frac{30}{7\pi}\right)^2 + \left(\frac{30}{9\pi}\right)^2} \\ &= \sqrt{1730.6459} \\ &= 41.601 \text{ amp} \end{aligned}$$

6.30 $I = I_b + I_{m1} \sin x + I_{m3} \sin 3x$

$I_b = 0.2 \text{ amp}$	$i_{\text{min}} = I_b - I_{m1} + 2I_{m2}$
$I_{m1} = 0.07 \text{ amp}$	$= 0.2 - 0.07 + 2 \times 0.005$
$I_{m3} = 0.005 \text{ amp}$	$= 0.14$
$= 0.28$	$i_{\text{max}} = I_b + I_{m1} + 2I_{m2}$
$i_{\text{avg}} \Rightarrow I_b = 0.2$	$= 0.2 + 0.07 + 2 \times 0.005$

6.31

$$\begin{aligned} P &= \frac{100 \times 20 + (-50) \times 10 + (25) (-5)}{2} \\ &= 687.5 \text{ watt} \end{aligned}$$

6.32 Same as 31

$$\begin{aligned} \text{6.33 } p.f. &= \frac{687.5}{\sqrt{\frac{100^2 + 50^2 + 25^2}{2}} \times \sqrt{\frac{20^2 + 10^2 + 5^2}{2}}} \\ &= \frac{687.5}{81.0092 \times 16.20185} \\ &= 0.5238 \end{aligned}$$

6.34 Same as 33.

6.35 (a) $P = \frac{100 \times 10 - 50 \times 5}{2} = 375$

$$\begin{aligned} \text{(b) } p.f. &= \frac{375}{\sqrt{\frac{100^2 + 50^2}{2}} \sqrt{\frac{10^2 + 5^2}{2}}} \\ &= \frac{375}{79.05 \times 7.91} \\ &= 0.5997 \end{aligned}$$

6.36

$$V_{\text{eff}} = 81 \text{ volt}$$

$$\text{So } V(t) = \sqrt{2} \times 81 \sin \omega t$$

$$p.f. = 0.5238$$

$$\theta = 58.4125$$

$$\therefore i(t) = \sqrt{2} \times 16.20185 \sin(\omega t - 58.4125)$$

6.38

$$V = 100 \sin(\omega t + 30^\circ) - 50 \sin(3\omega t + 60^\circ) + 30 \cos 5\omega t$$

$$R = 6 \text{ ohms}$$

$$C = 88.4 \mu\text{f}$$

$$L = 0.01061 \text{ H}$$

$$z = 6 + j \left(\omega \times 0.01 - \frac{10^6}{\omega \times 88.40} \right)$$

$$= 6 + j \left(377 \times 0.01 - \frac{106}{377 \times 88.4} \right)$$

$$= 6 + j(-26.235) = 26.91 \angle -77.1178, \theta = 77.1178$$


$$V_{\text{eff}} = \sqrt{\frac{100^2 + 50^2 + 30^2}{2}}$$

$$= 81.85 \text{ volts}$$

$$\therefore I_{\text{rms}} = \frac{81.85}{26.91} = 3.041 \text{ amp}$$

$$\begin{aligned} \therefore P_{\text{power}} &= V_{\text{rms}} \times I_{\text{rms}} \cos \theta \\ &= 81.85 \times 3.041 \times \cos(-77.187) \\ &= 488.466 \text{ watts} \end{aligned}$$

6.39 Similar to 38.

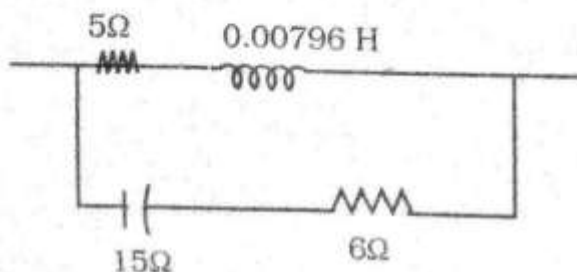6.40

$$\begin{aligned} X_L &= 0.00796 \times 377 \\ &= 3\Omega \end{aligned}$$

$$\begin{aligned}\therefore Z &= (5 + i3 \Omega)^{-1} + (6 - 15j)^{-1} \\ &= 0.172 \angle -10.25^\circ \\ e &= 100 \sin(\omega t + 30^\circ) - 50 \cos(3\omega t - 30^\circ)\end{aligned}$$

$$\begin{aligned}e_{\text{rms}} &= \sqrt{\frac{100^2 + 50^2}{2}} \\ &= 111.8 \text{ volt}\end{aligned}$$

$$\therefore I_{\text{rms}} = \frac{111.8}{0.172} = 650 \text{ amp}$$

$$I_{\text{rms}} = \sqrt{\frac{I_1^2 + I_2^2}{2}} \text{ and phase shift} = -10.25^\circ$$

So find the equation.

6.41 Ammeter reading = 650 amp

6.42 Power = $111.8 \times 650 \times \cos 10.25^\circ$
= 71510.2375 watts

6.43 pf = 0.9840

VA = 72670 VA

6.44

$$i_1 = 20 \sin(\omega t + 30^\circ) - 10 \sin(2\omega t - 30^\circ) + 5 \sin(3\omega t - 40^\circ)$$

$$i_2 = 15 \cos \omega t + 10 \cos(2\omega t - 60^\circ) + 10 \cos(3\omega t + 50^\circ)$$

$$i_{m1}' = 20(\cos 30^\circ + j \sin 30^\circ) = (8.66 + 5j) \times 2 = 17.32 + 10j$$

$$i_{m1}'' = -10(\cos 30^\circ - j \sin 30^\circ) = -8.66 + 5j$$

$$i_{m1}''' = 5(\cos -90^\circ - j \sin 40^\circ) = 3.83 - 3.2139j$$

$$\therefore i_{m2}' = 15$$

$$i_{m2}'' = 10 [\cos 60^\circ - j \sin 60^\circ] = 5 - 8.66j$$

$$i_{m2}' = 10 [\cos 50^\circ + j \sin 50^\circ] = 6.43 + 7.66j$$

So, $i_{\text{result}} = i_{m1}' + i_{m2}'$

$$i_{\text{result}} = i_{m1}'' + i_{m2}''$$


and $i_{\text{result}} = i_{m1}''' + i_{m2}'''$

Find yourself.

45. Similar to 44.

Chapter-7 Coupled Circuits

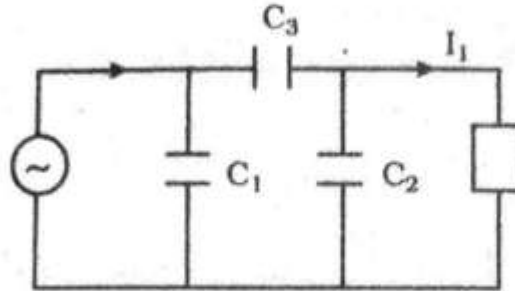
7.2. Let the voltage drop across c_1 is v_1



∴ Voltage developed across condenser c_1 per unit current is—

$$X_{\text{coupling}} = \frac{V_1}{I_2} = \frac{\frac{V_2}{X_1 + X_3} \cdot X_1}{V_2 \left(\frac{1}{X_2} + \frac{1}{X_1 + X_3} \right)} = \frac{\frac{X_1}{X_1 + X_3}}{\frac{X_1 + X_3 + X_3}{X_2(X_1 + X_3)}} = \frac{X_1 X_2}{X_1 + X_2 + X_3}$$

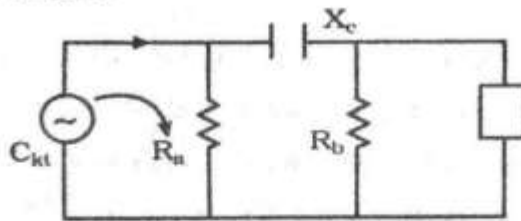
7.3. When Z_{coupling} is measured then CKt-2 is to be considered as circuit.



If V_b be the voltage developed across R_b then the coupling impedance between the two circuit is

$$\begin{aligned} Z_{\text{coupling}} = \frac{V_b}{I_1} &= \frac{\frac{V_a}{R_b - j \times c} \times R_b}{V_a \left(\frac{1}{R_a} + \frac{1}{R_a - j \times c} \right)} \\ &= \frac{\frac{R_b}{R_b} - j \times c}{\frac{R_b + R_a - j \times c}{R_a (R_b - j \times c)}} = \frac{R_a R_b}{R_a + R_b - j \times c} \\ &= \frac{R_a^2 R_b + R_a R_b^2 + j R_a R_b \times X_c}{(R_a + R_b)^2 + X_c^2} \end{aligned}$$


7.4.

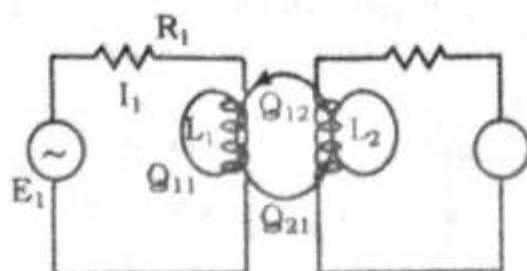

$$(a) M_{12} = N_2 \times \frac{\phi_{12}}{I_1} = \frac{500 \times 27500 \times 10^{-8}}{5} = 0.0275 \text{ h}$$

$$(b) L_1 = N_1 \frac{\phi_1}{I_1} = \frac{50 \times 30.000 \times 10^{-8}}{5} = 3 \text{ mh}$$

7.5

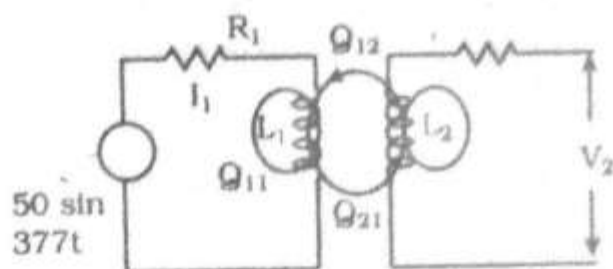

$$V = 50 \sin 3.77t \therefore \omega = 377 \text{ rad/sec}$$

$$\therefore X_m = \omega_m = 377 \times 0.02 = 7.54 \text{ ohm}$$

The voltage across the open circuited terminals of neighbouring coil is—

$$\text{Now, } \frac{50}{\sqrt{2}} = I_1 \left(10 + j377 \times \frac{1}{37.7} + 0 \right)$$

$$\text{or, } I_1 = \frac{35.55}{10 + j10} = 2.5 \angle -45^\circ$$

$$\begin{aligned} \text{Now, } V_2 &= I_2(j\omega L_2 + R_2) + I_1(j\omega m) = 0 + (2.5 \angle -45^\circ)(j377 \times 0.02) \\ &= 2.5 \angle -45^\circ (7.54 \angle 90^\circ) = 18.85 \angle 45^\circ \end{aligned}$$

\therefore The value of X_2 is 18.85 Volt

$$7.7. \quad V_1 = \frac{50}{\sqrt{2}} = 35.355 \angle 0^\circ \text{ Volt}$$

$$I_1 = 2.5 \angle -45^\circ$$

$$I_1 R_1 = (2.5 \angle 45^\circ) (10) = 25 \angle -45^\circ \text{ Volts}$$

$$j \times L_1 I_1 = \left(j 377 \times \frac{1}{37.7} \right) (2.5 \angle -45^\circ)$$

$$= (10 \angle 90^\circ) (2.5 \angle -45^\circ) = 25 \angle 45^\circ \text{ Voltz}$$

$$j \times m I_1 = (j 377 \times 0.02) (2.5 \angle -45^\circ)$$

$$= (7.54 \angle 90^\circ) (2.5 \angle -45^\circ) = 18.84 \angle 45^\circ$$

$$E_{21} = -V_2 = 18.85 \angle 45^\circ = -13.329 - j13.329 = 18.85 \angle -135^\circ$$

Now draw vector diagram by yourself.

$$7.8. \quad I_1 = 0.094 \text{ h} \quad \therefore M = K \sqrt{L_1 L_2}$$

$$L_2 = 0.0108 \text{ h} \quad = 0.0256$$

$$K_m = 0.805$$

$$7.9. \quad N_1 = 1000 \text{ turns, } \frac{\phi_1}{i_1} = 9400 \text{ Max watts/amp} = 9400 \times 10^{-8}$$

⁸ waber/amp

$$N_2 = 338 \text{ turns, } K = 0.805$$

$$L_1 = N_1 \frac{\phi_1}{i_1} = 1000 \times 9400 \times 10^{-8} = 0.094 \text{ h}$$

$$\frac{L_1}{L_2} = \frac{N_1^2}{N_2^2} L = \frac{N \phi}{i} \text{ again } Ni = R \phi$$

$$\therefore L_2 = L_1 \times \frac{N_2^2}{N_1^2} = 0.094 \times \frac{338^2}{1000^2} = 0.0107 \text{ h}$$


$$\therefore M = K \sqrt{L_1 L_2} = 0.805 \sqrt{L_1 L_2} = 0.0255 \text{ h}$$

1.10. Voltage of self-inductance in the L_2 coil considered as an induced voltage acts in a clack-wise direction around CKt-2 when $\frac{di_2}{dt}$ is considered positive. Since $M \frac{di_1}{dt}$ acts oppositely to $L_2 \frac{di_2}{dt}$ in ckt - 2, M must be considered - ve if L_2 considered as + X_e . The general expression for voltage equilibrium in the ckt 2 is $-R_2 i_2 + L_2 \frac{di_2}{dt} - M \frac{di_1}{dt} = c_{ba}$

7.11. Here, $M = -3\text{mh}$, $Z_c = R_a + R_b + j(I_s + b_r - 2m)$
 $= (1 + 6) + j(1000)(0.004 + 0.009 - 0.006)$
 $= 7 - j7 = 9.90 \angle -45^\circ$

$$I = \frac{V}{z_c} = \frac{40.5}{9.9} = 4.09 \text{ amp}$$

7.12.

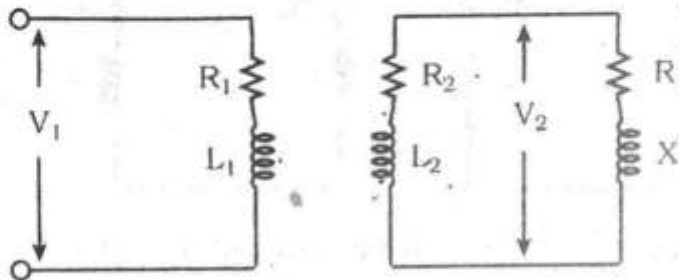

The equations are $I_1 Z_1 + I_2 Z_m = V$

$$I_1 Z_m + I_2 Z_2 = V$$

$$\therefore I_1 = \frac{\begin{vmatrix} V & Z_m \\ V & Z_2 \end{vmatrix}}{\begin{vmatrix} Z_1 & Z_m \\ Z_m & Z_2 \end{vmatrix}} = \frac{V(Z_2 - Z_m)}{Z_1 Z_2 - Z_m^2}$$

$$I_2 = \frac{\begin{vmatrix} Z_1 & V \\ Z_m & V \end{vmatrix}}{\begin{vmatrix} Z_1 & Z_m \\ Z_m & Z_2 \end{vmatrix}} = \frac{V(Z_1 - Z_m)}{Z_1 Z_2 - Z_m^2}$$

$$I = I_1 + I_2 = \frac{V(Z_1 + Z_2 - 2Z_m)}{Z_1 Z_2 - Z_m^2}$$

$$Z_c = \frac{V}{I} = \frac{Z_1 Z_2 - Z_m^2}{Z_1 + Z_2 - 2Z_m}$$

$$= \frac{(35.5 \angle 84.7^\circ)(4.17 \angle 79.29^\circ) - (9.65 \angle 90^\circ)^2}{3.3 + j35.4 + 0.775 + j4.07 - j19.30}$$

$$= \frac{63.9 \angle 140.3^\circ}{20.578 \angle 78.58^\circ} = 3.1 \angle 61.7^\circ$$


$$I = \frac{V}{Z_c} = \frac{50 \angle 0^\circ}{3.1 \angle 61.7^\circ} = 16.13 \angle -61.7^\circ \text{ A}$$

$$I_2 = \frac{V(Z_1 - Z_2)}{Z_1 Z_2 - Z_m^2}$$

$$= \frac{50 \angle 0^\circ (3.3 + j35.4 - j9.65)}{63.9 \angle 140.3^\circ} = 4.41 \angle -27.2^\circ$$

$$P = VI \cos \theta = 50 \angle 0^\circ \times 16.13 \times \cos(61.7^\circ) = 382.352 \text{ watts}$$
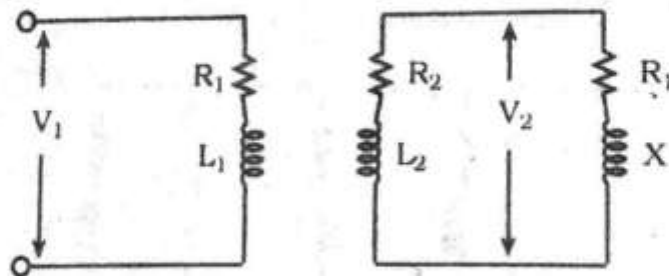
$$\begin{array}{ll}
 \mathbf{7.13} & R_1 = 3.3 \text{ ohms} & M = 0.0256 \text{ H} \\
 & L_1 = 0.094 \text{ H} & Z = 28.15 \\
 & R_2 = 0.775 \text{ ohms} & W = 377 \text{ rad/sec} \\
 & L_2 = 0.0108 \text{ H} & V_1 = 50 \angle 0 \text{ volts}
 \end{array}$$



$$\begin{aligned}
 \text{(a)} \quad Z_{c1} &= Z_1 - \frac{Zm^2}{Z_2 + Z} \cdot Z_2 + Z = (0.775 + j377)(0.0108) + 28.15 \\
 &= 28.925 + j4.07 = 29.21 \angle 8^\circ \text{ ohms}
 \end{aligned}$$

$$\begin{aligned}
 Z_{c1} &= 3.3 + j35.4 + \frac{(9.65)^2 \angle 0}{29.21 \angle 80^\circ} \\
 &= 3.3 + j35.4 + 3.16 - j0.444 \\
 &= 6.46 + j34.96 = 35.55 \angle 79.53 \text{ ohms}
 \end{aligned}$$

$$I_1 = \frac{50 \angle 0^\circ \angle 79.53^\circ}{35.55} = 1.407 \angle -79.53^\circ \text{ amp}$$

$$\begin{aligned}
 I_2 &= \frac{-I_1 Zm}{Z_2 + Z} = \frac{(1.407 \angle -79.53 + 180)(9.65 \angle 90^\circ)}{29.21 \angle 8^\circ} \\
 &= 0.465 \angle 182.42 \text{ amp}
 \end{aligned}$$


$$\begin{aligned}
 \text{(b)} \quad P_{in} &= X_1 I_1 \cos \theta \quad \left. \begin{array}{l} \uparrow V_1 \\ \downarrow I_1 \end{array} \right\} \\
 &= 50 \times 1.407 \times \cos 79.53 = 12.8 \text{ watts}
 \end{aligned}$$

$$\begin{aligned}
 P_{out} &= V_2 I_2 \cos \theta \quad \left. \begin{array}{l} \uparrow V_2 \\ \downarrow I_2 \end{array} \right\} \cdot V_2 = 2I_2 \\
 &= 28.15 \times 0.465 \angle 182.47 = 13.09 \angle 182.45^\circ
 \end{aligned}$$

$$\therefore P_{out} = 13.09 \times 0.465 \times \cos 182.47 = 6.08 \text{ watts}$$

$$\therefore \text{Efficiency of operation} = \frac{6.08}{12.8} = 0.475 \text{ i.e., } 47.5\%$$

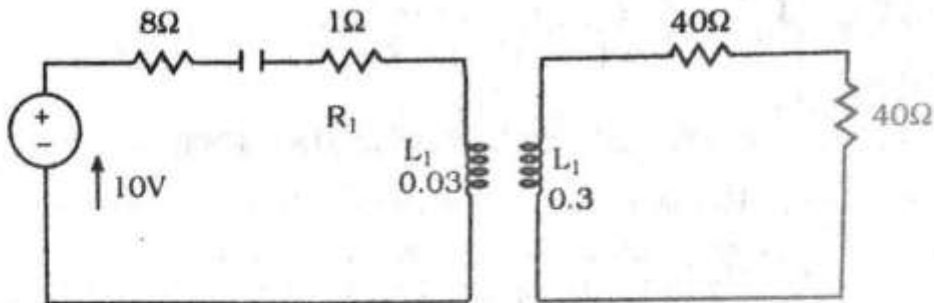7.14 $M = 0.275$ henry, $\omega = 1667$ rad/sec



$$(b) 2I_1 + 1I_1 - j8I_1 + j50.01I_1 + j458.425 I_2 = 10$$

$$\text{or. } (3 + j42.01) I_1 + j458.425 I_2 = 10$$

$$\text{or. } (100 + j500) I_2 + j1500I_2 + j458.425I_1 = 0$$

$$\text{or. } (100 + j5001)I_2 + j458.425I_1 = 0$$


$$\text{or. } j458.425I_1 + (100 + j5001)I_2 = 0$$

$$I_1 = \frac{\begin{vmatrix} 10 & j458.425 \\ 0 & 100 + j5001 \end{vmatrix}}{\begin{vmatrix} 3 + j4201 & j458.425 \\ j458.425 & 100 + j5001 \end{vmatrix}} = 2.589 \angle 0.09^\circ$$

$$\therefore I_1 = 2.589 \angle 0.09^\circ$$

$$I_2 = \frac{j458.425 \times 10}{19317.85 \angle 88.94} = 0.237 \angle 1.06$$

7.15

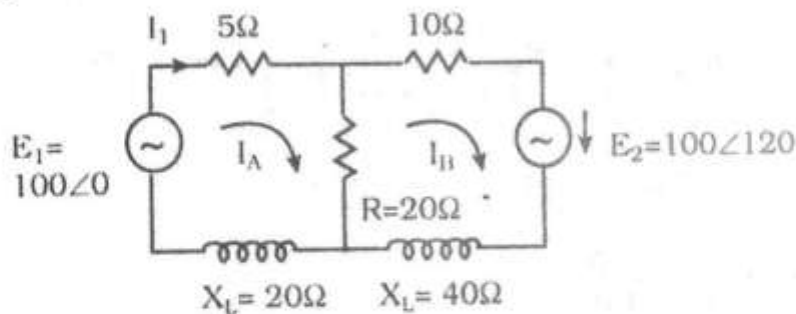

$$\text{Now, } E_1 = Z_{11} I_A - Z_{12} I_B$$

$$E_2 = Z_{21} I_A + Z_{22} I_B$$

$$\therefore I_A = \frac{\begin{vmatrix} E_1 & -Z_{12} \\ E_2 & Z_{22} \end{vmatrix}}{\begin{vmatrix} Z_{11} & -Z_{12} \\ Z_{21} & Z_{22} \end{vmatrix}} = \frac{E_1 Z_{22} + Z_2 Z_{12}}{Z_{11} Z_{22} - Z_{12}^2}$$

$$\text{and } I_{11} = \frac{\begin{vmatrix} Z_{11} & E_1 \\ Z_{21} & Z_2 \end{vmatrix}}{\begin{vmatrix} Z_{11} & -Z_{12} \\ Z_{21} & Z_{22} \end{vmatrix}} = \frac{E_1 Z_{22} + E_2 Z_{12}}{Z_{11} Z_{22} - Z_{12}^2}$$

$$\text{Where } Z_{11} = 5 + 20 + j20 = 25 + j20 = 32.018 \angle 38.66^\circ$$

$$Z_{22} = 10 + 20 + j40 = 30 + j40 = 50 \angle 53.13^\circ \quad Z_{12} = 20 \text{ ohm}$$

$$\therefore I_A = \frac{(100 \angle 0^\circ)(50 \angle 53.1^\circ) + (100 \angle 120^\circ)(20)}{(32.016 \angle 38.66^\circ)(50 \angle 53.13^\circ) - 20^2}$$

$$= 3.653 \angle -34.94^\circ$$

$$I_{11} = \frac{(32.016 \angle 38.66^\circ)(100 \angle 120^\circ) + (100 \angle 0^\circ)(20)}{1662.077 \angle 105.70^\circ}$$


$$= \frac{-2982.09 + j1165.067 + 2000}{1662.077 \angle 105.7} = 0.917 \angle 24.43^\circ$$

$$\text{Now, } I_1 = I_A = 3.653 \angle -34.94^\circ \text{ A } \quad I_2 = I_{11} = 0.917 \angle 24.43^\circ \text{ A}$$

$$I_{12} = I_A - I_{11} = 2.995 - j2.092 - 0.335 - j0.379$$

$$= 3.28 \angle -48.84^\circ$$

7.16

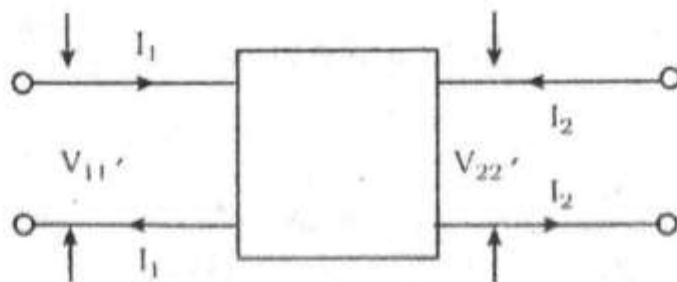


$$(a) \quad Z_{21} = \frac{V_{22}'}{I_1} = \frac{4 \angle 10^\circ}{1 \angle 90^\circ} = 4 \angle -80^\circ$$

$$Z_{12} = \frac{V_{11}'}{I_2} = \frac{6 \angle 0^\circ}{1.5 \angle 90^\circ} = 4 \angle -90^\circ$$

$$(b) \quad K = \frac{Z_{12}}{\sqrt{Z_{11}' Z_{22}'}} \quad \text{where } Z_{11}' = \frac{E_1}{I_1} = \frac{6 \angle 0^\circ}{1 \angle 90^\circ} = 6 \angle -90^\circ$$

$$= \frac{4 \angle -90^\circ}{\sqrt{24 \angle -90^\circ}} \quad Z_{22}' = \frac{6 \angle 0^\circ}{1.5 \angle +90^\circ} = 4 \angle -90^\circ$$

$$= 0.816$$

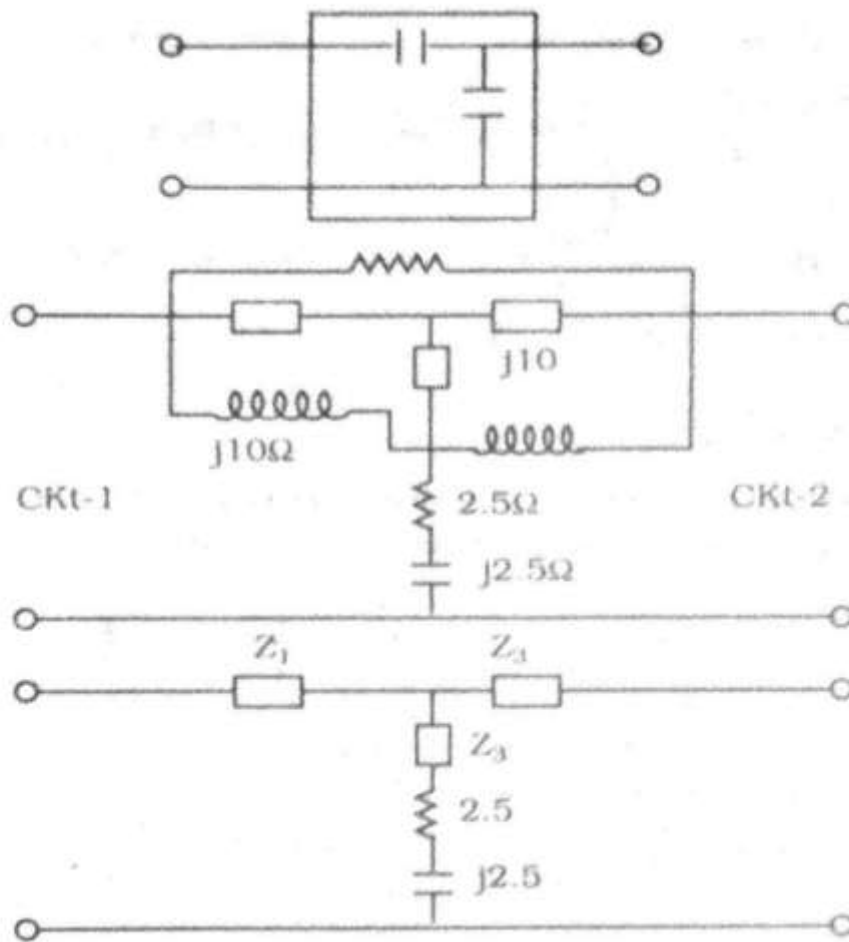

$$Z_1 = \frac{j10 \times 20}{20 + j10 + j10} = \frac{200 \angle 90^\circ}{28.284 \angle 45^\circ}$$

$$= 7.071 \angle 45^\circ$$

$$Z_2 = \frac{j10 \times j10}{28.284 \angle 45^\circ} = \frac{100 \angle 180^\circ}{28.284 \angle 45^\circ}$$

$$= 3.536 \angle 135^\circ$$


$$= -2.5 + 2.5$$

$$Z_3 = \frac{j10 \times 20}{28.284 \angle 45^\circ} = 7.071 \angle 45^\circ$$

Now, $Z_{12} = Z_2 + 2.5 - j2.5 = -2.5 + j2.5 + 2.5 - j2.5 = 0$

Now, $K = \frac{Z_{12}}{\sqrt{Z_{11} \cdot Z_{22}}} = 0$

7.17

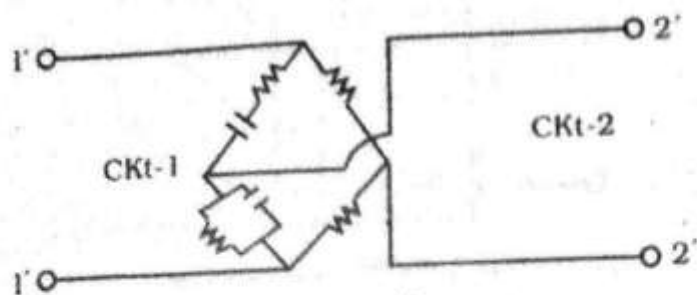

Let us assume that $K = 0 \therefore K = \frac{Z_{12}}{\sqrt{Z_{1'1'}Z_{2'2'}}} = 0 \Rightarrow Z_{12} = 0$

$$\Rightarrow \frac{V_{22'}}{Z_1} = 0 \Rightarrow V_{2'2} = 0$$


i.e., there is no potential difference between 11', the ckt is equivalent to a wheatstone bridge at balanced condition

$$\therefore \frac{P}{Q} = \frac{R}{S} \Rightarrow PS = QR \Rightarrow \frac{j \frac{1}{\omega C_2} \cdot R_2}{R_2 - j \frac{1}{\omega_1 C_2}} \cdot R_1 = R_1 \left(R_1 - j \frac{1}{\omega C_1} \right) \quad [R_1 = R_1]$$

$$\text{or, } R_1 R_2 - \frac{1}{\omega^2 C_1 C_2} - j \frac{R_2}{\omega C_1} - j \frac{\omega_2}{\omega C_2} = -j \frac{R_2}{\omega C_2}$$

$$\text{or, } \frac{1}{\omega^2 C_1 C_2} = R_1 R_2 \therefore \omega = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \quad [\text{Proved}]$$

7.18

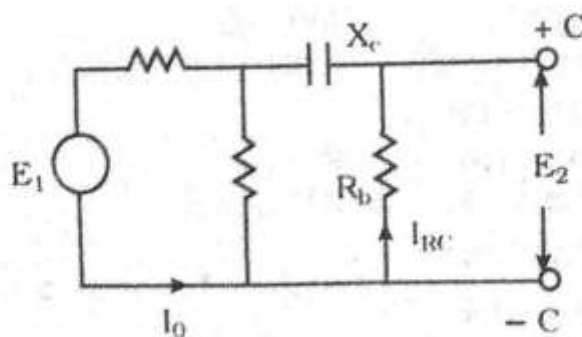

If R_c drops from a to b V_2 drop from c to d. E_2 from c to d will be negative


$$\text{Now, } Z_0 = R_p + \frac{R_b \left(R_c - \frac{1}{\omega C_p} \right)}{R_b + R_c - \frac{1}{\omega C_b}} \quad \left[I_0 = \frac{\mu E_0}{Z_0} \right]$$

$$\text{Now, } I_{RC} = \frac{R_b}{R_b + R_c - j \frac{1}{\omega C_b}}$$

∴ from KVL we have $E_2 + I_{RC} \times R_c = 0$

$$\text{or, } E_2 = -I_{RC} \times R_c$$

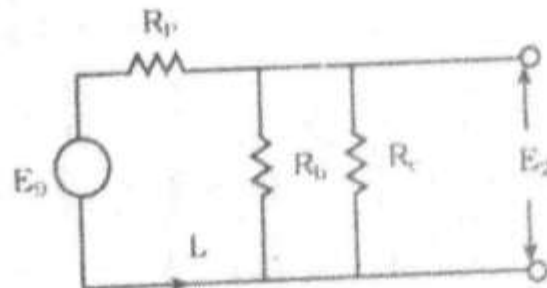
$$\begin{aligned} \text{or, } E_2 &= - \left(\frac{R_b R_c}{R_b + R_c - j \frac{1}{\omega C_b}} \right) \times \mu E_0 \times \frac{R_b + R_c - j \frac{1}{\omega C_b}}{R_p \left(R_b + R_c - j \frac{1}{\omega C_b} \right) + R_b \left(R_c - j \frac{1}{\omega C_b} \right)} \\ &= - \frac{\mu E_0 R_b R_c}{R_p R_b + R_p R_c + R_b R_c - j \frac{R_p + R_b}{\omega C_b}} \end{aligned}$$



$$Z_0 = R_b + \frac{R_b R_c}{R_b + R_c} = \frac{R_b(R_b + R_c) + R_b R_c}{R_b + R_c} \therefore I_0 = \frac{\mu E_0}{Z_0}$$


∴ $I_{RC} = \frac{R_b}{R_b + R_c} I_0$. Now from KVL we have $I_{RC} + E_2 = 0$
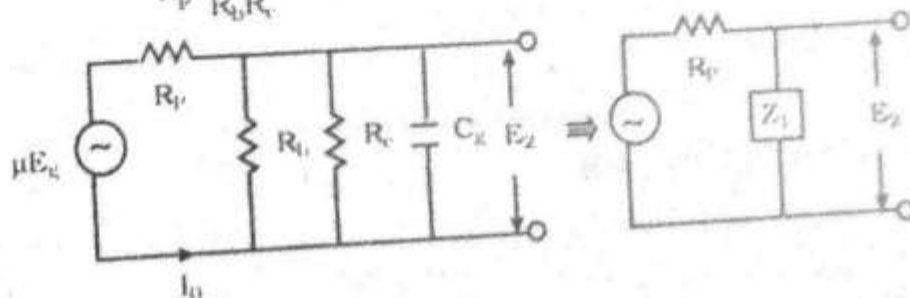
$$\begin{aligned} \text{or, } E_2 &= -R_c \times \frac{R_b}{R_b + R_c} \cdot \mu E_0 \times \frac{R_b + R_c}{R_p(R_b + R_c) + R_b R_c} \\ &= \frac{-\mu E_0 R_b R_c}{R_p(R_b + R_c) + R_b R_c} \\ &= \frac{-\mu E_0}{\frac{R_p}{R_b} + \frac{R_p}{R_c} + 1} \quad \text{[Proved]} \end{aligned}$$



$$\begin{aligned}
 \frac{1}{Z} &= \frac{1}{R_b} + \frac{1}{R_c} + \frac{1}{-j\omega C_g} \therefore Z_0 = R_p + \frac{R_b R_c \left(-j\frac{1}{\omega C_g}\right)}{R_b R_c + R_c \left(-j\frac{1}{\omega C_g}\right)} + R_b \left(-j\frac{1}{\omega C_g}\right) \\
 &= R_p + Z \therefore I_0 = \frac{\mu E_g}{Z_0} = \frac{\mu E_g}{R_p} \text{ from KVL we have} \\
 E_2 &= -Z I_0 \frac{-R_b R_c \left(-j\frac{1}{\omega C_g}\right)}{R_b R_c + R_b \left(-j\frac{1}{\omega C_g}\right) + R_c \left(-j\frac{1}{\omega C_g}\right)} \\
 &\quad \times \frac{E_g}{R_p + R_b R_c \left(-j\frac{1}{\omega C_g}\right)} \\
 &\quad \frac{R_b R_c + R_b \left(-j\frac{1}{\omega C_g}\right) + R_c \left(-j\frac{1}{\omega C_g}\right)}{R_b R_c + R_b \left(-j\frac{1}{\omega C_g}\right) + R_c \left(-j\frac{1}{\omega C_g}\right)} \\
 &= \frac{-\mu E_g E_b R_c \left(-j\frac{1}{\omega C_g}\right)}{R_p (R_b R_c + R_b \left(-j\frac{1}{\omega C_g}\right) + R_c \left(-j\frac{1}{\omega C_g}\right) + R_b R_c \left(-j\frac{1}{\omega C_g}\right))} \\
 &= \frac{-\mu E_g R_b R_c \left(-j\frac{1}{\omega C_g}\right)}{R_p R_b R_c + R_p \left(-j\frac{R_b + R_c}{\omega C_g}\right) + R_b R_c \left(-j\frac{1}{\omega C_g}\right)} \\
 &= \frac{-\mu E_g}{\frac{R_p}{-j\frac{1}{\omega C_g}} + R_p \frac{R_b + R_c}{R_b - R_c} + 1} = -\frac{\mu E_g}{jR_p \omega C_g + R_p \frac{R_b \times R_c}{R_b + R_c} + 1}
 \end{aligned}$$

7.23

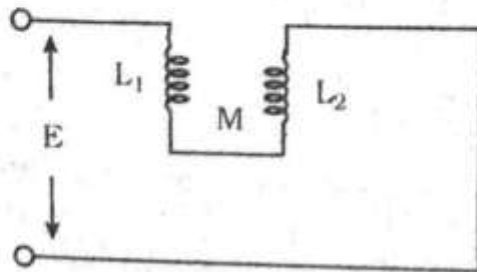

$$L_1 = 60 \text{ mh} = 0.06 \text{ h}$$

$$L_2 = 30 \text{ mh} = 0.03 \text{ h}$$


Now, L_e (add) = $L_1 + L_2 + 2m$ or, $0.12 = 0.06 + 0.03 + 2m$

$$\therefore 2m = 0.03 \text{ h}$$

(a) L_e (sub) = $L_1 + L_2 - 2m = 0.06 + 0.03 - 0.03 = 60 \text{ mh}$

$$(b) K = \frac{M}{\sqrt{L_1 L_2}} = \frac{0.03/2}{\sqrt{0.06 \times 0.03}} = 0.354$$

7.24

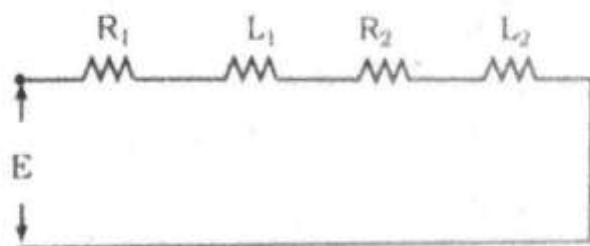

For additive combination = $I^2(R_1 + R_2) = 200$

$$\therefore R_1 + R_2 = \frac{200}{5^2} = 80 \text{ ohm}$$

Now, magnitude of Z_0 is = $\frac{100}{5} = 20$

$$\therefore 20 = \sqrt{(R_1 + R_2)^2 + (L_1 + L_2 + 2m)^2 \times (2\pi \times 69.5)^2} \quad | Z = \sqrt{R^2 + X_L^2}$$

$$\text{or, } 400 = 64 + (L_1 + L_2 + 2m)^2 (2\pi \times 69.5)^2$$

$$\therefore L_1 + L_2 + 2m = 0.04198$$


For subtractive combination $Z = \frac{100}{8} \sqrt{8^2 + (2\pi \times 69.5 (L_1 + L_2 - 2m))^2}$

$$\therefore L_1 + L_2 - 2m = 0.022$$

$$4m = 0.04198 - 0.022$$

$$\therefore M = 0.005 \text{ h} = 5 \text{ mh}$$

7.25

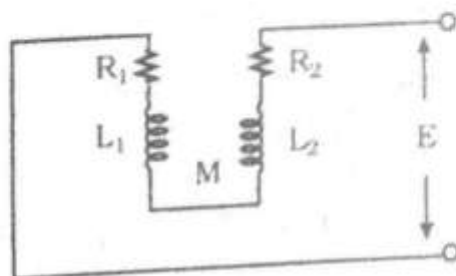

$$R_1 = R_2 = 4 \text{ ohm}$$

$$V = IR_1 + j\omega L_1 I + j\omega M I$$

$$\frac{V}{I} = R_1 + j(L_1 + M)\omega$$

$$\text{or, } \frac{26.05}{5} = 4 + j\omega(L_1 + 0.005)$$

$$\text{or, } (7.21)^2 = 4^2 + \omega^2(L_1 + 0.005)^2$$

$$\text{or, } (7.21)^2 = 4^2 + (2\pi \times 69.5)^2 (L_1 + 0.005)^2$$

$$\therefore L_1 = 8.737 \text{ mh}$$

$$\text{Now, } L_1 + L_2 + 2M = 0.04198$$


$$\begin{aligned} \therefore L_2 &= 0.04198 - 2 \times 0.005 - 0.008737 \\ &= 23.249 \text{ mh} \end{aligned}$$

Now,

$$Z_2 = \sqrt{4^2 + (L_2 + M)^2 (\omega^2)} = 12.96 \text{ ohm}$$

$$\therefore V_2 = IZ_2 = 5 \times 12.96 = 64.8 \text{ Volts}$$
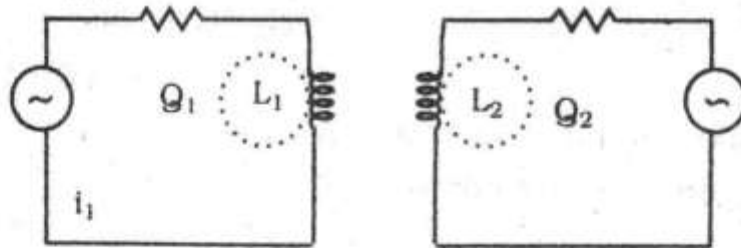
$$(b) K = \frac{M}{\sqrt{L_1 L_2}} = 0.35 \text{ Ans.}$$



$$\begin{aligned} L_1 &= 0.1 \text{ h, } L_2 = 0.05 \text{ h } M = K\sqrt{L_1 L_2} \\ &= 0.56\sqrt{0.1 \times 0.05} \\ &= 0.0356 \text{ h} \end{aligned}$$

Now the voltage induced in the 0.05 h winding as a result of

$$L_1 \text{ is } -M \frac{di_1}{dt} = 0.0396 - \frac{d}{dt} (10 \sin 377t)$$

$$= 0.0396 \times 10 \times 377 \cos 377t$$

$$X_2 = Z_m I_1 = \omega M I_1 = 377 \times 0.4 = X \frac{10}{\sqrt{2}} = 105.56 \text{ V}$$

$$\therefore \text{effective value} = -\frac{142.292}{\sqrt{2}} = 105.56 \text{ V}$$


Now, the induced voltage in 0.1 henry winding is—

$$L_1 = \frac{di_1}{dt} = 0.1 \times 10 \times 377 \cos 377t \approx 377 \cos 377t$$

$$\therefore \text{r.m.s value} = \frac{377}{\sqrt{2}} = 266.58 \text{ V}$$

$$\text{Again } V_1 = I_1 \times L_1 = \frac{10}{\sqrt{2}} \times 377 \times 0.1 = 266.58 \text{ V}$$

7.27

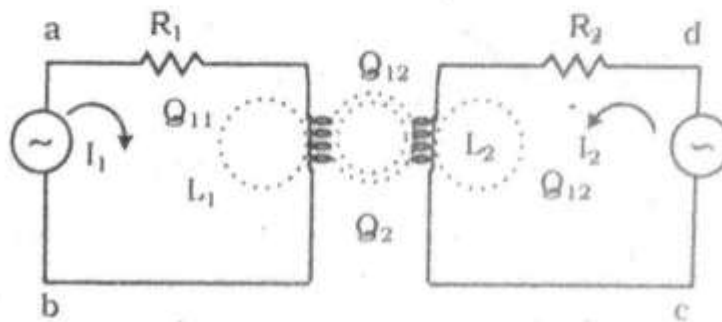

$$M = K_M \sqrt{L_1 L_2} = 0.4 \sqrt{0.056 \times 0.07} = 0.025 \text{ h, } M \text{ will be neg}$$

$$Z_1 I_1 - Z_M I_2 = E_{ba}$$

$$\text{and } -Z_M I_1 + Z_2 I_2 = E_{cd}$$

$$I_1 = I_{ba} = \frac{\begin{vmatrix} E_{ba} & -Z_M \\ E_{cd} & Z_2 \end{vmatrix}}{\begin{vmatrix} Z_1 & -Z_M \\ -Z_M & Z_2 \end{vmatrix}} = \frac{E_{ba} Z_2 + E_{cd} Z_M}{Z_1 Z_2 - Z_M^2}$$

$$= \frac{100 \angle 0^\circ \times (72 + j0.07 \times 1131) + (50 \angle -90^\circ) (j1131 \times 0.025)}{(50 + j0.056 \times 1131) (72 + j0.07 \times 1131) - (j1131 \times 0.025)^2}$$

$$= \frac{7199.846 + j7917.528 + 1413.75}{(80.694 \angle 51.71^\circ) (107.013 \angle 47.72^\circ) + 28.275^2}$$

$$= \frac{11699.26 \angle 42.59^\circ}{1414.83 + j8518.614 + 28.275^2} = \frac{116999.26 \angle 42.56^\circ}{3540.811 \angle 94.312^\circ}$$

$$= 1.37 \angle -51.54^\circ$$


$$I_2 = I_{cd} = \frac{\begin{vmatrix} Z_1 & E_{ba} \\ -Z_M & E_{cd} \end{vmatrix}}{\begin{vmatrix} Z_1 & -Z_M \\ -Z_M & Z_2 \end{vmatrix}} = \frac{Z_1 E_{cd} + Z_M E_{ba}}{Z_1 Z_2 - Z_M^2}$$

144 The Solution of Alternating Current Circuits


$$\begin{aligned}
 &= \frac{(80.694 \angle 51.71) (50 \angle -90^\circ) + (28.275 \angle 90^\circ) (100 \angle 0)}{8540.811 \angle 94.312^\circ} \\
 &= \frac{3166.774 - j2500 + j2827.5}{8540.81 \angle 94.312^\circ} = \frac{3183.656 \angle 5.9}{8540.81 \angle 94.312^\circ} \\
 &= 0.373 \angle -88.4^\circ
 \end{aligned}$$

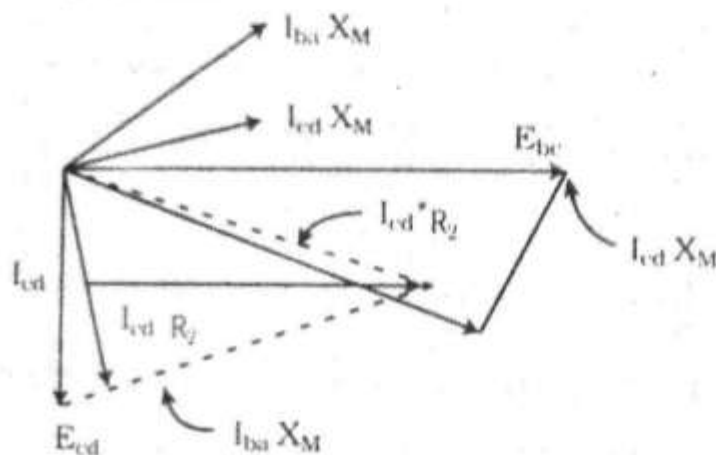(b) $P_{ba} = V_{ba} I_1 \cos \theta = 100 \times 1.37 \times \cos 51.54 = 85.21$ watt

$P_{cd} = V_{cd} I_2 \cos \theta = 50 \times 0.373 \cos \{-90 - (-88.4)\}$
 $= 17.64$ watts



(c)

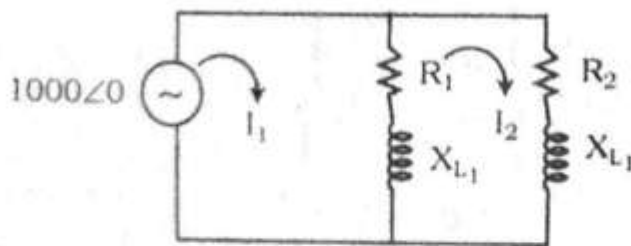

$R_1 = 2$ ohm

$X_{L1} = 3$ ohm

$X_{L2} = 12$ ohm

$$\begin{aligned}
 Z_M &= K \sqrt{X_{L1} \times X_{L2}} \\
 &= 0.8 \times \sqrt{3 \times 12} \\
 &= 4.8 \text{ ohm}
 \end{aligned}$$

Since mmf's are additive $\therefore M$ will be positive.

$Z_1 = 2 + j3 = 3.606 \angle 56.31$

$Z_2 = 5 + j12 = 13 \angle 67.38^\circ$

$Z_M = j4.8 = 4.8 \angle 90^\circ$

Now, $I_1 Z_1 + Z_2 Z_M = X$

and $I_1 Z_M + I_2 Z_2 = X$

$$\begin{aligned} \therefore I_1 &= \frac{\begin{vmatrix} V_1 & Z_M \\ V_1 & Z_2 \end{vmatrix}}{\begin{vmatrix} Z_1 & Z_M \\ Z_M & Z_2 \end{vmatrix}} = \frac{V(Z_2 - Z_M)}{Z_1 Z_2 - Z_M^2} \\ &= \frac{(100 \angle 0^\circ)(5 + j12 - 43j)}{(3.606 \angle 56.31^\circ)(13 \angle 67.38^\circ) - (4.8 \angle 90^\circ)^2} \\ &= \frac{876.584 \angle 56.2^\circ}{-22 + j39 + 23.04} = \frac{876.584 \angle 55.22^\circ}{39.112 \angle 94.34^\circ} \\ &= 22.41 \angle -39.12^\circ \end{aligned}$$

$$\begin{aligned} I_2 &= \frac{\begin{vmatrix} Z_1 & V \\ Z_M & V \end{vmatrix}}{\begin{vmatrix} Z_1 & Z_M \\ Z_M & Z_2 \end{vmatrix}} = \frac{V(Z_1 - Z_M)}{Z_1 Z_2 - Z_M^2} = \frac{(100 \angle 0^\circ)(2 + j3 - j4.8)}{39.112 \angle 94.34^\circ} \\ &= \frac{269.07 \angle -42^\circ}{39.112 \angle 94.34^\circ} = 6.879 \angle -136.34^\circ \text{ A} \end{aligned}$$

Power supplied conductively branch (2) is

$$\begin{aligned} &= VI_2 \cos \theta = 100 \times 6.879 \times \cos(-136.34^\circ) \\ &= -497.66 \text{ watts} \end{aligned}$$

Power dissipated in branch (2) is $= I_2^2 R_2$

$$= (6.879)^2 \times 5 = 236.6 \text{ watts}$$

\therefore Power supplied electromagnetically is

$$\begin{aligned} &= P_{\text{conductivity}} + P_{\text{dissipated}} \\ &= 497.66 + 236.6 = 734.26 \text{ watts} \end{aligned}$$

Again, power supplied electromagnetically in branch (1) is--


$$\begin{aligned} P_{\text{elect}} &= -P_{\text{conductivity}} + P_{\text{dissipated}} = -VI \cos \theta + I_1^2 R \\ &= -1738.63 + 1304.42 = -734.21 \text{ watts} \end{aligned}$$

The voltage drop across only the inductance of branch (2) is

$$\begin{aligned} V_2 &= X_{L2} I_2 + I_1 Z_M \\ &= (12 \angle 90^\circ)(6.879 \angle -136.34^\circ) + (22.41 \angle -39.12^\circ) \times (4.8 \angle 90^\circ) \\ &= 57 - j59.72 + 67.87 + j83.454 = 127.1 \angle 10.76^\circ \end{aligned}$$

$\therefore I_2$ lags V_2 by $(10.76 - (-136.34)) = 147.1^\circ$

7.29

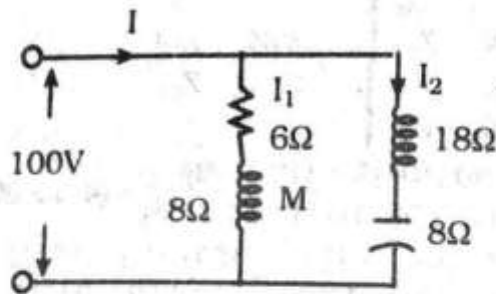

$$X_M = K\sqrt{X_{L1}X_{L2}} = 0.5\sqrt{8 \times 18} = 6 \text{ ohm}$$

Here, M will be negative

Now, $Z_1 I_1 - Z_M I_2 = V$ Where $Z_1 = 6 + j8$
 $-Z_M I_1 + Z_2 I_2 = V$ $Z_2 = -j8 + j18 = j16$


$$\therefore I_1 = \frac{\begin{vmatrix} V & -X_M \\ V & Z_2 \\ -Z_M & Z_2 \end{vmatrix}}{\begin{vmatrix} Z_1 & -Z_M \\ -Z_M & Z_2 \end{vmatrix}} = \frac{V(Z_2 + Z_M)}{Z_1 Z_2 - Z_M^2}$$

$$= \frac{(100 \angle 0^\circ) \{(-j8 + j18) + j6\}}{(6 + j8)(-j8 + j18) - (j6)^2}$$

$$= \frac{1600 \angle 90^\circ}{j60 - 80 + 36} = \frac{1600 \angle 70^\circ}{74.404 \angle 126.25^\circ}$$

$$= 21.5 \angle -36.25^\circ \text{ A}$$

7.30

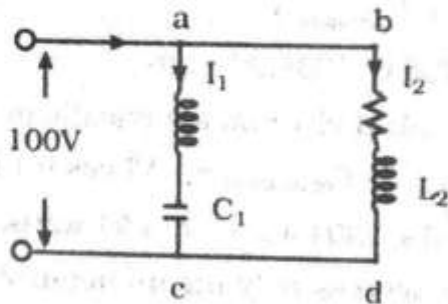

Now,

$$X_{L1} = 5 \text{ ohm, } X_{C1} = 5 \text{ ohm}$$

$$X_{L2} = 5 \text{ ohm, } X_M = 4 \text{ ohm}$$

$$R = 10, \text{ M is - ve}$$

$$\therefore (5j - 5j) I_1 - 4j I_2 = 100 \angle 0^\circ$$

or. $(4 \angle -90^\circ) I_2 = 100 \angle 0$

$\therefore I_2 = 25 \angle 90^\circ$

Again,

$(10 + j5)I_2 - j4I_1 = 100 \angle 0$

or. $(10 + j5)(j25) - 4jI_1 = 100$

or. $250j - 125 - 4jI_1 = 100$

or. $4jI_1 = 250j - 125 - 100$

$I_1 = 84.085 \angle 41.9872$

From KVL we have now,

$V_{bc} + V_{ca} + V_{ab} = 0$


or. $V_{bc} = V_{ac} - V_{ab} = R_2 I_2 - (X_{L1} I_1 - X_M I_2)$

$= 10 \times (25 \angle 90^\circ) - \{j5(84.085 \angle 42^\circ) - j4(25 \angle 90^\circ)\}$

$= 250 \angle 90^\circ - \{-281.319 + j312.437 + 100\}$

$= 191.8 \angle -19^\circ$ Vots

7.31

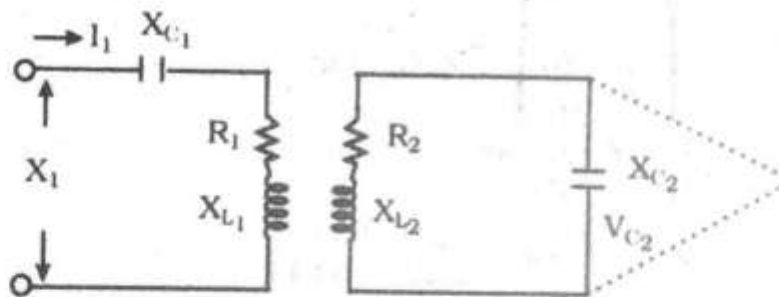

$R_1 = 4$ ohms

$R_2 = 100$ ohms

$X_{L1} = 40$ ohms

$X_{L2} = 100$ ohms

$X_{c1} = 40$ ohms

$X_{c2} = 120$ ohms

$X_M = 500$ ohms

$V_1 = 100$ volts

Since the direction of the mutual flux in the secondary of the circuit ϕ_{12} and current I_2 same. $\therefore M$ is positive.

Now,

$Z_1 = 4 + j40 - j40 = 4$ ohm

$$Z_2 = 10 + j100 - 120j = 10 - j20 = 22.36 \angle 63.43^\circ ;$$

$$Z_M = j50 = 50 \angle 90^\circ$$

Now,

$$Z_1 I_1 + Z_M I_2 = V_1 \text{ Here } Z_2 = Z_2 + Z \text{ of load}$$

$$Z_M I_1 + Z_2 I_2 = 0$$

$$I_2 = \frac{\begin{vmatrix} Z_1 & V_1 \\ Z_M & 0 \end{vmatrix}}{\begin{vmatrix} Z_1 & Z_M \\ Z_M & Z_2 \end{vmatrix}} = \frac{-V_1 Z_M}{Z_1 Z_2 - Z_M^2} = \frac{-(100 \angle 0^\circ)(50 \angle 90^\circ)}{(4)(22.36 \angle -63.43) - (50 \angle 90^\circ)^2}$$

$$= \frac{5000 \angle 90^\circ}{40 - j80 + 2500} = \frac{-5000 \angle 90^\circ}{2541.26 \angle -1.8} = -1.9675 \angle 91.8$$

$$\text{Now, } V_{C2} = I_2 X_{C2} = (1.9675 \angle 91.8)(120 \angle -90) = 236.1 \angle 1.8^\circ$$

7.32

From the previous problem we have—

$$I_1 = \frac{\begin{vmatrix} V_1 & Z_M \\ 0 & Z_2 \end{vmatrix}}{\begin{vmatrix} Z_1 & Z_M \\ Z_M & Z_2 \end{vmatrix}} = \frac{V_1 Z_2}{Z_1 Z_2 - Z_M^2}$$

$$\therefore Z_{C1} = \frac{V_1}{I_1} = \frac{Z_1 Z_2 - Z_M^2}{Z_2}$$

$$= Z_1 - \frac{Z_M^2}{Z_2} = 4 - \frac{(50 \angle 90^\circ)^2}{22.36 \angle -63.43}$$

$$= 4 - 111.8 \angle 243.43$$

$$= 4 + 50 + j100 = 54 + j100 = 113.65 \angle 61.63^\circ$$

$$\text{The reflected impedance into the primary} = \frac{Z_M^2}{Z_2}$$

$$= 111.8 \angle 243.43$$

$$= 50 + j100 = 111.8 \angle 63.43$$

Now, the value of reflected reactance into the primary = j100 which is inductive.

(33) and (34) For reference, hence,

7.33

$$R_1 = 3.3\Omega \quad R_2 = 0.094 \text{ H}$$

$$L_1 = 0.094 \text{ H} \quad X_L = \omega L = 35.4$$

$$C_1 = 83 \times 10^{-6} \text{ f} \quad X_C = \frac{1}{\omega C} = 31.95$$

So, $Z_1 = 3.3 + 35.1j - 31.95j$
 $= 33 + 3.44j$

$Z_2 = 0.775 + j4.07$

$Z_M = jM \mid Z = 14.5 + j21.2$

$$Z_{e1} = Z_1 - \frac{Z_M^2}{Z_2 + Z} = 3.3 + 3.44j + \frac{M^2}{15.28 + j25.3}$$

$$= 3.3 + 3.44j + M^2(0.0175 - 0.03j)$$

$$= 3.3 + 3.44j + M^2 \times 0.0175 - M^2 \times 0.03j$$

$$= (3.3 + M^2 \times 0.0175) + j(3.44 - M^2 \times 0.03)$$

$$= \sqrt{(3.3 + M^2 \times 0.0175)^2 + (3.44 - M^2 \times 0.03)^2}$$

$$\tan^{-1} \frac{3.44 - M^2 \times 0.03}{3.3 + M^2 \times 0.0175}$$

So, $\frac{3.44 - M^2 \times 0.03}{3.3 + M^2 \times 0.0175} = 0$


$$\frac{3.44}{0.03} = M^2$$

So $M = 10.708 \mid$ Here $M = \omega m'$

So, $M' = \frac{10.708}{377} = 0.0284 \text{ H}$

7.34 Do yourself

7.35

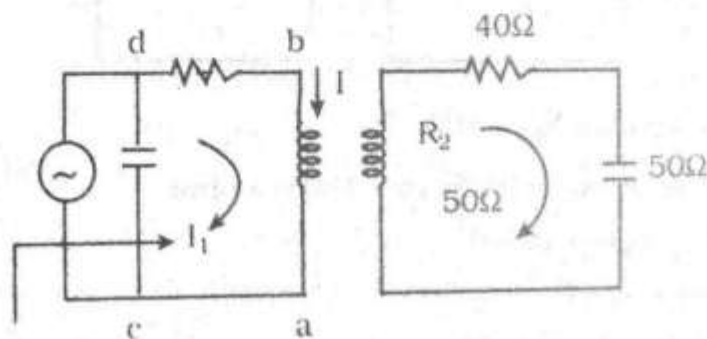

150 The Solution of Alternating Current Circuits

Let the capacitive reactance of c_{11} be X .

$$\begin{aligned} \text{Now, } Z_{cabd} &= Z_1 - \frac{Z_M^2}{Z_2} = 10 + j10 - \frac{(j20)^2}{10 + j50 - j50} \\ &= 10 + j10 + 10 \\ &= 20 + j10 = 22.36 \angle 20.57^\circ \end{aligned}$$

$$\begin{aligned} \text{Now, } Z_{01} &= \frac{(-jX)Z_{cabd}}{-jX + Z_{cabd}} = \frac{(X \angle -90^\circ)(22.36 \angle 20.57^\circ)}{-jX + 20 + j10} \\ &= \frac{22.36 x \angle -63.43}{\sqrt{20^2 + (10-x)^2} \tan^{-1} \frac{10-x}{20}} \\ &= \frac{22.36x}{\sqrt{20^2 + (10-x)^2}} \times \angle -63.43 - \tan^{-1} \frac{10-x}{20} \end{aligned}$$

For pure resistance phase angle will zero


$$\therefore \tan^{-1} = \frac{10-x}{20} = -63.43 \text{ or, } \frac{10-x}{20} = \tan(-63.43)$$

$$\therefore x = 50 \text{ ohm}$$

\therefore The value of the pure resistance

$$= \frac{22.36 \times 50}{\sqrt{20^2 + (10-50)^2}} = 25 \text{ ohm}$$

7.36

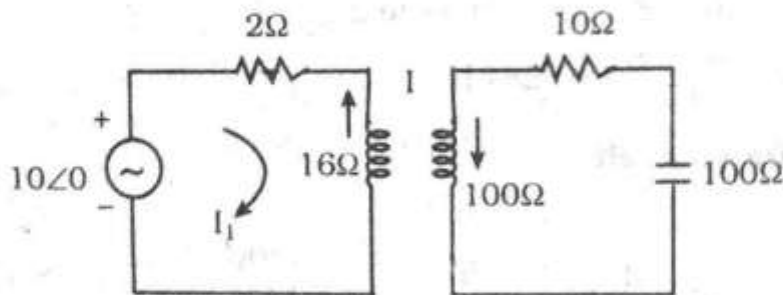

$$X_{L1} = 16 \text{ ohm } X_{L2} = 100$$

$$X_M = K\sqrt{X_{L1}X_{L2}} = 0.05\sqrt{16 \times 100} = 2 \text{ ohm}$$

$$\text{Now, } Z_1 I_1 + Z_M I_2 = 10 \angle 0^\circ$$

$$Z_M I_1 + Z_2 I_2 = 0$$

$$\begin{aligned} \therefore I_2 &= \frac{\begin{vmatrix} Z_1 & 10 \angle 0 \\ Z_M & 0 \end{vmatrix}}{\begin{vmatrix} Z_1 & Z_M \\ Z_M & Z_2 \end{vmatrix}} \\ &= \frac{-Z_M (10 \angle 0)}{Z_1 Z_2 - Z_M^2} = \frac{-j2(10)}{(2 + j16)(10 + j100 - j100 - (2j)^2)} \\ &= 0.1236 \angle -171.47^\circ \text{ A} \end{aligned}$$

$$\therefore V_{c2} = X_{c2} \times I_2 = 100 \times 0.1236 = 12.36 \text{ volt}$$

(b) At resonance, the impedance of CKt - 1 will be,

$$Z_1 = 2 + j16 - j16 = 2 \text{ ohm}$$

$$\therefore I_1 = \frac{-j(2 \times 10)}{2 \times 10 - (2j)^2} = \frac{20 \angle -90^\circ}{24} = 0.833 \angle -90^\circ$$

$$\therefore V_{c22} = 100 \times 0.833 = 83.3 \text{ Volt}$$

(c) At resonance the equation are

$$ZI_1 + Z_M I_2 = 10$$

$$\text{and } Z_M I_1 + 10 I_2 = 0$$

$$\begin{aligned} I_2 &= \frac{\begin{vmatrix} Z & 10 \\ Z_M & 0 \end{vmatrix}}{\begin{vmatrix} Z & Z_M \\ Z_M & 0 \end{vmatrix}} \\ &= \frac{-10 Z_M}{20 - Z_M} = \frac{-10 \times Z_M \angle 90^\circ}{20 - (X_M \angle 90^\circ)} = \frac{-10 X_M \angle 90^\circ}{20 + X_M} \end{aligned}$$

$$\begin{aligned} \therefore V_{c22} &= (100 \angle -90^\circ) \left(\frac{-10 X_M \angle 90^\circ}{20 + X_M} \right) = \frac{-1000 X_M}{20 + X_M} \\ &= \frac{-1000}{\frac{20}{X_M} + X_M} = \frac{-1000}{0} \end{aligned}$$

$$\text{When denominator } D = \frac{20}{X_M} + X_M$$


V_{c22} will be maximum it's D will be minimum

$$\therefore \frac{dD}{dX_M} = -\frac{20}{X_M^2} + 1 = 0$$

$$\text{or, } X_M^2 = 20 \text{ or, } X_M = \sqrt{20} = 4.472 \text{ ohm}$$

$$\therefore X_{c22} = \frac{1000 \times 4.472}{20 + 20} = 111.8 \text{ Volt}$$

37.

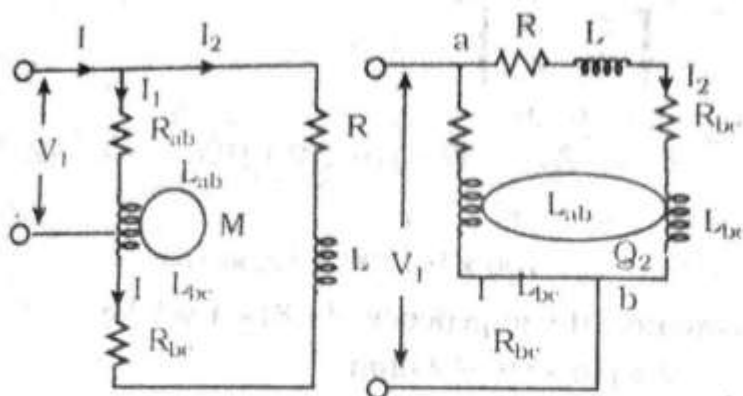

Here M will be negative

∴ The general differential equations are—

$$R_{ab}i_1 + L_{ab}\frac{di_1}{dt} - M\frac{di_2}{dt} = V_1$$

$$= V_1 (R + R_{bc}) i_2 + (L + L_{bc}) \frac{di_2}{dt} - M\frac{di_1}{dt} = V_1$$

7.38 Let

$$Z_{ab} = R_{ab} + j\omega L_{ab}$$

$$Z_{bc} = R_{bc} + j\omega L_{bc}$$

$$Z = R + j\omega L$$

$$Z_M = j\omega M$$

Now the equations become—

$$Z_{ab}i_1 - Z_M i_2 = V_1$$

$$-Z_M i_1 + (Z_{bc} + Z) i_2 = V_1$$

$$\therefore i_1 = \frac{\begin{vmatrix} V_1 & -Z_M \\ V_1 & Z_{bc} + Z \end{vmatrix}}{\begin{vmatrix} Z_{ab} & -Z_M \\ -Z_M & Z_{bc} + Z \end{vmatrix}} = \frac{V_1 (Z_{bc} + Z + Z_M)}{Z_{ab} (Z_{bc} + Z) - Z_M^2}$$

$$\therefore i_2 = \frac{\begin{vmatrix} Z_{ab} & V_1 \\ Z_M & V_1 \end{vmatrix}}{\begin{vmatrix} Z_{ab} & -Z_M \\ -Z_M & Z_{bc} + Z \end{vmatrix}} = \frac{V_1 (Z_{ab} + Z_M)}{Z_{ab} (Z_{bc} + Z) - Z_M^2}$$

7.39

$$Z_{ab} = 4 + j377 \times 0.07 = 4 + j26.39$$

$$= 26.69 \angle 81.38 \text{ ohm}$$

$$Z_{bc} = 0.5 + j377 \times 0.01 = 0.5 + j3.77 = 3.8 \angle 82.45^\circ \text{ ohm}$$

$$Z = 10 + j0 = 10 \text{ ohm}$$

$$Z_M = j377 \times 0.02 = 7.54 \angle 90^\circ \text{ ohm}$$

$$I_1 = \frac{(100 \angle 0) (0.5 + j3.77 + 10 + j7.5)}{(26.8 \angle 81.38) (0.5 + j3.77 + 10) - (j7.54)^2}$$

$$I_2 = \frac{(100 \angle 0) (4 + j26.39 + j7.54)}{292.16 \angle 90.12}$$

$$= \frac{2316.5 \angle 83.28}{292.16 \angle 90.12} = 1169 \angle -6.84 \text{ ohm}$$

$$I = I_1 + I_2 = 5.28 \angle -43 + 1169 \angle -6.89$$

$$= 16.25 \angle -17.9 \text{ ohm}$$

$$\therefore \text{Total power supplied} = V_1 I \cos 417.9 = 1545.9 \text{ watts}$$

$$\text{Power dissipated in circuit 1} = I_1^2 R_{ab} = 111.5 \text{ watts}$$


$$2 = I_2^2 (R_{bc} + R) = 11.69^2 \times$$

$$(0.5 + 10) = 1443.9 \text{ watts}$$

40, 41, 42, 43, 44, 45 are out of syllabus, it will be studied in higher level and term.

Chapter-8 Balanced Polyphase Circuits

8.1

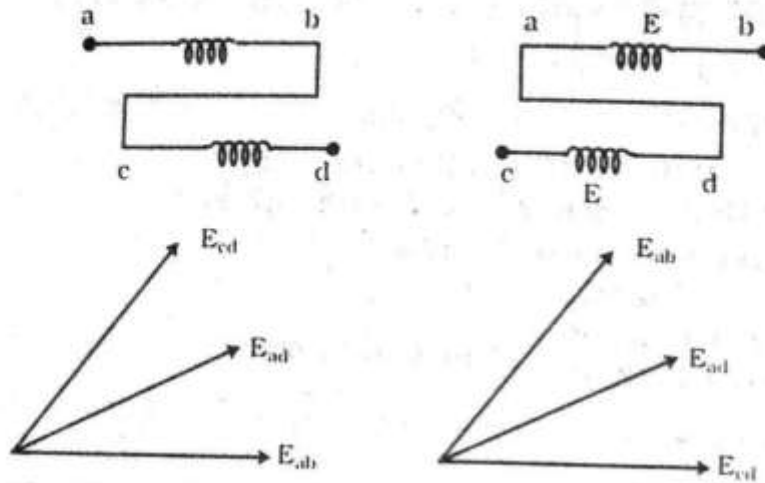



$$E_{ac} = E^2 + 2^2 + 2E^2 \cos 60^\circ = 2E^2 (1 + \cos 60^\circ) = 2E^2 \cdot 2 \cos^2 30^\circ$$

$$E_{cb} = 2E \cos 30^\circ = 1.732 E$$

$$E_{ab} = 2E \cos 30^\circ = 1.732 E$$

$$\therefore E_{ad} = E_{cd}$$


8.2

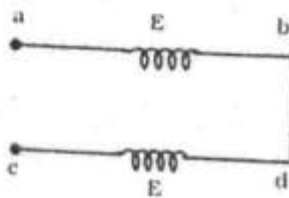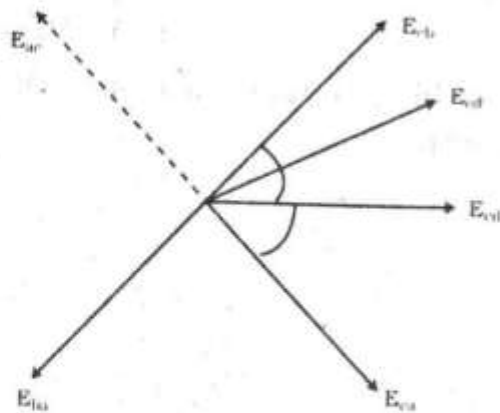

(a) $\bar{E}_{ca} = \bar{E}_{cd} + \bar{E}_{bc} = E_{cd} - E_{ab} = 120 \angle 0 - 120 \angle 60^\circ$
 $= 120 + j0 - 60 - j103.923 = 60 - j103.923 = 120 \angle -60^\circ$

(b) $E_{ac} = E_{ab} + E_{dc} = E_{ab} - E_{cd}$
 $= 120 \angle 60^\circ - 120 \angle 0^\circ = 60 + j103.923 - 120$
 $= -60 + j103.923 = 120 \angle 120^\circ$


8.3

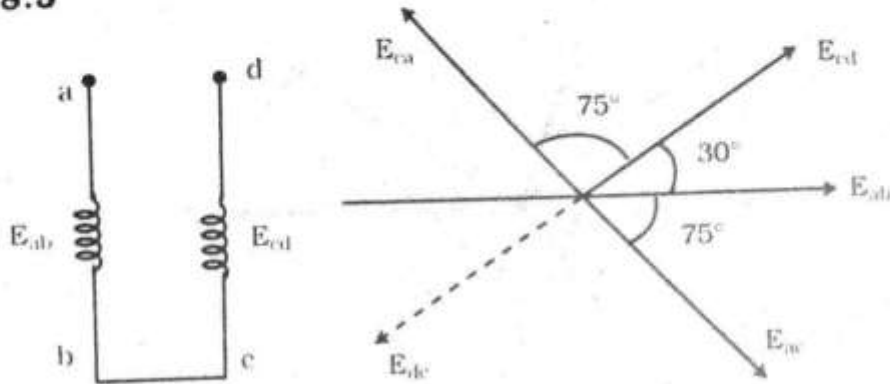

$\bar{E}_{ac} = \bar{E}_{ab} + \bar{E}_{dc} = 100 \angle 0 + 100 \angle -150^\circ$
 $= 100 + j0 + 86.6 - j50$
 $= 13.397 - j50$
 $= 51.76 \angle -75^\circ$

$\bar{E}_{am} = 51.76 \angle 105^\circ$

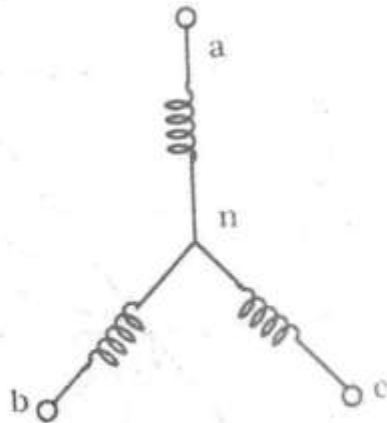8.4 From oscillogram 1, phase sequence : a - b - c



$V_{ab/\max} = 141 \text{ volts} = \sqrt{3} \text{ (max. voltage per phase)}$

$V_m = \frac{141}{\sqrt{3}} = 81.406 \text{ Volts}$


$V_m = 81.406 \text{ Volts (magnitude)}$

$$\therefore V_{rms} = \frac{V_m}{\sqrt{2}} = 57.6 \text{ Volts}$$

$$V_{ab} = V_{bn} - V_{an} = 57.6 \text{ Volts (magnitude only)}$$

Phase voltage sequence : an - bn - cn

8.5

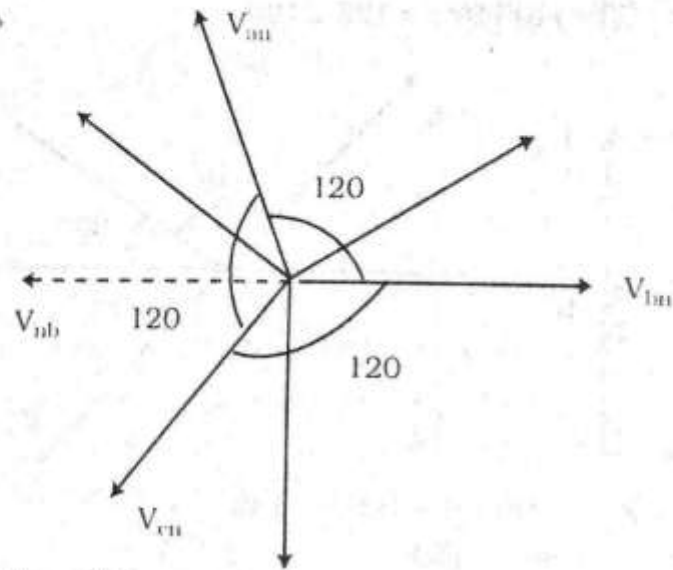

8.6 $n = 6$, $I_p = 100$ amp

$$I_1 = 2I_p \sin \frac{180^\circ}{n} = 2 \times 100 \times \sin \frac{180}{6} = 100 \text{ amp}$$


$\therefore I_p = I_1 = 100$ amp

8.7

$$E_{ab} = E_{an} + E_{nb}$$

$\therefore 1 \text{ cm} = 50$ volts


$$E_L = 25.61 \text{ volts}$$

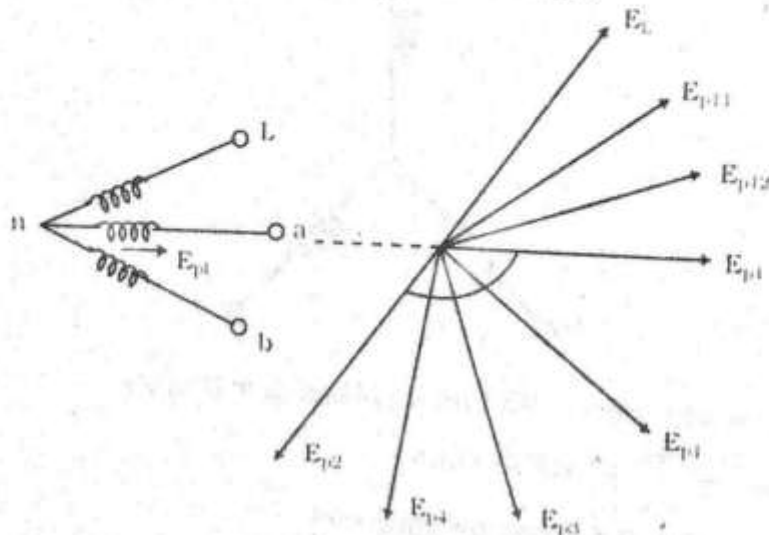

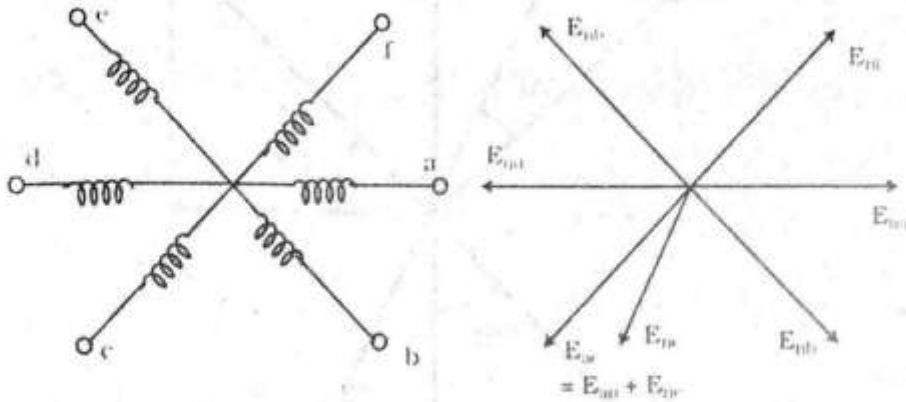2.1 cm = 25.61 volts

$$E_{L_1} = 2 \times 50 \times \sin \frac{180}{12} = 25.08 \text{ volts}$$

$$B_{ab} = 25.61 \angle -105 \text{ volts}$$



$$E_{na} = E_{nb} = E_{nc} = E_{nd} = E_{ne} = E_{nf} = E_p = 132.8 \text{ volts}$$

1 cm = 33.2 volts

$$\frac{360}{6} = 60$$

$E_{av} = 6.9 \text{ cm} = 230 \text{ volts}$

$$\begin{aligned} E_{av} &= 2E_p \sin \frac{360}{11} \\ &= 2 \times 132.8 \times \sin \frac{360}{6} \\ &= 230 \text{ volts} \end{aligned}$$

$$V_L = 2300 \text{ V}, V_p = 2300/\sqrt{3} = 1327.9 \text{ Volts}$$


$$Z_p = 100 + j173.2 = 200 \angle 60^\circ$$


$$\therefore I_p = \frac{1327.9}{200 \angle 60} = 6.634 \angle -60^\circ \text{ amp}$$

$$I_L = 6.64 \text{ amp}$$

$$\text{Power phase} = (6.64)^2 \times 100 = 5.5 \text{ Kw}$$
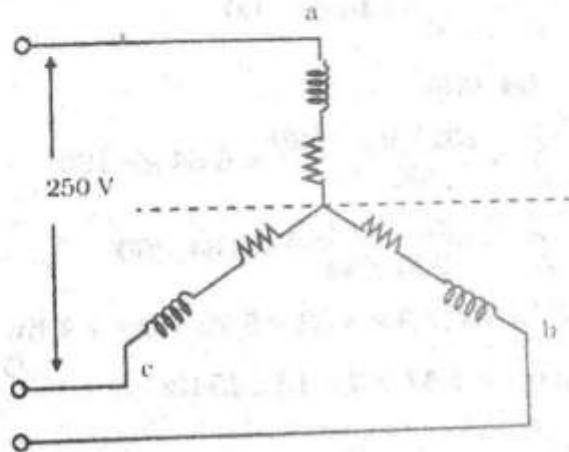
$$P_t = 3 \times P_{\text{phase}} = 3 \times 4.4 = 13.22 \text{ Kw}$$



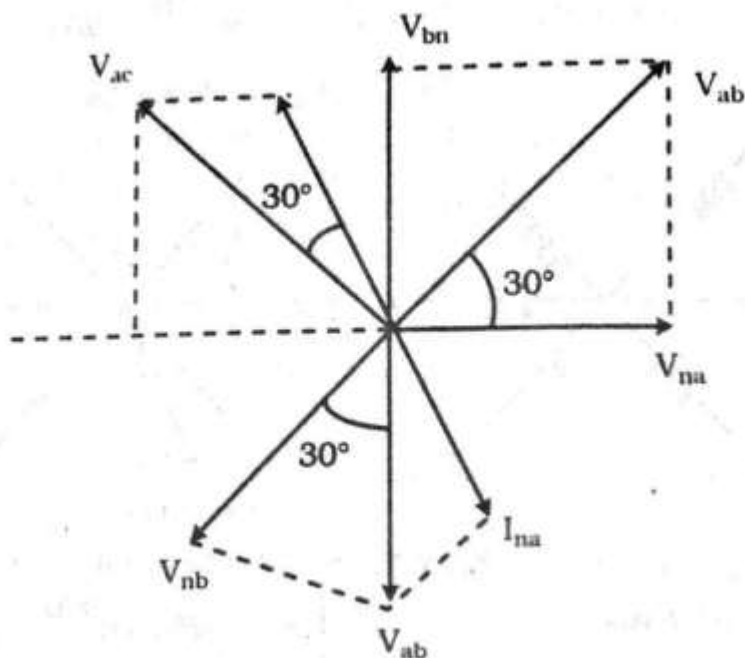

By vector—

$$V_{na} = 1327.7 \angle 0 = 1327.9 + j0$$

$$V_{nb} = 1327.9 \angle -120 = 663.96 - j1150$$

$$V_{nc} = 1327.9 \angle +120 = -669 + j1150$$

$$\begin{aligned} V_{ba} &= V_{bn} + V_{na} = -V_{nb} + V_{na} \\ &= +603.96 + 1150 + 1327.9 + j0 \\ &= 1991.87 + j1150 = 2300 \angle 30^\circ \end{aligned}$$

$$I_{an} = \frac{V_{na}}{Z_{na}} = \frac{1327.9 \angle 0}{100 \angle 60^\circ} = 46.64 \angle 60^\circ$$

$$I_1 = I_{na} = 6.64 \text{ amp}$$


$$I_L = I_{nb} = \frac{V_{nb}}{Z} = \frac{1327.9 \angle -120}{200 \angle 60^\circ} = 6.64 \angle -180^\circ$$

$$I_L = I_{nc} = \frac{V_{nc}}{Z} = \frac{1327.9 \angle 120}{200 \angle 60^\circ} = 6.64 \angle 60^\circ$$

$$P_{na} = VI + V'I' = 1327.9 \times 3.32 + 5.75 \times 0 = 4.4 \text{ Kw}$$

$$\therefore \text{Total power} = 4.41 \times 3 = 13.225 \text{ Kw}$$

8.10

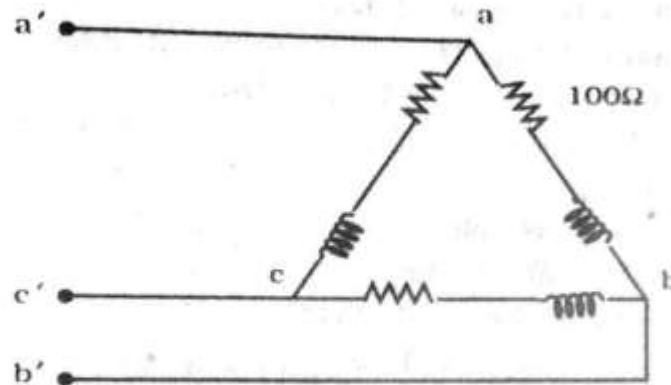

$$V_{ba} = 2300 \angle 0$$

$$V_{cb} = 2300 \angle -120$$

$$= 1150 - j1991.80$$

$$V_{ac} = 2300 \angle -240$$

$$= 1156 + j1991.8$$

$$I_{ba} = \frac{2300 \angle 0^\circ}{200 \angle 60} = 11.5 \angle -60 = 5.75 - j9.96$$

$$I_{ab} = \frac{V_{ab}}{Z} = \frac{2300 \angle -120}{200 \angle 60} = 11.5 \angle -180 = -11.5$$

$$I_{ac} = \frac{2300 \angle -240}{200 \angle 60} = 11.5 \angle -300 = 5.75 + j9.96$$


$$\therefore |I_p| = 11.44, I_L = \sqrt{3} \times 11.5 = 19.92 \text{ amp}$$

$$I_{b'b} = I_{bc} + I_{ba} = -I_{cb} + I_{ba} = 11.5 - j0 + 5.75 - j9.96$$

$$= 19.92 \angle -30^\circ \text{ amp}$$

$$I_{a'a} = I_{cb} + I_{ca} = I_{cb} - I_{ac} = -11.5 + j6 - 5.75 - j9.96$$

$$= -17.25 - j9.9 = 19.92 \angle -150$$

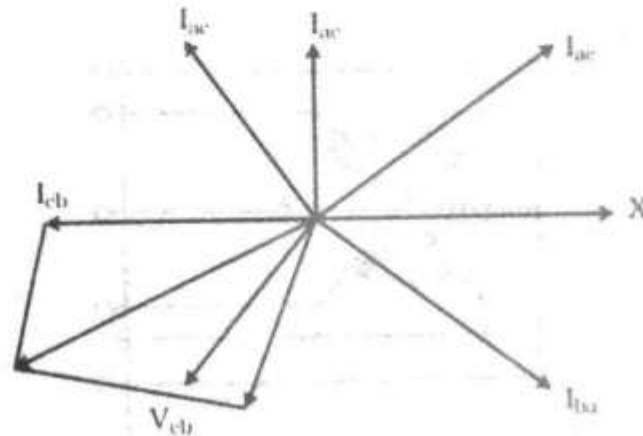

$$P_{ba} = |V_{ba}| |I_{ba}| \cos (\theta_2 - \theta_1)$$

$$= 2300 \times 11.5 \cos (0 - (-60))$$

$$= 2300 \times 11.5 \cos 60^\circ = 13225 \text{ watt} = 13.23 \text{ Kw}$$

$$P_i \text{ of three phase} = 13.23 \times 3 = 39.69 \text{ Kw}$$

8.11


$$VA_p = V_p I_p$$

$$V_L = 440 \angle 0^\circ \text{ volt}$$

$$\text{let } V_{ab} = 440 \angle 0 \text{ volts}$$

$$Z_p = 8 + j6 \text{ ohms} = 10 \angle 36.87^\circ$$
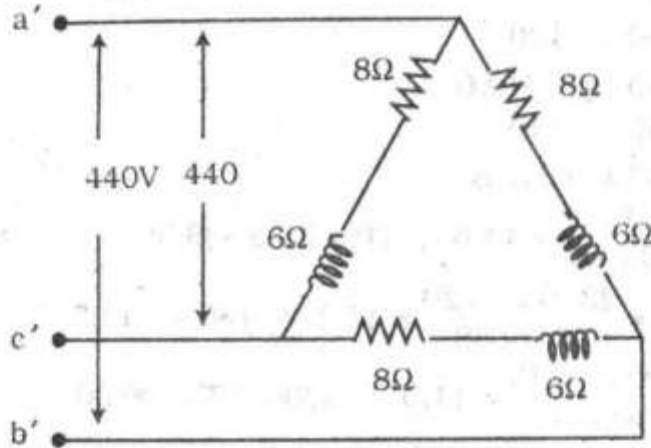
$$\therefore I_p = I_{ab} = \frac{V_{ab}}{Z_{ab}} = \frac{440 \angle 0}{10 \angle 36.87} = 44 \angle -36.87^\circ$$




$$VA_p = 440 \times 44 = 19360 \text{ r.f} = \sin \theta_p = \sin 36.87 = 0.6$$

$$rVA_p = 440 \times 44 \times 0.6 = 11616$$

$$VA_t = VA_p = 58080, \text{ vV}_{at} = rVA_t = 3 \times 11616 = 34848$$

r.f of the system remains the same.

8.14

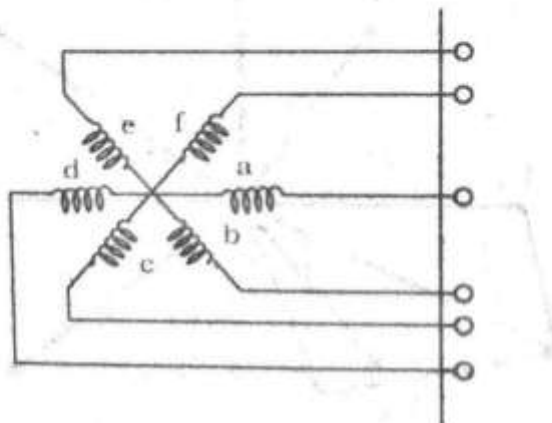

$$V_{an} + V_{nb} = 156 \text{ volts}$$

$$2V_p = 156 \text{ volts}$$

$$V = 78 \text{ volts}$$

$$V_L = 2V_p \times \sin \frac{180^\circ}{n}$$

$$= 2 \times 78 \sin 30 = 70 \text{ volts}$$

8.15

$$E_L = 2E_p \sin \frac{180}{n} \text{ or, } 100 = 2E_p \sin \frac{180}{12}$$

$$E_p = \frac{100}{2 \times \sin \frac{180}{12}} = 193.18 \text{ volts}$$

$$E_E = 2E_p \sin \frac{360}{11} = 2 \times 193 \sin \frac{180}{6} = 193.185$$

$$\text{Greatest voltage} = 2E_p = 2 \times 193.18 = 386.37 \text{ volts}$$

8.16

$$I_L = 2I_p \sin \frac{180}{n}$$

$$10 = 2I_p \sin \frac{180}{6}$$

$$\therefore I_p = 10$$

$$I_L = 2I_p \sin \frac{180}{12}$$

$$10 = 2 \times I_p \sin 15^\circ$$


$$\therefore I_p = 19.3 \text{ amp}$$

8.21

$$Z_p = 16 + j12 = 20 \angle 36.87^\circ$$

$$V_p = \frac{V_L}{\sqrt{3}} = \frac{230}{\sqrt{3}} = 132.73 \text{ volts}$$
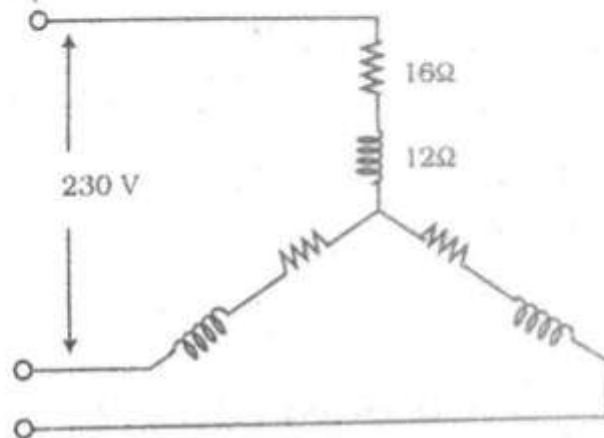
$$\therefore I_p = \frac{V_p}{Z_p} = \frac{230}{20 \angle 30.87}$$




For balanced wye load,

$$I_L = I_p = 6.64 \angle -36.87^\circ \text{ A}$$

Total power,
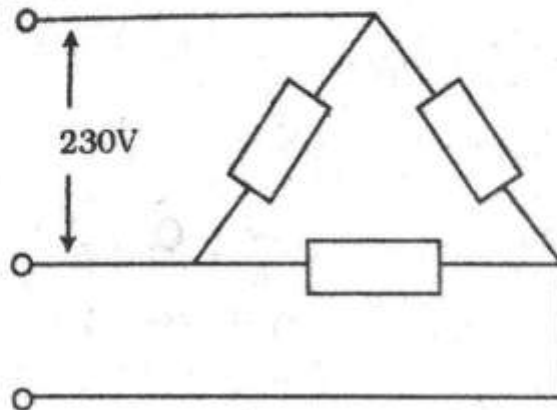
$$P_t = 3 V_p I_p \cos \theta_p \\ = 2116.14 \text{ watts}$$



For Delta Connection :

Here,

$$V_L = V_p = 230 \text{ V}$$

$$I_p = \frac{V_p}{Z_p} = \frac{230}{20 \angle 30.87^\circ}$$

$$\therefore I_L = \sqrt{3} I_p = \frac{230}{\sqrt{3}} \times 11.5 = 19.9 \text{ A}$$

$$P_t = \sqrt{3} V_L I_L \cos \theta_p = 6348.44 \text{ watts}$$

8.22

$$I_L = 2 I_p \sin \frac{180}{n} \cdot 10 = 2 \times I_p \sin \frac{180}{12}$$


$$I_p = 19.32 \text{ amp}$$

$$E_L = E_p = I_p Z_p = 19.32 \times 9.43 \angle -58^\circ \\ = 182.18 \angle -58 \text{ volt}$$

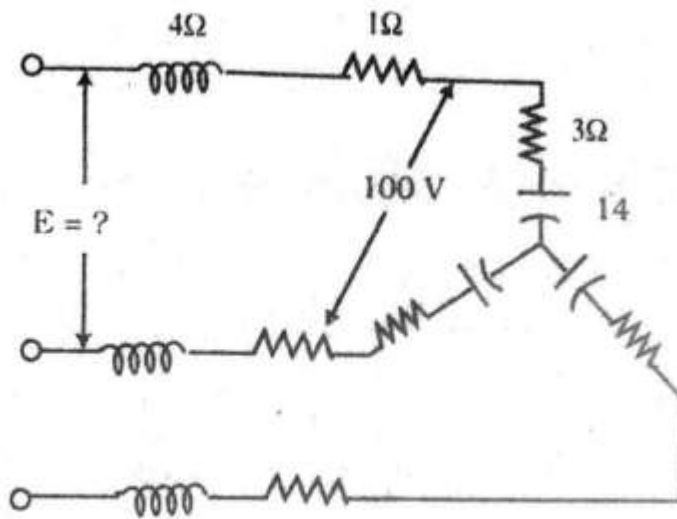8.23

$$V_L = 100 \text{ V}$$

$$I_p = \frac{V_p}{Z_p} = \frac{57.735}{\sqrt{3^2 + 4^2}} = 11.547 \text{ amp}$$



Now,

$$E_p = I_p (j4 + 1 + 3 - j4) = 11.547 \times 4 = 46.108 \text{ volts}$$


$$\therefore E_L = \sqrt{3}E_p = 80 \text{ volts}$$

8.24

Sending voltage $E_L = 250 \text{ V}$

$$\therefore E_p = \frac{250}{\sqrt{3}} = 144.39 \text{ Volt}$$
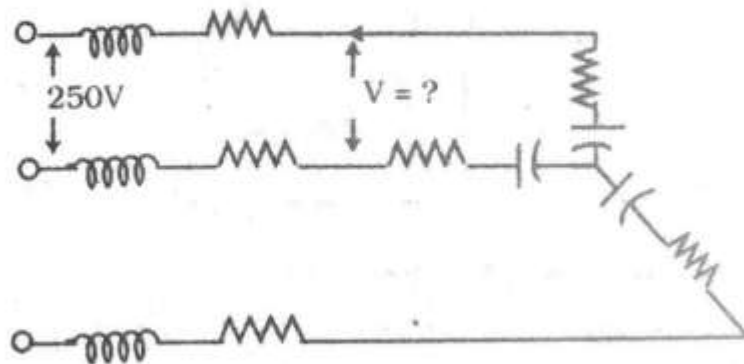
$$\therefore I_p = \frac{E_p}{1 + j2 + 8 + j6} = \frac{144.39}{12.042 \angle 41.63^\circ} = 11 \angle -41.63^\circ$$



$$\therefore V_p = I_p(8 + j6) = (12 \angle -41.63^\circ)(10 \angle 36.87^\circ) = 120 \angle -4.76^\circ$$

$$V_L = \sqrt{3}V_p = 207.85 \text{ volt}$$


8.25

Here,

$$V_p = V_l = 115 \text{ V}$$

$$\therefore I_p = \frac{V_p}{Z_p} = \frac{115}{12 - j16} = 5.73 \angle 53.13^\circ$$

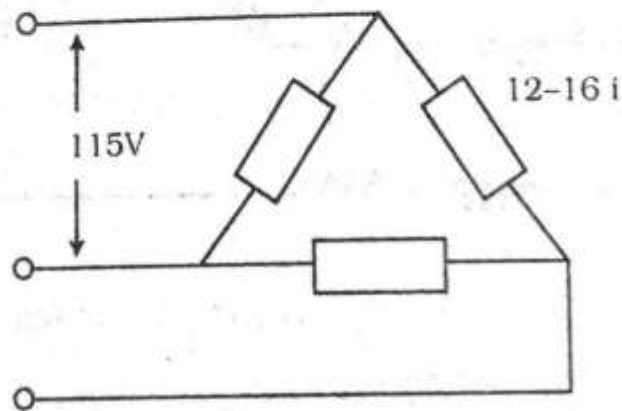
$$\therefore I_l = \sqrt{3}I_p = 9.96 \angle 53.13^\circ$$



$$Z_{\text{perphase}} = 12 - j16 = 20 \angle -53.13^\circ$$

$$V_p = 115 \text{ volt}$$

$$|I_p| = \frac{115}{20} = 5.75 \text{ amp}$$

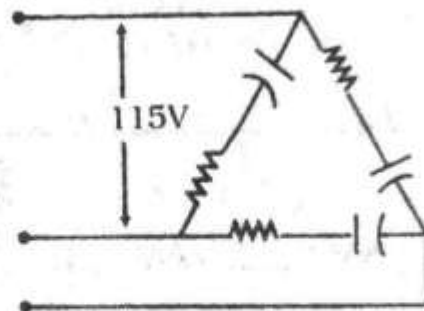

$$V_{ab} = 115 \angle 0^\circ, V_{bc} = 115 \angle -120^\circ$$


$$V_{ca} = 115 \angle -240^\circ$$

$$I_{ab} = \frac{V_{ab} \angle 0^\circ}{Z} = \frac{115 \angle 0^\circ}{20 \angle -53.13^\circ} = 5.75 \angle 53.13^\circ = 3.45 + j4$$

$$I_{bc} = \frac{V_{bc} \angle -120^\circ}{Z} = \frac{115 \angle -120^\circ}{20 \angle -53.13^\circ} = 5.75 \angle -66.87^\circ = 2.26 - j5.29$$

$$\begin{aligned}
 I_{ca} &= V_{bc} \angle -120/Z \\
 &= 115 \angle +120/20 \angle -53.13 \\
 &= 5.75 \angle -186.87 \\
 &= 5.71 + j0.68 \\
 I_{a'a} &= I_{ab} + I_{ac} = I_{ab} - I_{ca} = 3.45 + j4.6 + j5.71 - j0.69 \\
 &= 9.16 + j3.91 = 9.96 \angle 23.41 \\
 I_{b'b} &= I_{ba} + I_{bc} = I_{bc} - I_{ab} = 2.26 - j5.29 - 3.45 + j4.6 \\
 &= 1.19 - j9.89 = 9.96 \angle -96.93 \\
 I_{c'c} &= I_{ca} + I_{cb} = I_{ca} - I_{bc} = -5.71 + j0.69 - 2.26 + j5.29 \\
 &= -7.97 + j5 + j5.98 = 9.96 \angle 113.118 \\
 \therefore \text{Line to line } (I_{line}) &= 9.95 \text{ amp}
 \end{aligned}$$

8.26

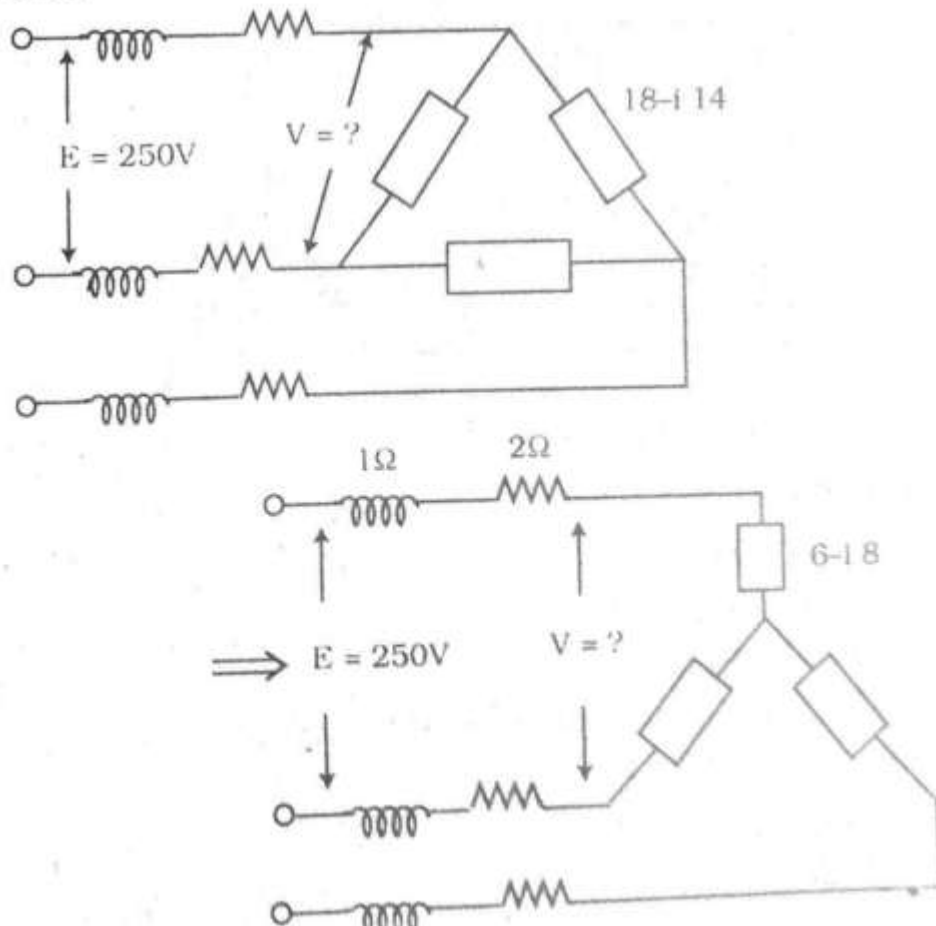

Equivalent wye of delta load.

$$Z_p = \frac{18 - j24}{3} = 6 - j8 \text{ ohm}$$

Now, $E_p = \frac{F_L}{\sqrt{3}} = \frac{250}{\sqrt{3}} = 144.34 \text{ volts}$

$$\therefore I_p = \frac{E_p}{Z_p} = \frac{144.34}{1 + j2 + 6j8} = 15.656 \angle 40.6^\circ$$

$$\therefore V_p = I_p(6 - j8) = 156.56 \angle -12.53^\circ$$


$$V_L = \sqrt{3}V_p = 271.17 \angle -12.53^\circ$$

Total power consumed = $3I_p^2 R_p = 3(15.656)^2 \times 6 = 4412 \text{ watts}$

Again $P_t = 3V_p I_p \cos \theta_p$

$$= 3 \times 156.56 \times 15.656 \times \cos \{40.6 - (-12.83)\} = 4412 \text{ watts}$$

8.27

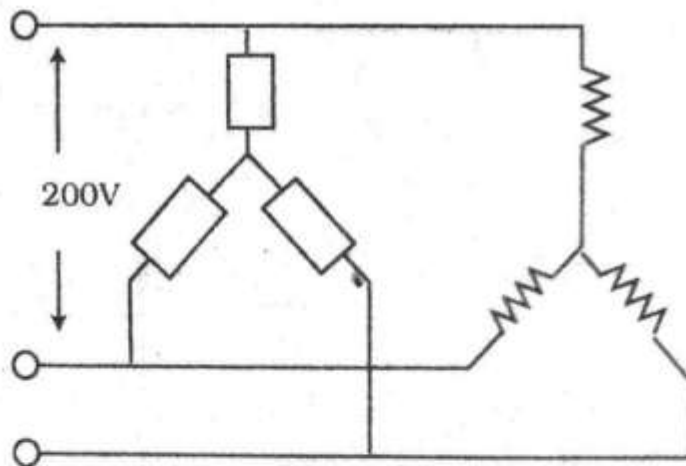

1st Method :

For balanced inductive load, $p = \sqrt{3} V_L I_L \cos \theta_p$

or, $5.4 \times 10^3 = \sqrt{3} \times 200 \times I_3 \times 0.6$

$$\therefore I_{L1} = 25.98 \text{ amp}$$

Since p.f is 0.6 and the load is inductive.

$$\therefore I_{L1} = 25.98 \angle -53.13^\circ$$

$$\therefore \cos \theta = 0.6$$

$$\theta = 63.13$$

For balanced resistive load, $p = \sqrt{3}V_L I_L \cos \phi$

$$\text{or, } 5 \times 10^3 = \sqrt{3} \times 200 \times I_L^2 \times 1$$

Since the load is resistive

$$\therefore I_{L2} = 14.43 \angle 0^\circ$$

$$\therefore \text{Resultant current} = 25.98 \angle 53.13 + 14.43 \angle 0$$

$$= 15.588 - j20.784 + 14.43$$

$$= 36.5 \angle -34.7^\circ$$

$$I_L = 10 \angle 36.87$$

$$\therefore \text{Line drop per phase } V_p = 10 \angle 36.87 (1 + j5)$$

$$= 51 \angle 115.56^\circ$$

$$\therefore V_{line} = \sqrt{3} \times 51 \angle 115.56 = 88.33 \angle 115.56^\circ$$

$$\therefore \text{Voltage at the load terminal is } -230 \angle 0 - 88.33 \angle 115.56$$

$$= 238 + 38.11 - j79.69 = 279.7 \angle -16.55 \text{ Ans.}$$

$$I_L = 14.484 \text{ amp}$$

Since it is star connection,

I_p is the same of I_L i.e., 14.484 amp

$$X_{cp} = \frac{V_p}{I_p} = \frac{132.8}{14.484} = 9.14 \text{ ohm}$$

$$V_p = \frac{V_L}{\sqrt{3}} = 230/\sqrt{3} = 132.8$$

$$\frac{1}{2\pi f c} = X_{cp} = 9.14$$

$$c = 289 \mu f$$

When p.f leading $\sqrt{3} X_L I_L = 11.55 \times 10^3$

$$\therefore I_L = \frac{11.55 \times 10^3}{\sqrt{3} \times 236} = 29 \text{ amp}$$

$$\therefore I_p = 29 \text{ amp}$$

$$X_{cp} = \frac{V_p}{I_p} = \frac{132.8}{29} = 4.58 \text{ ohm}$$

$$\frac{1}{2\pi f c} = 4.58$$

$$c = \frac{1}{\pi f \times 4.58} = 5.79 \times 10^{-7} = 579.11 \mu f$$

8.32.

For the load, $P = \sqrt{3}V_L I_L \cos \theta = 10 \times 0.5 = 5 \text{ Kw}$

$$\therefore P_X = 10 \sin \theta = 10 \times \sin 60^\circ = 8.66 \text{ K vars}$$

For capacitive bank $p = 0$

$$P_X = x \text{ (say)}$$

Since the p.f is reduced to 0.866 (lagging) from 0.5 (lagging)

$$\text{We have } = \tan (\cos^{-1} 0.866) = \frac{8.66 - x}{5}$$

$$\therefore x = 5.773 \text{ K vars}$$

8.33

When they are Delta connected and p.f is 0.866 lagging

$$P_X = \sqrt{3}V_L I_L \sin \theta_p$$

$$\text{or, } 5.773 \times 10^3 = \sqrt{3} \times 230 \times I_1 \times \sin (\cos^{-1} 0.866)$$

$$\therefore I_1 = 28.98 \therefore I_p = \frac{28.98}{\sqrt{3}}$$


$$\text{Now, } Z_p = \frac{V_p}{I_p} = \frac{230}{\frac{28.98}{\sqrt{3}}} = 13.746 \text{ ohm}$$

$$\therefore Z_p = \frac{1}{\omega c} \text{ or, } c = \frac{1}{\omega Z_p} = \frac{1}{2\pi \times 60 \times 19.746} = 193.4$$

For star

When p.f 0.866 load we got before line to line voltage

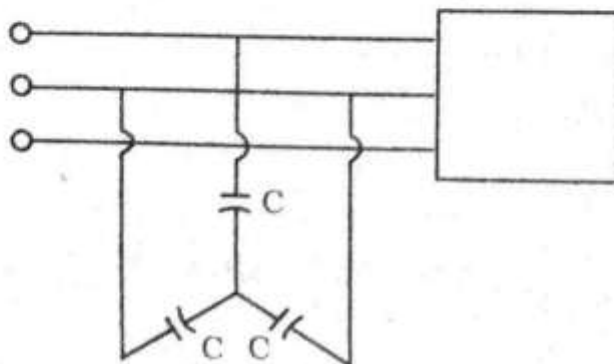
$$= \sqrt{3} \times 52 = 90.07 \text{ volts}$$



Power loss in the supply lines = $3I_L^2R_L = 3 \times (10.4)^2 \times 1$
 = 325 watt

Power dissipated in the load = $3 \times (10.4)^2 \times 2.5$
 = 812.76 watts

8.34

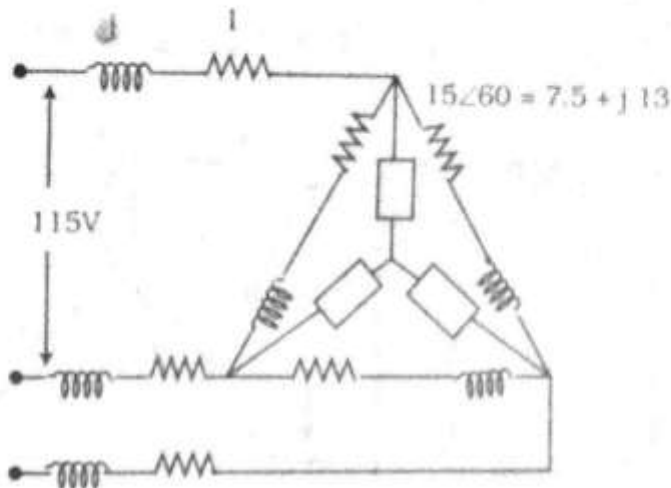


Converting to wye $Z_p = \frac{7.5 + j13}{3} = 2.5 + j4.33$

Now, current, $I_p = \frac{V_p}{Z_{rp}} = \frac{\frac{115}{\sqrt{3}}}{1 + j + 2.5 + j4.33} = 10.4 \angle -56.7^\circ$

Voltage across the load is, $V_p = (10.4 \angle -56.7^\circ)(2.5 + j4.33)$
 = $52 \angle 3.3^\circ$

8.35

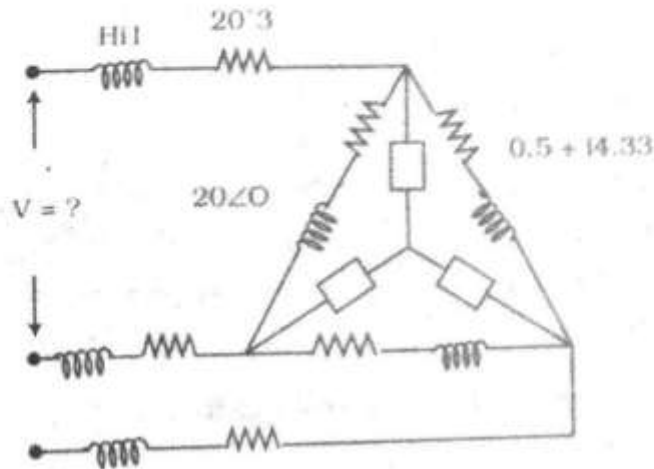

Phase current in delta = 20A


Line current in = $20\sqrt{3}$ A

\therefore Impedance in wye = $\frac{15 \angle 60}{3} = 5 \angle 60 = 2.5 + j4.33$


$\therefore V_p = I_p Z = 20\sqrt{3} (2.5 + j4.33 + 1 + j1)$
 $= 20\sqrt{3} \times 6.376 \angle 56.7$

$\therefore V_L = \sqrt{3} V_p = 20 \times \sqrt{3} \times 6.376 \angle 56.7 = 382.6 \angle 56.7$ volt

8.36

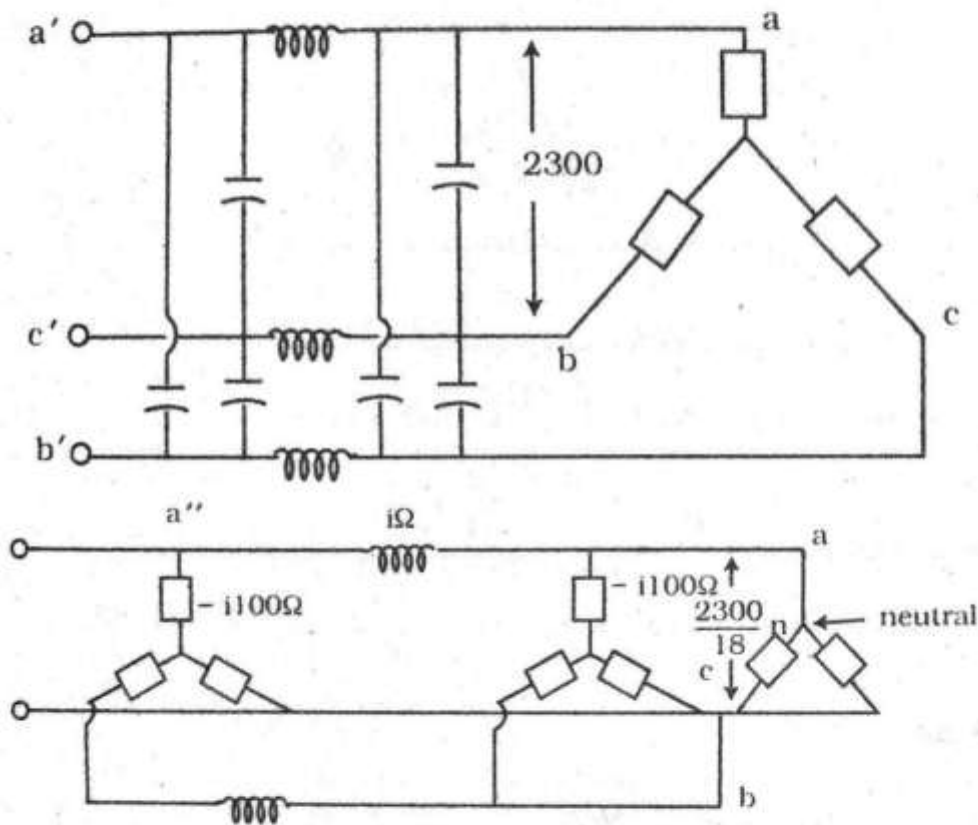

8.37

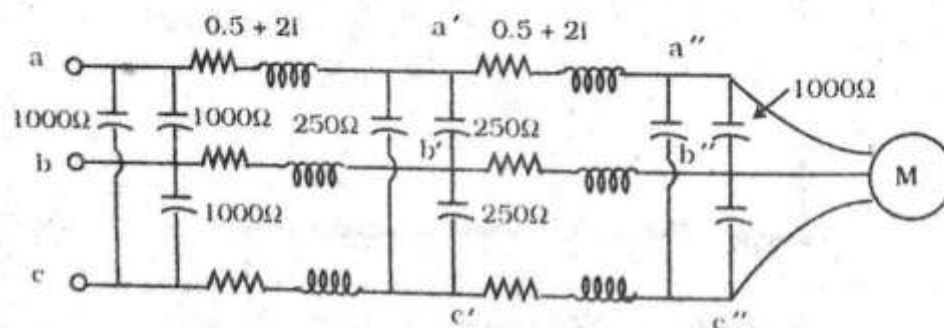

$$I_L = \frac{P_L}{\sqrt{3} V_L \cos\theta} = \frac{VA}{\sqrt{3} V_L} = \frac{120 \times 10^3}{\sqrt{3} \times 2300} = 30.122A$$

$$\begin{aligned} V_{a'n} &= V_{a'n} + (0.5 + 2j) (30.122 \angle 53.13) \\ &= 1327.91 + (0.5 + 2j) (30.122 \angle 53.13) \\ &= 1289.65 \angle 2.14168 \end{aligned}$$

$$\begin{aligned} V_{b'n} &= V_{b'n} + (2.06 \angle 75.96) (30.122 \angle (53.13 - 120)) \\ &= 1327.91 \angle -120^\circ + (2.06 \angle 75.96) (30.122 \angle (53.13 - 120)) \\ &= 1289.68 \angle -117.85 \end{aligned}$$

Similarly $V_{c'n} = 1289.68 \angle 122.14$

Again at a, b, c


$$\begin{aligned} V_{an} &= V_{a'n} + (0.5 + 2j) (30.122 \angle 53.13) \\ &= 1289.65 \angle 2.1418 + (0.5 + j) (30.122 \angle 53.13) \\ &= 1253.303 \angle 4.41 \end{aligned}$$

$V_{bn} = 1253.303 \angle -115.59$

Similarly, $V_{cn} = 1253.303 \angle 124.41$

8.38 Similar to 37 but take the voltage of a, b, c as input then subtract the voltage drop at $(0.5 + 2j)$

8.39

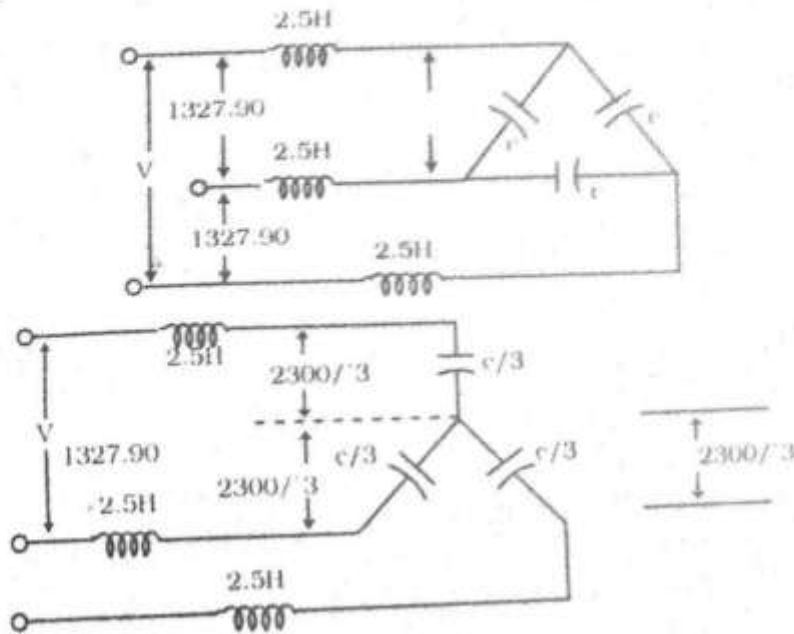

For resonance,

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$

$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi} \times \frac{1}{\sqrt{2.5 \times 10^{-3} \times 8.683 \times 10^{-6}}}$$

$$= 341.59 \text{ Hz}$$

$$V = \frac{2300}{\sqrt{3}}$$

$$I_L = I_{\text{phase}}$$

$$= \frac{10 \times 10^3}{2300/\sqrt{3} \times \sqrt{3}} = 4.347 \text{ A}$$

$$\therefore Z_1 = \frac{V}{I_L} = 305.476$$

As R_c is negligible.


$$X_c = 305.4$$

$$\frac{1}{\omega C} = 305.476$$

$$C = \frac{1}{\omega \times 305.476}$$

$$= 8.683 \mu\text{f}$$

8.40

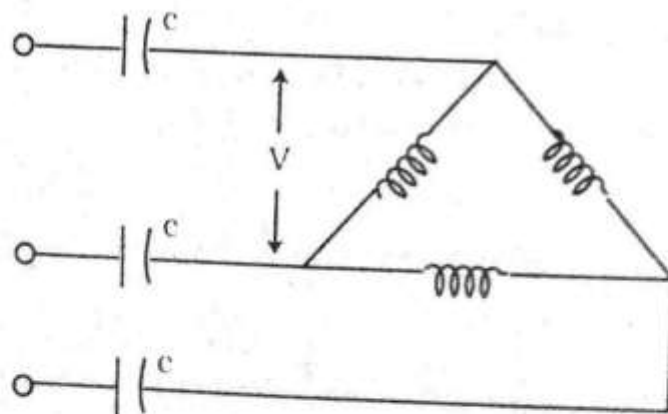

$$36 + (100 \times 2\pi \times 800 \times 10^{-3})j = 36 + 105.02j$$


As resonant frequency,

$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi} \times \frac{1}{\sqrt{100 \times 10^{-3} \times c}}$$

$$\frac{P_X}{W_p} = \sqrt{3}$$

8.41.

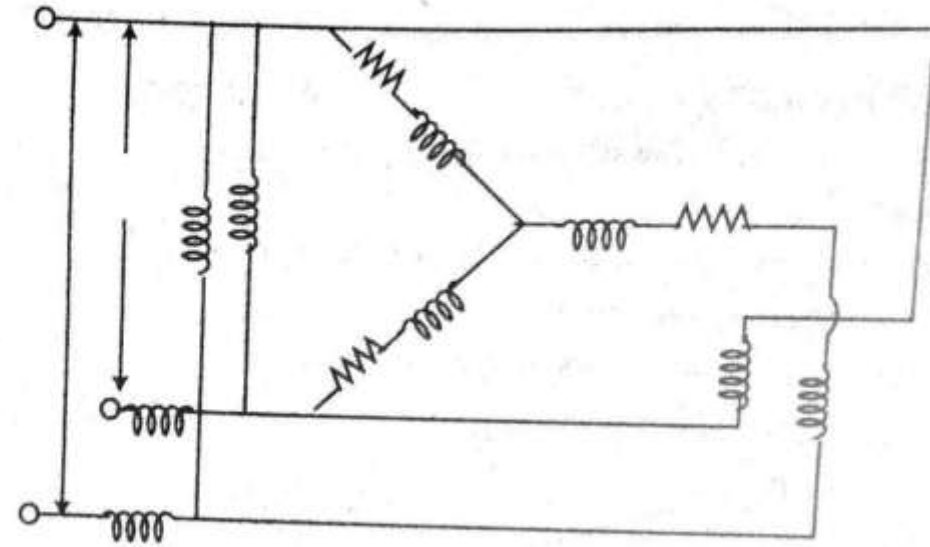

Phase sequence V_{ua}, V_{uc}, Y_{ub} (a, c, b) X_{ac}, V_{cb}, V_{ba}

$$V_{ua} = 100 \angle 0$$

$$V_{uc} = 100 \angle -120$$

$$V_{ba} = 100 \angle 120$$

$$\left. \begin{aligned} W_a &= V_{ac} I_{aa} \cos \theta \\ W_b &= V_{bc} I_{bb} \cos \theta \end{aligned} \right\} \begin{array}{l} I_{aa} \\ V_{ac} \\ I_{bb} \\ V_{bc} \end{array}$$

$$V_p = \frac{100}{\sqrt{3}} = 57.74 \text{ V}$$

$$V_{ua} = 57.74 \angle 0 \text{ vots}$$

$$V_{uc} = 57.74 \angle -120$$

$$V_{ub} = 57.74 \angle 120$$

$$\begin{aligned} V_{ac} &= V_{ua} + V_{uc} \\ &= V_{uc} - V_{ua} \\ &= 57.74 \angle -120^\circ - 57.74 \angle 0 \\ &= -28.87 - j50 - 57.74 \\ &= 100 \angle -150^\circ \end{aligned}$$

$$Z_p = 3 + j10 = 10.44 \angle 73.3^\circ$$

$$I_p = V_p / Z_p = 57.74 / 10.44 \angle 73.3 = 5.53 \angle -73.3$$

$$W_a = (100 \angle -150) \times (5.53) \cos (-103.3) = 127.22 \text{ watt}$$

$$W_b = 100 \times 5.53 \cos 43.3 = 402.46 \text{ watt}$$

$$\text{Power in each phase} = (W_a + W_b) / 3 = 1.75 \text{ watt}$$

8.42.

Power, $w_a + w_b = 5000$ reactive power $= \sqrt{3} (w_a - w_b) = 20,000$

or, $w_a - 5000 + w_a = 20000/\sqrt{3} \therefore w_a = 8273.5$ watt

$$w_b = -3273.5 \text{ watt}$$


8.43

The reading of W_R in $W_R = V_{cb} I_{na} \cos (V_{cb} I_{na})$

$$= V_L I_L \cos (90 - 73.3)$$

$$= V_L I_L \sin 73.3 = 100 \times 5.53 \sin 73.3$$

$$= 529 \text{ Watts}$$

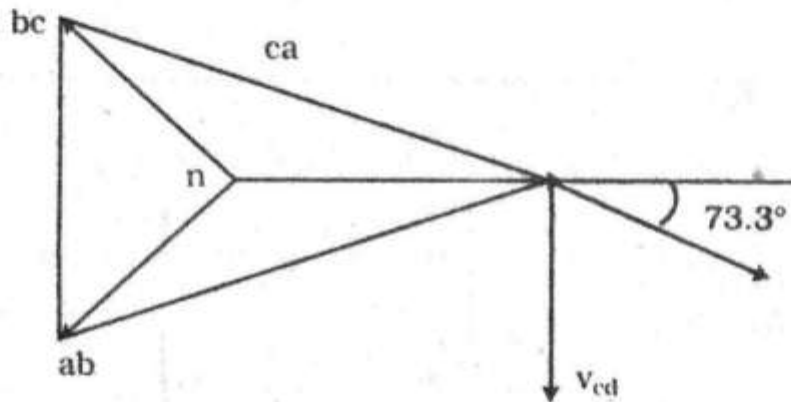

Total reactive volt - amp taken by the load is—

$$P_X = \sqrt{3} V_L I_L \sin \theta = 917.43 \text{ vars}$$

$$\therefore \frac{P_X}{W_R} = \frac{\sqrt{3} V_L I_L \sin 73.3}{V_L I_L \sin 73.3} = \sqrt{3}$$

8.44

If phase angle is θ then, $W_R = V_L I_L \sin \theta$

$$P_X = \sqrt{3} V_L I_L \sin \theta$$

50.51 is similar to number 49.

8.45.

$$W_a = V_L I_L \cos (\theta - 30)$$

$$w_b = V_L I_L \cos (\theta + 30^\circ)$$

$$\begin{aligned} \therefore W_a + W_b &= V_L I_L [\cos(\theta - 30^\circ) + \cos(\theta + 30^\circ)] \\ &= \sqrt{3} V_L I_L \cos \theta \\ W_a - W_b &= V_L I_L [\cos(\theta - 30^\circ) - \cos(\theta + 30^\circ)] \\ &= V_L I_L \sin \theta \end{aligned}$$

8.46.

$$\tan \theta = \frac{\sqrt{3}(1200 + 400)}{1200 - 400}$$

$$\therefore \theta = 73.9^\circ \text{ p.f.} = \cos \theta = 0.277$$

$$\text{Power } Z = W_a + W_b = 800 \text{ watt Now. } p = \sqrt{3} V_L I_L \cos \theta$$


$$\text{or. } P \times \cos \theta \therefore P_X = \frac{P}{\cos \theta} = 2888 \text{ VA}$$

8.47.

$$W_a = 1000 \text{ Watts}$$

$$W_b = 400 \text{ Watts}$$

$$P = 1400 \text{ watts}$$

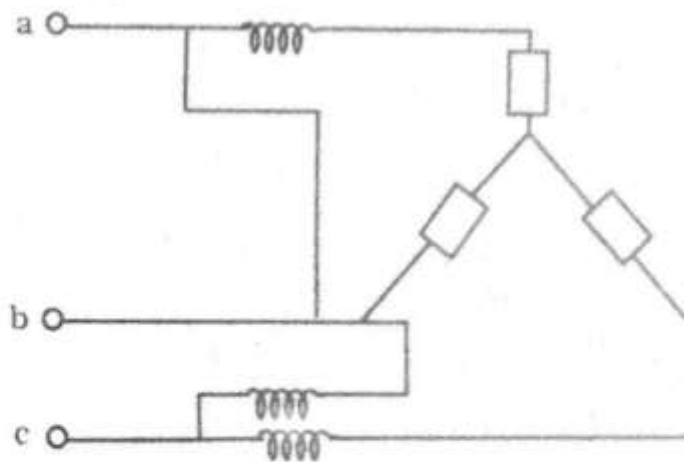

$$P_X = \sqrt{3} (W_a - W_b) = 1039.28 \text{ vars}$$


$$\text{p.f.} = \frac{P}{\sqrt{P^2 + P_X^2}} = 0.802$$

$$\therefore W_a = \sqrt{3} V_L I_L \cos(\theta - 30^\circ), W_b = \sqrt{3} V_L I_L \cos(\theta + 30^\circ)$$

\therefore The voltage sequence is ACB.

$$800^2 = \left(\frac{1}{2\pi}\right)^2 \times \frac{1}{\frac{100}{3} \times 10^{-3} \times C}$$

$$C = 2.968 \times 10^{-7} \text{ f}$$

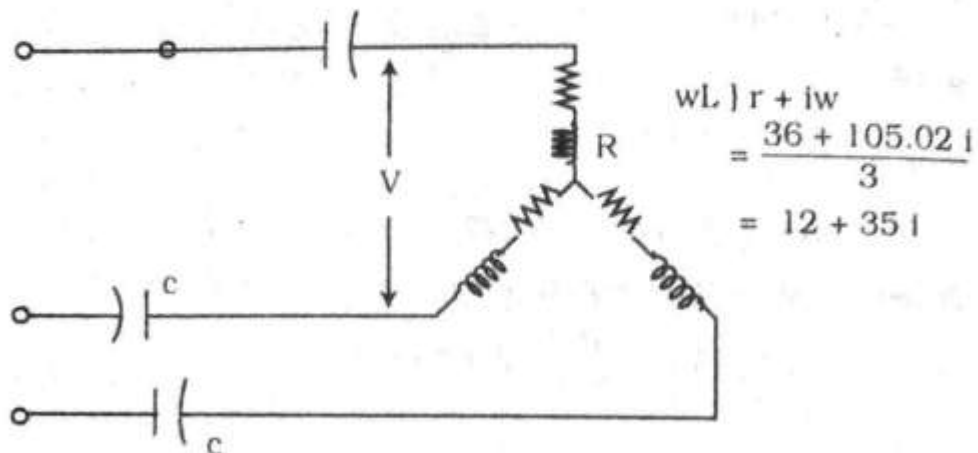

(b) Do yourself (Hints. parallel resonance)

[Previous page 41, 42]

8.48

$$V_L = 51.76 \text{ volts}$$

$$V_L = V_p \sin \frac{180}{n}$$

$$\text{or, } 51.76 = V_p \sin \frac{180}{12}$$

$$\therefore V_p = 100 \text{ V}$$

$$Z_p = 5 + j4$$

$$\therefore I_p = \frac{V_p}{Z_p} = \frac{100}{5 \angle 53.13} = 20 \angle -53.13^\circ$$

$$\text{Power} = V_p I_p \cos \theta = 12 \times 100 \times 20 \times \cos (53.13) = 14400 \text{ watts}$$

$$\text{pf} = \cos 53.13 = 0.6$$

$$I_p = I_L = 20 \text{ amp}$$

8.49

$$e_{na} = 127 \sin \omega t + 50 \sin (3\omega t - 30^\circ) + 30 \sin (5\omega t + 40^\circ)$$

$$e_{nb} = 127 \sin (\omega t - 120^\circ) + 50 \sin (3\omega t - 30 - 120^\circ) + 30 \sin (5\omega t + 40 - 120^\circ)$$

$$e_{nc} = 127 \sin (\omega t - 240^\circ) + 50 \sin (3\omega t - 30 - 240^\circ) + 30 \sin (5\omega t + 40 - 240^\circ)$$

$$\therefore e_{ab} = e_{na} - e_{nb}$$

$$= [127 \sin \omega t + 50 \sin (3\omega t - 30^\circ) + 30 \sin (5\omega t + 40)] -$$

$$[127 \sin (\omega t - 120^\circ)$$

$$+ 50 \sin (3\omega t - 30 - 120) + 30 \sin (5\omega t + 40 - 120)]$$

= Do the rest of the math yourself.

Chapter-9

Unbalanced polyphase circuits

9.1

$$Z_{an} = 10 + j0$$


$$Z_{bn} = 10 + j10$$

$$Z_{cn} = 0 - j20$$

$$I_{an} = I_{a'n} = 3.66 \angle 15 \text{ amp}$$

$$I_{bn} = I_{b'n} = 14.56 \angle -125.1 \text{ amp}$$
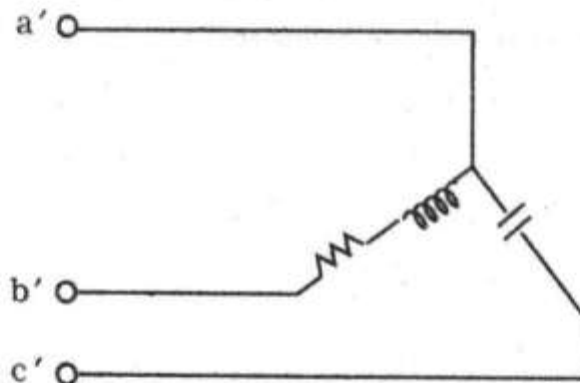
$$I_{cn} = I_{c'n} = 11.98 \angle 66.7 \text{ amp}$$



$$\therefore V_{an} = I_{an} Z_{an} = (3.66 \angle 15) (10 \angle 0) = 36.6 \angle 15 \text{ volts}$$

$$V_{bn} = I_{bn} Z_{bn} = (14.56 \angle -125.1) (19.192 \angle 45^\circ) = 205.9 \angle -80^\circ$$

$$V_{cn} = I_{cn} Z_{cn} = (11.98 \angle 66.2) (20 \angle -90^\circ) = 239.6 \angle 23.8 \text{ volts}$$

$$\begin{aligned} \mathbf{9.2} \quad P_{an} &= V_{an} I_{an} \cos \theta \int_{I_{an}}^{V_{an}} = 36.6 + 3.66 \times \cos(15 - 15) \\ &= 134 \text{ watts} \end{aligned}$$

$$P_{bn} = 205.9 \times 14.56 \cos(-80.1 + 105.1) = 2119.84 \text{ watts}$$

$$P_{cn} = 239.6 \times 11.98 \cos(23.8 - 66.2) = 0 \text{ watts}$$

$$\mathbf{9.4} \quad \frac{E_{n'a} - I_{n'n} Z_n}{Z_a} + \frac{E_{n'b} - I_{n'n} Z_n}{Z_b} + \frac{E_{n'c} - I_{n'n} Z_n}{Z_c} = I_{n'n}$$

$$\text{or, } E_{n'a} Z_b Z_c + E_{n'b} Z_c Z_a + E_{n'c} Z_a Z_b = I_{n'n} Z_n (Z_b Z_c + Z_c Z_a + Z_a Z_b)$$

$$\therefore I_{n'n} = \frac{E_{n'a} Z_b Z_c + E_{n'b} Z_c Z_a + E_{n'c} Z_a Z_b}{Z_a Z_b Z_c + Z_n (Z_b Z_c + Z_c Z_a + Z_a Z_b)}$$

9.7 Soln :


$$W_{ba} = V_{ba} I_{b'b} \cos \theta \left. \begin{array}{l} V_{ba} \\ I_{b'b} \end{array} \right\} \begin{array}{l} V_{ba} = V_{ab} \angle 80^\circ \\ V_{b'b} = 37.55 \angle 45.55^\circ \end{array}$$

$$= 200 \times 35.06 \cos(180 - 145)$$

$$= 5742.25$$

$$W_{ca} = 200 \times 21.66 \cos(120 - (-126.75)) = 4301.97$$

9.11

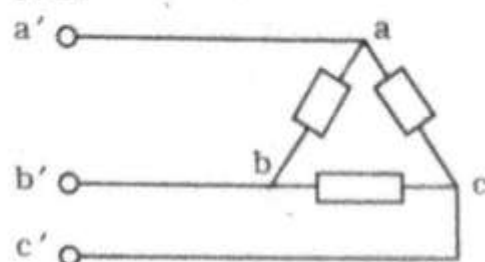

$$Z_{ab} = 10 \angle -60^\circ, Z_{bc} = 5 \angle 0^\circ$$


$$Z_{ca} = 10 \angle 60^\circ$$

Since the three phase supply voltage are balanced and the phase sequence is cb - ba - ac.

$$\therefore V_{cb} = 100 \angle 0$$

$$V_{ba} = 100 \angle -120$$

$$V_{ac} = 100 \angle 120^\circ$$

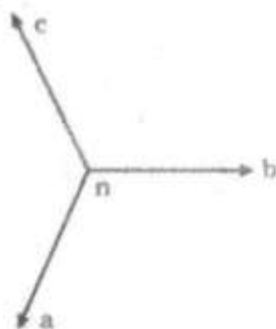

$$Z = 100 - j100 = 141.4 \angle -45^\circ \left[\begin{array}{l} \text{3}\phi \text{ sequence is always} \\ \text{connected in the clockwise} \\ \text{direction.} \end{array} \right]$$

Now,

$$I_{ba} = \frac{V_{ba}}{Z_{ab}} \text{ [Since the impedance are bilateral } Z_{an} = Z_{bn}]$$

$$= \frac{100 \angle 120}{10 \angle -10^\circ} = 10 \angle -60 \text{ amp}$$

$$I_{cb} = \frac{V_{cb}}{Z_{cb}} = \frac{100 \angle 0}{5 \angle 0} = 20 \angle 0^\circ$$

$$I_{ac} = \frac{V_{ac}}{Z_{ca}} = \frac{100 \angle 120}{10 \angle 60^\circ} = 10 \angle 60^\circ$$

Now,

$$\begin{aligned} I_{a'a} &= I_{ac} + I_{ab} = I_{ac} - I_{ba} = 10 \angle 60 - 10 \angle -60 \\ &= 8 + j8.66 - 8 + j8.66 \\ &= 17.32 \angle 90^\circ \end{aligned}$$

$$\begin{aligned} I_{b'b} &= I_{ba} - I_{ab} = 10 \angle -60 - 20 \angle 0^\circ = 5 - j8.66 - 20 + j0 \\ &= 17.32 \angle 150 \end{aligned}$$

$$\begin{aligned} I_{c'c} &= I_{cb} - I_{ac} = 20 \angle 0 - 10 \angle 60 = 20 - 5 - j8.66 \\ &= 17.32 \angle -30^\circ \end{aligned}$$

For opposite sequence the sequence will be $cb - ac - ba$

$$\therefore V_{cb} = 100 \angle 0 \quad V_{ac} = 100 \angle -120^\circ \quad V_{ba} = 100 \angle 120^\circ$$

$$\therefore I_{ba} = \frac{V_{ba}}{Z_{ab}} = \frac{100 \angle 120^\circ}{10 \angle -60} = 10 \angle 180^\circ$$

$$\therefore I_{cb} = \frac{V_{cb}}{Z_{bc}} = \frac{100 \angle 0}{5 \angle 0} = 20 \angle 0$$


$$I_{ac} = \frac{V_{ac}}{Z_{ca}} = \frac{100 \angle -120}{10 \angle 60} = 10 \angle -180^\circ$$

$$\therefore I_{a'a} = I_{ac} - I_{ba} = 10 \angle -180 - 10 \angle 180^\circ = 10 + 10 = 0$$

$$I_{b'b} = I_{ba} - I_{cb} = 10 \angle 180 - 20 \angle 0 = -10 - 20 = 30 \angle 180^\circ$$

$$I_{c'c} = I_{cb} - I_{ac} = 20 \angle 0 - 10 \angle -180^\circ = 20 + 10 = 30 \angle 0^\circ$$

912.

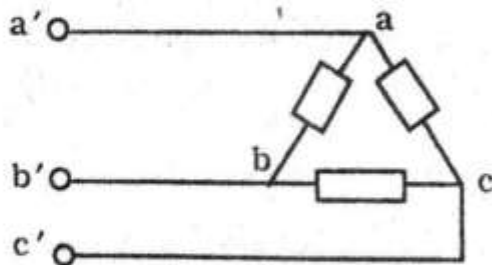

$$Z_{ab} = 5 \angle 40^\circ$$

$$Z_{bc} = 10 \angle -30^\circ$$

$$Z_{ca} = 8 \angle 45^\circ$$

Since the phase sequence is $cb - ac - ba$ and the line voltage are balanced.

$$\therefore V_{cb} = 115 \angle 0, \quad V_{ac} = 115 \angle -120 \quad V_{ba} = 115 \angle 120$$

$$\text{Now, } I_{cb} = \frac{V_{cb}}{Z_{bc}} = \frac{115 \angle 0}{10 \angle -30} = 11.5 \angle 30$$

$$I_{ac} = \frac{V_{ac}}{Z_{ca}} = \frac{115 \angle -120^\circ}{8 \angle 45^\circ} = 14.375 \angle -165^\circ$$

$$I_{ba} = \frac{V_{ba}}{Z_{ab}} = \frac{115 \angle 120^\circ}{5 \angle 40^\circ} = 23 \angle 80^\circ$$


Since the currents are leaving the terminals.

$$\begin{aligned} \therefore I_{aa'} &= I_{ba} + I_{ca} = I_{ba} - I_{ac} = 23 \angle 80^\circ - 14.375 \angle -165^\circ \\ &= 4 + j22.65 + 13.885 + j3.72 \\ &= 31.863 \angle 55.85^\circ \text{A} \end{aligned}$$

$$\begin{aligned} I_{bb'} &= I_{ca} - I_{ba} = 11.5 \angle 30^\circ - 23 \angle 80^\circ = 9.96 + j5.751 - 4 - j22.65 \\ &= 17.92 \angle -70.57^\circ \end{aligned}$$

$$\begin{aligned} I_{cc'} &= I_{ac} - I_{cb} = 14.375 \angle -165^\circ - 11.5 \angle 30^\circ \\ &= -13.885 - j3.72 - 9.96 - j5.75 \\ &= 25.66 \angle -158.34^\circ \end{aligned}$$

9.13

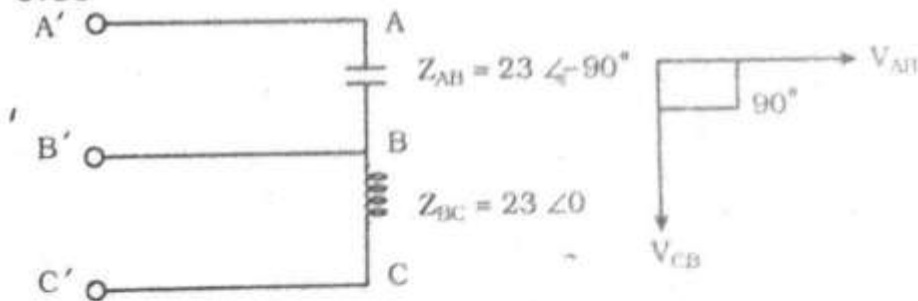

Since the voltage sequence is AB - CB

$$\begin{aligned} \therefore V_{AB} &= 115 \angle 0^\circ \quad V_{CB} = 115 \angle -180^\circ - (-90^\circ) \\ &= 115 \angle -90^\circ \end{aligned}$$

$$\therefore I_{AB} = \frac{V_{AB}}{Z_{AB}} = \frac{115 \angle 0^\circ}{23 \angle -90^\circ} = 5 \angle 90^\circ$$


$$I_{CB} = \frac{V_{CB}}{Z_{BC}} = \frac{115 \angle -90^\circ}{23 \angle 0^\circ} = 5 \angle -90^\circ \text{ amp}$$

$$\begin{aligned} I_{BB'} &= I_{AB} + I_{CB} = 5 \angle 90^\circ + 5 \angle -90^\circ = 0 + j50 + 0 - 5j \\ &= 0 \text{ Ans.} \end{aligned}$$

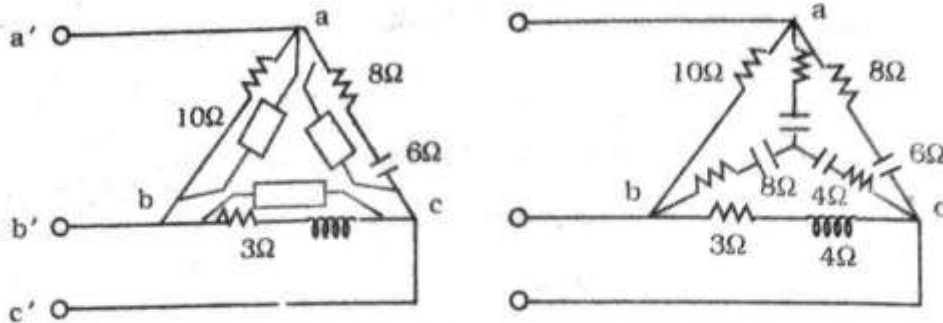9.15

Every impedance of Y is $4 - 3j = 5 \angle -36.87^\circ$

∴ Equivalent impedance of Y to ∇ is $3 \times 5 \angle -36.87^\circ = 15 \angle -36.87^\circ$



$$\text{Now } Z_{ab} = \frac{10 \times 15 \angle -36.87^\circ}{10 + 15 \angle -36.87^\circ} = \frac{150 \angle -36.87^\circ}{23.77 \angle -22.25^\circ} = 6.31 \angle -14.62^\circ$$

$$Z_{bceq} = \frac{(3 + 4j)(15 \angle -36.87^\circ)}{3 + 4j + 15 \angle -36.87^\circ} = 4.74 \angle 34.7^\circ$$

$$Z_{cacq} = \frac{(8 - j6)(15 \angle -36.87^\circ)}{8 - j6 + 15 \angle -36.87^\circ} = 6 \angle -36.87^\circ$$

Let the reference voltage be $V_{b'c'}$

$$\therefore V_{b'c'} = 230 \angle 0^\circ, V_{a'b'} = 230 \angle -120^\circ, V_{c'a'} = 230 \angle 120^\circ$$

$$I_{ab} = \frac{V_{a'b'}}{Z_{ab}} = \frac{230 \angle -120^\circ}{6.31 \angle -14.62^\circ} = 36.45 \angle -105.38^\circ$$

$$I_{bc} = \frac{230 \angle 0^\circ}{4.44 \angle 34.7^\circ} = 48.52 \angle -34.7^\circ$$

$$I_{ca} = \frac{230 \angle 120^\circ}{6 \angle -36.87^\circ} = 38.33 \angle 156.87^\circ$$

$$\therefore I_{a'a} = I_{ab} - I_{ca} = 36.45 \angle -105.38^\circ - 38.33 \angle 156.87^\circ$$

$$= -9.67 - j35.14 + 35.25 - j15.06$$

$$= 56.34 \angle -63^\circ \text{ Amp}$$

$$I_{b'b} = I_{bc} - I_{ab} = 48.52 \angle -34.7^\circ - 36.45 \angle -105.38^\circ$$


$$= 50.13 \angle 8.63^\circ$$

$$I_{c'c} = I_{ca} - I_{bc} = 38.33 \angle 156.87^\circ - 48.52 \angle -34.7^\circ$$

$$= 86.42 \angle -150^\circ$$

Hence the meter $a'a$, $b'b$, $c'c$ readings will be 56.34 A, 50.13 A, 86.42 A respectively.

9.6

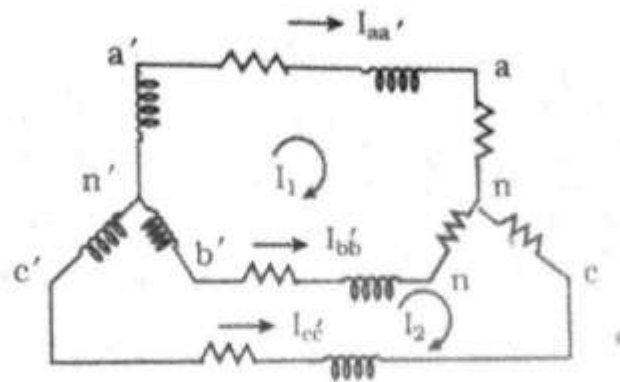

$$I_1(2 - j + 1 - 3) - (1 - 3) I_2 = 100 \angle 0^\circ - 100 \angle -120^\circ$$

$$\text{or, } 5 \angle -53.13 I_1 - 3.162 \angle -71.5 I_2 = 173.2 \angle 30^\circ$$

$$\Rightarrow (1 - 3) I_1 + (1 - j3 + 3 + 4) I_2$$

$$= 100 \angle -120^\circ - 100 \angle -240^\circ$$

$$\text{or, } -3.162 \angle -71.57 I_1 + 4.123 \angle 14.04 I_2 = 173.2 \angle -90^\circ$$

$$I_1 = \frac{\begin{vmatrix} 173.2 \angle 30^\circ & -3.162 \angle -71.57 \\ 173.2 \angle -90^\circ & 4.123 \angle 14.04 \end{vmatrix}}{\begin{vmatrix} 5 \angle -33.13 & -3.162 \angle -71.57 \\ -3.162 \angle -71.57 & 4.123 \angle 14.04 \end{vmatrix}}$$

$$= \frac{513.34 + j496.42 - 519.57 - j173.14}{16 - j13 + 8 + j6}$$

$$= \frac{323.34 \angle 91.1}{25 \angle -16.26} = 12.93 \angle 107.39 \text{ amp}$$

$$I_2 = \frac{\begin{vmatrix} 5 \angle -53.13 & 173.2 \angle 30^\circ \\ -3.162 \angle -71.57 & 173.2 \angle -90^\circ \end{vmatrix}}{25 \angle -16.26}$$

$$= \frac{-692.8 - j519.6 + 409.73 - j363.39}{25 \angle -16.26}$$

$$= \frac{927.25 \angle -107.77}{25 \angle -16.26}$$

$$= 37.09 \angle -91.5$$

$$\text{Now } I_{a'a} = I_1 = 12.93 \angle 107.36^\circ \text{ Amp}$$


$$I_{b'b} = I_2 - I_1 = 37.09 \angle -91.5 - 12.93 \angle 107.33$$

$$= -0.97 - j37.08 + 3.86 - j12.34$$

$$= 49.5 \angle -35.65^\circ \text{ Amp}$$

$$I_{c'c} = -I_2 = 37.09 \angle -91.5 = 37.09 \angle 99.5$$

9.17

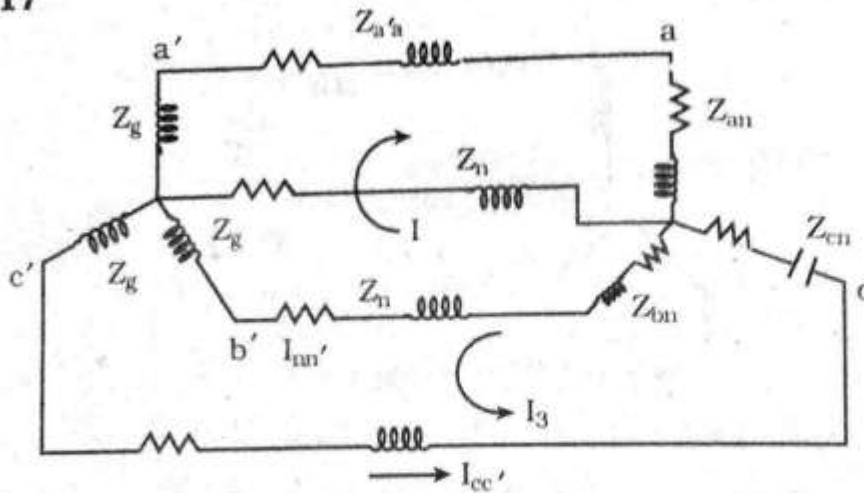

$$E_{n'a'} = 1000 + j0 = 1000 \angle 0$$

$$E_{n'b'} = -500 - j866 = 1000 \angle -120$$

$$E_{n'c'} = -500 + j866 = 1000 \angle 120$$

$$Z_g = 2 + j8 = 8.25 \angle 76^\circ$$

$$Z_{an} = 20 - 20j$$

$$Z_{bn} = 50 + j0$$

$$Z_{cn} = 30 + j52$$

$$Z_L = 1 + j1$$

$$Z_n = 2.5 + j$$

$$Z_g = 2 + j8$$

$$Z_a = Z_g + Z_g + Z_{an} = 2 + j8 + 1 + j + 20 - 20j = 23 - j11$$

$$Z_b = Z_g + Z_g + Z_{bn} = 2 + j8 + 1 + j + 50 + j0 = 53 + 9j$$

$$Z_c = Z_g + Z_g + Z_{cn} = 2 + j8 + 1 + j + 30 + 52j = 33 + j61$$

$$I_{nn'} = \frac{E_{n'a'} Z_b Z_c + E_{n'b'} E_c Z_a + E_{n'c'} Z_a Z_b}{Z_a Z_b Z_c + Z_n (Z_b Z_c + Z_c Z_a + Z_a Z_b)}$$

$$= \frac{100 \angle 0 \times 53.75 \angle 9.64 \times 69.35 \angle 61.59 + 1000 \angle 120 \times 69.35 \angle 61.59 \times 25.5 \angle -25.56 + 100 \angle 120 \times 25.5 \angle -25.56 \times 53.75 \angle 9.64}{3727562.3 \angle 71.23 + 1768425 \angle -83.97 + 1370625 \angle 104.08}$$

$$= \frac{25.5 \angle -25.56 \times 53.75 \angle 9.64 \times 69.35 \angle 61.59 + 2.70 \angle 21.8 \times (53.75 \angle 9.64 \times 69.35 \angle 61.58 + 69.35 \angle 61.58 \times 25.5 \angle -25.56 + 25.5 \angle -25.56 \times 53.75 \angle 9.63)}{3727562.3 \angle 71.23 + 1768425 \angle -83.97 + 1370625 \angle 104.08}$$

$$= \frac{95381.794 \angle 45.67 + 2.70 \angle 21.8 (3727.5625 \angle 71.22 + 1768.425 \angle 36.02 + 1370.625 \angle -15.93)}{3727562.3 \angle 71.23 + 1768425 \angle -83.97 + 1370625 \angle 104.08}$$

$$\begin{aligned}
 & 1199417 + j3529322.8 + 185771.59 - j1758640.4 - 33440.78 \\
 & \qquad \qquad \qquad + j1329447.3 \\
 = & \frac{95381.794 \angle 45.67 + 2.70 \angle 21.8 (3727.5625 \angle 71.22 + \\
 & \qquad \qquad \qquad 1768.425 \angle 36.02 + 1370.625 \angle -15.93)}{1051748.5 - j3100129.7} \\
 = & \frac{95381.794 \angle 45.67 + 2.70 \angle 21.8 (3948.3466 - j4192.8814)}{3273679.7 \angle -71.26} \\
 = & \frac{45381.794 \angle 45.67 + 15550.147 \angle -27.92}{3273679.7 \angle -71.26} \\
 = & \frac{46565.202 + j25910.73}{53288.685 \angle 29.093} = 61.43 \angle -42.167
 \end{aligned}$$

$$\therefore I_{nn'} = 61.43 \angle -42.167$$

$$\begin{aligned}
 I_{nn'} &= \frac{E_{n'a'} - I_{nn'} Z_n}{Z_a} = \frac{1000 \angle 0 - 61.43 \angle -42.167 \times 2.70 \angle 21.8}{25.5 \angle -25.56} \\
 &= \frac{100 + j0 - 165.861 \angle 20.367}{25.5 \angle -25.56} \\
 &= \frac{100 + j0 - 155.4918 + j57.73}{25.5 \angle -25.56} \\
 &= \frac{846.47907 \angle 3.9106162}{25.5 \angle -25.56} \\
 &= 33.2 \angle 29.471
 \end{aligned}$$

$$\begin{aligned}
 I_{b'b} &= \frac{E_{n'b'} - I_{nn'} Z_n}{Z_b} \\
 &= \frac{-500 - j866 - 61.43 \angle -42.167 \times 2.7 \angle 21.8}{53.75 \angle 9.64} \\
 &= \frac{-500 - j866 - 155.4918 + j57.73}{53.75 \angle 9.64} \\
 &= 19.361 \angle -138.68
 \end{aligned}$$

$$\begin{aligned}
 I_{c'c} &= \frac{E_{n'c'} - I_{nn'} Z_n}{Z_c} = \frac{-500 + j866 - 155.4918 + j57.73}{69.35 \angle 61.59} \\
 &= 16.33 \angle 63.77
 \end{aligned}$$

$$Z_{cn} = \frac{10 \times 60 \times 10 \angle -60}{20} = 5 \angle 0^\circ = 5 + j0$$

Voltage sequence is $b'a' - a'c' - c'b'$

$$\therefore E_{b'a'} = 100 \angle 0$$

$$E_{a'c'} = 100 \angle -120$$

$$E_{c'b'} = 100 \angle 120$$

From Fig. 2.

$$(0.5 + j0.5 + 2.5 - j4.33 + 2.5 + j4.33 + 0.5 + j0.5) I_1 - (2.5 + j4.33 + 0.5 + j0.5) = E_{b'a'}$$

$$- (2.5 + j4.33 + 0.5 + j0.5) I_1 + (0.5 + j0.5 + 2.5 + j4.33 + 5 + j0 + 0.5 + j0.5) I_2 = E$$

$$\text{or, } 6.08 \angle 9.46 I_1 - 5.69 \angle 58.15 I_2 = 100 \angle 120^\circ$$

$$- 5.69 \angle 58.15 I_1 + 10.03 \angle 32.09 I_2 = 100 \angle 120^\circ$$

$$\therefore I_1 = \frac{\begin{vmatrix} 100 \angle 0 & -5.69 \angle 98.15 \\ 100 \angle 120 & 10.03 \angle 32.09 \end{vmatrix}}{\begin{vmatrix} 6.08 \angle 9.46 & -5.69 \angle 58.15 \\ -5.69 \angle 58.15 & 10.03 \angle 32.09 \end{vmatrix}}$$

$$= \frac{849.76 + j532.84 - 568.7 + j18.37}{45.64 + j40.45 + 14.34 - j29.02}$$

$$= 10.13 \angle 52.1$$

$$I_2 = \frac{\begin{vmatrix} 6.08 \angle 9.46 & 100 \angle 0 \\ -5.69 \angle 58.15 & 100 \angle 15 \end{vmatrix}}{61.06 \angle 10.8}$$

$$= \frac{386.41 + j469.42 + 300.26 + j433.33}{61.06 \angle 10.8}$$

$$= \frac{956.64 \angle 95.17}{61.06 \angle 10.8} = 15.67 \angle 84.37$$

9.18 Equivalent Y-loads of

loads as follows.

$$Z_{an} = \frac{Z_{ab}Z_{ac}}{Z_{ab} + Z_{bc} + Z_{ca}}$$

$$= \frac{50 \times 5 \angle -60^\circ}{5 \angle 0 + 5 \angle 60 + 5 \angle -60}$$

$$= 2.5 \angle 60^\circ$$


$$Z_{ab} = 5 \angle 0 = Z_{bc} = 5 \angle 60^\circ$$

$$Z_{ca} = 5 \angle -60^\circ$$

$$Z_{ab} + Z_{bc} + Z_{ca} = 10 \angle 0, Z_{bn} = \frac{Z_{ab} \times Z_{bc}}{10 \angle 0} = \frac{5 \angle 0 \times 5 \angle 60}{10} = 2.5 \angle 60^\circ$$

$$Z_{cn} = \frac{Z_{ca} Z_{bc}}{10 \angle 0} = \frac{5 \angle -60 \times 5 \angle 60}{10} = 2.5 \angle 0$$

9.19.

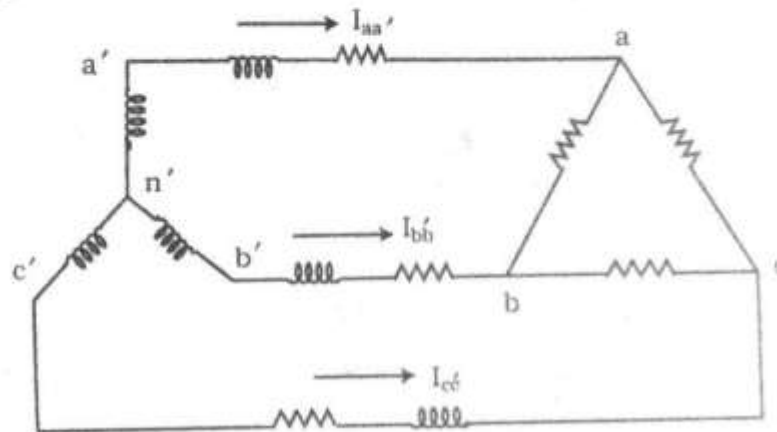


In fig. 1 :

$$Z_{ab} = 10 \angle 0 = 10 + j0$$

$$Z_{bc} = 10 \angle 60 = 5 + j8.66$$
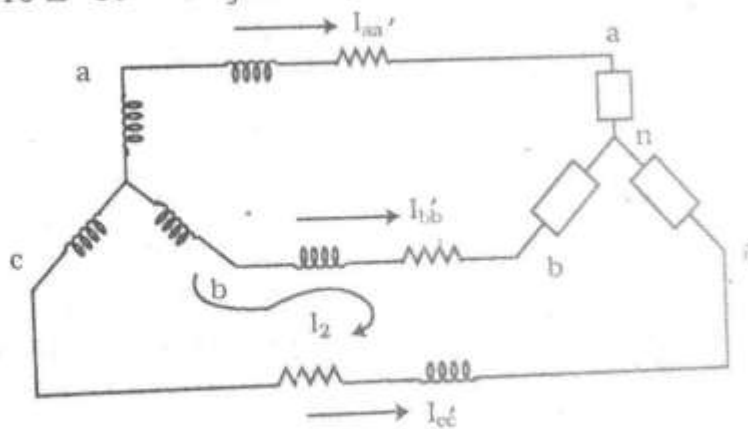
$$Z_{ca} = 10 \angle -60^\circ = 5 - j8.66$$



In fig. 2 :

$$Z_{an} = \frac{10 \angle 0 \times 10 \angle -60}{10 + 5 + j8.66 + 5 - j8.66} = 5 \angle -60 = 2.5 - j4.33$$

$$Z_{bn} = \frac{10 \angle 0 \times 10 \angle 60}{20} = 5 \angle 60 = 2.5 + j4.33$$

Now, $I_{a'a} = I_1 = 10.13 \angle 52.1$ amp

$$I_{b'b} = I_2 - I_1 = 15.67 \angle 84.37 - 10.13 \angle 52.1$$

$$= 1.54 + j15.59 - 6.22 - j7.99$$

$$= 8.93 \angle 121.62 \text{ amp}$$

Now, from fig. 1 : $V_{cb} + I_{a'a} Z_{a'a} - I_{b'b} Z_{b'b} = E_{b'a}$

or, $V_{ab} = 100 + j0 - (10.13 \angle 52.1) (0.5 + j0.5) + (8.93 \angle 121.62) \times (0.5 + j0.5)$

$$= 100 + j0 + 0.89 - j7.11 - 6.14 + j1.46$$

$$= 94.92 \angle -3.41^\circ$$

$$\therefore I_{ab} = \frac{V_{ab}}{Z_{ab}} = \frac{94.92 \angle -3.41}{10 \angle 0} = 9.49 \angle -3.41 \text{ amp}$$

Now, $I_{ab} + I_{ac} = I_{a'a}$

or, $I_{ca} = I_{ab} - I_{a'a} = 9.47 - j56 - 6.22 - j7.99$


$$= 9.15 \angle -69.19^\circ \text{ amp}$$

$$I_{bc} + I_{ba} = I_{b'b} \text{ or, } I_{bc} = I_{b'b} + I_{ab}$$

$$= -4.68 + j7.6 + 9.47 - j0.56$$

$$= 8.52 \angle 55.77$$

9.20

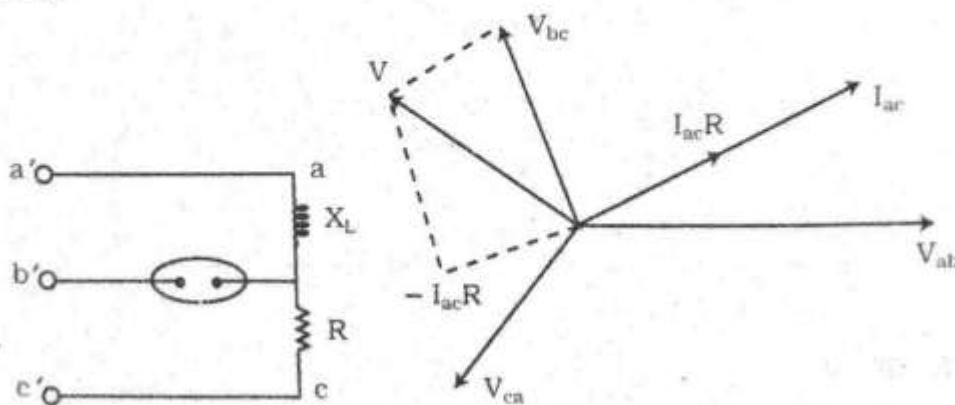

The sequence is $ab - ca - bc$

Let, the magnitude of line voltage be 141.4 volts

$$\begin{aligned} X_L &= 100 \text{ ohm} \\ R &= 100 \text{ ohm} \\ \therefore V_{ab} &= 141.4 \angle 0 \\ V_{ca} &= 141.4 \angle -120 \\ V_{ca} &= 141.4 \angle 120 \end{aligned}$$

Since the current through the voltmeter is negligible, we can assume X_L and R are connected in series across the voltage V_{ac} .

$$\therefore I_{ac} = \frac{V_{ac}}{Z_{ac}} = \frac{-141.4 \angle -120^\circ}{100 + j100} = \frac{141.4 \angle 60^\circ}{141.4 \angle 45^\circ} = 1 \angle 15^\circ$$


$$\begin{aligned} \text{Now, from KVL } -V_{bn} + V_{nc} &= V_{bc} \text{ or, } V_m = V_{bc} - I_{ac}R \\ &= 141.4 \angle 120^\circ - 1 \angle 15^\circ ; 100 = -70.7 + j122.46 - 96.59 \\ &\qquad\qquad\qquad - j25.98 \\ &= 193.17 \angle 150 \text{ volts} \end{aligned}$$

\therefore The voltmeter read above the line voltage.

9.21 Not important.

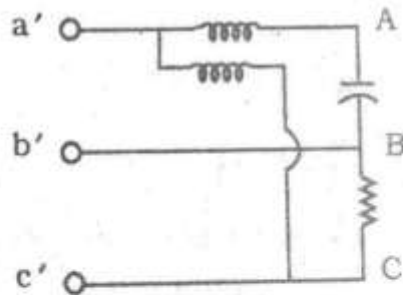9.22


From prob 13 $I_{A'A} = I_{AB} = 5 \angle 90^\circ$



$$\begin{aligned} V_{AC} &= V_{AB} + V_{BC} = V_{AB} - V_{CB} \\ &= 115 \angle 0 - 115 \angle -90^\circ \\ &= 115 + j0 + 0 + j115 \\ &= 162.63 \angle 45^\circ \end{aligned}$$

$$\begin{aligned} \therefore W_{Ac-A'A} &= V_{AC} I_{A'A} \cos \theta \Big|_{A'A}^{AC} = 162.63 \times 5 \times \cos(45 - 90) \\ &= 575 \text{ watts} \end{aligned}$$

9.23

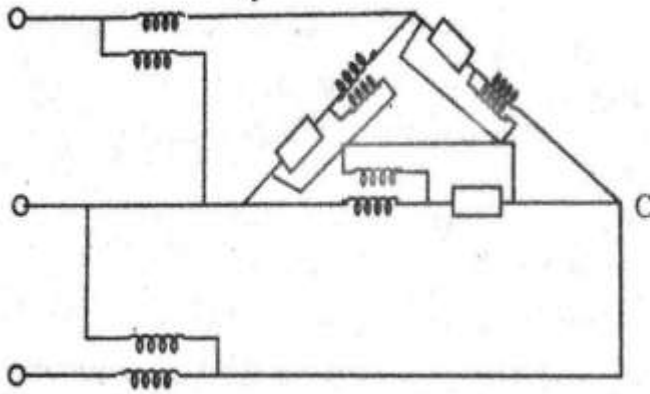

Given,

$$V_{ab} = 20 \text{ V}$$

$$V_{bc} = 141.4 \text{ V}$$

$$V_{ca} = 141.4 \text{ V}$$

Sequence

ab - bc - ca

$$Z_{ab} = Z_{bc} = Z_c$$

$$= (8 - j6)$$

Since the sequence is ab - bc - ca

$$\therefore V_{ab} = 200 \angle 0$$

$$V_{bc} = 141.4 \angle -120^\circ$$

$$V_{ca} = 141.4 \angle 120^\circ$$

$$I_{ab} = \frac{V_{ab}}{Z_{ab}} = \frac{200 \angle 0}{10 \angle -36.87} = 20 \angle 36.97^\circ$$

$$I_{bc} = \frac{V_{bc}}{Z_{bc}} = \frac{141.4 \angle -120}{10 \angle -36.87} = 14.14 \angle -83.13$$

$$I_{ca} = \frac{V_{ca}}{Z_{ca}} = \frac{141.4 \angle 120}{10 \angle -36.87} = 14.14 \angle 15.87^\circ$$

$$W_{ab} = V_{ab} I_{ab} \cos \theta = 200 \times 20 \cos (0 - 36.87) = 3200 \text{ watts}$$


$$\text{Now, } I_{a'a} = I_{ab} - I_{ca} = 18 + j12 - 13 - j5.55 = 29.7 \angle 12.54$$

$$I_{c'c} = I_{ca} - I_{bc} = -13 - j15.55 - (-1.89 + j14) = 24.45 \angle 126.92^\circ$$

$$\text{Now } W_a = V_{ab} I_{a'a} \cos \theta \int_{I_{a'a}}^{V_{ab}} = 200 \times 29.7 \cos (0 - 12.54) = 5798.3 \text{ watts}$$

$$W_b = V_{bc} I_{c'c} \cos \theta \int_{I_{c'c}}^{V_{bc}} = 141.4 \times 24.45 \cos (60 - 121.92) = 1627.3317 \text{ watts}$$

9.24

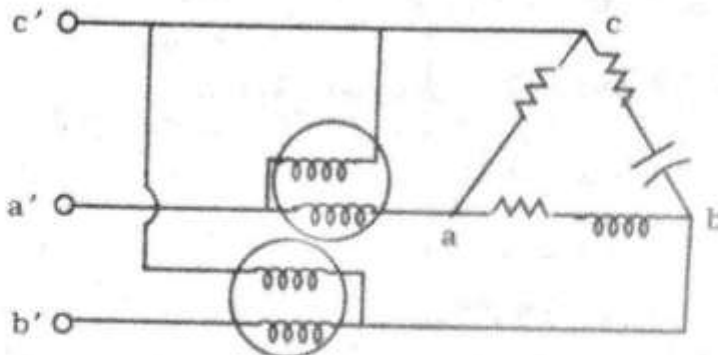

Since the voltage sequence is $ab - ca - bc$, from example 1 We have

$$(a) W_a = V_{ac} I_{a'a} \cos \theta \quad \int_{I_{a'a}}^{V_{ac}} V_{ac} = -V_{ca} = -100 \angle -120^\circ = 100 \angle 60^\circ$$

So,

$$W_a = V_{ac} I_{a'a} \cos \theta \int_{I_{a'a}}^{V_{ac}} = 100 \times 9.26 \times \cos(60 - 23.4) = 106.13 \text{ watts}$$


$$W_b = V_{bc} I_{b'b} \cos \theta \int_{I_{b'b}}^{V_{bc}} = 100 \times 2.9 \times \cos(120 - 146.9) = 2586.2 \text{ watts}$$

(b) If W_a and W_b are varmeters then their reading will be

$$P_{xa} = 100 \times 9.26 \sin(60 + 23.4) = 919.86 \text{ var (inductive)}$$

$$P_{xb} = 100 \times 2.9 \sin(120 - 145.9) = 1312.06 \text{ vars (capacitive)}$$

9.25

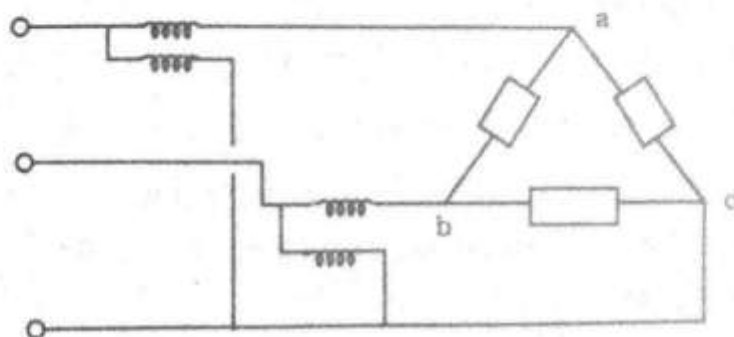

Taking calculations from problem 11 we have


$$(a) \quad W_a = V_{ac} I_{a'a} \cos \theta \quad \left. \begin{array}{l} V_{ac} = 100 \times 17.32 \cos (120 - 90^\circ) \\ I_{a'a} = 1500 \text{ watts} \end{array} \right\}$$

$$\begin{aligned} W_b &= V_{bc} I_{b'b} \cos \theta \quad \left. \begin{array}{l} V_{bc} \\ I_{b'b} \end{array} \right\} \\ &= 100 \times 17.32 \times \cos(180 + 150^\circ) \\ &= 1500 \text{ watts} \end{aligned}$$

$$(b) \quad P_{xc} = 100 \times 17.325 \sin (120^\circ - 90^\circ) = 866 \text{ vars (inductive)}$$

$$P_{xb} = 100 \times 17.32 \sin (180 + 150^\circ) = 866 \text{ vars (capacitive)}$$

9.26

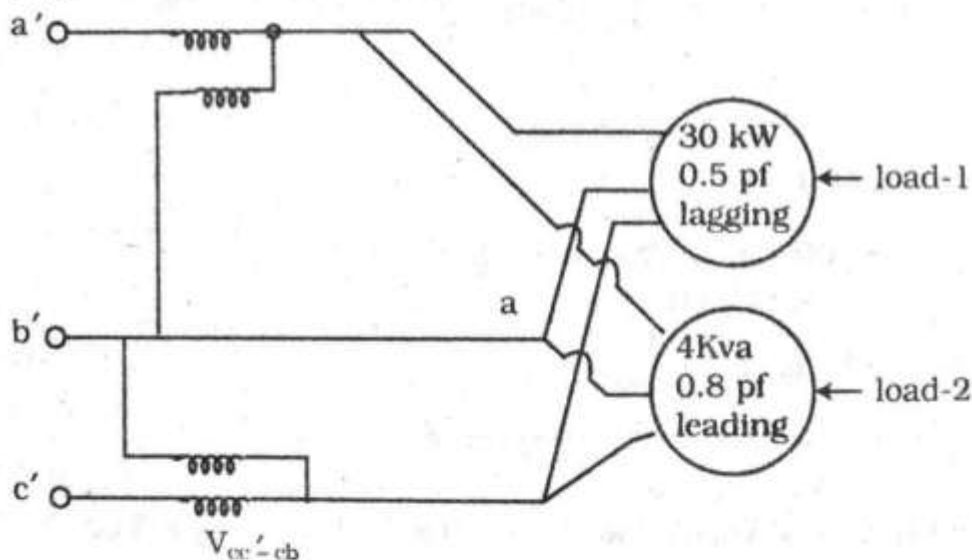

Since the phase sequence is a'b' - b'c' - c'a'

$$V_{ab} = V_{a'b'} = 200 \angle 0^\circ, \quad V_{bc} = V_{b'c'} = 200 \angle -120^\circ$$

$$V_{ca} = V_{c'a'} = 200 \angle 120^\circ$$

Let us assume that both the three phase loads are connected

$$\begin{aligned} \therefore \text{Per phase current in load 1 is, } I_{\phi 1} &= \frac{3000}{j \times 200 \times 0.5} \\ &= 10 \text{ amp} \end{aligned}$$

and these phase currents lag the applied voltage by $\cos^{-1} 0.5 = 60^\circ$

Per phase current in load 2 is $I_{\phi 2} = \frac{4000}{3 \times 200} = 6.67$ amp

and these phase currents load the applied volt by

$$\cos^{-1} 0.8 = 36.87^\circ$$

The unity p.f load current is in phase with V_{bc}

∴ Since these loads are parallel.

$$\therefore I_{ab} = 10 \angle(0 - 60^\circ) + 6.67 \angle(0 + 36.87)$$

$$= 5 - j8.66 + 5.34 + j4$$

$$= 11.34 \angle -24.2^\circ$$

$$I_{bc} = 10 \angle(-120 - 60) + 6.67 \angle(120 + 36.87) + \frac{4000}{200} \times \angle -120$$

$$= -10 + j0 + 0.8 - j6.62 - 10 - j17.32 = 30.69 \angle -128.73$$

$$I_{ca} = 10 \angle(120 - 60^\circ) + 6.67 \angle(120^\circ + 36.87^\circ)$$

$$= 5 + j8.66 - 6.13 + j2.68 = 11.34 \angle 95.72$$

$$\therefore I_{a'a} = I_{ab} - I_{ca} = 10.34 - j4.66 + 1.13 - j11.28$$

$$= 1964 \angle -54.26^\circ$$

$$I_{c'c} = I_{ca} - I_{bc} = -1.23 + j11.28 + 19.2 + j23.94$$

$$= 39.59 \angle 62.84^\circ = 2294.38 \text{ watts}$$

$$W_{c'c-cb} = 200 \times 39.59 \cos(60 - 62.84)$$

$$= 7908.28 \text{ watts}$$


$$V_{cb} = -V_{bc} = -200 \angle -120^\circ = 200 \angle 60^\circ$$

$$(b) \quad \sum VI \cos \theta = 2294.38 + 7908.28 = 10202.66 \text{ watts}$$

$$\sum VI \sin \theta = 3183.26 - 392.31 = 2795.95 \text{ vars}$$

$$\therefore \text{Vector p.f} = \frac{10202.66}{\sqrt{(10202.66)^2 + (2795.95)^2}} = 0.964$$

9.27

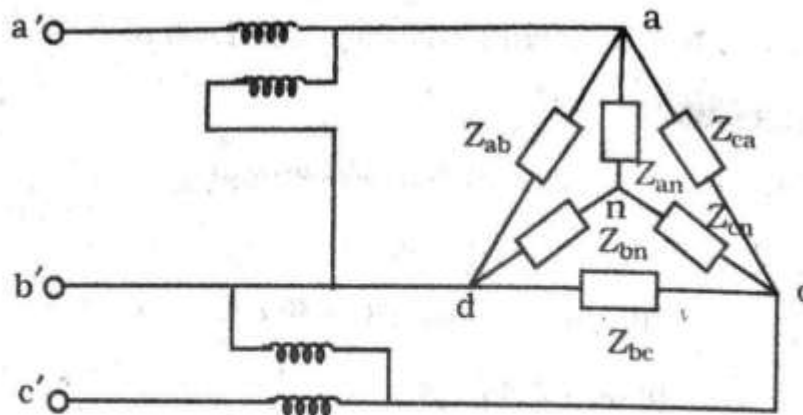

$$Z_{an} = 10 \angle 0^\circ \quad Z_{bn} = 10 \angle -60^\circ$$

$$Z_{cn} = 10 \angle 90^\circ$$

The voltage sequence is—

$$a'b' - c'a' - b'c'$$

$$V_{ab} = V_{a'b'} = 100 \angle 0^\circ$$

$$V_{bc} = V_{b'c'} = 100 \angle 120^\circ$$

$$V_{ca} = V_{c'a'} = 100 \angle -120^\circ$$

Transferring from Y

$$\therefore W_{a'a-ab} = 200 \times 14.14 \cos(0 + 45^\circ) = 2000 \text{ watts}$$

$$\therefore W_{c'c-cb} = 200 \times 10 \cos(60 - 30) = 1732 \text{ watts}$$

9.29 Since the phase sequence is $n'a' - n'b' - n'c'$

Let

$$E_{n'a'} = 115.4 \angle 0^\circ, E_{n'b'} = 115.4 \angle -120^\circ, E_{n'c'} = 115.4 \angle 120^\circ$$

$$V_{ab} = E_{n'a'} - E_{n'b'} = 115.4 \angle 0^\circ - 115.4 \angle -120^\circ = 15.4 \angle 120^\circ$$

$$V_{bc} = E_{n'b'} - E_{n'c'} = 115.4 \angle -120^\circ - 115.4 \angle 120^\circ$$

$$= 57.7 - j100 + 57.7 - j100$$

$$= 200 \angle -90^\circ$$

$$V_{ca} = E_{n'c'} - E_{n'a'} = -57.7 + j100 - 115.4 = 200 \angle 150^\circ$$

Taking V_{ab} as reference we can write—

$$(a) V_{ab} = 200 \angle 0^\circ$$


$$E_{n'a'} = 175.4 \angle -30^\circ$$

$$V_{bc} = 200 \angle (-90^\circ - 30^\circ) = 200 \angle -120^\circ$$

$$E_{n'b'} = 115.4 \angle -150^\circ$$

$$V_{ca} = 220 \angle (-150 - 30^\circ) = 200 \angle 120^\circ$$

$$E_{n'c'} = 115.4 \angle 90^\circ$$

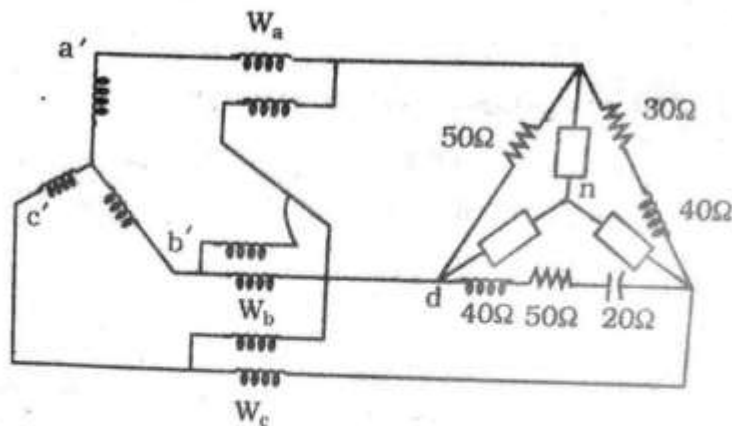

$$Z_{ab} = 50 \text{ ohm}, Z_{bc} = 40 + j(50 - 20) = 50 \angle 36.87^\circ$$

$$Z_{ca} = 30 + j40 = 50 \angle 53.13^\circ$$

$$(b) \quad I_{ab} = \frac{V_{ab}}{Z_{ab}} = \frac{200 \angle 0}{50 \angle 0} = 4 \angle 0 \text{ amp}$$

$$I_{bc} = \frac{V_{bc}}{Z_{bc}} = \frac{200 \angle -120}{50 \angle 36.87} = 4 \angle -156.87^\circ \text{ amp}$$

$$I_{ca} = \frac{200 \angle 120^\circ}{50 \angle 53.13} = 4 \angle 66.87^\circ \text{ amp}$$

$$(c) \quad I_{a'a} = I_{ab} - I_{ca} = 4 - 1.57 - j3.68 = 4.41 \angle -56.56^\circ$$

$$I_{b'b} = I_{bc} - I_{ab} = -3.68 - j1.57 - 4 = 7.84 \angle -168.4^\circ$$

$$I_{c'c} = I_{ca} - I_{bc} = 1.57 + j3.68 + 3.62 + j1.57 = 7.42 \angle 45^\circ$$

(d) Transferring term Δ to Y we get.

$$Z_{an} = \frac{50 \times 50 \angle 53.13^\circ}{50 + 40 + j30 + 30 + j40} = \frac{50 \times 50 \angle 53.13}{138.92 \angle 30.26} = 18 \angle 22.87^\circ$$

$$Z_{bn} = \frac{50 \times 30 \angle 36.87}{138.92 \angle 30.26} = 18 \angle 6.61^\circ$$

$$Z_{cn} = \frac{50 \angle 36.87 \times 50 \angle 53.13}{138.92 \angle 30.26} = 18 \angle 59.74^\circ$$

$$\text{Now, } W_a + W_b + W_c = \sum V_{w\Delta} I_{w\Delta} \cos \theta$$

$$= 79.38 \times 4.41 \cos(-33.69 + 56.56) + 14.12 \times 7.84 \times \cos$$

$$(-161.79 + 168.4) + 133.56 \times 7.42 \cos(104.74 - 45)$$

$$= 1920.97 \text{ watts}$$

$$(e) \quad W_a = V_{ab} I_{a'a} \cos \theta = 200 \times 4.41 \cos(0 + 56.56) = 486.04 \text{ watts}$$

$$W_b = V_{b'b} \cos \theta = \text{Do yourself}$$


$$W_c = V_{c'b} I_{c'c} \cos \theta = 200 \times 7.42 \cos(60 - 45) = 1435 \text{ watts}$$

9.30

There may be two types of voltage sequence :

(i) $ab - bc - ca$ (ii) $ab - ca - bc$

When the sequence is $ab - bc - ca$

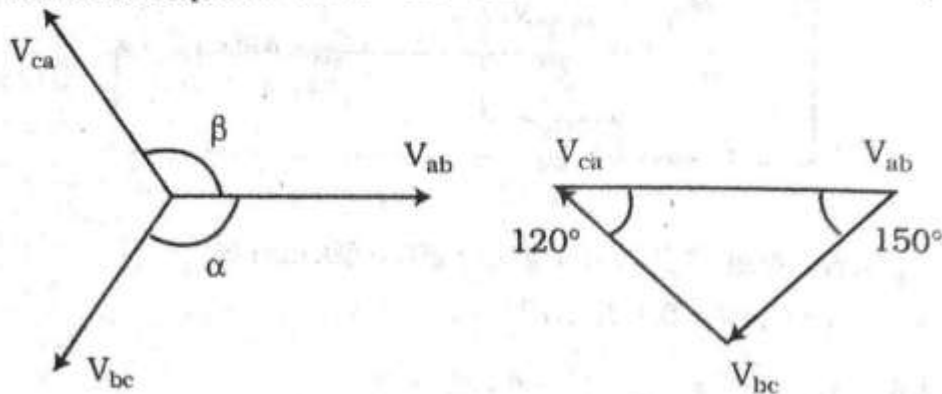

$$\cos \alpha = \frac{200^2 + 150^2 - 120^2}{2 \times 200 \times 150}$$

$$\therefore \alpha = 36.71^\circ$$

Since α is measured in clockwise direction.

$$= -(180 - 36.71) = -143.29^\circ$$

$$\cos \beta = \frac{200^2 + 120^2 - 150^2}{2 \times 200 \times 120}, \beta = 48.35^\circ$$


Since β is measured in anticlockwise direction,

$$\therefore \beta = 180 - 48.35 = 131.65^\circ$$

$$\therefore V_{ab} = 200 \angle 0, V_{bc} = 150 \angle -143.29^\circ,$$

$$V_{ca} = 120 \angle 131.65^\circ$$

(ii) When the sequence is $ab - ca - bc$

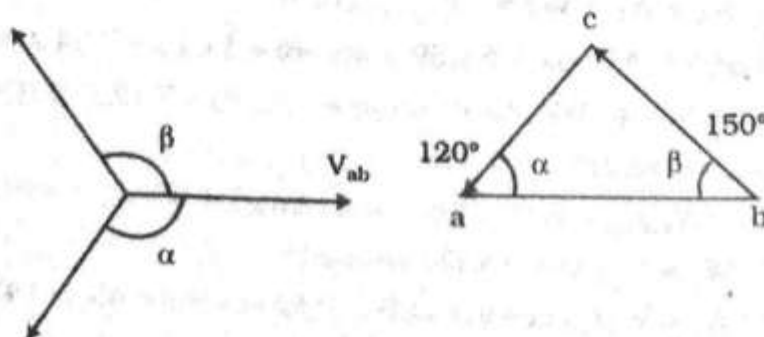

Here, $\cos \alpha = \frac{200^2 + 120^2 - 150^2}{2 \times 200 \times 120}$

$\therefore \alpha = 48.35^\circ$

Since α is measured in the clockwise direction.

$\therefore \alpha = (180 - 48.35) = -131.65^\circ$, $\cos \beta = \frac{220^2 + 150^2 - 120^2}{2 \times 200 \times 150}$


$\therefore \beta = 36.71^\circ$

Since β is measured in the anticlockwise direction


$\beta = 180 - 36.71 = 143.29^\circ$

$\therefore V_{ab} = 200 \angle 0^\circ$, $V_{ca} = 120 \angle -131.65^\circ$, $V_{bc} = 150 \angle 143.29^\circ$

9.31

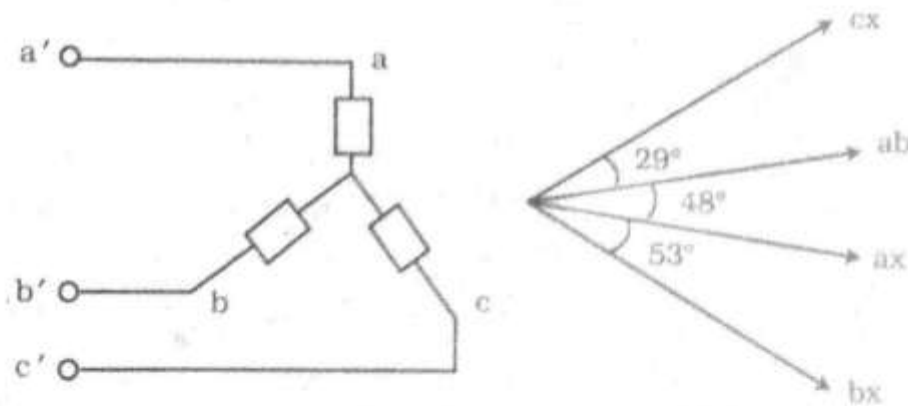

Since the voltage sequence is abc

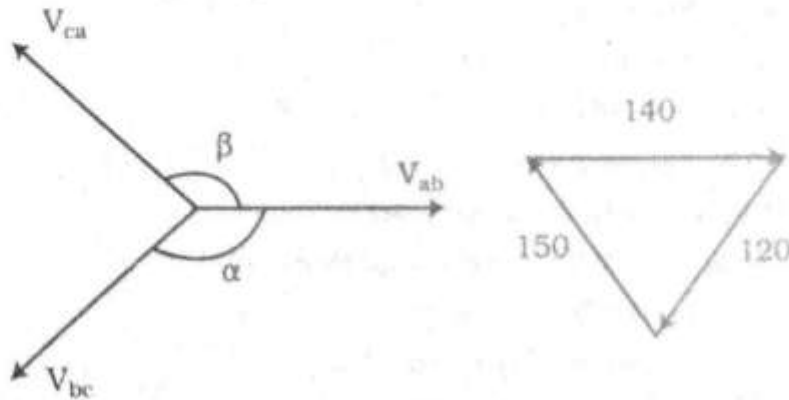


$\cos \alpha' = \frac{140^2 + 120^2 - 150^2}{2 \times 140 \times 120} \therefore \alpha = 70^\circ$

Since α is measured in the clockwise direction

$$\begin{aligned} \therefore \alpha &= -(180 - 70) = -110^\circ \\ \cos \beta &= \frac{140^2 + 150^2 - 120^2}{2 \times 140 \times 150} \\ \therefore \beta &= 48.74^\circ \\ \therefore \beta &= 180 - 48.74 = 131.26^\circ \\ \therefore V_{ab} &= 140 \angle 0^\circ \\ V_{bc} &= 120 \angle -110^\circ \\ V_{ca} &= 150 \angle 131.26^\circ \end{aligned}$$

Let,
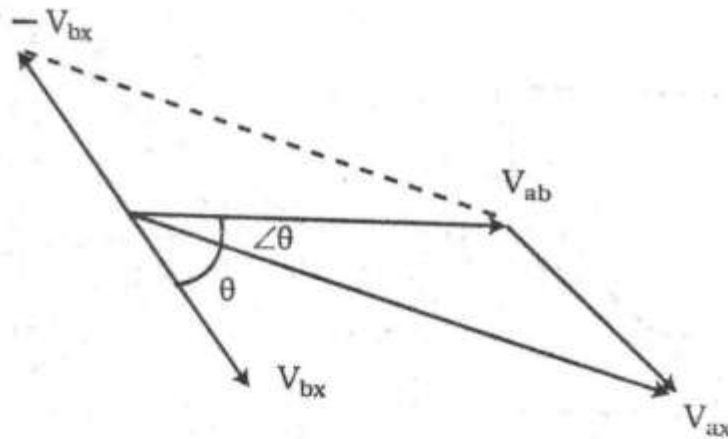
$$\begin{aligned} V_{an} &= 200 \angle 0, V_{bn} = 80 \angle \phi \\ V_{cn} &= 104.2 \angle \tau \end{aligned}$$



Now, $V_{an} - V_{bn} = V_{ab}$

or, $200 \angle 0 - 80 \angle \phi = 140 \angle 0$

$\therefore 200 \cos \theta - 80 \cos \phi = 140 \dots\dots\dots (i)$

$200 \sin \theta - 80 \sin \theta = 0 \dots\dots\dots (ii)$

[Equating real and imaginary parts]

or, $10 \sin \theta = 4 \sin \phi$ [From equation (ii)]

or, $10^2 \sin^2 \theta = 16(1 - \cos^2 \theta)$

or, $10^2(1 - \cos^2 \theta) = 16(1 - \cos^2 \theta)$

or, $10^2 - 10^2 \cos^2 \theta = 16 - 16 \cos^2 \theta$

or, $16 \cos^2 \phi = 16 - 10^2 + 10^2 \cos^2 \theta = 10^2 \cos^2 \theta - 84$

From (i) $\Rightarrow 10 \cos \theta + 7 = 4 \cos \varphi$

or, $4 \cos^2 \varphi = (10 \cos \theta + 7)^2$

So, $10^2 \cos^2 \theta - 84 = 100 \cos^2 \theta + 2 \times 10 \times 7 \cos \theta + 49$

or, $10^2 \cos^2 \theta = 100 \cos^2 \theta + 140 \cos \theta + 49 + 84$

or, $\cos \theta = \frac{133}{140} = 0.95$

$\therefore \theta = 18.1948$

From (ii) $200 \sin(-18.2) = 80 \sin \varphi$

$\varphi = -51.34^\circ$

Again,

$V_{bn} - V_{cn} = V_{bc}$

$\therefore 80 \sin \varphi - 104.2 \sin \sigma = -112.76$


or, $\sigma = 28.9^\circ$

$\therefore V_{an} = 200 \angle -18.2^\circ$


$V_{bn} = 80 \angle -51.34^\circ$

$V_{cn} = 104.2 \angle 28.9^\circ$

9.32

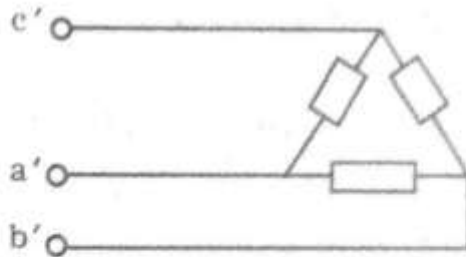

$I_{a'c} + I_{b'b} + I_{c'c} = 0$

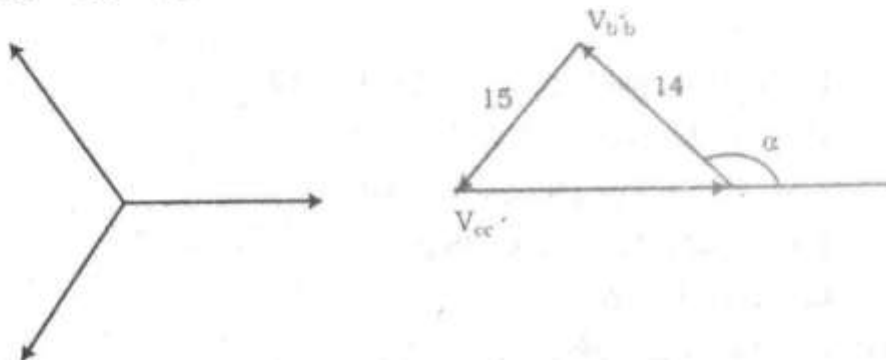

$$I_{a'a} = 20, I_{b'b} = 14, I_{c'c} = 15$$

Let us first take $I_{a'a}$ as reference

$$\therefore \cos \alpha' = \frac{20^2 + 14^2 - 15^2}{2 \times 20 \times 14}$$

$$\begin{aligned} \therefore \alpha &= 48.5^\circ \\ &= 180^\circ - 48.5^\circ \\ &= 131.5^\circ \end{aligned}$$

$$\cos \beta' = \frac{20^2 + 15^2 - 14^2}{2 \times 20 \times 15}$$

$$\begin{aligned} \therefore \beta' &= 44.36^\circ \\ \therefore \beta &= -180^\circ + 44.36 = -135.64 \end{aligned}$$

$$\therefore I_{a'a} = 20 \angle 0, I_{b'b} = 14 \angle 131.5^\circ, I_{c'c} = 15 \angle -135.64^\circ$$

$$\text{Let, } I_{ab} = 12 \angle \theta, I_{bc} = 2 \angle \phi, I_{ca} = 15 \angle r \quad I_{ab} - I_{ca} = I_{a'a}$$

$$\text{or, } 12 \angle \theta - 15 \angle r = 20 \angle 0$$

$$\text{or, } 12 \cos \theta - 15 \cos r = 20 \dots\dots\dots (i)$$

$$12 \sin \theta - 15 \sin r = 0 \dots\dots\dots (ii)$$

$$\Rightarrow 15^2 \cos^2 r = 15^2 - 12^2 + 12^2 \cos^2 \theta$$

From (i)

$$\Rightarrow 12^2 \cos^2 \theta - 24 \times 20 \cos \theta + 20^2 = 15^2 - 12^2 + 12^2 \cos \theta$$

$$\therefore \theta = -48.35^\circ$$

From (ii)

$$\Rightarrow 12 \sin(-48.35) = 15 \sin r$$

$$\therefore r = -143.29$$

Again,

$$I_{bc} - I_{ab} = I_{b'b} \text{ or, } 2 \angle \phi - 12 \angle \theta = 14 \angle 131.5$$

$$\therefore 2 \cos \phi - 12 \cos \theta = -9.277$$

$$\therefore 2 \cos \phi = -9.277 + 12 \cos(48.35)$$

$$\therefore \phi = 130.62 \therefore I_{ab} = 12 \angle -48.35^\circ$$

$$\therefore I_{bc} = 2 \angle 130 : 62$$

$$\text{and } I_{ca} = 15 \angle -143.29^\circ$$

Now transferring the reference from $I_{a'a}$ to I_{ab} by adding 48.35° we have—

$$I_{a'a} = 20 \angle 48.35^\circ, I_{b'b} = 14 \angle 179.85^\circ$$


$$I_{c'c} = 15 \angle -87.29^\circ, I_{ab} = 12 \angle 0^\circ$$

$$I_{bc} = 2 \angle 179^\circ, I_{ca} = 15 \angle -94.95^\circ$$

9.33 Same as problem 16.

9.34 More or less same as example 13.

9.35

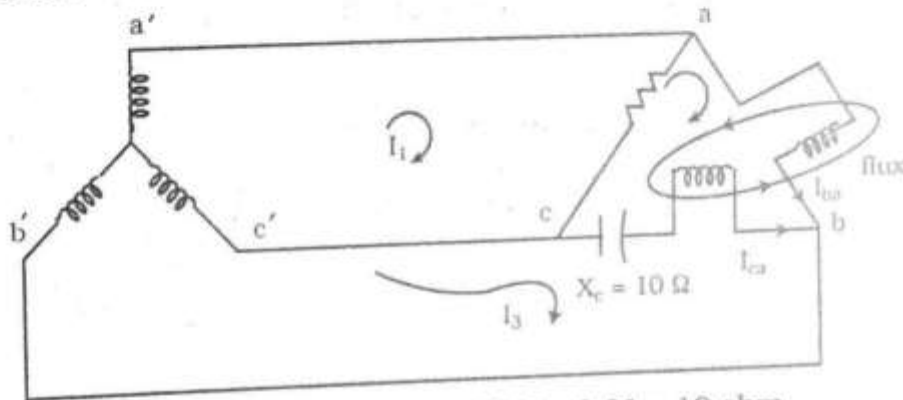

$$L_{ab} = L_{cb} = 0.01 \text{ H}, X_{Lab} = X_{Lcb} = 1000 \times 0.01 = 10 \text{ ohm}$$

$$X_M = 0.5 \sqrt{10 \times 10} = 5 \text{ ohm}$$

The loop equations are

$$10 I_1 - 10 I_2 = 57.7 \angle 90^\circ - 57.7 \angle 210^\circ$$

$$\text{or, } I_1 - I_2 = 10 \angle 60^\circ \dots\dots\dots (i)$$

$$-10 I_1 + \{10 + j(10 + 10 + 5 + 5)\} I_2 - j(10 - 10 + 5) I_3 = 0$$

$$\text{or, } -10 I_1 + 22.36 \angle 63.43^\circ I_2 + 5 \angle -90^\circ I_3 = 0 \dots\dots\dots (ii)$$

$$-j(10 - 10 + 5) I_2 + (j10 - j10) I_3 = 57.7 \angle 210^\circ - 57.7 \angle -30^\circ$$

$$\text{or, } 5 \angle -90^\circ I_2 = 100 \angle 180^\circ \dots\dots\dots (iii)$$

$$\therefore I_2 = 20 \angle 270^\circ$$

$$= 20 \angle -90^\circ$$

$$\text{From (i) } I_1 = 10 \angle 60^\circ + 20 \angle -90^\circ = 5 + j8.66 + 0 - j20$$

$$= 12.39 \angle -66.21^\circ$$

202 The Solution of Alternating Current Circuits

From (ii) $5 \angle -90^\circ I_3$

$$= 10 \times 12.39 \angle -66.21 - (22.36 \angle 63.43) \times (20 \angle -90^\circ)$$

$$= 50 - j113.37 - 400 + j200 = 360.56 \angle 166.1$$

$$\therefore I_3 = 72.11 \angle 256.1^\circ$$

The line currents are

$$I_{a'a} = I_1 = 12.39 \angle -66.21^\circ, I_{b'b} = -I_3$$

$$= -72.11 \angle 256.1 = -72.11 \angle 76.1$$

$$I_{c'c} = I_3 - I_1 = 17.32 - j70 - 5 + j11.34 = 62.76 \angle -110.83^\circ$$

The phase currents are - $I_{ac} = I_1 - I_2$

$$= 5 - j11.34 + j20 = 10 \angle 60^\circ$$


$$I_{cb} = I_3 - I_2 = 72.11 \angle 256.1 + j20 = -17.32 - j70 + j20$$

$$= 52.91 \angle -109.1$$

$$\therefore I_{ba} = -I_2 = -20 \angle -90^\circ = 20 \angle 90^\circ$$

36. Similar to 35.

37.

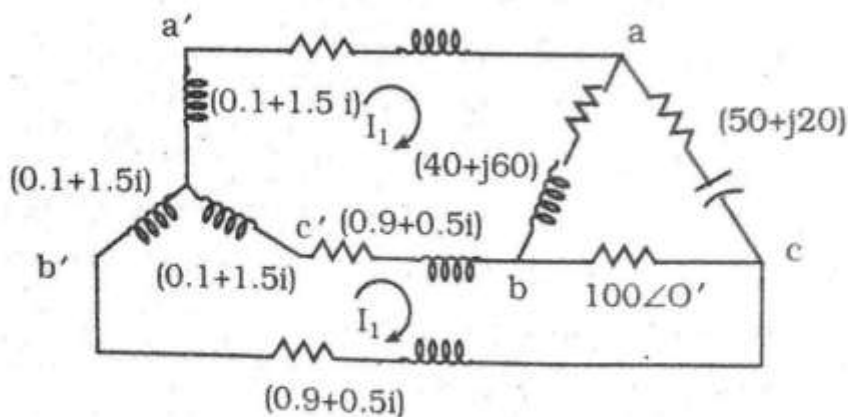

$$Z_{ab} = 40 + j60$$

$$Z_{bc} = 100$$

$$Z_{ca} = 50 - j20$$

$$Z_{a'n} = 0.1 + 1.5j = Z_{b'n} = Z_{c'n}$$

Since only two + loop current is necessary.

$$-E_{an} + E_{bn} + (0.9 + 0.5j + 0.9 + 0.5j) I_1 + (-0.9 - 0.5j) I_2 - 0.1 - 1.5j + 40 + j60 + 2 \times (0.1 + 1.5j) = 0$$

$$(2 + 44.6j) I_1 + (-1 - 2j) I_2 = E_{an} - E_b = 1350 \angle 0 - 675 - j1170$$

$$= 675 - 1170j$$

$$(2 + 44.6j) I_1 + (-1 - 2j) I_2$$

$$\text{and, } +E_{cn} - E_{bn} + (0.9 + 0.5j + 0.9 + 0.5j + 100 + 2 \times (0.1 + 1.5j) I_2 + (-0.9 - 0.5j - 0.1 - 1.5j) I_1 = 0$$

$$(102 + 4j) I_2 + (-1 - 2j) I_1 = E_{bn} - E_{cn}$$

$$= -675 - 1170j - (-675 + 1170j)$$

$$= -675 - 1170j + 675 - 1170j$$

$$= -2 \times 1170j = -2340j$$

$$\text{So } (2 + 44.6j) I_1 + (-1 - 2j) I_2 = 675 - 1170j$$

$$(102 + 4j) I_2 + (-1 - 2j) I_1 = -2340j$$

Solve this equation hence find out I_1 and I_2 .

[Tips : In complex mode normal scientific calculator does not operate in equation solving but how can we do that ? Simple click **CALC** button after making equation for 2×2 Matrix like (AB - CM) parameters in

Chapter-11
Electric Wave Filters


11.1 Here,

$$L_1 = 0.047 \text{ H} \quad : \quad Z_{OT} = ?$$

$$R_1 = 0 \quad : \quad \text{at } 50 \text{ cycle}$$

$$C_2 = 300 \mu\text{f} \quad : \quad \text{at } 100 \text{ cycle}$$
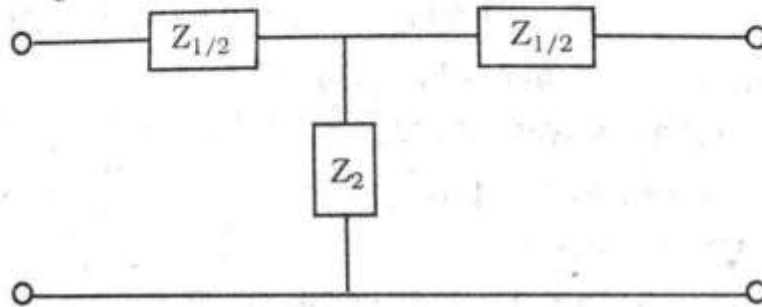
$$Z_{1/2} = 0 + j2\pi fL_1 = 0 + j2\pi \times 50 \times 0.0477 \angle 90^\circ$$



$$\therefore Z_1 = 29.54 \angle 90^\circ$$

$$Z_2 = \frac{1}{j\omega C_2} = \frac{10^6}{j2\pi \times 50 \times 300} = 10.61 \angle -90^\circ$$

$$Z_1 Z_2 = 29.54 \angle 90^\circ \times 10.61 \angle -90^\circ = 313.42 \angle 0^\circ = 313.42 + j0$$


$$Z_1^2/4 = \frac{(29.54 \angle 90^\circ)^2}{4} = 218.153 \angle 180^\circ = -218.153$$

$$Z_{OT} = \sqrt{Z_1 Z_2 + Z_1^2/4} = \sqrt{313.42 + j0 - 218.153 + j0}$$

$$= 95.267 \angle 0^\circ = 9.76 \angle 0^\circ$$

$$\therefore Z_{OT} = 9.76 \angle 0 \text{ ohm}$$

11.2 Similarly find Z_{OT} at 100 Hz.

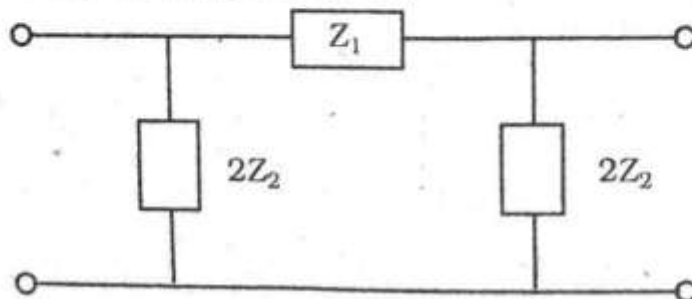

at 200 Hz

$$Z_1 = j\omega L_1 = j2\pi \times 200 \times 0.02 = 25.13 \angle 90^\circ$$

$$2Z_2 = \frac{1}{j\omega C_2/2} = -j \frac{1}{2\pi f C_2/2} = \frac{j \times 10^6}{2 \times 200 \times 2} = 397.89 \angle -90^\circ$$


$$\therefore Z_2 = 198.94 \angle -90^\circ$$

$$\begin{aligned} \text{Now, } 1 + \frac{Z_1}{4Z_2} &= 1 + \frac{25.13 \angle 90^\circ}{4 \times 198.94 \angle 90^\circ} = 1 + 0.0315 \angle 180^\circ \\ &= 0.9685 \angle 0^\circ \end{aligned}$$

$$\therefore Z_1 Z_2 = 4999.36 \angle 0^\circ$$

$$Z_{0\pi} = \sqrt{\frac{Z_1 Z_2}{1 + Z_1/4Z_2}} = \sqrt{\frac{4999.36 \angle 0^\circ}{0.9685 \angle 0^\circ}} = 71.85 \angle 0^\circ$$

11.3

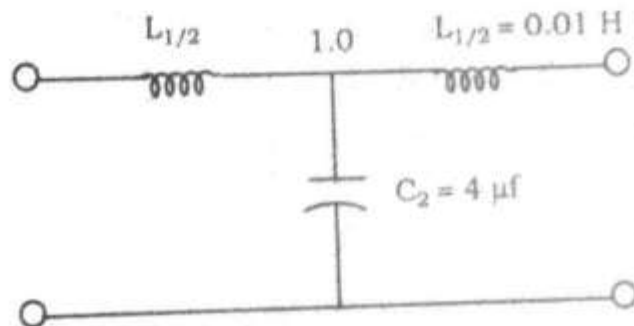

$$Z_{1/2} = j\omega L_{1/2} = j \times 2\pi \times 200 \times 0.01 = 12.57 \angle 90^\circ \text{ ohm}$$

$$\therefore Z_1 = 25.14 \angle 90^\circ \text{ ohm}$$

$$\therefore Z_2 = \frac{1}{j\omega C_2} = \frac{10^6}{j \times 2\pi \times 200 \times 4} = 108.94 \angle -90^\circ \text{ ohm}$$

$$Z_{oc} = \frac{Z_1}{2} + Z_2 = 12.57 \angle 90^\circ + 198.94 \angle -90^\circ$$

$$Z_{oc} = 186.37 \angle -90^\circ$$


$$Z_{sc} = \frac{Z_{1/2} \times Z_2}{Z_{1/2} + Z_2} + Z_{1/2} = \frac{j12.57 \times -j198.94}{j12.57 - j198.94} + j12.57 \angle 90^\circ$$

$$= \frac{2500.6758}{186.37 \angle -90^\circ} + j12.57 = 25.99 \angle 90^\circ$$

$$\therefore Z_{sc} = 26 \angle +90^\circ \text{ ohm}$$

$$Z_{\pi} = \sqrt{Z_{oc} Z_{sc}} = 69.61 \angle 0^\circ \text{ ohm}$$

11.4

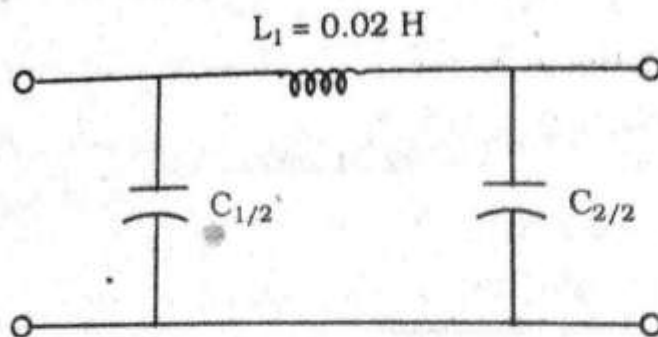

$$Z_1 = j\omega L_1 = j \times 2\pi \times 200 \times 0.02 = 25.13 \angle 90^\circ$$

$$\therefore Z_1 = 25.13 \angle 90^\circ \text{ ohm}$$

$$2Z_2 = \frac{1}{j\omega C_{2/2}} = \frac{j \times 10^6}{2\pi \times 200 \times 2.0} = 397.89 \angle -90^\circ$$


$$\therefore Z_2 = 198.94 \angle -90^\circ \text{ ohm}$$

$$Z_{ac} = \frac{Z_1 \times 2Z_2}{Z_1 + 2Z_2} = \frac{(j25.13) \times (-j397.89)}{j25.13 - j397.83}$$

$$\begin{aligned} \therefore Z_{sc} &= \frac{(2Z_2 + Z_1) \times 2Z_2}{Z_1 + 4Z_2} \\ &= \frac{-j372.76 \times -j397.89}{j25.13 - j795.76} = 196.46 \angle -90^\circ \end{aligned}$$

$$Z_{oc} = 192.49 \angle -90^\circ$$

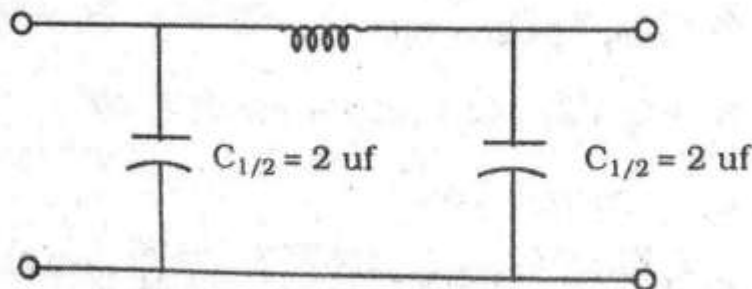11.5 $Z_{on} = \sqrt{Z_{oc}Z_{sc}} = 71.85 \angle 0^\circ \Omega$



at 200 Hz

$$Z_1 = j\omega L_1 = 2\pi \times 200 \times 0.02j = j25.13, \quad 2Z_2 = \frac{-j}{2\pi f C_{2/2}}$$

$$\text{or, } = \frac{-j \times 10^6}{2\pi \times 200 \times 2} = -j397.09$$

$$\text{Now, } 1 + Z_1/4Z_2 = 1 + \frac{25.13 \angle 0}{2 \times 307.89 \angle -90^\circ}$$

$$= 1 - 0.04j = 1 \angle 2.336$$

$$Z_1 Z_2 = (25.13 \angle 90) (-j397.89) = 9998.9757 \angle 0^\circ$$

$$Z_{OT} = \sqrt{Z_1 Z_2} = 99.994 \text{ ohm}$$


$$\text{Now, } \frac{I_1}{I_2} = \frac{2Z_2 + Z_{OT}}{2Z_2 - Z_{OT}}$$

$$\frac{I_1}{I_2} = \frac{-j397.89 + 99.994}{-j397.89 - 99.994} = 1 \angle 28.213$$

$$\therefore I_1/I_2 = 1 \angle 28.213$$

For 2000 Hz, Similarly proceed

11.6

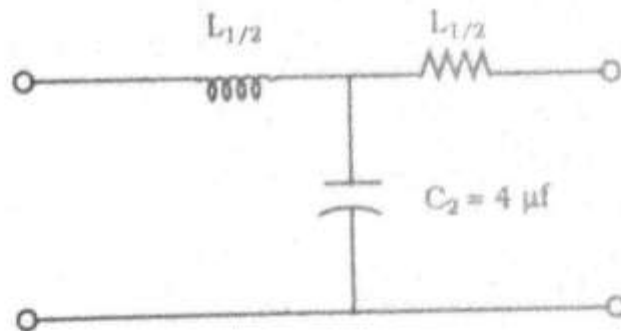

At 200 Hz

$$\frac{Z_1}{2} = 12.57 \angle 90^\circ \pi$$

$$Z_2 = 198.94 \angle -90^\circ \pi$$

$$Z_{OT} = 69.61 \angle 0^\circ \text{ ohm}$$

$$\frac{I_1}{I_2} = \frac{Z_{OT} + Z_{1/2}}{Z_{OT} - Z_{1/2}} = \frac{69.61 + j12.57}{69.61 - j12.57} = \frac{70.74 \angle 10.24}{70.74 \angle -10.24} = 1.0 \angle 20.48^\circ$$

$$\therefore I_1/I_2 = 1.11 \angle 113^\circ \Rightarrow I_1/I_2 = e^{\alpha + j\beta}$$

$$\therefore e^{(\alpha + j\beta)} = 1.11 \angle 113$$

$$\text{or, } e^\alpha \cdot e^{j\beta} = 1.11 \angle 113$$

$$\text{or, } e^\alpha = 1.11$$


$$\alpha = 0.1043 \text{ neper}$$

and $e^{\beta} = 0.6277$ [in radian]

$j\beta = (0.6277)$ logarith of e bare

Do yourself.

11.9

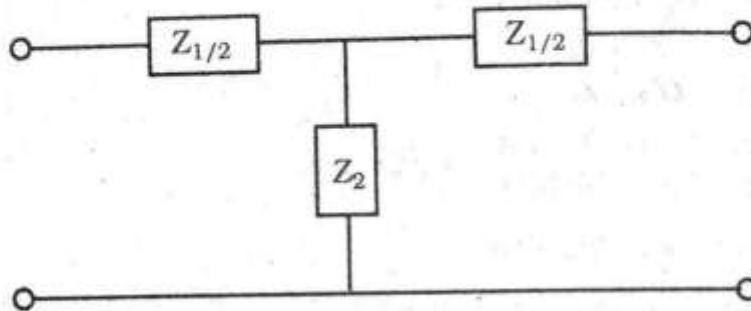

$$\frac{Z_1}{2} = -j 10^6 / \omega c_2 = \frac{-j \times 10^6}{1257 \times 7.96}$$

$$Z_2 = 4 + j\omega L_1 = 4 + j1257 \times 0.0159 = 20.38 \angle 76.6^\circ \Omega$$

$$\text{at } 200 \text{ Hz, } Z_1 = 200 \angle -90^\circ, Z_2 = 20.4 \angle 78.7^\circ$$

$$\frac{Z_1}{4Z_2} = \frac{200 \angle -90^\circ}{4 \times 20.4 \angle 78.7^\circ} = 2.45 \angle -168.7^\circ$$

$$\sqrt{\frac{Z_1}{4Z_2}} = 1.57 \angle -84.35^\circ = 0.15 - j1.56$$

$$1 + \frac{Z_1}{4Z_2} = 1 + 2.45 \angle -168.7^\circ = 1 - 2.40 - j0.48$$

$$= -1.4 - j0.48$$

$$= 1.48 \angle -161^\circ$$

$$\sqrt{1 + \frac{Z_1}{4Z_2}} = 1.22 \angle -80.54^\circ = 0.2 - j1.2$$

$$\therefore \sqrt{1 + \frac{Z_1}{4Z_2}} + \sqrt{\frac{Z_1}{4Z_2}} = 0.2 - j1.2 + 0.15 - j1.56$$

$$= 2.78 \angle -82.77^\circ$$

$$\therefore \alpha = 2.05 \text{ neper} = 2.05 \times 8.68 = 17.8063 \text{ db}$$

$$\text{and } \beta = 2.89 \text{ rad/sec}$$

11.10. Here $Z_1 = 200 \angle 90^\circ$, $Z_2 = 50 \angle -90^\circ$

$$\sqrt{\frac{Z_1}{4Z_2}} = \sqrt{\frac{200 \times 1 \angle 90^\circ}{200 \angle -90^\circ}} = 1 \angle 90^\circ$$

$$\sqrt{1 + \frac{Z_1}{4Z_2}} = \sqrt{1 + 1 \angle 180^\circ} = \sqrt{1 - 1} = 0$$

$$\text{Now, } \alpha + j\beta = 2 \log (1 \angle 80^\circ) = 2 \log e(1) + 2j \times \frac{90}{57.3}$$

$$\therefore \alpha + j\beta = 0 + j3.141$$

Hence $\alpha = 0$

$$\beta = 3.14 = \pi$$

11.11 $Z_1 = j\omega L_1$

$$Z_2 = \frac{1}{j\omega C_2}$$

$$\therefore \frac{Z_1}{4Z_2} = \frac{\omega^2 L_1 C_1}{4} \angle 180^\circ \text{ if } \omega = 1.5/\sqrt{L_1 C_2}$$

$$\therefore \frac{Z_1}{4Z_2} = \frac{-L_1 C_2}{4} \times \frac{1.5^2}{L_1 C_2} \times \frac{9^2}{L_1 C_2}$$

$$= 2.25 \angle 180^\circ \text{ ohm} = -2.25 \text{ ohm}$$

$$(a) \sqrt{\frac{Z_1}{4Z_2}} = \sqrt{0.5625 \angle 180^\circ} = 0.75 \angle 90^\circ$$

$$\therefore \sqrt{1 + \frac{Z_1}{4Z_2}} = \sqrt{1 - 0.5625 + j0}$$

$$= \sqrt{0.4375} \angle 0^\circ$$

$$= 0.6614 \angle 0^\circ$$

$$\therefore \alpha + j\beta = 2 \log [0.6614 + j0 + j0.75] = 2 \log [1 \angle 48.59]$$

$$= 2 \log 1 + j \frac{2 \times 48.59}{57.3} = 0 + j1.7$$

$$\therefore \alpha = 0, \beta = 1.7 \text{ rad}$$

$$11.12 \quad \frac{W_1}{W_2} = \frac{I_1^2}{I_2^2} = (e^{\alpha} \cdot e^{j\beta})^2 = e^{2\alpha} \cdot e^{j2\beta} = 1$$

$$\therefore \alpha = 0$$

Similarly proceed in the same way.

11.13 Given, $R_k = 600 \text{ k ohm}$, $f_c = 940 \text{ Hz}$

$$R_k^2 = \frac{L_1}{C_2} \quad F_c = \frac{1}{\pi \sqrt{L_1 C_2}} \quad \therefore C_2 = \frac{L_1}{R_k^2} = \frac{1}{\pi R_k f_c}$$

$$\therefore C_2 = \frac{L_1}{R_k^2} = \frac{1}{\pi \times 600 \times 940}$$


$$= \frac{1}{\pi \sqrt{\frac{L_1}{R_k^2} \times L_1}} = 0.564 \pi f$$

$$= \frac{R_k}{\pi L_1}$$


$$\therefore L_1 = \frac{R_k}{\pi f_c} = \frac{600}{\pi \times 940}$$

$$= 0.203 \text{ H}$$

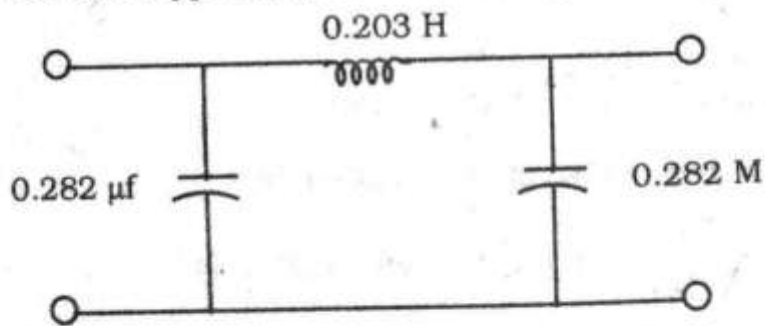\therefore T section K type low pass filter is diagram.



11.16

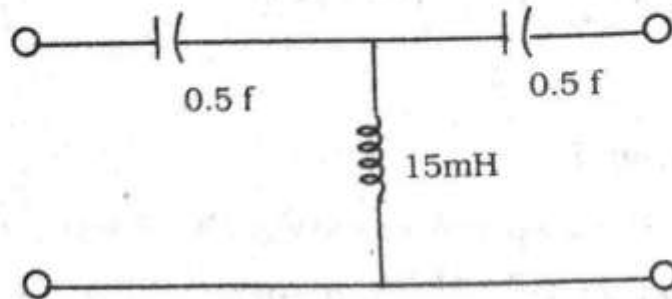


$$2C_{1K} = 1 \mu f : L_{2K} = 15 \text{ mH}$$

$$\therefore C_{1K} = 0.5 \mu f : = 0.015 \text{ H}$$

$$\therefore R_K = \sqrt{\frac{L_2 K}{C_{1K}}} = \sqrt{\frac{0.015}{0.5 \times 10^{-6}}} = 173.2 \text{ ohm}$$
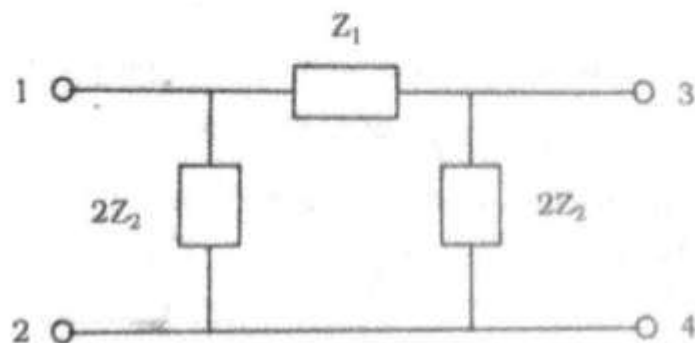
$$\begin{aligned} \therefore f_c &= \frac{1}{4\pi \sqrt{L_2 C_{1K}}} \\ &= \frac{1}{4\pi \sqrt{0.015 \times 0.5 \times 10^{-6}}} \\ &= 919 \text{ Hz} \end{aligned}$$



at 500 Hz

$$Z_1 = 50 + j2\pi \times 500 \times 100 \times 10^{-3} = 318.11 \angle 80.96^\circ$$

$$2Z_2 = -j \frac{10^6}{2\pi \times 500 \times 0.3} = 1061 \angle -90^\circ$$

$$\begin{aligned} \therefore Z_{oc} &= \frac{(Z_1 + 2Z_2) 2Z_2}{Z_1 + 2Z_2} \\ &= \frac{(50 + j314.16 - j1061) (1061 \angle -90^\circ)}{50 + j314 - j212} \\ &= \frac{794171.07 \angle -176.17^\circ}{1808.53 \angle -88.42^\circ} \end{aligned}$$

$$= 439.12 \angle -87.75^\circ$$


$$\begin{aligned} Z_{sc} &= \frac{Z_1 \cdot 2Z_2}{Z_1 + 2Z_2} \\ &= \frac{(318.11 \angle 80.96^\circ) (1061 \angle -90^\circ)}{50 + j314.16 - j1061} \\ &= \frac{337515.71 \angle -9.04^\circ}{748.51 \angle -86.17^\circ} \end{aligned}$$

$$(b) \text{ Characteristics impedance } Z_{on} = \sqrt{Z_{sc} Z_{oc}}$$

$$= 444.97 \angle -5.31^\circ$$

Similar calculation for other cycles.

11.18

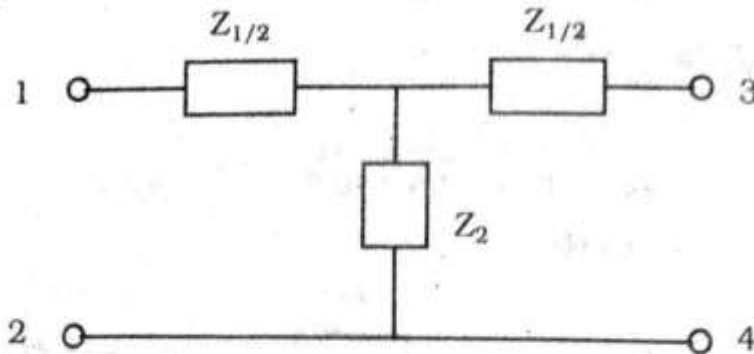

$$(a) \frac{Z_1}{2} = -j \frac{10^6}{2\pi \times 200 \times 0.6} = 2652.53 \angle -90^\circ$$

$$Z_2 = j\omega L + R = 60 + j251.33 = 258.4 \angle 76.57^\circ$$

$$\therefore \frac{Z_1}{4Z_2} = \frac{2652.58 \angle -90^\circ}{4 \times 258.4 \angle 76.57^\circ} = 2.566 \angle -166.57^\circ$$

$$\begin{aligned} \text{Characteristics impedance } Z_{OT} &= \sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4Z_2}\right)} \\ &= 1050.55 \angle -85.35^\circ \end{aligned}$$

Propagation constant is γ

$$\begin{aligned} \gamma &= \alpha + j\beta = 2 \log_e \left\{ \sqrt{1 + \frac{Z_1}{4Z_2}} + \sqrt{\frac{Z_1}{4Z_2}} \right\} \\ &= 2 \log_e \left\{ \sqrt{1 - 2.496 - j0.596} + \sqrt{2.566 \angle -166.57^\circ} \right\} \\ &= 2 \log_e \{1.269 \angle -79.14^\circ + 1.6 \angle -33.235^\circ\} \\ &= 2 \log_e \{0.239 - j1.25 + 0.187 - j1.589\} \\ &= 2 \log_e \{2.871 \angle -81.47^\circ\} \end{aligned}$$

$$\therefore \alpha = 2.11 \text{ neper and } \beta = -162.94^\circ$$

11.19 When the output terminals open circuited—

$$R = 10 \text{ ohm, } L = -190 \times 10^{-3} \text{ H, } Z_{oc}$$

$$= 10 + j2\pi \times 400 \angle -190 \times 10^{-3}$$


$$= 10 - j477.52 = 477.63 \angle -88.8^\circ$$

$$\text{Similarly, } Z_{sc} = 20 + j2\pi \times 400 \times (250 \times 10^{-3})$$

$$= 628.64 \angle 88.2^\circ$$

$$\therefore Z_{OT} = \sqrt{Z_{oc} Z_{sc}} = 547.96 \angle -0.3^\circ$$

11.20

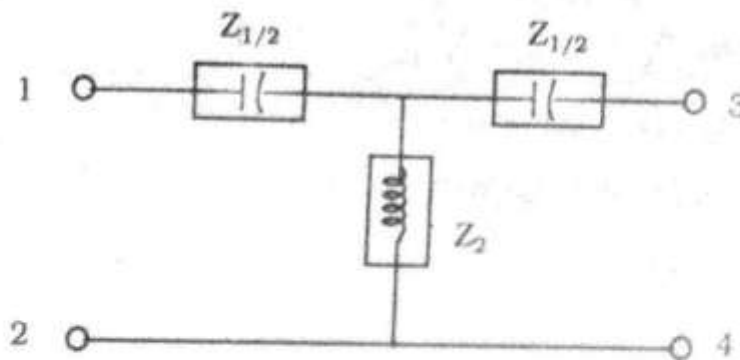

(a) $\frac{Z_1}{2} = -j100$

$\therefore Z_1 = 200 \angle -90^\circ$

$Z_2 = j100 = 100 \angle 90^\circ$

$$Z_{OT} = \sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4Z_2}\right)} = \sqrt{Z_1 Z_2 + \frac{Z_1^2}{4}}$$

$$= \sqrt{(200 \angle -90^\circ)(100 \angle 90^\circ) + \left(\frac{200 \angle 90^\circ}{4}\right)^2}$$

$$= \sqrt{20000 - 10000} = 100 \angle 0$$

(b) At half frequency - $Z_1 = -j400 = 400 \angle -90^\circ$

$Z_2 = 50 \angle 90^\circ$

$$Z_{OT} = \sqrt{(50 \angle 90^\circ)(400 \angle -90^\circ) + (400 \angle -90^\circ)^2}$$

$$= \sqrt{20000 - 400000} = 141.42 \angle -90^\circ$$

(For high filter (i.e. if C is in series arm) phase shift will be negative)

(c) $\frac{Z_1}{4Z_2} = \frac{-j200}{4 \times j100} = 0.5$ since $0 \geq \frac{1}{4Z_2} \geq -1$

\therefore The frequency is within the pass band

(d) $\frac{Z_1}{4Z_2} = \frac{-j400}{4 \times j50} = -2$ since $\frac{Z_1}{4Z_2} < -1$

\therefore The frequency is within the stop band

$$\begin{aligned}
 \text{(e) } r &= 2 \log_e \left\{ \sqrt{1 + \frac{Z_1}{4Z_2}} + \sqrt{\frac{Z_1}{4Z_2}} \right\} \text{ or } \alpha + j\beta \\
 &= 2 \log_e \{ \sqrt{1 - 0.5} + \sqrt{-0.5} \} \\
 &= 2 \log_e (0.707 + j0.707) \\
 &= 0 + j90^\circ
 \end{aligned}$$

$$\therefore \alpha = 0$$

$$\beta = \frac{\pi}{2} \text{ rad}$$

$$\text{For half frequency } r = 2 \log \{ \sqrt{1 - 2} + \sqrt{-2} \}$$

$$\therefore \alpha = 1.76 \text{ and } \beta = -\pi \text{ rad}$$

(f) From (a) & (b) We can say that the characteristics impedance in the pass band is pure resistive and in the attenuation band (i.e. Stop band) is pure reactive.

(9) Yes.

$$11.21 \quad R_K = \sqrt{\frac{L_{1K}}{C_{2K}}} \text{ or, } C_{2K} = \frac{L_{1K}}{R_K^2}$$

$$f_{0\pi} = \frac{1}{\pi \sqrt{L_{1K} C_{2K}}}$$

$$\pi = \frac{1}{\pi \sqrt{L_{1K} \frac{L_{1K}}{R_K^2}}}$$

$$L_{1K} = \frac{R_K}{\pi f_{c1}}$$

$$= \frac{800}{\pi \times 10}$$

$$= 0.0255 \text{ H}$$

$$C_{1K} = \frac{L_{1K}}{R_K^2}$$


$$= \frac{0.0255}{(800)^2}$$

$$= 3.98 \times 10^{-8} \text{ Farad}$$

1000, 4000, 7000, 10,000 Hz are within pass band phase

$$\text{Shift } \beta = \cos^{-1} \left(1 + \frac{Z_1}{2Z_2} \right)$$

Now

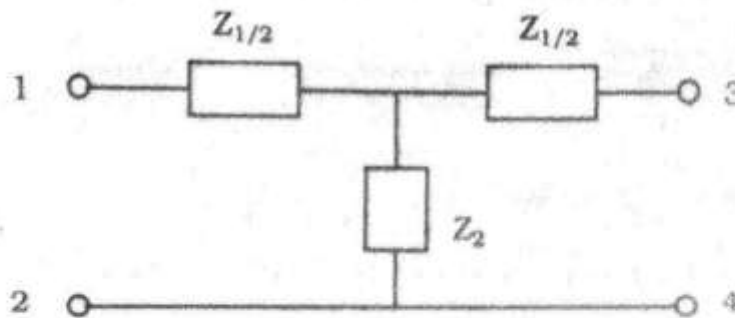

Now, $Z_1 = j2\pi \times f \times 0.0255 = -j0.1602f$, Z_2

$$= -j \frac{1}{2\pi f \times 0.04 \times 10^{-6}}$$

$$= -j3.98 \times 10^6$$


$$\therefore \frac{Z_1}{2Z_2} = \frac{j0.1602f}{2 \left(\frac{-j3.98 \times 10^6}{f} \right)} = -2.013 \times 10^{-8} f^2$$

$$\therefore \beta_{1000} = \cos^{-1} [1 - 2.013 \times 10^{-8} \times 10^6] = 11.5^\circ$$

$$\beta_{400} = 47.32^\circ, \beta_{7000} = 39.2^\circ, \beta_{10,000} = 180^\circ$$

Attention $\alpha = \cos^{-1} \left(-1 - \frac{Z_1}{2Z_2} \right)$. find your self.

11.22

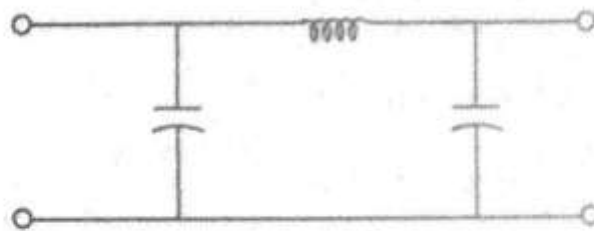

Here $Z_1 = j\omega L_1 = (2\pi f L_1) j = j \times 2\pi \times f \times 0.1$

$$\therefore Z_1 = j628f$$

and $c_1 = \frac{c}{2}$

$$\therefore 2Z_2 = \frac{-1}{2\pi f c_1} = \frac{-1 \times 10^6}{2\pi f \times 0.3} = \frac{-j530516.48}{f}$$

$$\therefore Z_2 = \frac{-j265258.24}{f}$$

$$\text{Now, } \sqrt{\frac{Z_1}{4Z_2}} = \sqrt{5.92 \times 10^{-7} f^2 \angle 180^\circ} = 7.694 \times 10^{-4} f \angle 90^\circ$$

$$\sqrt{1 + \frac{Z_1}{4Z_2}} = \sqrt{1 + 5.92 \times 10^{-7} f^2 \angle 180^\circ}$$

$$\text{We know, } \alpha + j\beta = 2 \log_e \left(\sqrt{1 + \frac{Z_1}{4Z_2}} + \sqrt{\frac{Z_1}{4Z_2}} \right)$$

$$\therefore \alpha + j\beta = 2 \log_e (\sqrt{1 + 5.92 \times 10^{-7} f^2 \angle 180^\circ} + 7.694 \times 10^{-4} f \angle 90^\circ)$$

At 500 Hz

$$\alpha + j\beta = 2 \log_e (\sqrt{1 + 5.92 \times 10^{-7} \times (500)^2 \angle 180^\circ} + 7.694 \times 10^{-4} \times 500 \angle 90^\circ)$$

$$\alpha + j\beta = 2 \log_e (0.923 + j0.3847)$$

$$\alpha = 0 \text{ and } \beta = 0.79 \text{ rad} = 45.26^\circ$$

For others similar way.

$$11.23 \text{ (a) Decibel} = 10 \log_{10} \frac{W_{\text{general}}}{W_{\text{reference}}}$$

$$\Rightarrow \text{dB} = 10 \log_{10} \frac{0.00001}{1 \times 10^{-3}} = -20 \quad \boxed{\text{dB} = 20}$$

$$\text{(b) dB} = 10 \log_{10} \frac{W_{\text{general}}}{W_{\text{reference}}} = 10 \log_{10} \frac{6}{1 \times 10^{-3}}$$

$$\boxed{\text{dB} = 37.78}$$

$$11.24 \text{ Here } L_{1K} = 20H \frac{C_{2K}}{2} = 8\mu f \therefore C_{2K} = 16 \times 10^{-6} f$$

We know for low pass filter—

$$f_c = \frac{1}{\pi \sqrt{L_{1K} C_{2K}}} = \frac{1}{\pi \sqrt{20 \times 16 \times 10^{-6}}} = 17.79 \text{ Hz}$$

$$\therefore f_c = 17.79 \text{ Hz}$$


at 200 Hz

$$Z_{1K} = j2\pi L_{1K} f = j2\pi \times 200 \times 20 = 25132.74 \angle 90^\circ \text{ ohm}$$

$$2Z_{2K} = \frac{-j \times 10^6}{2\pi f \times 8} = 99.4 \angle -90^\circ \quad Z_{2K} = 49.74 \angle -90^\circ$$

$$\text{Now, } Z_{\text{onk}} = \sqrt{\frac{Z_{1K} Z_{2K}}{\left(1 + \frac{Z_{1K}}{4Z_{2K}}\right)}} = \sqrt{\frac{1250102.488 \angle 0}{1 + 126 \angle 180^\circ}} = 99.87j$$

11.25

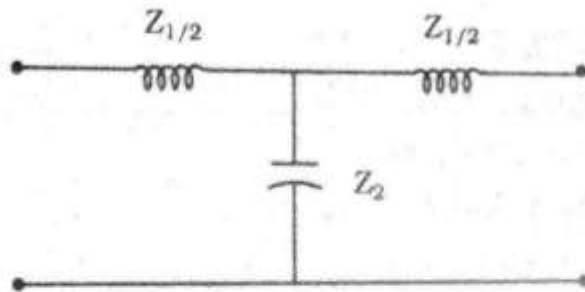

$$Z_{1/2} = j100$$

$$Z_1 = 200 \angle 90^\circ$$

$$Z_2 = -j1000$$

$$= 1000 \angle -90^\circ$$

$$\therefore \frac{Z_1}{4Z_2} = \frac{200 \angle 90^\circ}{4 \times 1000 \angle -90^\circ} = 0.05 \angle 180^\circ = -0.05$$

$$Z_{OT} = \sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4Z_2} \right)}$$

$$= \sqrt{(200 \angle 90^\circ) (1000 \angle -90^\circ) (1 - 0.05)}$$

$$= 435.89 \angle 0^\circ$$

$$r = 2 \log_e \left\{ \sqrt{1 + \frac{Z_1}{4Z_2}} + \sqrt{\frac{Z_1}{4Z_2}} \right\}$$

$$\therefore \alpha + j\beta = 2 \log_e \{ \sqrt{0.05} + \sqrt{0.05} \}$$

$$= 2 \log_e \{ 0.97468 + j0.2236 \}$$

$$= 2 \log_e \{ 1 \angle 12.92^\circ \}$$

$$= 0 + j25.84^\circ$$

$$\therefore \alpha = 0, \beta = 25.84^\circ$$

(c) Since alternation zero

\therefore The frequency is within the pass band.


(d) For 5 times frequency $Z_1 = 1000 \angle 90^\circ$, $Z_2 = 200 \angle -90^\circ$

$$\therefore \frac{Z_1}{4Z_2} = \frac{1000 \angle 90^\circ}{4 \times 200 \angle -90^\circ} = 1.25 \angle 180^\circ = -1.25$$

$$\begin{aligned} \therefore Z_{OT} &= \sqrt{(1000 \angle 90^\circ)(200 \angle -90^\circ)(1 - 1.25)} \\ &= 2 \log_e \{j0.5 + j1.110\} \\ &= 2 \log_e \{1.618 \angle 90^\circ\} \\ &= 0.96238 + j180^\circ \end{aligned}$$

$$\therefore \alpha = 0.96238 \text{ Neper}$$

$$\text{Phase shift } \beta = \pi \text{ rad}$$

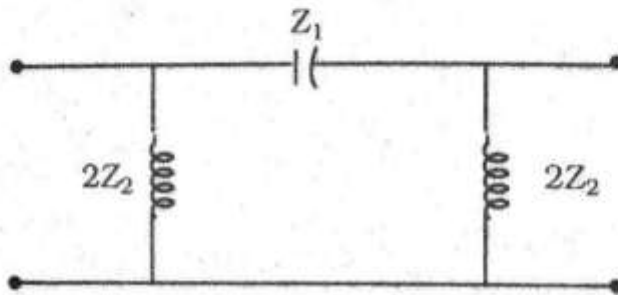11.26


$$Z_1 = -j100 = 100 \angle -90^\circ$$

$$2Z_2 = j500$$

$$\therefore Z_2 = 250 \angle 90^\circ = -j250$$

$$\frac{Z_1}{4Z_2} = \frac{100 \angle -90^\circ}{4 \times 250 \angle 90^\circ} = 0.1 \angle -180^\circ = -0.1$$

$$\begin{aligned} \text{(a) } Z_{OT} &= \sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4Z_2}\right)} \\ &= \sqrt{100 \angle -90^\circ (250 \angle 90^\circ) / (1 - 0.1)} \\ &= 166.667 \angle 0^\circ \end{aligned}$$


$$\text{(b) } r = \alpha + j\beta = 2 \log_e \left\{ \sqrt{1 + \frac{Z_1}{4Z_2}} + \sqrt{\frac{Z_1}{4Z_2}} \right\}$$

$$\begin{aligned} \therefore \alpha + j\beta &= 2 \log_e \{ \sqrt{1 - 0.1} + \sqrt{-0.1} \} \\ &= 2 \log_e \{0.94868 - j0.31628\} \\ &= 2 \log_e \{1 \angle -18.435^\circ\} \\ &= 0 - j36.87^\circ \end{aligned}$$

$$\therefore \alpha = 0, \beta = 36.87^\circ$$

(c) Since alternation is zero. The reactances given are at pass band.

11.27

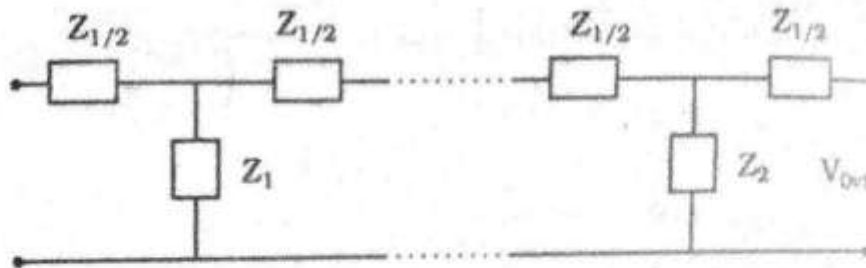

$$\alpha + j\beta = 2 \log_e \sqrt{\frac{Z_1}{4Z_2} + 1} + \sqrt{\frac{Z_1}{4Z_2} + 1}$$

$$\frac{Z_1}{4Z_2} = \frac{j500 \times 2}{4 \times -j200} = -1.25$$

$$\therefore \alpha + j\beta = 2 \log_e (\sqrt{-1.25 + 1} + \sqrt{-1.25 + 1})$$

$$= 2 \log_e (1.118j + 0.5j)$$

$$= 2 \log_e (1.618 \angle 90^\circ)$$

$$\alpha + j\beta = 2 \log_e 1.618 + j90^\circ$$

$$\therefore \alpha = 0.962$$

$$\beta = 90^\circ$$

So, at ninth section = $\alpha^9 = 0.708$

So, output voltage = $(1 - 0.708) \times 100 = 29.18$ volt.

11.28

$$f_c = 5000 \text{ Hz}$$

$$R_k = 600 \text{ ohms}$$

$$\text{So, } \sqrt{\frac{L_{2k}}{C_{1k}}} = R_k = 600 \text{ ohm}$$

$$\therefore L_{2k} = 600^2 \times C_{1k}$$

$$\text{and } C_{1k} = \frac{1}{4\pi \times 600 \times f_c}$$

$$= \frac{1}{4\pi \times 600 \times 5000}$$

$$= 2.65 \times 10^{-8} \text{ f}$$

So find L_{1k} yourself.

11.29 Do yourself

11.30 $f_c = 5000 \text{ Hz}$

$R_k = 600 \text{ oh}$


$f_\infty = 4500 \text{ Hz}$

for low pass,

$$m = \sqrt{1 - \left(\frac{5000}{4500}\right)^2} = 0.484 j$$

and $L_{1k}C_{2k} = 600^2$

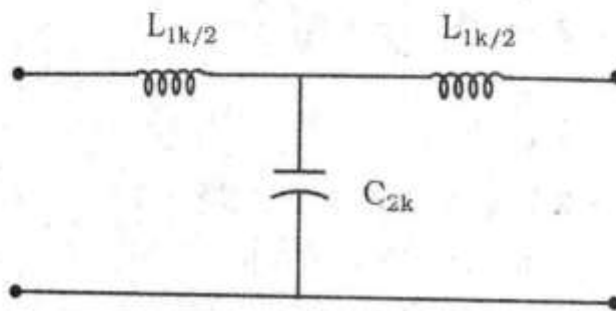Find L_{1k} and C_{2k} from the above formulae then, $L_{1k/2} \ L_{1k/2}$




11.31 $L_{1k} = 0.30 \text{ H}$

$C_{2k} = 0.03 \mu f$

$m = 0.60$

$f_c = 800 \text{ Hz}$

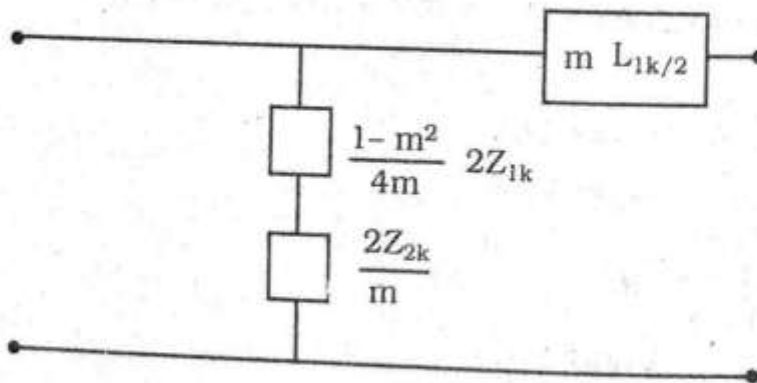

$$Z_{1k} = j2\pi \times 800 \times 0.3 = 1507.964j$$

$$Z_{2k} = \frac{j \times 10^6}{2\pi \times 800 \times 0.03} = -6631.454 j$$

So do yourself.

$$11.32 \quad Z_{1m} = m L_{1k} = L_{1m}$$

$$Z_{2m} = \left(\frac{1 - m^2}{4m} \right) L_{1k} = L_{2m}$$

So in series $m c_{2k} = c_{2m}$

$$\therefore f_c = \frac{1}{\pi \sqrt{L_{1k} c_{2k}}}$$

$$\text{R.H.S} = \frac{1}{\pi \sqrt{(L_{1m} + c_1 L_{2m}) (c_{2m})}}$$

$$= \frac{1}{\pi \sqrt{(ML_{1k} + \frac{4(1 - m^2)}{4m} L_{1k}) (m c_{2k})}} = \text{Do yourself}$$

33. Not important

Chapter-14

Transient Analysis

14.1 Graph plotting → Try yourself.

$$y = 311 \sin 377 t$$

14.2 Transient current conection.

$$i = \frac{E_m}{z} \sin (\omega t + \lambda + \theta) - \frac{E_m}{z} \sin (\lambda - \theta) e^{-Rt/L}$$

if $L \rightarrow 0$ then

$$z = \sqrt{(\omega L)^2 + R^2}$$

$$\theta = \tan^{-1} \frac{\omega L}{R}$$

$$= R$$

or, $\tan \theta = \frac{\omega L}{R}$


so $\theta = 0$ [$\because L \rightarrow 0$]

$$\therefore i = \frac{E_m}{R} \sin (\omega t + \lambda) - \frac{E_m}{R} \lambda e^{-\dots}$$

steady state term

$$= \frac{E_m}{R} \sin (\omega t + \lambda)$$

14.3

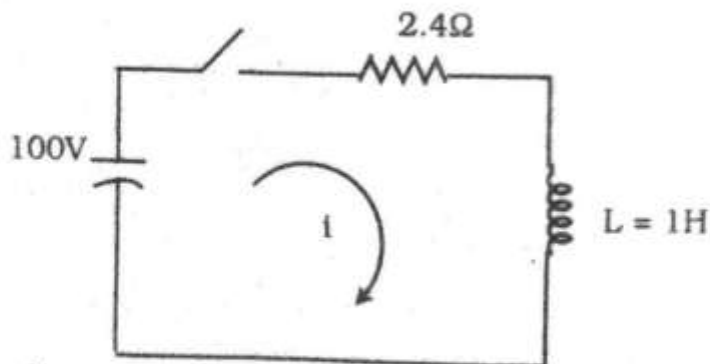

$$0.4 i \frac{di}{dt} = 10$$

or, $\frac{di}{dt} + 0.4 i = 10$

\therefore The complete solution is $i = I_s + I_p = c_1 e^{-0.4t} + \frac{10}{0.4}$

$$= c_1 e^{-0.4t} + 25$$

At $t = 0, i = 0 \therefore 0 = c_1 + 25$

$\therefore c_1 = -25$

$\therefore i = -25e^{-0.4t} + 25$
 $= 25(1 - e^{-0.4t})$

(a) at $t = 1$ sec, $i = 25(1 - e^{-0.4}) = 8.242$ amp

(b) at $t = 2.5$ sec $i = 25(1 - e^{-0.4 \times 2.5}) = 15.8$ amp

(c) $V_L = L \frac{di}{dt} = 1 \cdot \frac{d}{dt} \{25(1 - e^{-0.4t})\} = 10e^{-0.4t}$

accelerating voltage at $t = 1$ sec is $10e^{-0.4} = 6.7$ volt

" " " $t = 2.5$ " " $10e^{-0.4 \times 2.5} = 3.68$ volt

(a) Here $L_1 = 1$ H, $R = 0.4$ ohm, $t = 1$ sec, $E = 10$ volt

We know that

$i = \frac{E}{R} (1 - e^{-Rt/L}) = 8.2$ amp

(b) After 2.5 sec, $i = \frac{E}{R} (1 - e^{-Rt/L}) = \frac{10}{0.4} \left(1 - e^{-\frac{0.4 \times 2.5}{1}}\right)$


$\therefore i = 15.802$ amp

(c) After 1 sec, the value of voltage accelerating the current the resisturn = $Ri = 0.4 \times 8.242 = 3.2960$ volts.

Across the inductance $V_L = L \frac{di}{dt} = -L \left[-\frac{E}{R} - \frac{R}{L} e^{-Rt/L} \right]$
 $= 6.703$ volts

\therefore The accelerating voltage is, $E - Ri = -3.2968$ volts

14.4

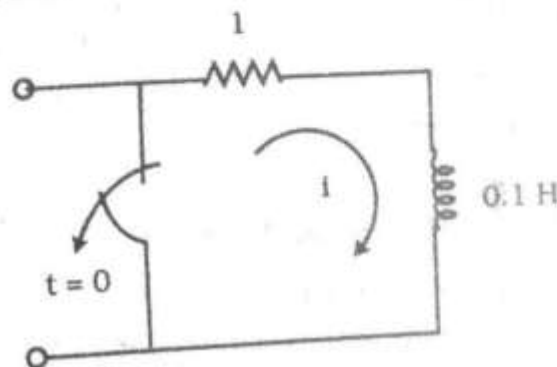

$\therefore i = 10e^{-10t}$


∴ After 0.1 sec, $i = 10e^{-10 \times 1} = 3.68$ amp

Let the time be t_1

∴ $0.1 = 10e^{-10t}$ or $-10t = \ln(0.01) = -4.605$

∴ $t = 0.4605$ sec

14.5 Let the resistance be R

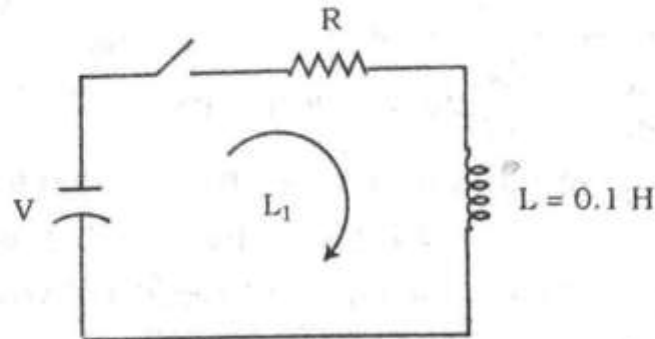

∴ $Ri + 0.1 \frac{di}{dt} = V$ or, $\frac{di}{dt} + 10 Ri = 10 V$

at $t = 0, i = 0 \therefore c_1 = -V/R \therefore i = V/R (1 - e^{-10Rt})$

The final value of current = V/R after 2 sec, $i = 0.632 \frac{V}{R}$

∴ $0.632 V/R = V/R (1 - e^{-10R \times 2})$ or, $e^{-10R} = 1 - 0.632$

or, $-20R = \ln(0.368)$

∴ $R = 0.05$ ohm

14.6 $0.1 i + \frac{di}{dt} = 10$ or, $\frac{di}{dt} + 0.1 i = 10$

∴ $i = 4e^{-0.1t} + \frac{10}{0.1}$

$= 4e^{-0.1t} + 100$ at $t = 0, i = 0 \therefore 4 = -100$

∴ $i = 100(-e^{-0.1t})$

$V_L = L \frac{di}{dt} = 1 \frac{d}{dt} \{100(1 - e^{-0.1t})\}$

$= 100 \times 0.1 e^{-0.1t} = 10e^{-0.1t}$

$P_L = V_L i = 10e^{-0.1t} \times 100(1 - e^{-0.1t})$

$= 1000(e^{-0.1t} - e^{-0.2t})$

(a) At $t = 10$ sec, $i = 100(1 - e^{-0.1 \times 10}) = 63.2$ amp

Stored energy = $V_2 \times Li^2 = \frac{1}{2} \times 1 \times (63.2)^2 = 1998$ Joule

$$\begin{aligned} \text{(b) Energy dissipated} &= iR^2 = R^2 - \frac{E}{R} (1 - e^{-Rt/L}) \\ &= ER (1 - e^{-Rt/L}) \text{ Joule} \end{aligned}$$

$$\begin{aligned} O_R &= \int_0^t i^2 R dt = R \int_0^t \frac{E^2}{R^2} (1 - e^{-Rt/L})^2 dt \\ &= \frac{E^2}{R} \int_0^t (1 - e^{-Rt/L})^2 dt \\ &= \frac{E^2}{R} \int_0^t (1 - 2e^{-Rt/L} + e^{-2Rt/L}) dt \\ &= \frac{E^2}{R} \left[t + \frac{2L}{R} e^{-Rt/L} - \frac{L}{2R} e^{-2Rt/L} \right]_0^t \\ &= \frac{E^2}{R} \left[t - \frac{2L}{R} e^{-Rt/L} - Re^{-2Rt/L} - \frac{2L}{R} + L/R \right] \text{ Joules} \end{aligned}$$

14.7

$$R_1 + \frac{1}{C} \int i dt = V \text{ or, } R \frac{dq}{dt} + \frac{q}{C} = V \text{ or } 1 \times 10^6 \frac{dq}{dt} + \frac{q}{50 \times 10^{-6}} = V$$

$$\text{or, } \frac{dq}{dt} + 0.02 q = 10^{-6}$$

$$\therefore q = c_1 e^{-0.02t} + \frac{10^{-6}}{0.02} V = 50 \times 10^{-6} V (1 - e^{-0.02t})$$

Let the time be t_1

$$\therefore 0.632 \times 50 \times 10^{-6} V = 50 \times 10^{-6} V (1 - e^{-0.02t_1})$$

$$\text{or, } e^{-0.02t_1} = 1 - 0.632$$

$$\text{or, } -0.02t_1 = \ln(0.368)$$


$$\text{or, } t_1 = 50 \text{ sec}$$

(a) Let the time be t_1

$$\therefore 0.001 = 0.1 e^{-20t_1} \text{ or, } -20t_1 = \ln(0.01)$$

$$\therefore t_1 = 0.23 \text{ sec}$$

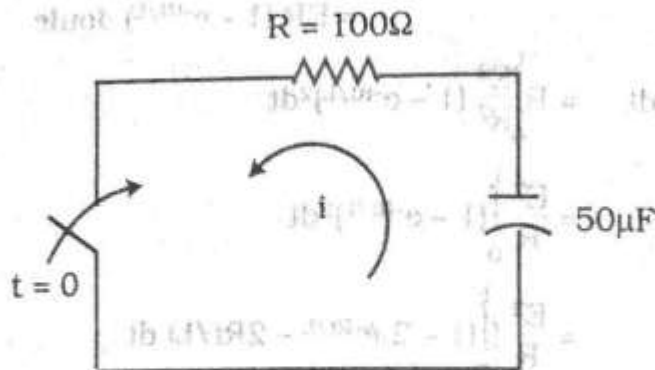(b) Initial voltage $V_c = \frac{0.1}{50 \times 10^{-6}}$



$$R_i + \frac{1}{c} = 0$$

$$\text{or, } 1000 \frac{dq}{dt} + \frac{q}{50 \times 10^{-6}} = 0$$

$$\text{or, } \frac{dq}{dt} + 20q = 0$$

$$\therefore q = c_1 e^{-20t} \text{ coulomb}$$

$$t = 0, q_0 = 0.1 \text{ c}$$

$$\therefore 0.1 = c_1 \therefore q = 0.1 e^{-20t}$$

$$\therefore i_c = \frac{2000}{1000} = 2 \text{ amp}$$

(c) Then

$$V_0 = \frac{0.001}{50 \times 10^{-6}}$$

$$= 20 \text{ V}$$

$$\therefore i = \frac{20}{1000} = 0.02 \text{ amp}$$

14.9 Soln : $Q_0 = 0.1$ coulomb $c = 100 \times 10^{-6} \text{ f}$, $R = 10 \text{ k ohm}$

Decay of charge in 1 sec, $q = CE e^{-t/RC}$

$$q = 100 \times 10^{-6} \times \frac{0.1}{100 \times 10^{-6}} \times e^{-\frac{1}{10,000 \times 100 \times 10^{-6}}}$$

$$= 0.0367 \text{ coulomb}$$

$$\text{We know, } W_c = \int_0^{\infty} P_0 dt = \int_0^{\infty} V_c i dt = \int_0^{\infty} \frac{q}{c} \cdot \frac{dq}{dt} \cdot dt$$

$$= \int_0^{\infty} \frac{q}{c} dq = \frac{1}{2} \frac{q^2}{c} \text{ But here}$$

$$W_c = \frac{(Q_0 - q)^2}{2c} = \frac{(0.1 - 0.0367)^2}{2 \times 100 \times 10^{-6}} = 20 \text{ Joules}$$

14.10 Soln :


$$R = 10,000 \text{ ohm}$$

$$c = 100 \times 10^{-6} \text{ f}$$

$$t = 1 \text{ sec}$$

$$w_c = 19.98 \text{ Joule in 1 sec}$$

$$Q_0 = 0, E = ?$$

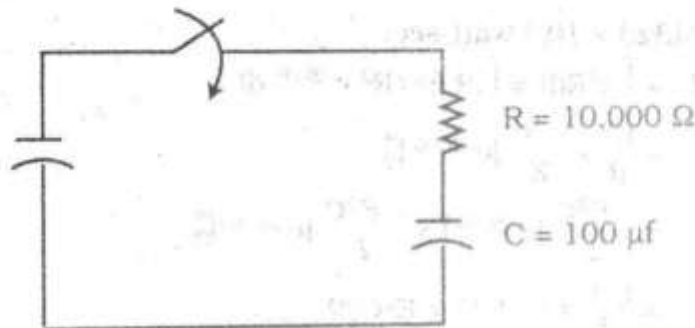

We know,

$$W_c = \int_0^{\infty} P_0 dt = \int_0^{\infty} V_c i dt + \int_0^{\infty} \frac{q}{c} \frac{dq}{dt} dt$$

$$W_c = \int_0^{\infty} \frac{q}{c} dq = \frac{q^2}{2c}$$

$$\therefore 19.98 = \frac{q^2}{100 \times 10^{-6}} = 632.133 \text{ volts}$$

14.11 (a)

$$\begin{aligned} q &= CE - (CE - Q)e^{-t/RC} \\ &= 10^{-6} \times 100 (1 - e^{-1/10^6 \times 10^{-6}}) \\ &= 10^{-4} \times (1 - e^{-1}) = 6.32 \times 10^{-5} \end{aligned}$$

Here given,

$$R = 1 \times 10^6$$

$$C = 1 \times 10^{-6} \text{ f}$$

$$E = 100 \text{ volts}$$

Energy stored,

$$E_s = \frac{q^2}{2c} = \frac{(6.32 \times 10^{-5})^2}{2 \times 10^{-6}}$$

$$= 1.99712 \times 10^{-3} \text{ watt/sec}$$

$$\begin{aligned}
 \text{(b) } E_R &= \int_0^t i^2 R dt = \int_0^t R \frac{E^2}{R} \cdot e^{-2t/Rc} dt \\
 &= \frac{E^2}{R} \int_0^t e^{-2t/Rc} dt = \frac{E^2}{R} \times \frac{Rc}{2} [e^{-2t/Rc}]_0^t \\
 &= \frac{-E^2c}{2} [e^{-2t/Rc}] + \frac{E^2C}{2} \\
 &= \frac{100^2 \times 10^{-6}}{2} \left[0 - \frac{20 \times 1}{10^6 \times 10^6} \right] + \frac{100^2 \times 10^{-6}}{2} \\
 &= 4323 \times 10^{-3} \text{ watt-sec}
 \end{aligned}$$

$$\begin{aligned}
 \text{(c) } E_R \text{ full} &= \int_0^\infty i^2 R dt = \int_0^\infty R \cdot E^2 / R^2 e^{-2t/Rc} dt \\
 &= \frac{E^2}{R} \times \frac{-Rc}{Z} [e^{-2t/Rc}]_0^\infty \\
 &= \frac{-E^2C}{2} [e^{-2t/Rc}] = \frac{-E^2C}{2} [e^{-2t/Rc}]_0^\infty \\
 &= \frac{E^2C}{2} e^{-2 \times 0/Rc} = E^2C/2 \\
 &= \frac{100^2 \times 10^{-6}}{2} = 5 \times 10^{-3} \text{ watt-sec}
 \end{aligned}$$


14.12 Do yourself

14.13 We know, $i = \frac{E_m}{Z} \sin(\omega t + \lambda - \theta) - \frac{E_m}{Z} \sin(\lambda - \theta) e^{-Rt/L}$

Steady state Transient state

Here, $E_m = 100$, $\omega t = 377t$, $\lambda = \frac{\pi}{4}$
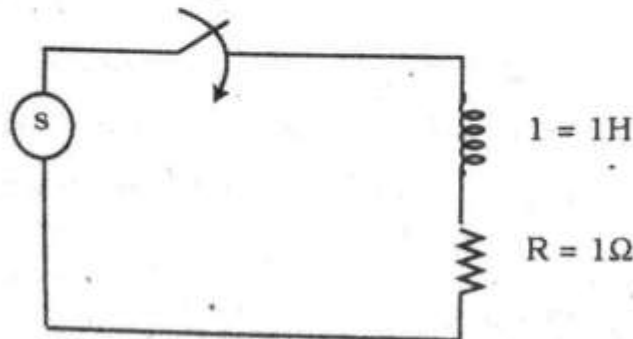
$$\theta = \tan^{-1} \frac{WL}{R} = \tan^{-1} \frac{377 \times 1}{1} = 89.848^\circ$$




$$\begin{aligned}
 L &= 1 \text{ H, } R = 1 \text{ oh, } Z = \sqrt{R^2 + (WL)^2} \\
 &= \sqrt{1^2 + (377 \times 1)^2} = 377 \text{ ohm}
 \end{aligned}$$

When, $t = 0$

$$i_{ss} = \frac{100}{377} \sin(\pi/4 - 89.848) = -0.187 \text{ amp}$$

$$i_{tr} = \frac{-100}{377} \sin(\pi/4 - 89.848) = 0.187 \text{ amp}$$

14.14 We know,

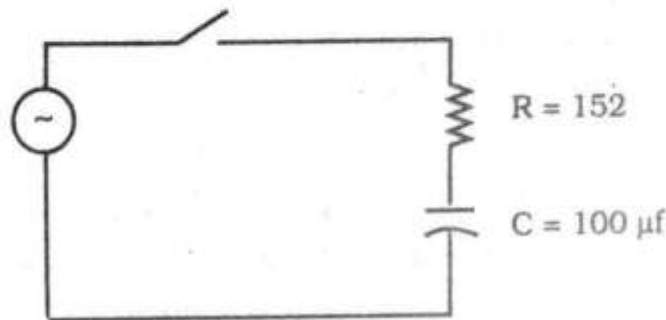

$$q = \frac{-E_m}{\omega \sqrt{R^2 + X_c^2}} \cos(\omega t + \lambda t + \theta) + \frac{E_m e^{-t/Rc}}{\omega \sqrt{R^2 t^2 + c^2}} \times \cos(\pi + \theta)$$

$$q = \frac{-100}{377 \sqrt{1^2 + \left(\frac{1}{377 \times 100 \times 10^{-6}}\right)^2}}$$

$$\cos\left(30^\circ + \tan^{-1} \frac{1}{377 \times 100 \times 10^{-6}}\right)$$

$$+ \frac{100 \times e^0}{377 \sqrt{1^2 + \left(\frac{1}{377 \times 100 \times 10^{-6}}\right)^2}}$$

$$\cos\left(30^\circ + \tan^{-1} \frac{1}{377 \times 100 \times 10^{-6}}\right)$$

$$= 0.00499 - 0.00499$$

$$\therefore q_{ss} = 0.00499$$

$$q_{tr} = -0.00499 \text{ coulb}$$

$$(b) i = \frac{E_m}{Z} \sin(\omega t + \lambda + \theta) - \frac{E_m}{WCRZ} \cos(\lambda + \theta) e^{-t/Rc}$$

230 The Solution of Alternating Current Circuits

When $t = 0$, $z = \sqrt{1^2 + \left(\frac{1}{77 \times 100 \times 10^{-6}}\right)^2} = 26.544$

$$i = \frac{100}{26.544} \sin(30 + 87.84) - \frac{100}{26.544} \cos(30 + 87.84) \times \frac{C^0}{377 \times 100 \times 10^{-6}}$$

$$= 3.33 + 46.67$$

$i_{ss} = 3.33$

and $i_{tr} = 46.67$ amp

14.15 $R = 100$ ohm, $L = 0.1$ Henry

$C = 200 \times 10^{-6}$ $Q_0 = 0$

$a = \frac{R}{2L} = 500$

$b = \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$
 $= 447.213$

$\therefore (-a + b) = 477.213 - 500$

$= -52.787$

$\therefore (-a + b)t = e^{-52.787 \times 0.01} = 0.589$

$(a - b) = -947.213$

$\therefore e^{-(a-b)t} = e^{-947.213 \times 0.01} = 7.696 \times 10^{-5}$

$\therefore [e^{(-a+b)t} - e^{-(a-b)t}] = 0.588$

$CE = 200 \times 10^{-6} \times 50 = 0.01$

$RC = 100 \times 200 \times 10^{-6} = 0.02$

$\sqrt{R^2C^2 - 4LC} = 0.0178$

We know that

$i = \frac{CE - Q_0}{R^2C^2 - 4LC}$

$\left[\frac{R_c + \sqrt{R^2C^2 - 4LC}}{2\sqrt{R^2C^2 - 4LC}} e^{(-a+b)t} - \frac{RC - R^2C^2 - 4LC}{2\sqrt{R^2C^2 - 4LC}} e^{-(a-b)t} \right]$

$= 0.01 - 0.01$

$\left[\frac{0.02 + 0.0178}{2 \times 0.0178} \times 0.589 - \frac{0.02 - 0.0178}{2 \times 0.0178} \times 7.696 \times 10^{-5} \right]$

$= 0.01 - 0.01 [0.625 - 4.75 \times 10^{-6}]$

$= 0.00375$ coulomb

14.16 According to Sir (Shaidulla).

$R = 4 \text{ ohm, } L = 0.1 \text{ H, } C = 200 \times 10^{-6}, t = 0.01 \text{ sec}$

$E = 1000 \text{ V, } Q_0 = 0$

$A = \frac{R}{2L} = \frac{4}{2 \times 0.1} = 20, B = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} = 222.204$

$\sqrt{4 \times 0.1 \times 200 \times 10^{-6} - (5 \times 200 \times 10^{-6})^2}$

$= 0.00888$

(a) $i = \frac{2(CE - Q_0)}{\sqrt{4LC - R^2C^2}} \sin Bt = \frac{2CEe^{-At}}{\sqrt{4LC - R^2C^2}} \sin Bt$

$= \frac{2 \times 200 \times 10^{-6} \times 1000e^{-25 \times 0.01}}{0.00888} \sin(222.204 \times 0.01)$

$= \frac{0.311}{0.00888} \times 0.769$

$= 35 \times 0.796 = 27.87 \text{ Ans.}$

(b) Yes

(c) $\pi = \frac{\beta}{2\pi} = \frac{222.204}{2\pi} = 35.36 \text{ Hz}$

$q = \frac{CE - 2(CE - \theta_0)Lce^{-t}}{\sqrt{4LC - R^2C^2}} \sin(Bt + \theta)$

$\phi = \tan^{-1} \frac{\sqrt{4LC - R^2C^2}}{RC}$

$= \tan^{-1} \frac{0.00888}{5 \times 200 \times 10^{-6}} = 83.57^\circ$

$q = \frac{200 \times 10^{-6} \times 1000 - 2 \times 200 \times 10^{-6} \times 1000 \sqrt{0.1 \times 200 \times 10^{-6}}}{0.0888}$

$\times e^{-25 \times 0.01} \sin(222.204 \times 0.01) + 1.45)$

$= 0.2 - \frac{1.39 \times 10^{-3}}{0.00888} \sin(3.67204)$

$= 0.2 - 0.1565 \sin\left(3.67204 \times \frac{180}{\pi}\right)$

$= 0.279 \text{ coulomb}$

14.18 Given.

$$e = 141. \sin(377t - 45^\circ) \text{ volts}$$

$$R = 1 \text{ ohm}$$

$$E_m = 141.0 \text{ volt}$$

$$L = 0.041 \text{ A}$$

$$\beta = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} = \text{Do yourself}$$

$$c = 18.7 \mu\text{f}$$

$$Q_0 = 0$$

$$(a) i = k_1 \sin(k_2 t + k_3) + k_4 e^{5t} \sin(k_6 t - k_7) \text{ amp}$$

$$\text{Where, } i = \frac{E_m}{z} \sin(\omega t + \lambda - \theta) + I_t e^{-at} \sin(\beta t - 6)$$

$$I_t = \sqrt{\left[\frac{E_d}{\beta L} \right]^2 + \left[\frac{E_m}{z} \sin(\lambda - \theta) \right]^2}$$

$$6 = \tan^{-1} \frac{E_m \beta L \sin(\lambda - \theta)}{E_d z}$$

Here,

$$K_1 = \frac{E_m}{z}$$

$$I_t = K_4$$

$$K_3 = \lambda \theta$$

$$a = 5$$

$$K_2 = K_2$$

$$K_6 = \beta$$

$$K_7 = 6$$

Find the corresponding values hence write the equation.

(b) Sketch yourself.